

DIGITAL LOGIC CIRCUITS

Logic Gates

Boolean Algebra

Map Specification

Combinational Circuits

Flip-Flops

Sequential Circuits


Memory Components

Integrated Circuits


LOGIC GATES

Digital Computers

 - Imply that the computer deals with digital information, i.e., it deals with the information that is represented by binary digits
 - Why *BINARY*? instead of Decimal or other number system ?
- * Consider electronic signal



BASIC LOGIC BLOCK - GATE -

 

Types of Basic Logic Blocks

- **Combinational Logic Block**

Logic Blocks whose output logic value depends only on the input logic values









- **Sequential Logic Block**

Logic Blocks whose output logic value depends on the input values and the state (stored information) of the blocks

Functions of Gates can be described by

- Truth Table
- Boolean Function
- Karnaugh Map

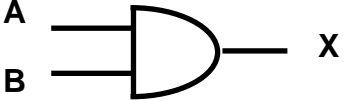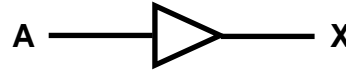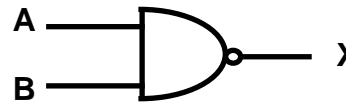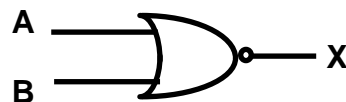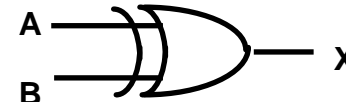COMBINATIONAL GATES

Name	Symbol	Function	Truth Table															
AND		$X = A \cdot B$ or $X = AB$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$X = A + B$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
I		$X = A$	<table border="1"> <thead> <tr> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	A	X	0	1	1	0									
A	X																	
0	1																	
1	0																	
Buffer		$X = A$	<table border="1"> <thead> <tr> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	A	X	0	0	1	1									
A	X																	
0	0																	
1	1																	
NAND		$X = (AB)'$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$X = (A + B)'$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR Exclusive OR		$X = A \oplus B$ or $X = A'B + AB'$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
XNOR Exclusive NOR or Equivalence		$X = (A \oplus B)'$ or $X = A'B' + AB$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

BOOLEAN ALGEBRA


Boolean Algebra

- * **Algebra with Binary(Boolean) Variable and Logic Operations**
- * **Boolean Algebra is useful in Analysis and Synthesis of Digital Logic Circuits**
 - **Input and Output signals can be represented by Boolean Variables, and**
 - **Function of the Digital Logic Circuits can be represented by Logic Operations, i.e., Boolean Function(s)**
 - **From a Boolean function, a logic diagram can be constructed using AND, OR, and I**


Truth Table

- * **The most elementary specification of the function of a Digital Logic Circuit is the Truth Table**
 - **Table that describes the Output Values for all the combinations of the Input Values, called *MINTERMS***
 - **n input variables $\rightarrow 2^n$ minterms**



LOGIC CIRCUIT DESIGN

 

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

$$F = x + y'z$$

  

BASIC IDENTITIES OF BOOLEAN ALGEBRA

[1] $x + 0 = x$

[3] $x + 1 = 1$

[5] $x + x = x$

[7] $x + x' = 1$

[9] $x + y = y + x$

[11] $x + (y + z) = (x + y) + z$

[13] $x(y + z) = xy + xz$

[15] $(x + y)' = x'y'$

[17] $(x')' = x$

[2] $x \cdot 0 = 0$

[4] $x \cdot 1 = x$

[6] $x \cdot x = x$

[8] $x \cdot x' = 0$

[10] $xy = yx$

[12] $x(yz) = (xy)z$

[14] $x + yz = (x + y)(x + z)$

[16] $(xy)' = x' + y'$


[15] and [16] : De Morgan's Theorem

Usefulness of this Table

- Simplification of the Boolean function
 - Derivation of equivalent Boolean functions to obtain logic diagrams utilizing different logic gates
 - Ordinarily ANDs, ORs, and Inverters
 - But a certain different form of Boolean function may be convenient to obtain circuits with NANDs or NORs
- Applications of De Morgans Theorem


$$x'y' = (x + y)'$$

I, AND → NOR

 

$$x' + y' = (xy)'$$




I, OR → NAND

 


EQUIVALENT CIRCUITS

Many different logic diagrams are possible for a given Function

   
$$\begin{aligned}
 F &= ABC + ABC' + A'C && \dots\dots\dots (1) \\
 &= AB(C + C') + A'C && [13] \dots\dots (2) \\
 &= AB \cdot 1 + A'C && [7] \\
 &= AB + A'C && [4] \dots\dots (3)
 \end{aligned}$$



SIMPLIFICATION

 

Unique

 


Many different expressions exist

Simplification from Boolean function

- Finding an equivalent expression that is least expensive to implement
- For a simple function, it is possible to obtain a simple expression for low cost implementation
- But, with complex functions, it is a very difficult task

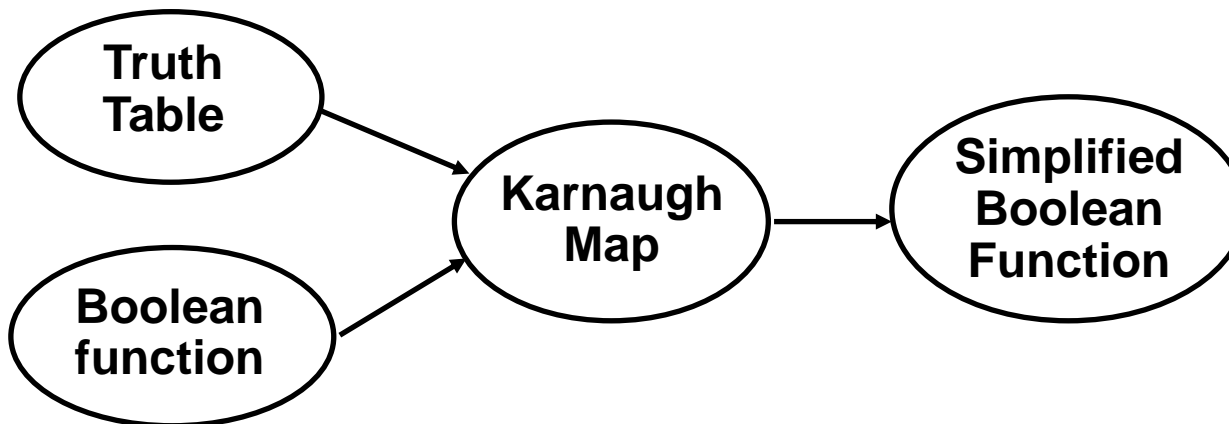Karnaugh Map (K-map) is a simple procedure for simplifying Boolean expressions.




KARNAUGH MAP

Karnaugh Map for an n-input digital logic circuit (n-variable sum-of-products form of Boolean Function, or Truth Table) is


- Rectangle divided into 2^n cells
- Each cell is associated with a *Minterm*
- An output(function) value for each input value associated with a minterm is written in the cell representing the minterm
→ 1-cell, 0-cell

Each Minterm is identified by a decimal number whose binary representation is identical to the binary interpretation of the input values of the minterm.

x	F
0	1
1	0

 



Karnaugh Map

 

$$F(x) = \sum (1)$$

1-cell

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

  

$$F(x,y) = \sum (1,2)$$

KARNAUGH MAP

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

		yz		y	
		00	01	11	10
x	0	0	1	3	2
	1	4	5	7	6

z

		yz		y	
		00	01	11	10
x	0	0	1	0	1
	1	1	0	0	0

$F(x,y,z) = \sum (1,2,4)$

u	v	w	x	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

		wx		w	
		00	01	11	10
uv	00	0	1	3	2
	01	4	5	7	6
u	11	12	13	15	14
	10	8	9	11	10

x



		wx		w	
		00	01	11	10
uv	00	0	1	1	0
	01	0	0	0	1
u	11	0	0	0	1
	10	1	1	1	0

$F(u,v,w,x) = \sum (1,3,6,8,9,11,14)$

IMPLEMENTATION OF K-MAPS - Sum-of-Products Form -

Logic function represented by a Karnaugh map can be implemented in the form of I-AND-OR

  A cell or a collection of the adjacent 1-cells can be realized by an AND gate, with some inversion of the input variables.




IMPLEMENTATION OF K-MAPS - Product-of-Sums Form -

Logic function represented by a Karnaugh map can be implemented in the form of I-OR-AND


If we implement a Karnaugh map using 0-cells, the complement of F , i.e., F' , can be obtained. Thus, by complementing F' using DeMorgan's theorem F can be obtained

$$F(x,y,z) = (0,2,6)$$

 

$$F' = xy' + z$$

$$F = (xy')z' \\ = (x' + y)z'$$

 



IMPLEMENTATION OF K-MAPS - Don't-Care Conditions -

In some logic circuits, the output responses for some input conditions are don't care whether they are 1 or 0.

In K-maps, don't-care conditions are represented by d's in the corresponding cells.

Don't-care conditions are useful in minimizing the logic functions using K-map.

  - Can be considered either 1 or 0
- Thus increases the chances of merging cells into the larger cells
--> Reduce the number of variables in the product terms



COMBINATIONAL LOGIC CIRCUITS

Half Adder


x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

	y
x	0 0
x	0 1

$c = xy$

	y
x	0 1
x	1 0

$s = xy' + x'y$
 $= x \oplus y$

 

Full Adder

x	y	c_{n-1}	c_n	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

	y
x	0 0
x	0 1
x	1 1
x	0 1

c_n

	y
x	0 1
x	1 0
x	0 1
x	1 0


s

$$c_n = xy + xc_{n-1} + yc_{n-1}$$

$$= xy + (x \oplus y)c_{n-1}$$

$$s = x'y'c_{n-1} + x'yc'_{n-1} + xy'c'_{n-1} + xyc_{n-1}$$
 
$$= x \oplus y \oplus c_{n-1} = (x \oplus y) \oplus c_{n-1}$$



COMBINATIONAL LOGIC CIRCUITS


Other Combinational Circuits

- Multiplexer**
- Encoder**
- Decoder**
- Parity Checker**
- Parity Generator**
- etc**

MULTIPLEXER


4-to-1 Multiplexer

Select		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


ENCODER/DECODER

Octal-to-Binary Encoder

 

2-to-4 Decoder


E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	d	d	1	1	1	1

 


FLIP FLOPS

Characteristics

 - 2 stable states
- Memory capability
- Operation is specified by a Characteristic Table



 
In order to be used in the computer circuits, state of the flip flop should have input terminals and output terminals so that it can be set to a certain state, and its state can be read externally.



S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	indeterminate (forbidden)


CLOCKED FLIP FLOPS

 In a large digital system with many flip flops, operations of individual flip flops are required to be synchronized to a clock pulse. Otherwise, the operations of the system may be unpredictable.




Clock pulse allows the flip flop to change state only when there is a clock pulse appearing at the c terminal.

 We call above flip flop a Clocked RS Latch, and symbolically as








operates when
clock is high

 

operates when
clock is low



RS-LATCH WITH PRESET AND CLEAR INPUTS

     

D-LATCH

D-Latch

  Forbidden input values are forced not to occur by using an inverter between the inputs




D	Q(t+1)
0	0
1	1

EDGE-TRIGGERED FLIP FLOPS

Characteristics


- State transition occurs at the rising edge or falling edge of the clock pulse

Latches

 

respond to the input only during these periods



Edge-triggered Flip Flops (positive)

 



respond to the input only at this time

POSITIVE EDGE-TRIGGERED

D-Flip Flop

  

JK-Flip Flop

 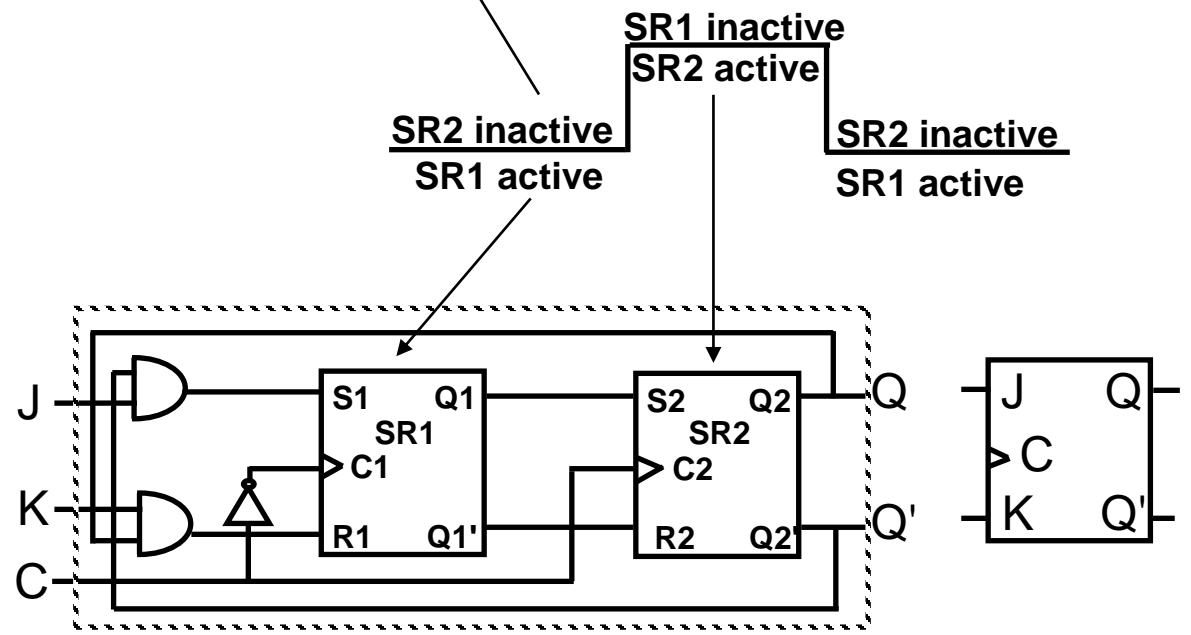


T-Flip Flop: JK-Flip Flop whose J and K inputs are tied together to make T input. Toggles whenever there is a pulse on T input.

CLOCK PERIOD

**Clock period determines how fast the digital circuit operates.
How can we determine the clock period ?**

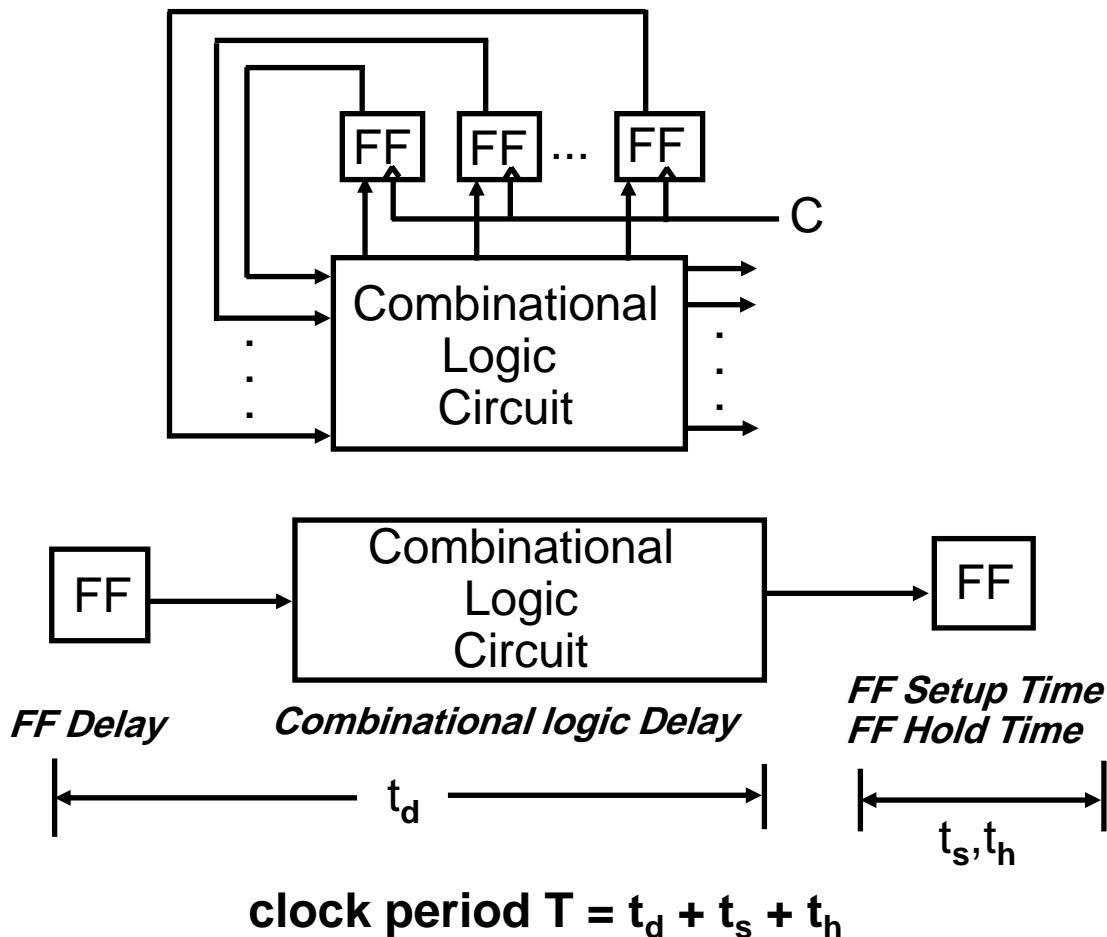Usually, digital circuits are sequential circuits which has some flip flops




DESIGN EXAMPLE

Design Procedure:


Specification \Rightarrow State Diagram \Rightarrow State Table \Rightarrow
 Excitation Table \Rightarrow Karnaugh Map \Rightarrow Circuit Diagram

 Example: 2-bit Counter \rightarrow 2 FF's




current state		input	next state		FF inputs			
A	B		x	A	B	Ja	Ka	Jb
0	0	0	0	0	0	d	0	d
0	0	1	0	1	0	d	1	d
0	1	0	0	1	0	d	d	0
0	1	1	1	0	1	d	d	1
1	0	0	1	0	d	0	0	d
1	0	1	1	1	d	0	1	d
1	1	0	1	1	d	0	d	0
1	1	1	0	0	d	1	d	1


 Ja = Bx	 Ka = Bx	 Jb = x	 Kb = x
-------------	-------------	------------	------------

 


SEQUENTIAL CIRCUITS - Registers

 

Shift Registers

 

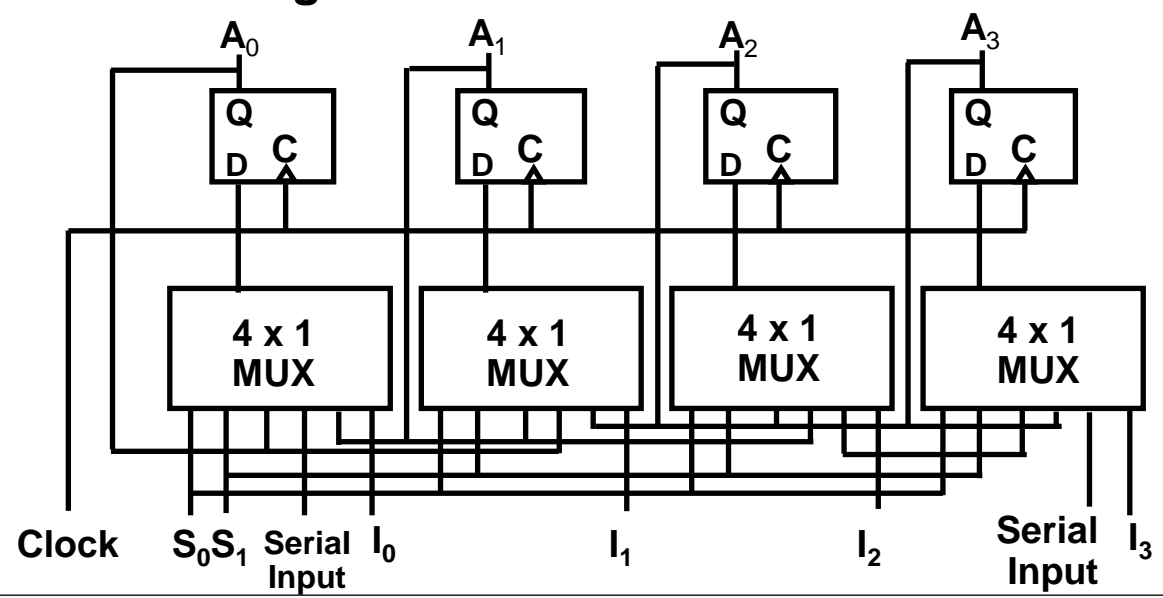Bidirectional Shift Register with Parallel Load



SEQUENTIAL CIRCUITS - Counters

