

## PLC Programming Languages

### **INTRODUCTION TO THE IEC 1131**



The International Electrotechnical Commission (IEC) SC65B-WG7 committee developed the IEC 1131 standard in an effort to standardize programmable controllers.

One of the committee's objectives was to create a common set of PLC instructions that could be used in all PLCs.

**It Defines three graphical languages and two text-based languages**


**The graphical languages use symbols to program control instruction while text-based used character strings to program the instructions**
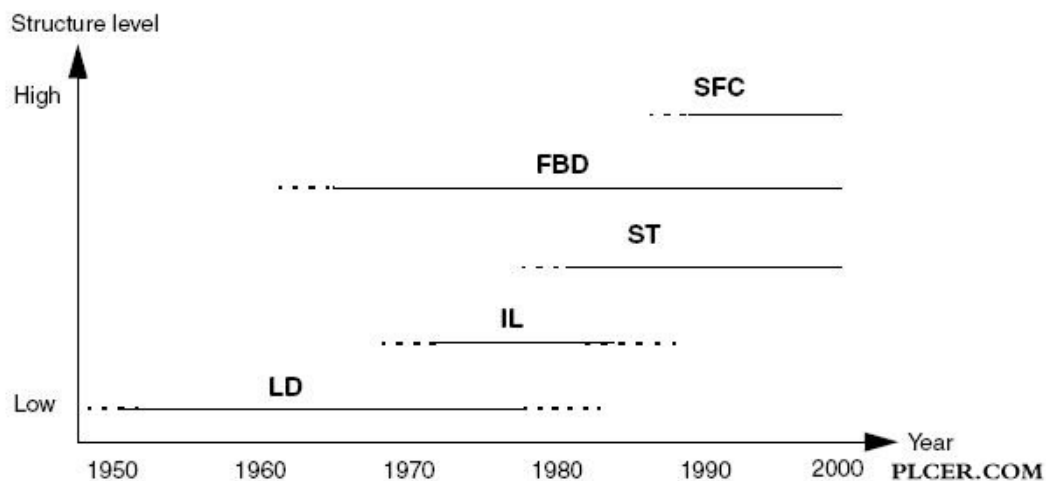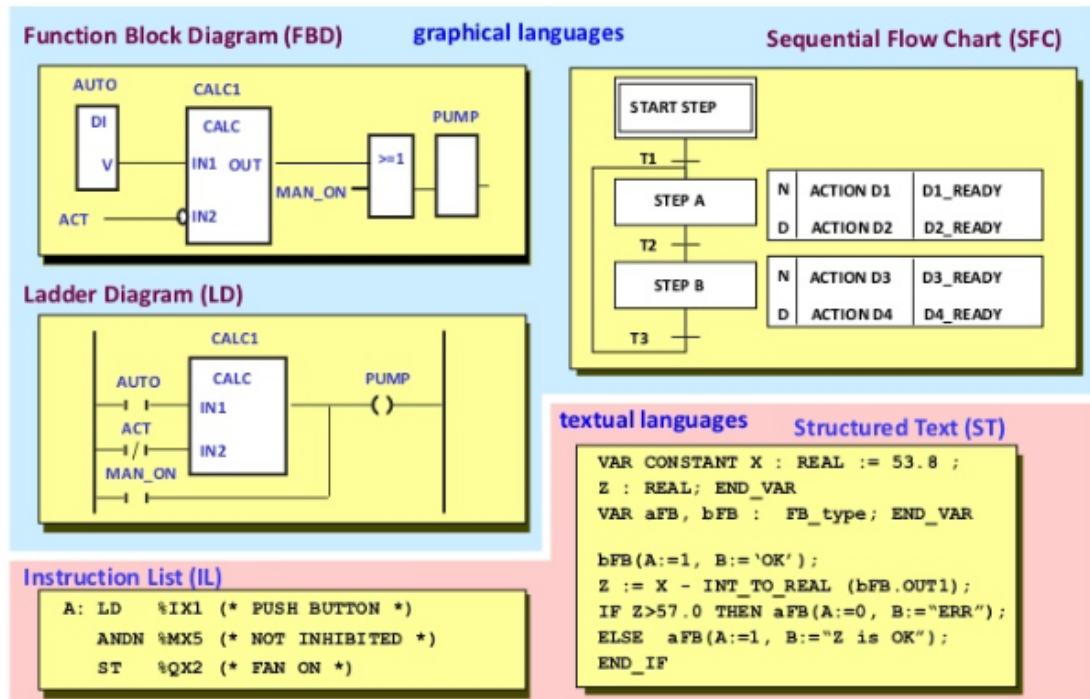
# The five IEC 61131-3 Programming languages




Programmers may choose from among five PLC languages.

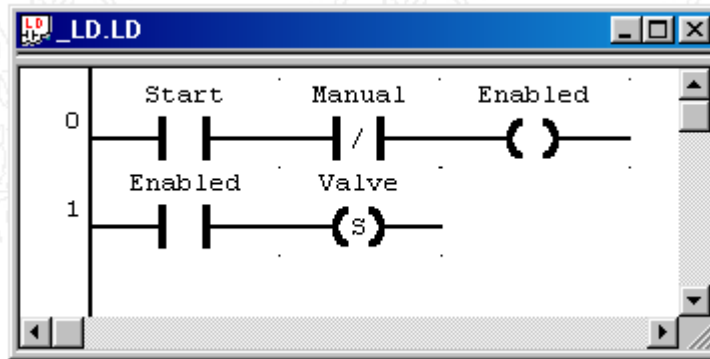
**Ladder diagram (LD)** is best for programs controlled by multiple files, subroutines and code sectioning.



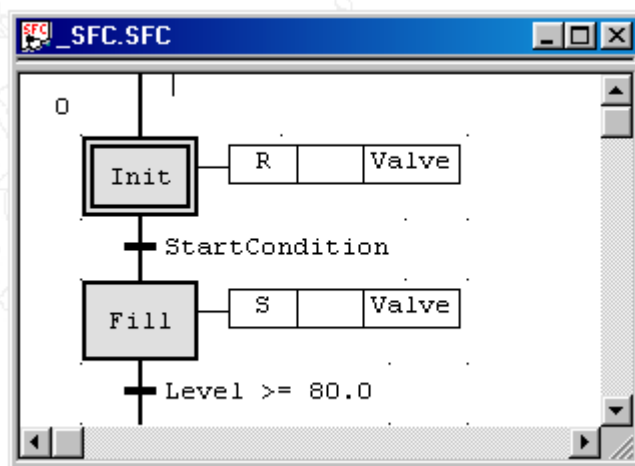**Sequential function charts (SFCs)** are used to program systems that are more advanced than those run by LD.




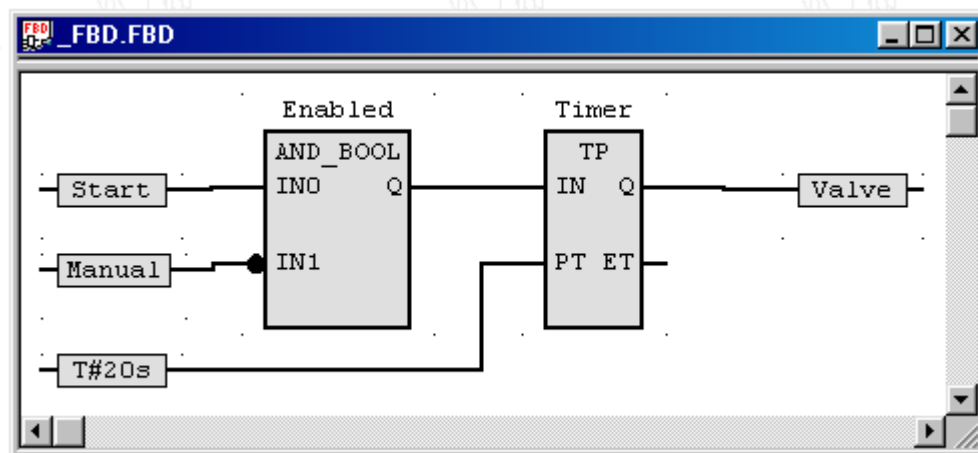**Function block diagram (FBD)** is a graphical language that drives data from inputs to outputs by sending through blocks of nested data.




**Structured text (ST)** resembles Basic or Pascal programming languages, in that it uses statements such as "If-Then-Else," "While" and "Repeat."

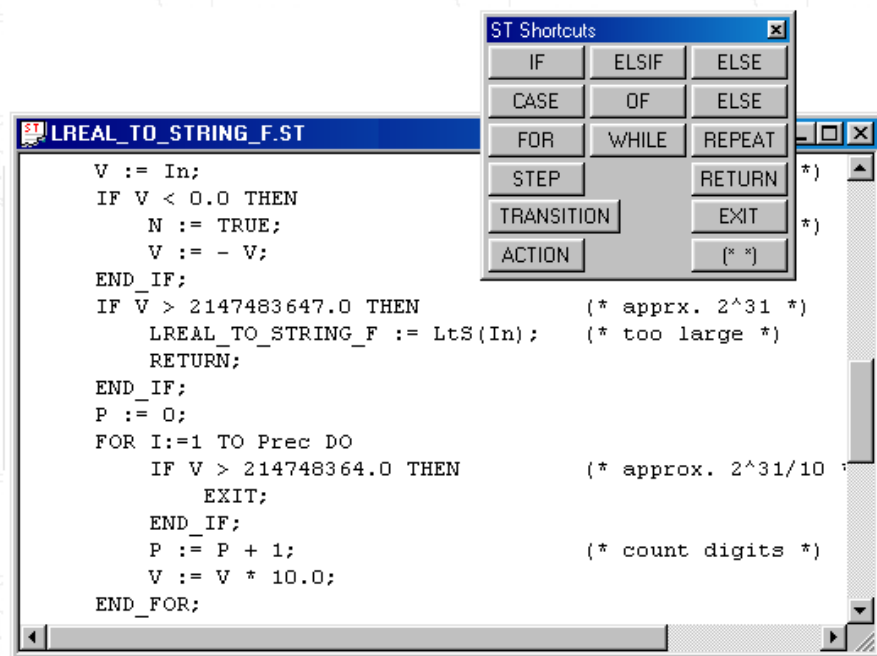**Structured Text (ST)** is a Pascal-like textual PLC programming language.



**Instruction list (IL)** uses mnemonic instructions from the ladder diagrams and sends the instructions to the PLC via a programming terminal.

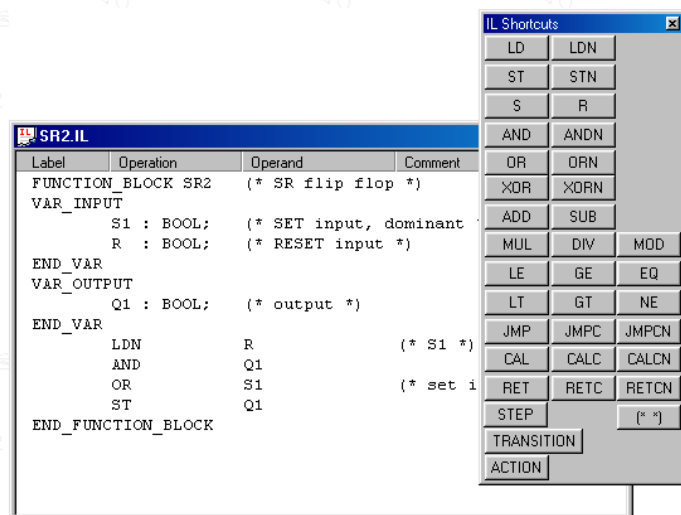Instruction List is one of the oldest, textual programming methods for PLCs. Large (and mostly incompatible) sets of instructions have been created. Instruction list reduced this set to a minimum and favours the usage of functions and function blocks for more complex tasks.



## PLC DVP ES (Delta Comp.)


 


### 2.1 ES2/EX2 Memory Map

| Specifications        |   |                  |  |  |                      |
|-----------------------|---|------------------|--|--|----------------------|
| Control Method        |   |                  | Stored program, cyclic scan system                         |  |                      |
| I/O Processing Method |   |                  | Batch processing method (when END instruction is executed) |  |                      |
| Execution Speed       |   |                  | LD instructions – 0.54μs, MOV instructions – 3.4μs         |  |                      |
| Program language      |   |                  | Instruction List + Ladder + SFC                            |  |                      |
| Program Capacity      |   |                  | 15872 steps  |  |                      |
| Bit Contacts          | X | External inputs  |  | X0~X377, octal number system, 256 points max, (*4)                                       | Total<br>256+16 I/O  |
|                       | Y | External outputs |  | Y0~Y377, octal number system, 256 points max, (*4)                                       |                      |
|                       | M | Auxiliary relay  | General  | M0~M511, 512 points, (*1)<br>M768~M999, 232 points, (*1)<br>M2000~M2047, 48 points, (*1) | Total<br>4096 points |
|                       |   |                  | Latched  | M512~M767, 256 points, (*2)<br>M2048~M4095, 2048 points, (*2)                            |                      |
|                       |   |                  | Special  | M1000~M1999, 1000 points, some are latched   |                      |

|  |   |         |   |   |                     |
|--|---|---------|---|---|---------------------|
|  | T | Timer   | 100ms<br>(M1028=ON,<br>T64~T126:<br>10ms) | T0~T126, 127 points, (*1)<br>T128~T183, 56 points, (*1)         | Total<br>256 points |
|  |   |         |   | T184~T199 for Subroutines, 16 points, (*1)                      |                     |
|  |   |         |   | T250~T255(accumulative), 6 points (*1)                          |                     |
|  |   |         | 10ms<br>(M1038=ON,<br>T200~T245: 1ms)     | T200~T239, 40 points, (*1)                                      |                     |
|  |   |         |   | T240~T245(accumulative), 6 points, (*1)                         |                     |
|  |   |         | 1ms                                       | T127, 1 points, (*1)<br>T246~T249(accumulative), 4 points, (*1) |                     |
|  | C | Counter | 16-bit count up                           | C0~C111, 112 points, (*1)<br>C128~C199, 72 points, (*1)         | Total<br>232 points |
|  |   |         |   | C112~C127, 16 points, (*2)                                      |                     |
|  |   |         |   | C200~C223, 24 points, (*1)                                      |                     |
|  |   |         | 32-bit count up/down                      | C224~C231, 8 points, (*2)                                       |                     |




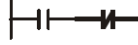





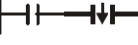



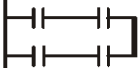


| Specifications |   |   |                                     |  |                      |
|----------------|---|---|-------------------------------------|--|----------------------|
|                |   | 32bit<br>high-<br>speed<br>count<br>up/down | Soft-<br>ware                       | C235~C242, 1 phase 1 input, 8<br>points, (*2)          | Total<br>23 points   |
|                |   |   | Hard-<br>ware                       | C232~C234, 2 phase 2 input, 3<br>points, (*2)          |                      |
|                |   |   |                                     | C243~C244, 1 phase 1 input, 2<br>points, (*2)          |                      |
|                |   |   |                                     | C245~C250, 1 phase 2 input, 6<br>points, (*2)          |                      |
|                |   |   |                                     | C251~C254 2 phase 2 input, 4<br>points, (*2)           |                      |
|                | S | Step<br>point                               | Initial step point                  | S0~S9, 10 points, (*2)                                 | Total 1024<br>points |
|                |   |   | Zero point return                   | S10~S19, 10 points (use with IST<br>instruction), (*2) |                      |
|                |   |   | Latched                             | S20~S127, 108 points, (*2)                             |                      |
|                |   |   | General                             | S128~S911, 784 points, (*1)                            |                      |
|                |   |   | Alarm                               | S912~S1023, 112 points, (*2)                           |                      |
|                | T | Current value                               | T0~T255, 256 words                  |  |                      |
|                | C | Current value                               | C0~C199, 16-bit counter, 200 words  |  |                      |
|                |   |   | C200~C254, 32-bit counter, 55 words |  |                      |

|               |   |                     |                     |  |                       |
|---------------|---|---------------------|---------------------|--|-----------------------|
| Word Register | D | Data register       | General             | D0~D407, 408 words, (*1)<br>D600~D999, 400 words, (*1)<br>D3920~D9999, 6080 words, (*1)  | Total<br>10000 points |
|               |   |                     | Latched             | D408~D599, 192 words, (*2)<br>D2000~D3919, 1920 words, (*2)  |                       |
|               |   |                     | Special             | D1000~D1999, 1000 words, some are latched  |                       |
|               |   |                     | For Special mudules | D9900~D9999 , 100 words , (*1), (*5)   |                       |
|               |   |                     | Index               | E0~E7, F0~F7, 16 words, (*1)   |                       |
| Pointer       | N | Master control loop |                     | N0~N7, 8 points  |                       |
|               | P | Pointer             |                     | P0~P255, 256 points  |                       |
|               | I | Interrupt Service   | External interrupt  | I000/I001(X0), I100/I101(X1), I200/I201(X2), I300/I301(X3), I400/I401(X4), I500/I501(X5), I600/I601(X6), I700/I701(X7), 8 points (01: rising-edge trigger  , 00: falling-edge trigger  ) |                       |

| Specifications      |   |             |  |   |
|---------------------|---|-------------|--|---|
|                     |   |             | Timer interrupt  | I602~I699, I702~I799, 2 points (Timer resolution = 1ms)                                       |
|                     |   |             | High-speed counter interrupt   | I010, I020, I030, I040, I050, I060, I070, I080, 8 points                                      |
|                     |   |             | Communication interrupt  | I140(COM1), I150(COM2), I160(COM3), 3 points, (*3)  |
| Constant            | K | Decimal     |  | K-32,768 ~ K32,767 (16-bit operation),<br>K-2,147,483,648 ~ K2,147,483,647 (32-bit operation) |
|                     | H | Hexadecimal |  | H0000 ~ HFFFF (16-bit operation),<br>H00000000 ~ HFFFFFFFF (32-bit operation)                 |
| Serial ports        |   |             | COM1: built-in RS-232 ((Master/Slave)<br>COM2: built-in RS-485 (Master/Slave)<br>COM3: built-in RS-485 (Master/Slave)<br>COM1 is typically the programming port. |   |
| Real Time Clock     |   |             | Year, Month, Day, Week, Hours, Minutes, Seconds  |   |
| Special I/O Modules |   |             | Up to 8 special I/O modules can be connected   |   |




The structure of a ladder diagram:

| Structure   | Explanation                                 | Instruction       | Devices Used     |
|---|---|-------------------|------------------|
|    | Normally open, contact A                    | LD                | X, Y, M, S, T, C |
|    | Normally closed, contact B                  | LDI               | X, Y, M, S, T, C |
|    | Normally open in series connection          | AND               | X, Y, M, S, T, C |
|    | Normally closed in series connection        | ANI               | X, Y, M, S, T, C |
|    | Normally open in parallel connection        | OR                | X, Y, M, S, T, C |
|    | Normally closed in parallel connection      | ORI               | X, Y, M, S, T, C |
|    | Rising-edge trigger switch                  | LDP               | X, Y, M, S, T, C |
|    | Falling-edge trigger switch                 | LDF               | X, Y, M, S, T, C |
|  | Rising-edge trigger in series connection    | ANDP              | X, Y, M, S, T, C |
|  | Falling-edge trigger in series connection   | ANDF              | X, Y, M, S, T, C |
|  | Rising-edge trigger in parallel connection  | ORP               | X, Y, M, S, T, C |
|  | Falling-edge trigger in parallel connection | ORF               | X, Y, M, S, T, C |
|  | Block in series connection                  | ANB               | -                |
|  | Block in parallel connection                | ORB               | -                |
|  | Multiple output                             | MPS<br>MRD<br>MPP | -                |
|  | Coil driven output instruction              | OUT               | Y, M, S          |



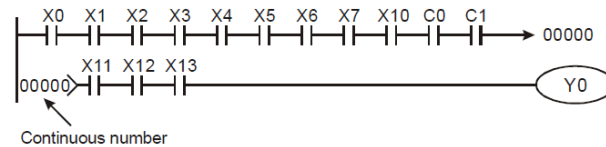
## How to Edit a PLC Ladder Diagram

The editing of the program should start from the left power line and ends at the right power line, a row after another. The drawing of the right power line will be omitted if edited from WPLSoft. A row can have maximum 11 contacts on it. If 11 is not enough, you can continuously connect more devices and the continuous number will be generated automatically. The same input points can be used repeatedly. See the figure below:




## Explanations on the basic structures in the ladder diagram:

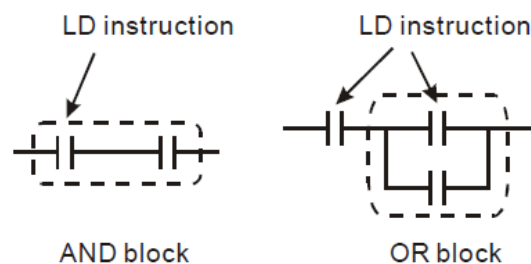
1. LD (LDI) instruction: Given in the start of a block.



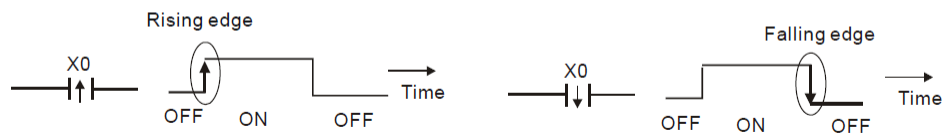The structure of LDP and LDF instructions are the same as that of LD instruction, and the two only differ in their actions. LDP and LDF instructions only act at the rising edge or falling edge when the contact is On, as shown in the figure below.




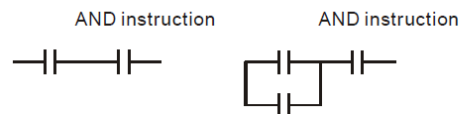2. AND (ANI) instruction: A single device connects to another single device or a block in series




The structure of ANDP and ANDF instructions are the same. ANDP and ANDF instructions only act at the rising edge or falling edge.

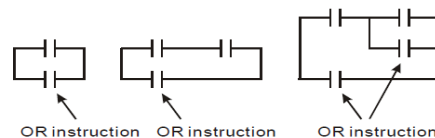3. OR (ORI) instruction: A single device connects to another single device or a block




The structure of ORP and ORF instructions are the same. ORP and ORF instructions only act at the rising edge or falling edge.

## EX 1

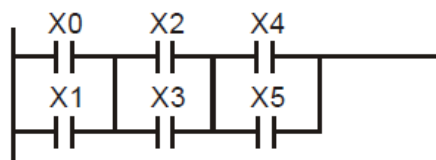

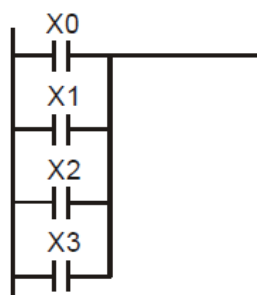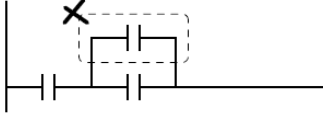
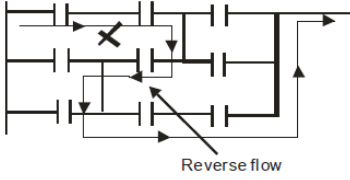

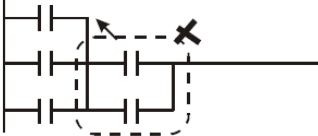
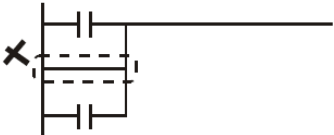
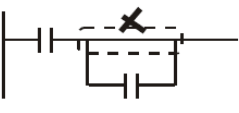
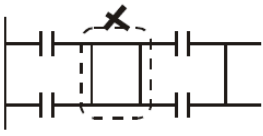
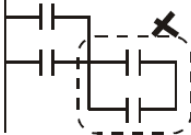
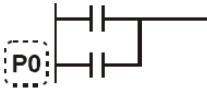
| Ideal way |    |
|-----------|----|
| LD        | X0 |
| OR        | X1 |
| LD        | X2 |
| OR        | X3 |
| ANB       |    |
| LD        | X4 |
| OR        | X5 |
| ANB       |    |

## EX2




| Ideal way |    |
|-----------|----|
| LD        | X0 |
| OR        | X1 |
| OR        | X2 |
| OR        | X3 |

## Incorrect Ladder

|   |   |
|---|---|
|    | OR operation upward is not allowed.   |
|    | "Reverse flow" exists in the signal circuit from the beginning of input to output.                                  |
|    | The up-right corner should output first.  |
|   | Combining or editing should be done from the up-left to the bottom-right. The dotted-lined area should be moved up. |
|  | Parallel operation with empty device is not allowed.  |
|  | Empty device cannot do operations with other devices.   |
|  | No device in the middle block.  |
|  | Devices and blocks in series should be horizontally aligned.  |
|  | Label P0 should be in the first row of a complete network.  |

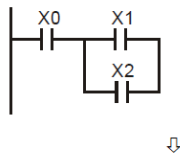
# Simplified Ladder

- When a series block is connected to a parallel block in series, place the block in the front to omit ANB instruction.



Ladder diagram complied into instruction

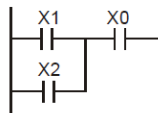
```
LD      X0
LD      X1
OR      X2
ANB
```



Ladder diagram complied into instruction


```
LD      X1
OR      X2
AND     X0
```

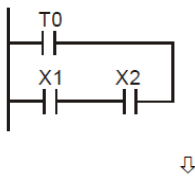- When a single device is connected to a block in parallel, place the block on top to omit ORB instruction.



Ladder diagram complied into instruction

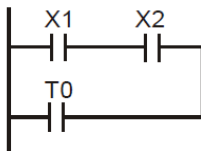
```
LD      T0
LD      X1
AND     X2
ORB
```



Ladder diagram complied into instruction


```
LD      X1
AND     X2
OR      T0
```

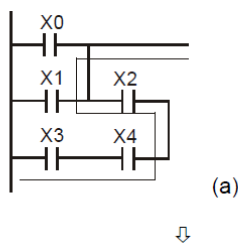- In diagram (a), the block on top is shorter than the block in the bottom, we can switch the position of the two blocks to achieve the same logic. Due to that diagram (a) is illegal, there is a "reverse flow" in it.



Ladder diagram complied into instruction

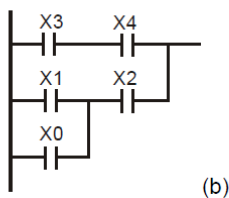
```
LD      X0
OR      X1
AND     X2
LD      X3
AND     X4
ORB
```



Ladder diagram complied into instruction


```
LD      X3
AND     X4
LD      X1
OR      X0
AND     X2
```

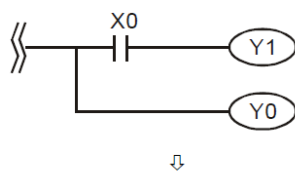- MPS and MPP instruction can be omitted when the multiple outputs in the same horizontal line do not need to operate with other input devices.



Ladder diagram complied into instruction
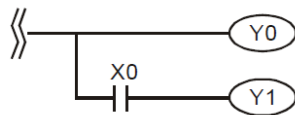
```
MPS
AND    X0
OUT    Y1
MPP
OUT    Y0
```



Ladder diagram complied into instruction

```
OUT    Y0
AND    X0
OUT    Y1
```


### Basic Program Designing Examples

#### ■ Start, Stop and Latched

In some application occasions, we need to use the transient close/open buttons for the start and stop of an equipment. To maintain its continuous action, you have to design latched circuits.

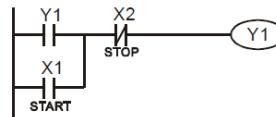
##### Example 1: Stop first latched circuit

When the normally open contact X1 = On and the normally closed contact X2 = Off, Y1 will be On. If you make X2 = On at this time, Y1 will be Off. It is the reason why this is called "stop first".


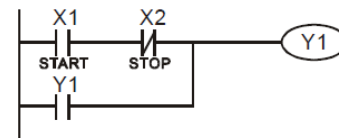
##### Example 2: Start first latched circuit

When the normally open contact X1 = On and the normally closed contact X2 = Off, Y1 will be On and latched. If you make X2 = On at this time, Y1 will continue to be On because of the latched contact. It is the reason why this is called "start first".





##### Example 3: Latched circuit for SET and RST instructions

See the diagram in the right hand side for the latched circuit consist of RST and SET instructions.

In the stop first diagram, RST is placed after SET. PLC executes the program from up to down, so the On/Off of Y1 will be determined upon its status in the end of the program.


Therefore, when X1 and X2 are enabled at the same time, Y1 will be Off. It is the reason why this is called "stop first".

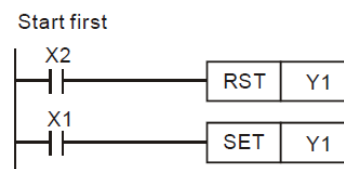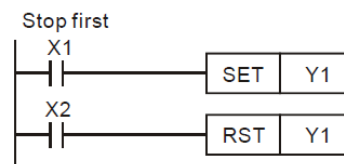In the start first diagram, SET is placed after RST. When X1 and X2 are enabled at the same time, Y1 will be On. It is the reason why this is called "start first".




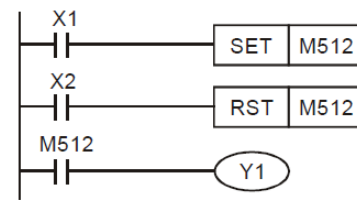
#### Example 4: Power shutdown latched

The auxiliary relay M512 is latched (see instruction sheets for DVP series PLC MPU). The circuit can not only be latched when the power is on, but also keep the continuity of the original control when the power is shut down and switched on again.





#### Frequently Used Control Circuit

##### Example 5: Conditional control

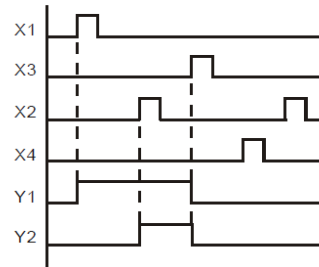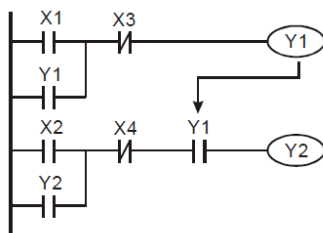


X1 and X3 enables and disables Y1; X2 and X4 enables and disables Y2, and all are latched. Due to that the normally open contact of Y1 is connected to the circuit of Y2 in series, Y1 becomes an AND condition for Y2. Therefore, only when Y1 is enabled can Y2 be enabled.

##### Example 6: Interlock control

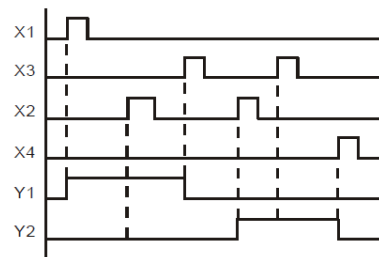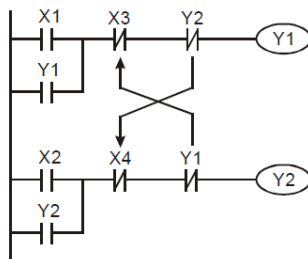

Which of the X1 and X2 is first enabled decides either the corresponding output Y1 or Y2 will be enabled first. Either Y1 or Y2 will be enabled at a time, i.e. Y1 and Y2 will not be enabled at the same time (the interlock). Even X1 and X2 are enabled at the same time, Y1 and Y2 will not be enabled at the same time due to that the ladder diagram program is scanned from up to down. In this ladder diagram, Y1 will be enabled first.



##### Example 7: Sequential control

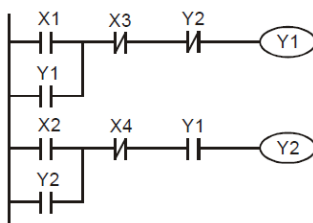

If we serially connect the normally closed contact of Y2 in example 5 to the circuit of Y1 as an AND condition for Y1 (as the diagram in the left hand side), the circuit can not only make Y1 as the condition for Y2, but also allow the stop of Y1 after Y2 is enabled. Therefore, we can make Y1 and Y2 execute exactly the sequential control.
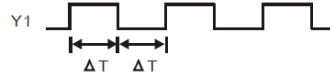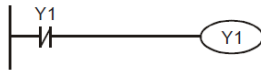
### Example 8: Oscillating circuit

An oscillating circuit with cycle  $\Delta T + \Delta T$



The ladder diagram above is a very simple one. When the program starts to scan the normally closed contact Y1, Y1 will be closed because coil Y1 is Off. When the program then scan to coil Y1 and make it On, the output will be 1. When the program scans to the normally closed contact Y1 again in the next scan cycle, because coil Y1 is On, Y1 will be open and make coil Y1 Off and output 0. The repeated scans will result in coil Y1 outputs oscillating pulses by the cycle  $\Delta T(\text{On}) + \Delta T(\text{Off})$ .

An oscillating circuit with cycle  $nT + \Delta T$

### Functions of timers:

The units of the timer are 1ms, 10ms and 100ms and the counting method is counting up. When the present value in the timer equals the set value, the output coil will be On. The set value should be a K value in decimal and the data register D can also be a set value.


The actual set time in the timer = timing unit  $\times$  set value

There are three types of timers:

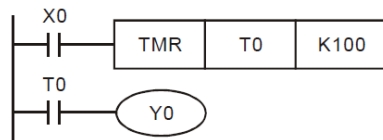
#### 1. General purpose timer:

For ES/SA series MPU: The timer executes once when the program reaches END instruction. When TMR instruction is executed, the output coil will be On when the timing reaches its target.

For EH2/SV/EH3/SV2 series MPU: The timer executes once when the program reaches TMR instruction. When TMR instruction is executed, the output coil will be On when the timing reaches its target.



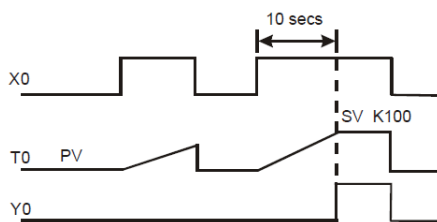- When X0 = On, The PV in timer T0 will count up by 100ms. When the PV = SV K100, the output coil T0 will be On.




- When X0 = Off or the power is off, the PV in timer T0 will be cleared as 0, and the output coil T0 will be Off.


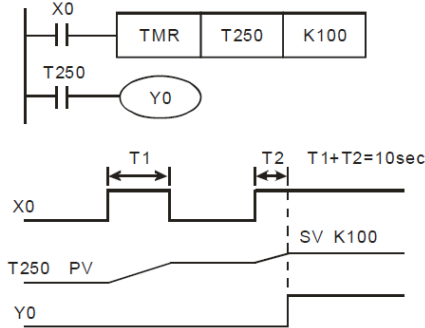
## 2. Accumulative type timer:

For ES/SA series MPU: The timer executes once when the program reaches END instruction. When TMR instruction is executed, the output coil will be On when the timing reaches its target.

For EH2/SV/EH3/SV2 series MPU: The timer executes once when the program reaches TMR instruction. When TMR instruction is executed, the output coil will be On when the timing reaches its target.




- When X0 = On, The PV in timer T250 will count up by 100ms. When the PV = SV K100, the output coil T0 will be On.
- When X0 = Off or the power is off, timer T250 will temporarily stop the timing and the PV remain unchanged. When X0 is On again, the timing will resume and the PV will count up and when the PV = SV K100, the output coil T0 will be On.

### 3:1 Delay ON Program
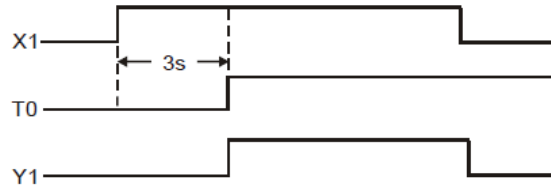
#### Control Purpose:


- Enabling the indicator to be ON after a 3 sec delay and OFF immediately by the switch



#### Devices:

| Device | Function                             |
|--------|--------------------------------------|
| X1     | X1 = ON when the switch is turned on |
| T1     | 3 sec timer, time base = 100ms       |
| Y1     | Output indicator                     |

#### Control Program:

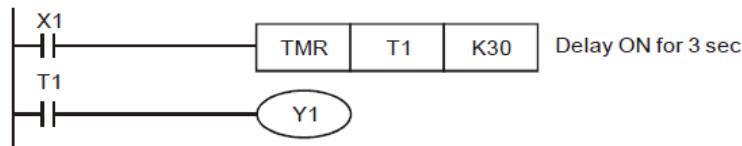


### 3:2
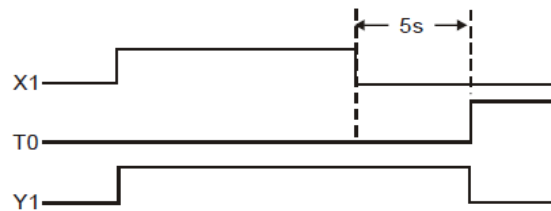
### 3.1 Delay OFF Program

Control Purpose:


- Enabling the indicator to be ON immediately and OFF after a 5 sec delay by the switch



Devices:

| Device | Function                               |
|--------|--|
| X1     | X1 = OFF when the switch is turned off |
| T1     | 5 sec timer. Time base = 100ms         |
| Y1     | Output indicator                       |


Control Program:

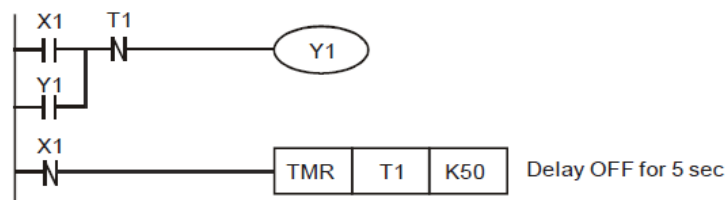
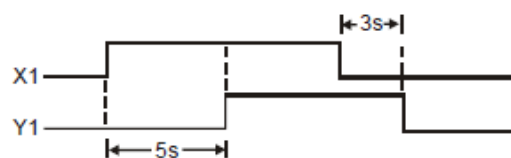
### 3.3 Delay ON/OFF Program

Control Purpose:


- Enabling the indicator to be ON after a 5 sec delay and OFF after a 3 sec delay by the switch




Devices:

| Device | Function                              |
|--------|---------------------------------------|
| X1     | X1 = ON when the switch is turned on. |
| T0     | 5 sec timer, time base = 100ms        |
| T1     | 3 sec timer, time base = 100ms        |
| Y1     | Output indicator                      |

Control Program:

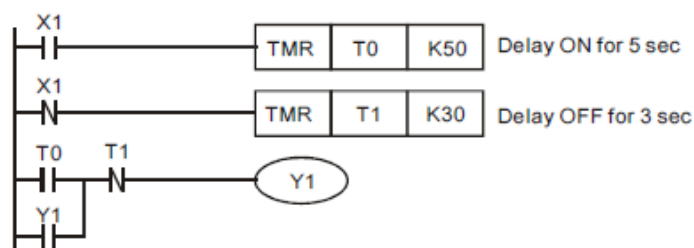

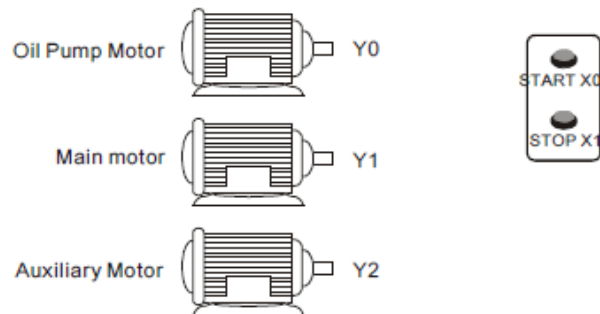
### 3.4 Sequential Delay Output (Starting 3 Motors Sequentially)



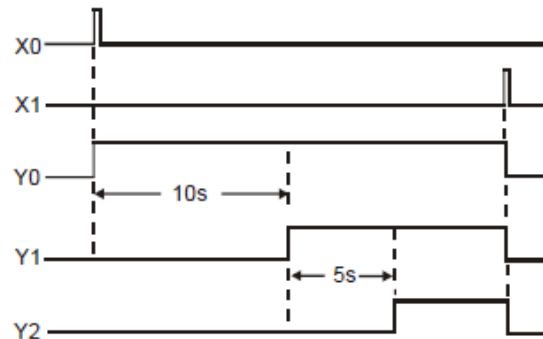
#### Control Purpose:

- Starting the oil pump motor immediately when START is pressed. The main motor will be started after a 10 sec delay and then the auxiliary motor after a 5 sec delay. In addition, stopping all motors immediately when STOP is pressed.



| Device | Function                       |
|--------|--------------------------------|
| X0     | X0 = ON when START is pressed. |
| X1     | X1 = ON when STOP is pressed.  |
| T0     | 10 sec timer. Time base: 100ms |
| T1     | 5 sec timer. Time base: 100ms  |
| Y0     | Starting the oil pump motor    |
| Y1     | Starting the main motor        |
| Y2     | Starting the auxiliary motor   |

## Control Program:

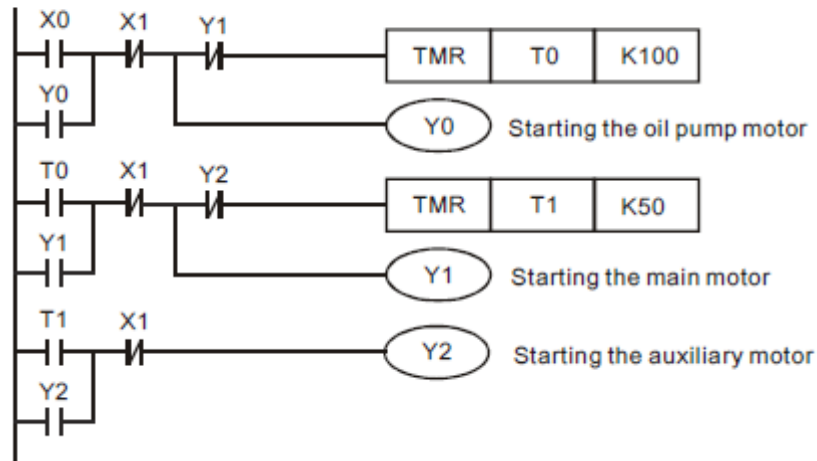


## Program Description:



- When START is pressed, the NO contact X0 will be activated, which makes Y0 to be ON and latched. The oil pump motor will start the lube system. At the same time, [TMR T0 K100] instruction will be executed. When T0 reaches its set value of 10 sec, the NO contact T0 will be ON.
- When the NO contact T0 is ON, Y1 will be ON and latched, which starts the main motor and stops timer T0. At the same time, [TMR T1 K50] is executed, and the NO contact T1 will be ON when timer T1 reaches its set value.
- When the NO contact T1 is ON, Y2 will be ON and latched, which starts the auxiliary motor and stops T1.
- When STOP is pressed, the NC contact X1 will be activated, which makes Y0, Y1 and Y2 OFF. The oil pump motor, main motor and auxiliary motor will stop working.
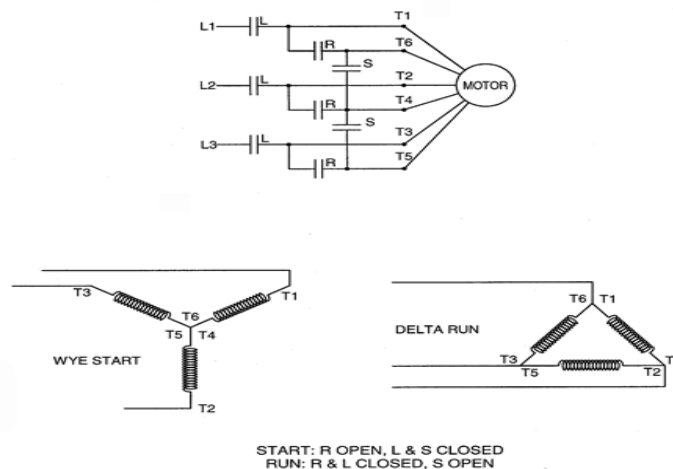
## Start Delta Run

This method is actually reduced voltage but is accomplished by changing the motor phase connections such that a winding that is designed to run with phase voltage equal to line voltage on delta connection is wye connected for starting to put less than line voltage on each phase. Effectively, the voltage is reduced by 1.732 factor. The impedance seen by the power system is 3 times the impedance of the delta run connection.


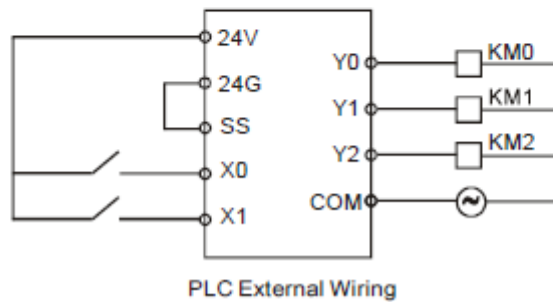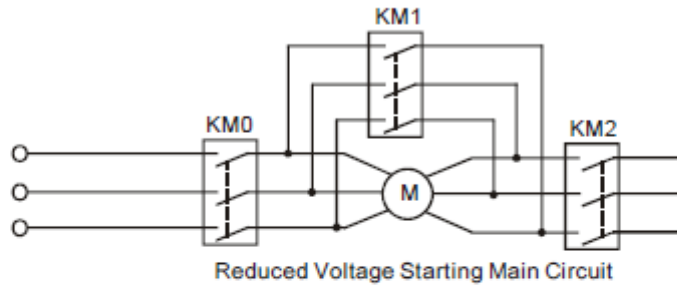
## Star-Delta Reduced Voltage Starter Control




### Control Purpose:

- Usually the starting current of the three-phase AC asynchronous motor is 5~7 times larger than the rated current. To reduce the effect of the starting current on the electrified wire fence, a star-delta reduced voltage starter should be applied.
- Starting process of a star-delta reduced voltage starter:  
When the switch is turned on, the contactors of both motor starter and "Star Reduced Voltage Starter" will be enabled first. After a 10 sec delay, the contactor of "Star Reduced Voltage Starter" will be disabled. Finally, the contactor of "Delta Reduced Voltage Starter" will be enabled after 1 sec, which operates the main motor circuit normally. The control purpose in this process is to assure the contactor of "Star Reduced Voltage Starter" is disabled completely before the contactor of "Delta Reduced Voltage Starter" is enabled.

### Devices:

| Device | Function                                      |
|--------|---|
| X0     | X0 = ON when START is pressed.                |
| X1     | X1 = ON when STOP is pressed.                 |
| T1     | 10 sec timer. Time base: 100ms                |
| T2     | 1 sec timer. Time base: 100ms                 |
| Y0     | Motor starting contactor KM0                  |
| Y1     | "Star Reduced Voltage Starter" contactor KM1  |
| Y2     | "Delta Reduced Voltage Starter" contactor KM2 |

### Control Program:

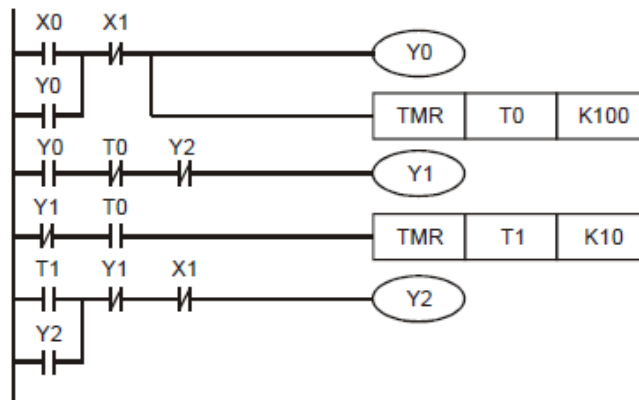

### Program Description:

- X0 = ON when START is pressed. Y0 will be ON and latched. The motor starting contactor KM0 will be ON and the timer T0 will start to count for 10 sec. At the same time, because Y0 = ON, T0 = OFF and Y2 = OFF, Y1 will be ON. The "Star Reduced Voltage Starter" contactor KM1 will be activated.
- When timer T0 reaches its set value, T0 will be ON and Y1 will be OFF. Timer T1 will start to count for 1 sec. After 1 sec, T1 = ON and Y2 = ON. "Delta Reduced Voltage Starter" contactor KM2 will be activated.
- X1 = ON when STOP is pressed. Y0, Y1 and Y2 will be OFF and the motor will stop running no matter it is in starting mode or running mode.

## Numbering and Functions of Counters [C]

No. of counters (in decimal)

### ■ ES/EX/SS series MPU:

|  |   |   |                     |
|--|---|---|---------------------|
| Counter C                                    | 16-bit counting up, for general purpose | C0 ~ C111, 112 points. Fixed to be non-latched.               | Total<br>141 points |
|  | 16-bit counting up, for latched         | C112 ~ C127, 16 points. Fixed to be latched.                  |                     |
| 32-bit counting up/down high-speed counter C | 1-phase 1 input                         | C235 ~ C238, C241, C242, C244, 7 points. Fixed to be latched. |                     |
|  | 1-phase 2 inputs                        | C246, C247, C249, 3 points. Fixed to be latched.              |                     |
|  | 2-phase 2 inputs                        | C251, C252, C254, 3 points. Fixed to be latched.              |                     |

### Functions of counters:


When the pulse input signals of the counter go from Off to On and the present value in the counter equals the set value, the output coil will be On. The set value should be a K value in decimal and the data register D can also be a set value.

#### **16-bit counters C0 ~ C199:**


1. The setup range of 16-bit counter: K0 ~ K32,767. K0 is the same as K1. The output contact will be On immediately when the first counting starts.
2. PV in the general purpose counter will be cleared when the power of the PLC is switched off. If the counter is a latched type, the counter will retain the PV and contact status before the power is off and resume the counting after the power is on again.
3. If you use MOV instruction, WPLSoft or HPP to send a value bigger than the SV to the present value register of C0, next time when X1 goes from Off to On, the contact of counter C0 will be On and its PV will equal SV.
4. The SV in the counter can be constant K (set up directly) or the values in register D (set up indirectly, excluding special data registers D1000~ D1999).
5. If you set up a constant K as the SV, it should be a positive value. Data register D as SV can be positive or negative. When the PV reaches up to 32,767, the next PV will turn to -32,768.

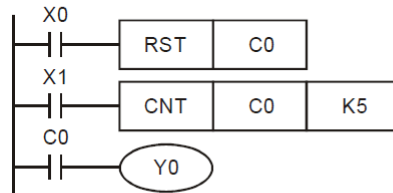Example:

```
LD    X0
RST   C0
LD    X1
CNT   C0 K5
LD    C0
OUT   Y0
```




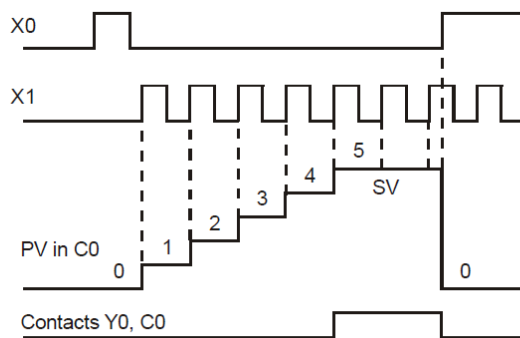- a) When X0 = On, RST instruction will be executed, PV in C0 will be "0" and the output contact will be reset to Off.
- b) When X1 goes from Off to On, the PV in the counter will count up (plus 1).
- c) When the counting of C0 reaches SV K5, the contact of C0 will be On and PV of C0 = SV = K5. The X1 trigger signal comes afterwards will not be accepted by C0 and the PV of C0 will stay at K5.





Product Mass Packaging

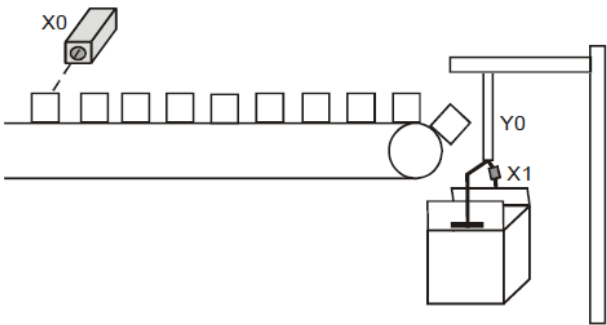


Control Purpose:


- Once the photoelectric sensor detects 10 products, the robotic arm will begin to pack up. When the action is completed, the robotic arm and the counter will be reset.

Devices:

| Device | Function  |
|--------|---|
| X0     | Photoelectric sensor for counting products. X0 = ON when products are detected. |
| X1     | Robotic arm action completed sensor. X1 = ON when packing is completed.         |
| C0     | Counter: 16-bit counting up (general purpose)                                   |
| Y0     | Robotic arm for packing   |

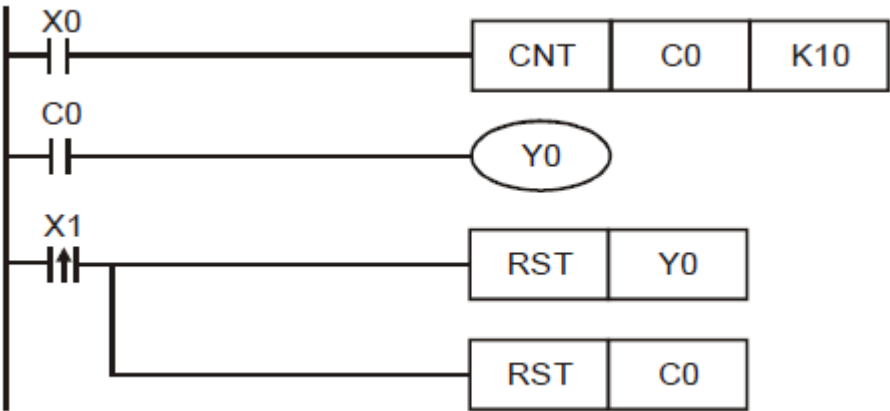

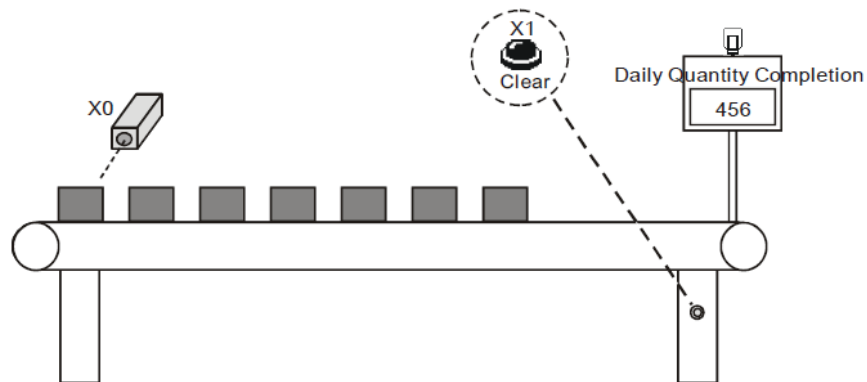
### Daily Production Record (16-bit Counting Up Latched Counter)



#### Control Purpose:

- The production line may be powered off accidentally or turned off for noon break. The program is to control the counter to retain the counted number and resume counting after the power is ON again.
- When the daily production reaches 500, the target completed indicator will be ON to remind the operator for keeping a record.
- Press the Clear button to clear the history records. The counter will start counting from 0 again.

| Device | Function  |
|--------|---|
| X0     | Photoelectric sensor. Once detecting the products, X0 will be ON. |
| X1     | Clear button  |
| C120   | Counter: 16-bit counting up (latched)                             |
| Y0     | Target completed indicator  |

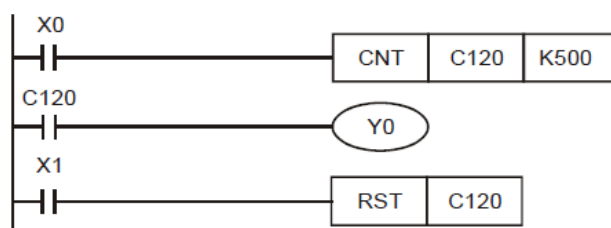

# Up/Down Counters

DCNT instruction enables the 32-bit high-speed counters C200 ~ C255.

For general purpose addition/subtraction counters C200~C234. When DCNT instruction is set from "Off" to "On", the present value in the counter will count up (plus 1) or count down (minus 1) according to the modes set in special M1200 ~ M1234.


For high-speed addition/subtraction counters C235 ~ C255. When the high-speed counter pulses go from "OFF" to "ON", the counter is executed.

High-speed counter pulse input device: X0 ~ X17

Counting actions: Counting up (present value plus "1"); counting down (present value minus "1")


When DCNT instruction goes "OFF", the counter stops counting, but the present value will not be cleared. RST C2XX instruction is for clearing the present values and contacts. High-speed addition/subtraction counters C235 ~ C254 can use assigned external input terminals to clear the present value and contacts.
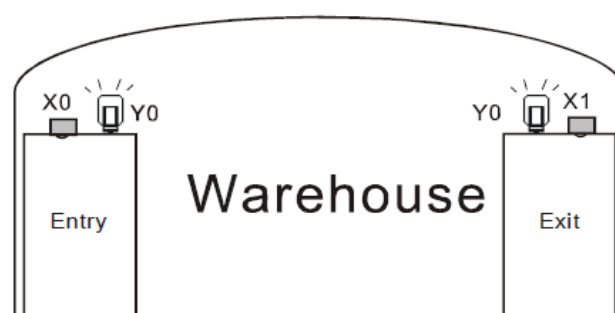
## Products Amount Calculation (32-bit Counting Up/Down Counter)




- This program is used for monitoring the product amount in the warehouse by photoelectric sensors at both entry and exit. When the amount reaches 40,000, the alarm will be enabled.

| Device | Function   |
|--------|--|
| X0     | Photoelectric sensors for monitoring incoming goods. X0 = ON when incoming detected. |
| X1     | Photoelectric sensors for monitoring outgoing goods. X1 = ON when outgoing detected. |
| M1216  | Counting mode of C216(ON: counting down)   |
| C216   | 32-bit counting up/down counter  |
| Y0     | Alarm  |

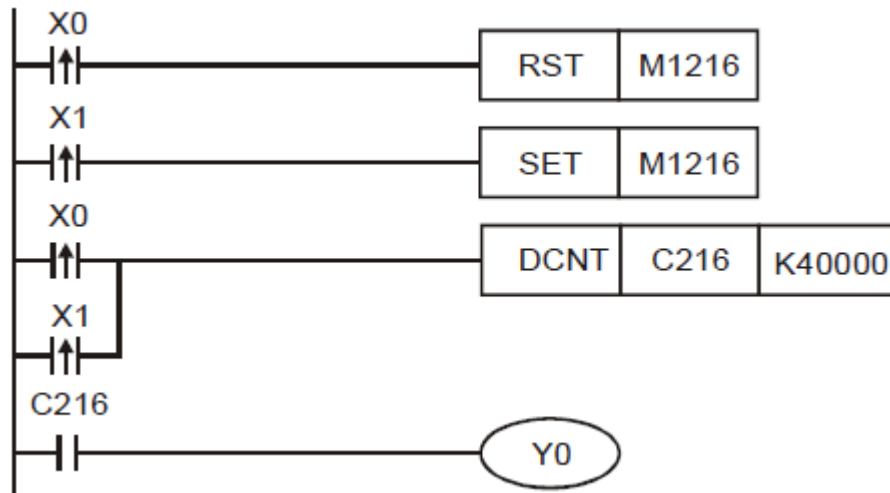

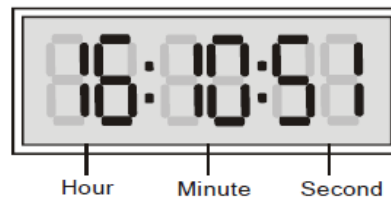
#### 24-hour Clock Operated by 3 Counters



- Using 3 counters together with the flag of M1013 (1s clock pulse) to operate a 24-hour clock.

| Device | Function         |
|--------|------------------|
| C0     | count per second |
| C1     | count per minute |
| C2     | count per hour   |
| M1013  | 1s clock pulse   |

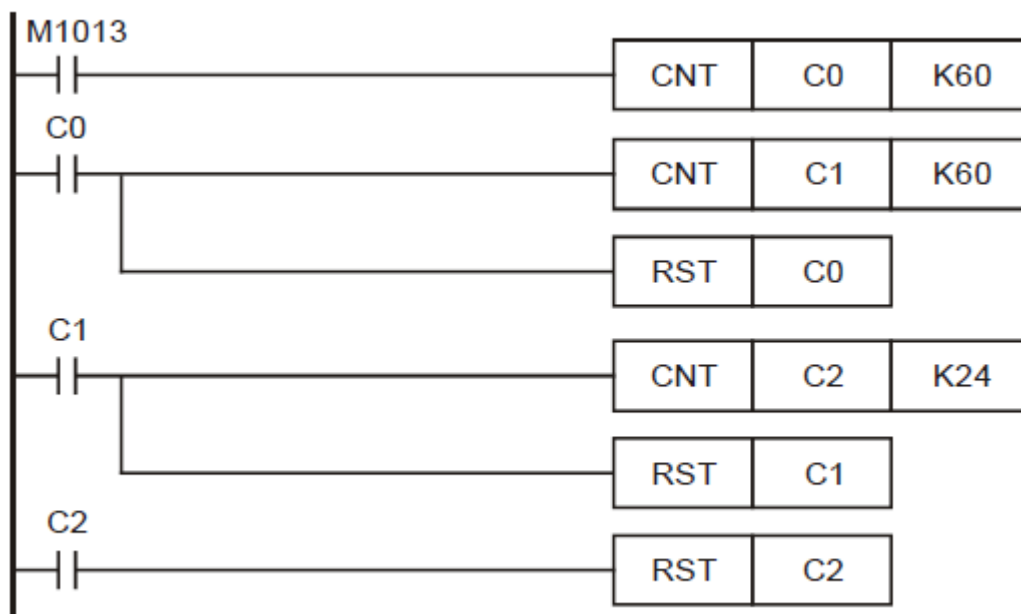

### 32-bit high-speed addition/subtraction counters C235 ~ C255:

1. The setup range of 32-bit counter: K-2,147,483,648 ~ K2,147,483,647
2. Addition or subtraction of C235 ~ C244 is designated by On/Off status of special auxiliary relays M1235 ~ M1244. For example, when M1235 = Off, C235 will be an addition counter; when M1235 = On, C235 will be a subtraction counter.
3. Addition or subtraction of C246 ~ C255 is designated by On/Off status of special auxiliary relays M1246 ~ M1255. For example, when M1246 = Off, C246 will be an addition counter; when M1246 = On, C246 will be a subtraction counter.
4. The SV can be constant K or data register D (excluding special data registers D1000 ~ D1999). Data register D as SV can be a positive or negative value and an SV will occupy two consecutive data registers.
5. If using DMOV instruction, WPLSoft or HPP to send a value which is large than the setting to any high-speed counter, next time when the input point X of the counter goes from Off to On, this contact will remain unchanged and it will perform addition and subtraction with the present value.
6. When the PV reaches up to 2,147,483,647, the next PV will turn to -2,147,483,648. When the PV reaches down to -2,147,483,648, the next PV will turn to 2,147,483,647.

■ High-speed counters for ES/EX/SS series MPU, total bandwidth: 20kHz

| Type<br>Input | 1-phase input |      |      |      |      |      |      | 1-phase 2 inputs |      |      | 2-phase 2 inputs |      |      |
|---------------|---------------|------|------|------|------|------|------|------------------|------|------|------------------|------|------|
|               | C235          | C236 | C237 | C238 | C241 | C242 | C244 | C246             | C247 | C249 | C251             | C252 | C254 |
| X0            | U/D           |      |      |      | U/D  |      | U/D  | U                | U    | U    | A                | A    | A    |
| X1            |               | U/D  |      |      | R    |      | R    | D                | D    | D    | B                | B    | B    |
| X2            |               |      | U/D  |      |      | U/D  |      |                  | R    | R    |                  | R    | R    |
| X3            |               |      |      | U/D  |      | R    | S    |                  |      | S    |                  |      | S    |

U: Progressively increasing input  
D: Progressively decreasing input




A: A phase input  
B: B phase input

S: Input started  
R: Input cleared

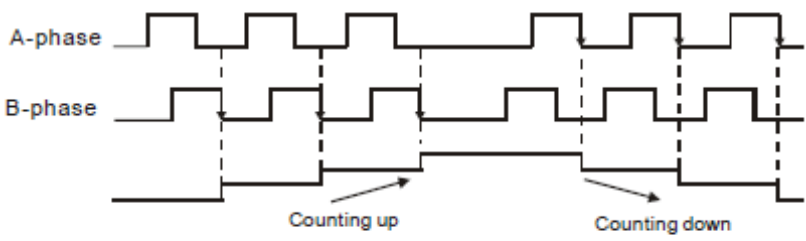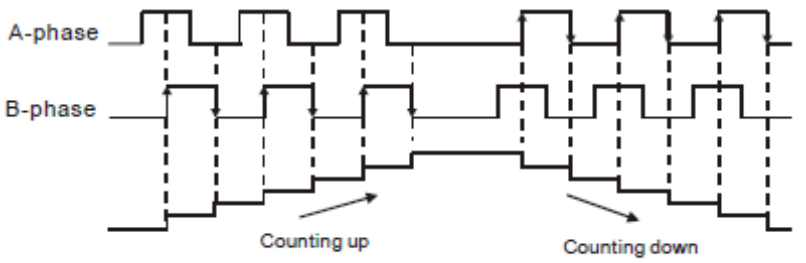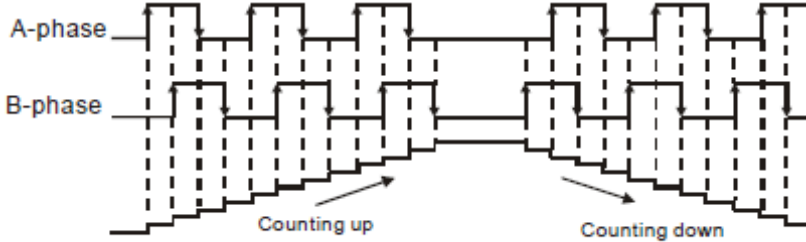
- Input points X0 and X1 can be planned as counters of higher speed with 1-phase 1 input reaching 20kHz. But the two counting frequencies added together has to be smaller or equal 20kHz. If the input is a 2-phase 2 input signal, the counting frequency will be approximately 4kHz. The 1-phase input of high-speed counters X2 and X3 and reach 10kHz.









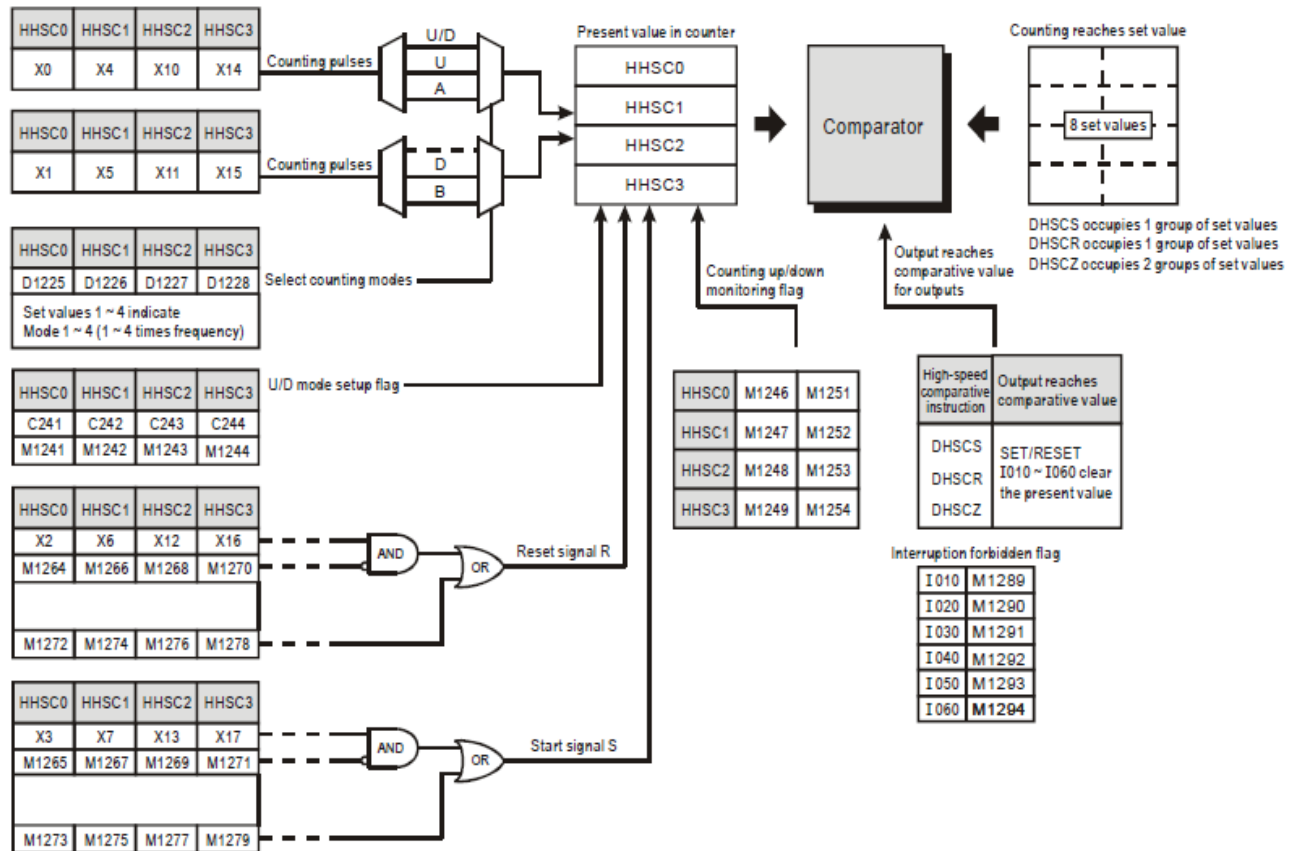











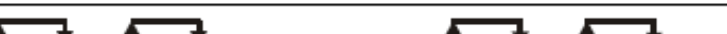

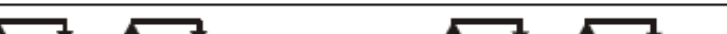









■ Features of counter:

|                    | 16 bits counters  | 32 bits counters  |  |
|--------------------|---|---|--|
| Type               | General purpose   | General purpose   | High speed   |
| Counting direction | Counting up   | Counting up, counting down  |  |
| Set value          | 0 ~ 32,767  | -2,147,483,648 ~ +2,147,483,647   |  |
| SV designation     | Constant K or data register D   | Constant K or data register D (designating 2 values)  |  |
| Present value      | Counting will stop when the SV is reached.  | Counter will continue when the SV is reached.   |  |
| Output contact     | On and being retained when the counting reaches SV.   | On and keeps being On when counting up reaches SV.<br>Reset to Off when counting down reaches SV. |  |
| Reset              | PV will be return to 0 when RST instruction is executed and the contact will be reset to Off. |   |  |
| Contact action     | Acts when the scanning is completed.  | Acts when the scanning is completed.  | Acts immediately when the counting reaches its target, has nothing to do with the scan period. |

| Counting mode    |                          | Counting wave pattern   |
|------------------|--------------------------|---|
| 2-phase 2 inputs | 1<br>(Normal frequency)  |   |
|                  | 2<br>(Double frequency)  |   |
|                  | 4<br>(4 times frequency) |  |





| Counting modes      |                          | Wave pattern  |  |
|---------------------|--------------------------|---|--|
| Type                | Set value in special D   | Counting up(+1)   | Counting down(-1)  |
| 1-phase<br>1 input  | 1<br>(Normal frequency)  | U/D <br>U/D FLAG  | <br>     |
|                     | 2<br>(Double frequency)  | U/D <br>U/D FLAG  | <br>     |
| 1-phase<br>2 inputs | 1<br>(Normal frequency)  | U <br>D           | <br>     |
|                     | 2<br>(Double frequency)  | U <br>D           | <br>     |
| 2-phase<br>2 inputs | 1<br>(Normal frequency)  | A <br>B           | <br>     |
|                     | 2<br>(Double frequency)  | A <br>B           | <br>     |
|                     | 3<br>(Triple frequency)  | A <br>B       | <br> |
|                     | 4<br>(4 times frequency) | A <br>B       | <br> |


### 1-phase 1 input high-speed counter

Example:


```

LD    X10
RST   C241
LD    X11
OUT   M1241
LD    X12
DCNT  C241 K5
LD    C241
OUT   Y0

```

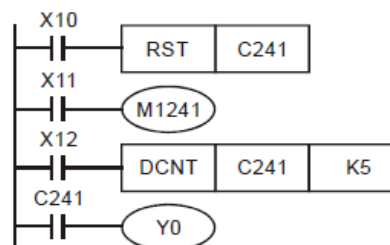

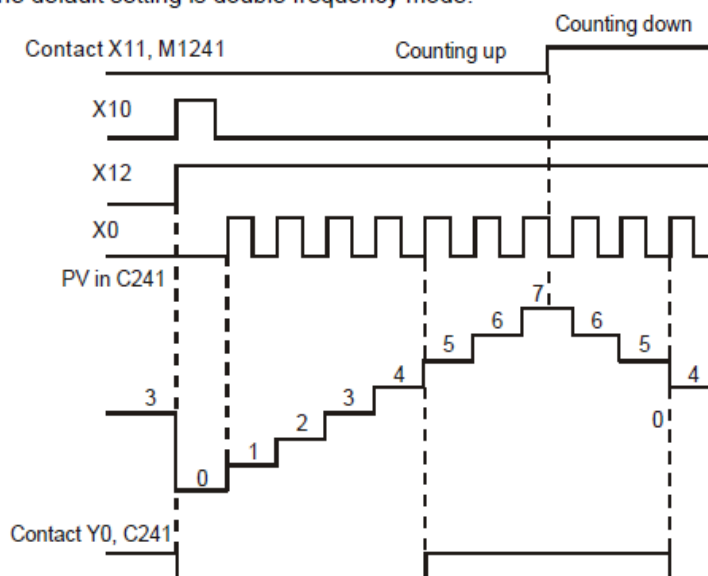
1. X11 drives M1241 to determine whether C241 is an addition or subtraction counter.
2. When X10 is On, RST instruction will be executed and the PV in C241 will be cleared to "0" and the contact will be Off.
3. In C241, when X12 is On and C241 receives the signals from X0, the PV in the counter will count up (plus 1) or count down (minus 1).
4. When the counting of C241 reaches SV K5, the contact of C241 will be On. If there are still input signals from X0, the counting will continue.
5. C241 in ES/EX/SS and SA/SX/SC series MPU has external input signals to reset X1.
6. C241 in EH/EH2/SV series MPU has external input signals to reset X2 and start X3.
7. The external input contact of reset signal of C241 (HHSC0) in EH/EH2/SV series MPU is disabled by M1264. The external input contact of start signal is disabled by M1265.
8. The internal input contact of reset signal of C241 (HHSC0) in EH/EH2/SV series MPU is disabled by M1272. The internal input contact of start signal is disabled by M1273.
9. The counting modes (normal frequency or double frequency) of C246 (HHSC0) in EH/EH2/SV series MPU can be set up by D1225. The default setting is double frequency mode.



## 1-phase 2 inputs high-speed counter


Example:

```
LD    X10
RST   C246
```

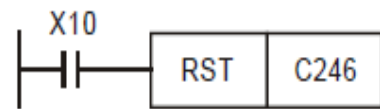

```
LD    X11
DCNT  C246 K5
LD    C246
OUT   Y0
```

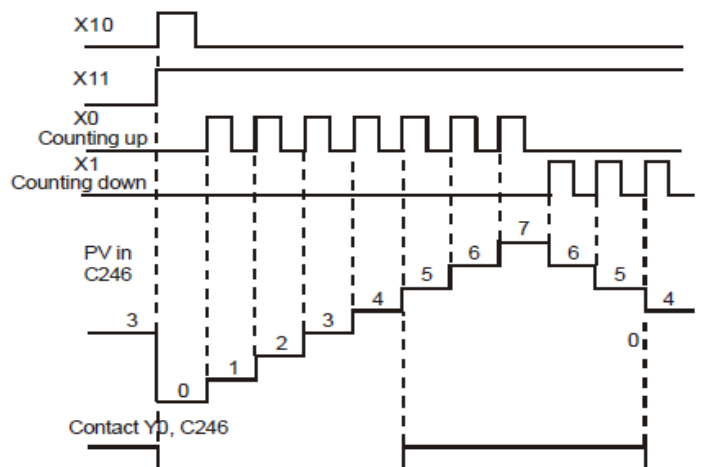1. When X10 is On, RST instruction will be executed. The PV in C246 will be cleared to "0" and the output contact will be reset to be Off.
2. In C246, when X11 is On and C246 receives the signals from X0, the PV in the counter will count up (plus 1) or count down (minus 1).
3. When the counting of C246 reaches SV K5, the contact of C246 will be On. If there are still input signals from X0, the counting will continue.
4. C246 in EH/EH2/SV series MPU has external input signals to reset X2 and start X3.




5. The counting modes (normal frequency or double frequency) of C246 (HHSC0) in EH/EH2/SV series MPU can be set up by D1225. The default setting is double frequency mode.
6. The external input contact of reset signal of C246 (HHSC0) in EH/EH2/SV series MPU is disabled by M1264. The external input contact of start signal is disabled by M1265.
7. The internal input contact of reset signal of C246 (HHSC0) in EH/EH2/SV series MPU is disabled by M1272. The internal input contact of start signal is disabled by M1273.

## 2-phase AB input high-speed counter

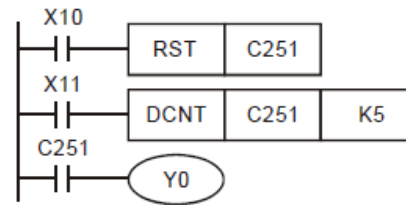Example:


```



LD      X10
RST     C251
LD      X11
DCNT    C251 K5
LD      C251
OUT     Y0
  
```





1. When X10 is On, RST instruction will be executed. The PV in C251 will be cleared to "0" and the output contact will be reset to be Off.
2. In C251, when X11 is On and C251 receives the A-phase signals from X0 and B-phase signals from X1, the PV in the counter will count up (plus 1) or count down (minus 1). You can select different counting modes if you use EH/EH2/SV series MPU.
3. When the counting of C251 reaches SV K5, the contact of C251 will be On. If there are still input signals coming in, the counting will continue.
4. The counting modes (normal frequency, double frequency or 4 times frequency) of C251 (HHSC0) in ES/SA series MPU can be set up by D1022. The default setting is double frequency mode.
5. C251 in EH/EH2/SV series MPU has external input signals to reset X2 and start X3.
6. The counting modes (normal frequency, double frequency, triple frequency or 4 times frequency) of C251 (HHSC0) in EH/EH2/SV series MPU can be set up by D1225. The default setting is double frequency mode.
7. The external input contact of reset signal of C246 (HHSC0) in EH/EH2/SV series MPU is disabled by M1264. The external input contact of start signal is disabled by M1265.
8. The internal input contact of reset signal of C246 (HHSC0) in EH/EH2/SV series MPU is disabled by M1272. The internal input contact of start signal is disabled by M1273.
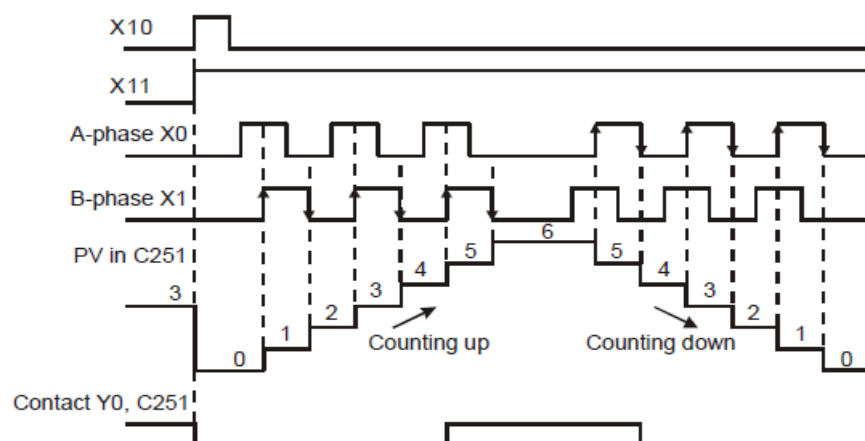
## ES/EX/SS and SA/SX/SC series MPU (double frequency)





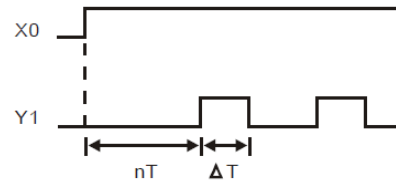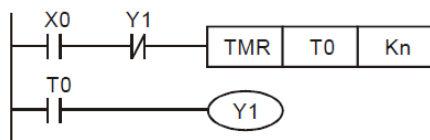

#### Example 9: Flashing circuit

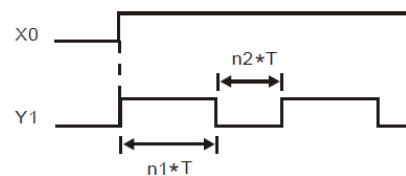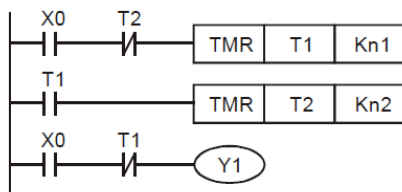


#### Example 10: Trigger circuit

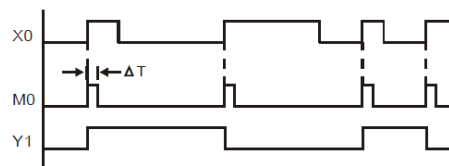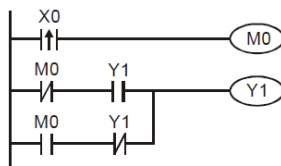


The rising-edge differential instruction of X0 makes coil M0 generate a single pulse of  $\Delta T$  (one scan cycle). Coil Y1 will be On during this scan period. In the next scan period, coil M0 will be Off and the normally closed contact M0 and Y1 will all be closed, making coil Y1 continue to be On until another rising-edge arrives in input X0, making coil M0 On for another scan period and Y1 Off. Such kind of circuit relies on an input to make two actions execute interchangeably. Also from the timing diagram on the last page, we can see that input X0 are square pulse signals of the cycle T and coil Y1 output are square pulse signals of the cycle 2T.

#### Example 11: Delay circuit

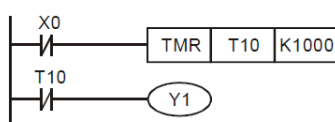



Time base:  $T = 0.1 \text{ sec}$

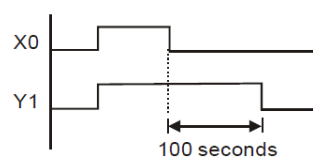


When input X0 is On, due to that its corresponding normally closed contact is Off, time T10 will be Off and the output coil Y1 will be On. T10 will be On and start to count until input X0 is Off. Output coil Y1 will be delayed for 100 seconds ( $K1,000 \times 0.1 \text{ sec} = 100 \text{ secs}$ ) and be Off. See the timing diagram above.
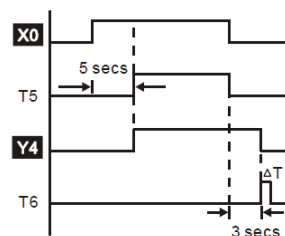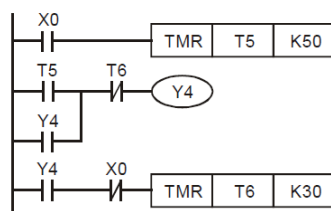
#### Example 12: Output delay circuit

The output delay circuit is the circuit composed of two timers. When input X0 is On and Off, output Y4 will be delayed.




#### Example13: Timing extension circuit

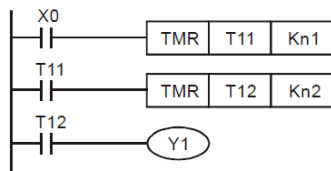


Timer = T11, T12

Clock cycle: T

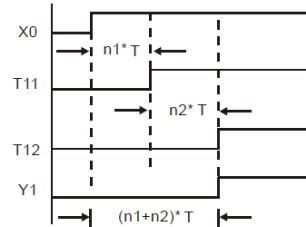The total delay time from input X0 is closed to output Y1 is On =  $(n1+n2) \cdot T$ . T refers to the clock cycle.



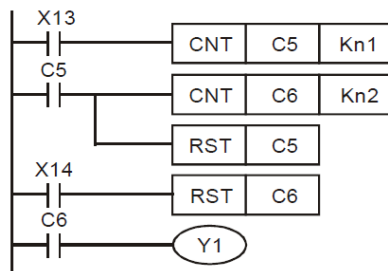
#### Example 14: How to enlarge the counting range



The counting range of a 16-bit counter is 0 ~ 32,767. As the circuit in the left hand side, using two counters can increase the counting range to  $n1 \cdot n2$ . When the counting of counter C5 reaches  $n1$ , C6 will start to count for one time and reset for counting the pulses from X13. When the counting of counter C6 reaches  $n2$ , the pulses from input X13 will be  $n1 \cdot n2$ .

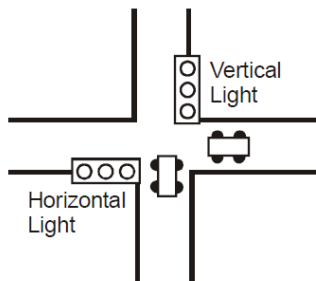
#### Example 15: Traffic light control (by using step ladder instruction)



Traffic light control


|                  | Red light | Yellow light | Green light | Green light flashes |
|------------------|-----------|--------------|-------------|---------------------|
| Vertical light   | Y0        | Y1           | Y2          | Y2                  |
| Horizontal light | Y10       | Y11          | Y12         | Y12                 |
| On time          | 35 secs   | 5 secs       | 25 secs     | 5 secs              |

#### Timing Diagram:

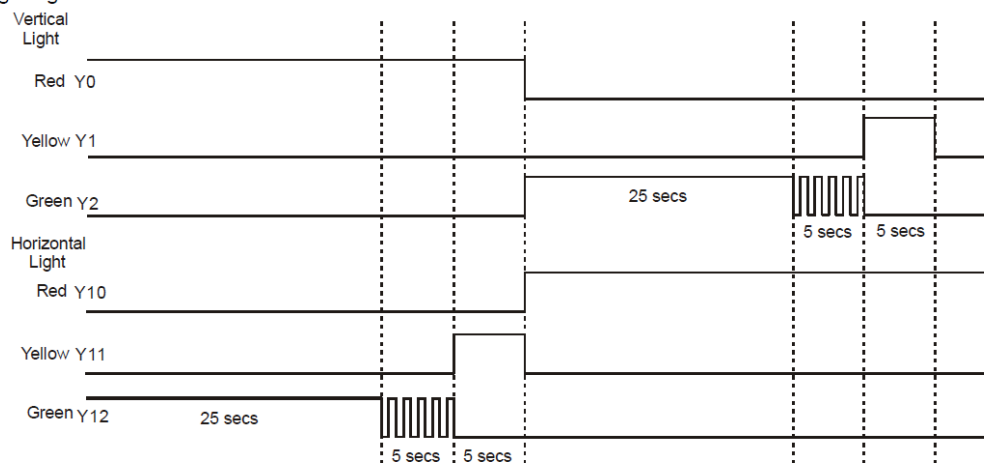



SFC Figure:

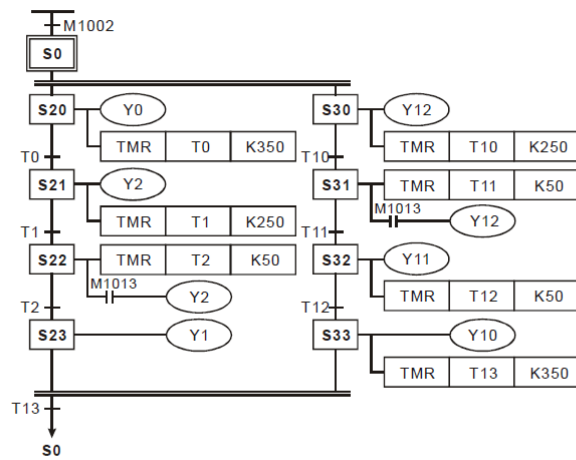

Ladder Diagram:

