



University: *Tikrit*
College: *Petroleum Processes Engineering*
Department: *Petroleum Systems Control Engineering*
Subject: *Electrical Engineering Fundamentals*
Assistant Lecturer: *Waladdin Mezher Shaher*
2023-2024



Electrical Engineering Fundamentals



First class

AC & DC Examples

University: Tikrit
College: Petroleum Processes Engineering
Department: Petroleum Systems Control Engineering
Assistant Lecturer: Waladdin Mezher Shaher
2024-2025

$$V = IR$$
$$P = IV$$

Ohm Law

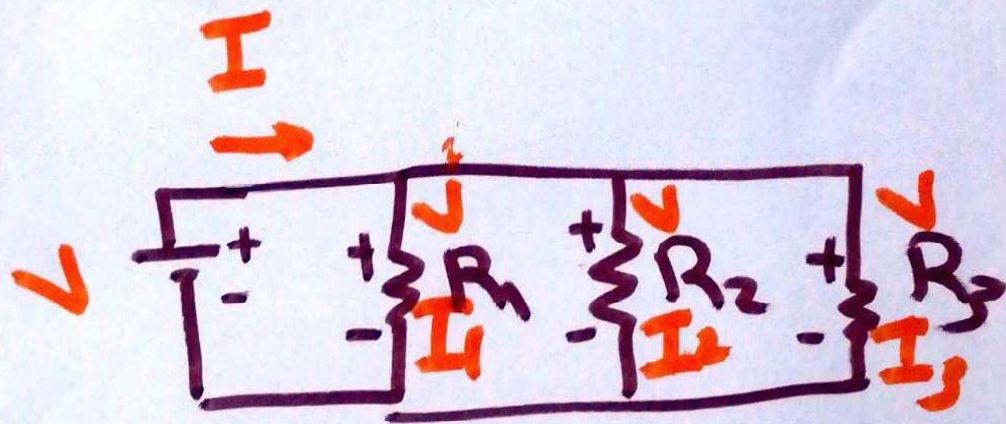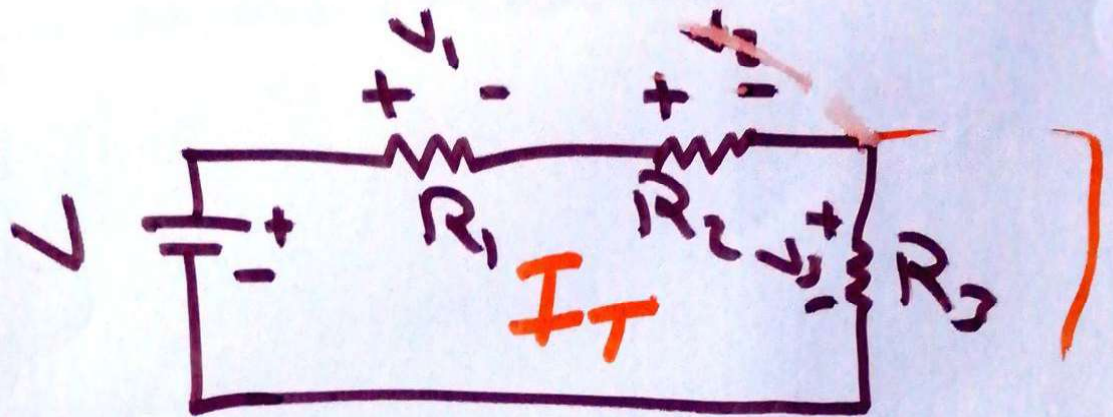


Kirchoff's Law

① Kirchoff's Current Law (KCL)


$$\sum I_n = 0$$
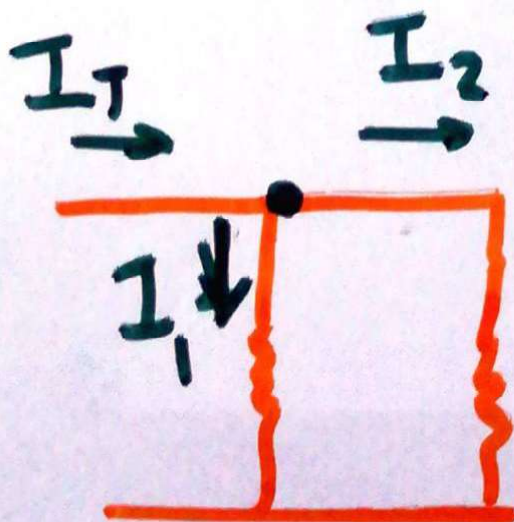
$$\sum_{m \in I} I_m = \sum_{n=1}^N I_n$$





$$I_T - I_1 - I_2 = 0$$

$$I_T = I_1 + I_2$$

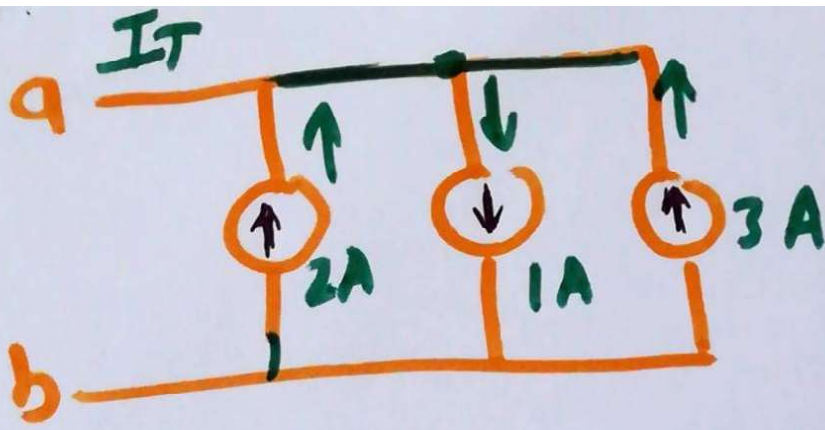


$$I_T = 2 - 1 + 3 = 4$$

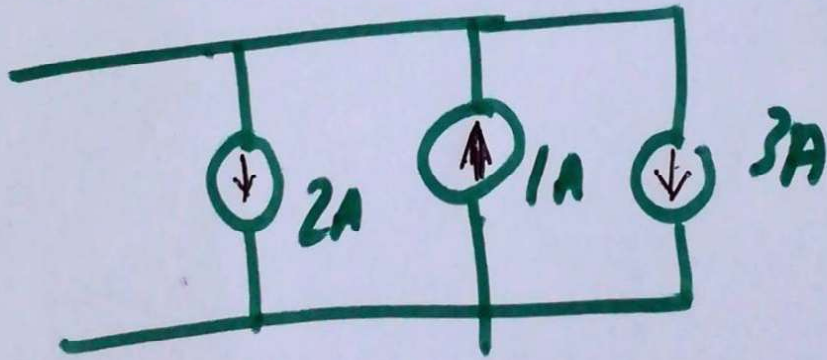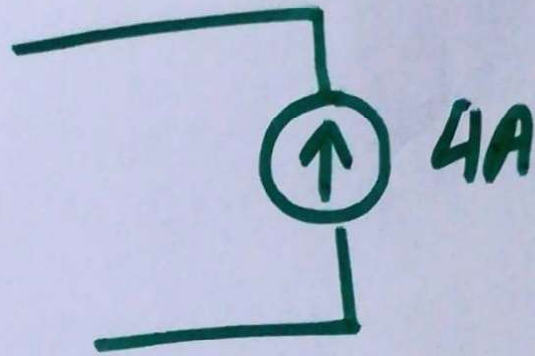

$$2 - 1 + 3 = 4A$$


$$-2 + 1 + 3 = -4$$

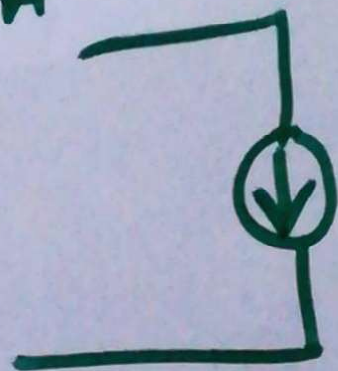

② Kirchoff's Voltage Law (KVL)

$$\sum_{m=1}^M v_m = 0$$

EX:

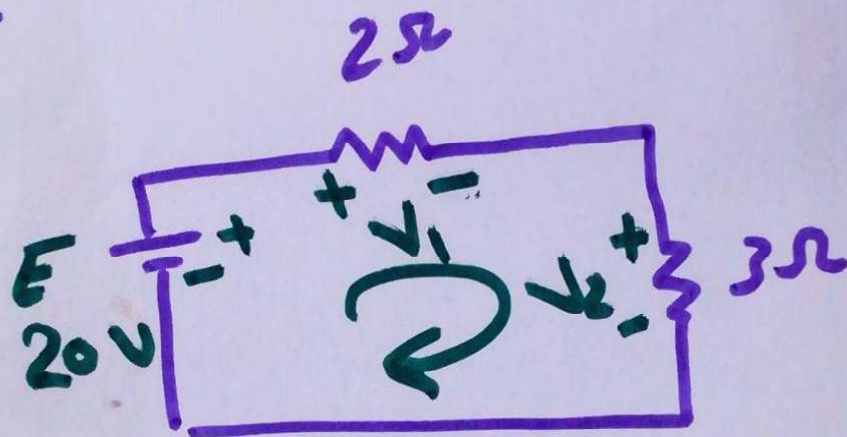

$$+E - v_1 - v_2 = 0$$
$$\boxed{20 - v_1 - v_2 = 0}$$
$$v = IR$$

$$v_1 = I R_1 = I(2) = 2I \text{ --- ①}$$

$$v_2 = I R_2 = 3I \text{ --- ②}$$

$$20 - 2I - 3I = 0$$

$$20 - 5I = 0$$


$$I = 4$$

$$V_1 = 4 * 2 = 8 \text{ V}$$

$$V_2 = 4 * 3 = 12 \text{ V}$$

$$20 - 8 - 12 = 0$$

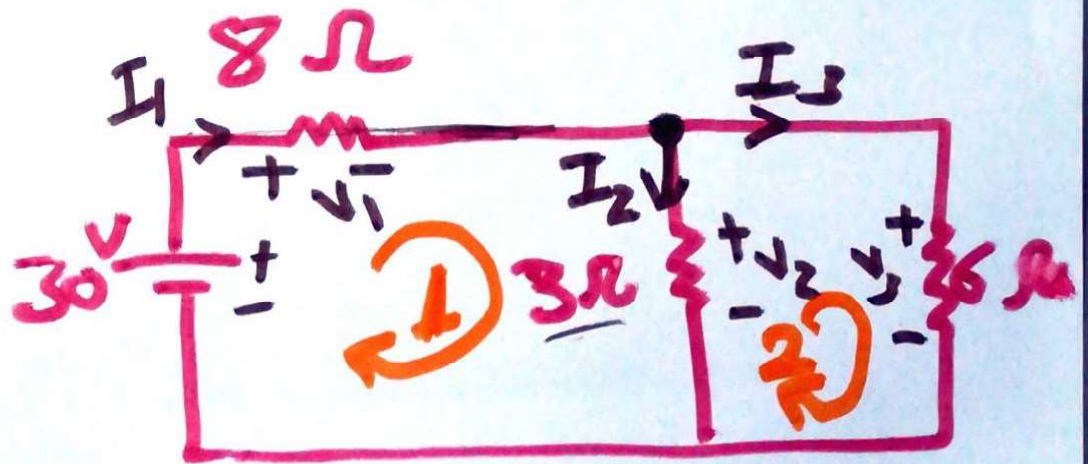Example: Calculate the current and voltage



KCL

$$V_1 = I_1 R_1 = I_1 \cdot 8$$

KVL

$$V_2 = I_2 R_2 = 3 I_2$$

$$V_3 = I_3 R_3 = 6 I_3$$

$$I_1 = I_2 + I_3$$

$$I_1 - I_2 - I_3 = 0 \quad \text{--- (1)}$$

Loop 1

$$E - V_1 - V_2 = 0$$

$$30 - 8 I_1 - 3 I_2 = 0$$

$$I_1 = \frac{30 - 3 I_2}{8} \quad \text{--- (2)}$$

$$+V_2 - V_3 = 0$$

$$3I_2 - 6I_3 = 0$$

$$I_3 = \frac{3I_2}{6} \quad \text{--- (3)}$$

Sub in ~~(1)~~ equ (2) and (3)
I in (1)

$$I_1 - I_2 - I_3 = 0$$

$$\frac{30 - 3I_2}{8} - I_2 - \frac{3I_2}{6} = 0$$

$$\frac{30 - 3I_2}{8} - \frac{(6I_2 + 3I_2)}{6} = 0$$

$$I_2 = 2A$$

$$I_2 = \frac{30 - 3I_2}{8}$$

$$= \frac{30 - 46}{8}$$

$$I_1 = 3A$$


$$I_3 = \frac{3 \times 2}{6} = 1$$

$$V_1 = 3 \times 8 = 24 \text{ V}$$

$$V_2 = 3 I_2 = 3 \times 2 = 6 \text{ V}$$

$$V_3 = 6 \times 1 = 6 \text{ V}$$
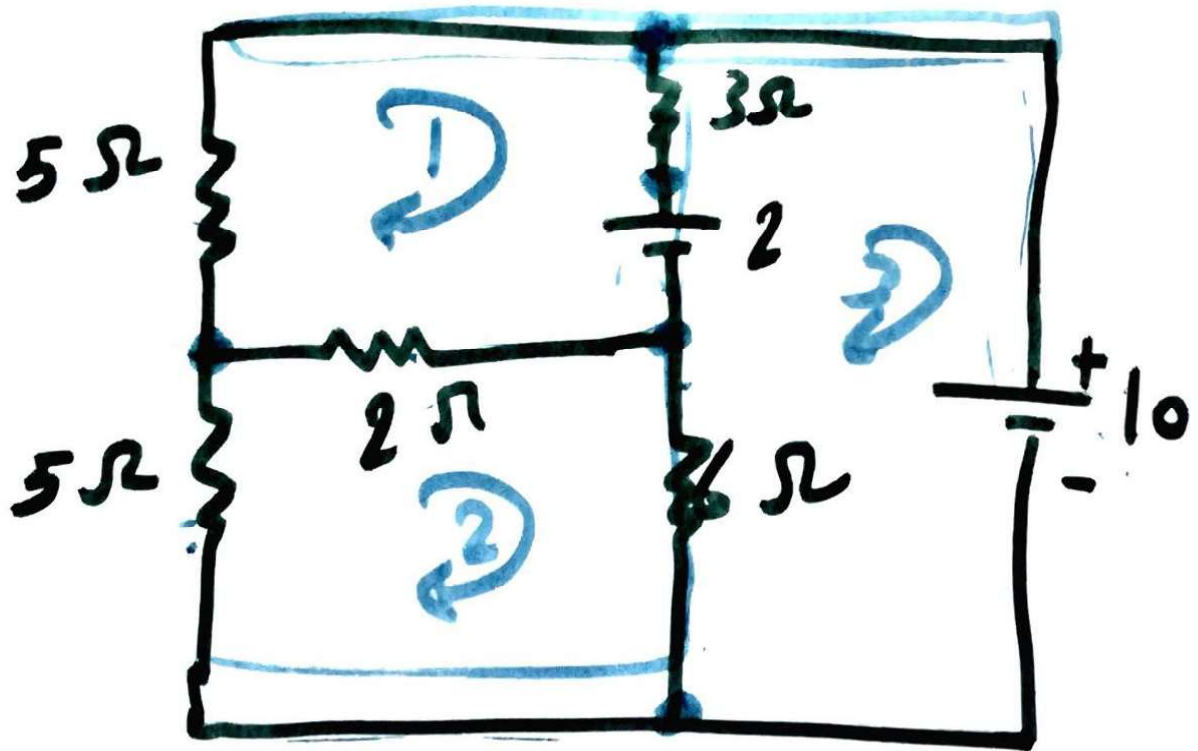
$$3 \text{ A} - 2 \text{ A} - 1 \text{ A} = 0$$




$$\text{branches } (b) = 7$$

$$\text{nodes } (n) = 5$$

$$\text{Loop } (L) = 3$$

$$b = L + n - 1$$

$$= 3 + 5 - 1 = 7$$

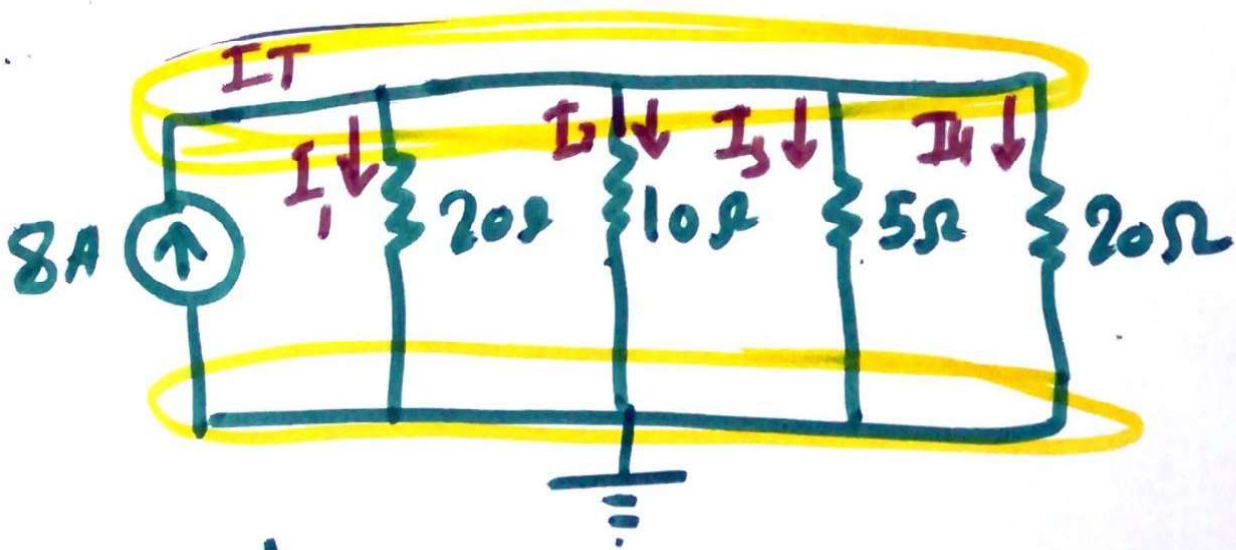

KCL

$$I_T = I_1 + I_2 + I_3 + I_4$$

~~V = IR~~ $V = IR$

$$V = I_1 (20) \Rightarrow I_1 = \frac{V}{20}$$

$$V = I_2 (10) \Rightarrow I_2 = \frac{V}{10}$$

$$V = I_3 (5) \Rightarrow I_3 = \frac{V}{5}$$

$$V = I_4 (20) \Rightarrow I_4 = \frac{V}{20}$$

$$8 = \frac{V}{20} + \frac{V}{10} + \frac{V}{5} + \frac{V}{20}$$

$$V = 20V$$

$$I_1 = \frac{20}{20} = 1 \text{ A}$$


$$I_2 = \frac{20}{10} = 2 \text{ A}$$

$$I_3 = \frac{20}{5} = 4 \text{ A}$$

$$I_4 = \frac{20}{20} = 1 \text{ A}$$

$$I_T = I_1 + I_2 + I_3 + I_4$$
$$= 1 + 2 + 4 + 1$$

$$I_T = 8$$

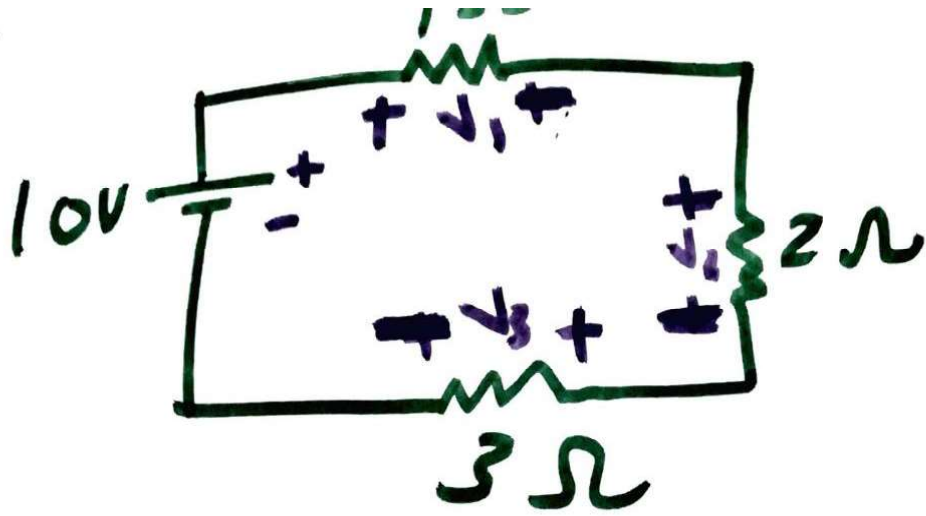

$I, V = ?$

$$E - V_1 - V_2 - V_3 = 0 \quad \text{--- (1)}$$

$$V_1 = IR_1 = 1I \quad \text{--- (2)}$$

$$V_2 = IR_2 = 2I \quad \text{--- (3)}$$

$$V_3 = IR_3 = 3I \quad \text{--- (4)}$$

$$10 - I - 2I - 3I = 0$$

$$10 - 6I = 0$$

$$I = \frac{10}{6} \text{ A}$$

$$V_1 = \frac{10}{6} \times 1 = \frac{10}{6} \text{ V}$$

$$V_2 = \frac{10}{6} \times 2 = \frac{10}{3} \text{ V}$$



$$V_3 = \frac{10}{6} \times 3 = \frac{10}{2} = 5 \text{ V}$$



Series Circuits

$$I = I_1 = I_2 = I_3 = I_4$$

$$E = V_1 + V_2 + V_3 + V_4$$

$$R_T = R_1 + R_2 + R_3 + R_4$$

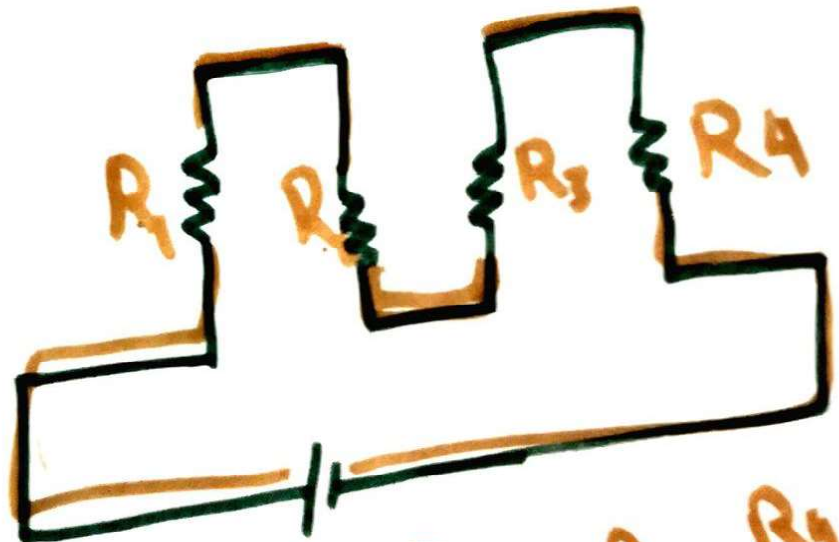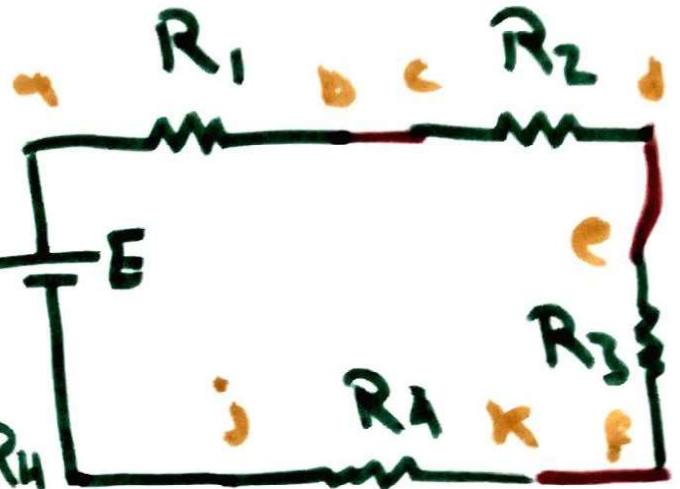

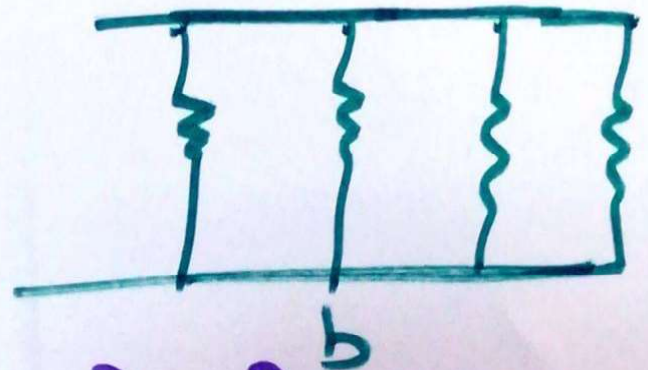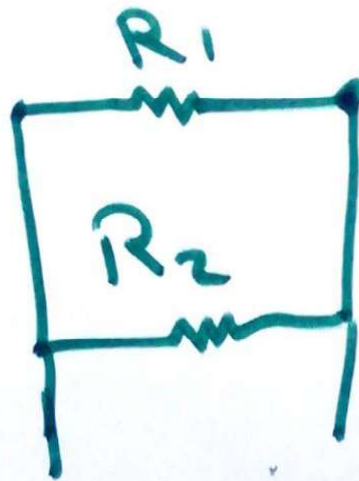

$$V = IR$$

$$I = I_1 = I_2 = I_3$$

$$R_T = R_1 + R_2 + R_3$$

$$E = V_1 + V_2 + V_3$$

$$E = IR_1 + IR_2 + IR_3$$

$$E = I(R_1 + R_2 + R_3)$$


$$E = IR_T$$

$$I = \frac{E}{R_T}$$



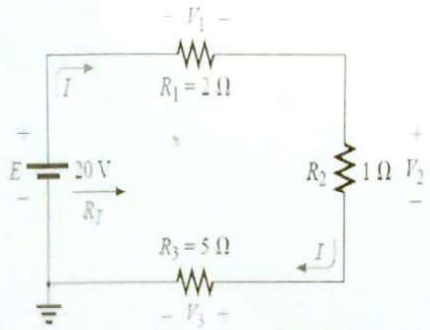EXAMPLE


- Find the total resistance for the series circuit of Fig. 5.7.
- Calculate the source current I_s .
- Determine the voltages V_1 , V_2 , and V_3 .
- Calculate the power dissipated by R_1 , R_2 , and R_3 .
- Determine the power delivered by the source, and compare it to the sum of the power levels of part (d).



$$R_T = R_1 + R_2 + R_3$$

$$R_T = 2 + 1 + 5$$

$$R_T = 8 \Omega$$

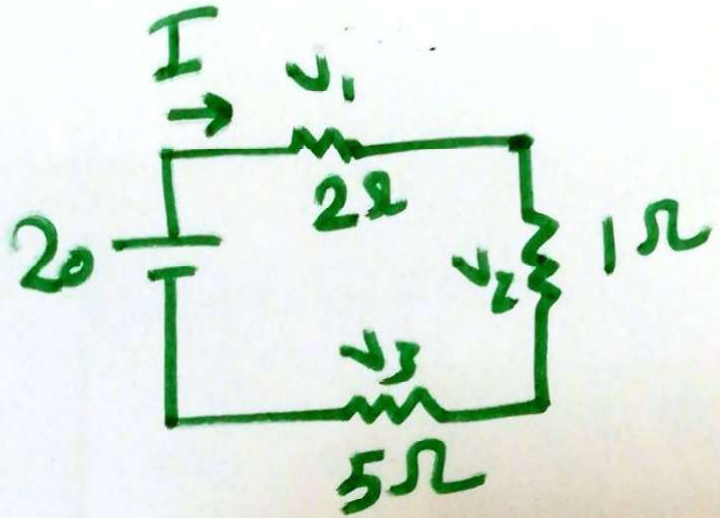

$$I = \frac{E}{R_T} = \frac{20}{8} = 2.5 A$$

KVL

$$V = IR$$

$$V_1 = IR_1 = 2.5 * 2 = 5 V$$

$$V_2 = IR_2 = 2.5 * 1 = 2.5 V$$

$$V_3 = IR_3 = 2.5 * 5 = 12.5 V$$

$$\cancel{E} + E = V_1 + V_2 + V_3 = 5 + 2.5 + 12.5 = 20$$

$$* P = VI$$

$$P_1 = V_1 I = 5 * 2.5 = 12.5$$

$$P_2 = V_2 I = 2.5 * 2.5 = 6.25$$


$$P_3 = V_3 I = ~~2.5~~ 12.5 * 2.5 = 31.25$$

$$P_T = EI = 20 * 2.5 = \underline{\underline{50}}$$


$$P = P_1 + P_2 + P_3 = 12.5 + 6.25 + 31.25$$

$$= \underline{\underline{50}}$$


VOLTAGE SOURCES IN SERIES

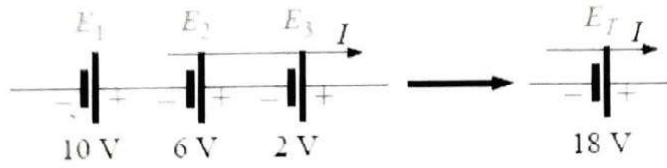


(a)

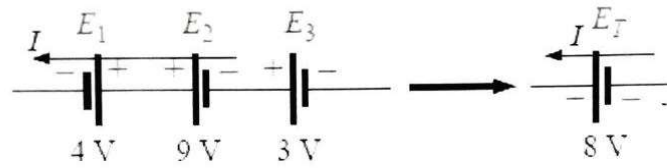

(b)

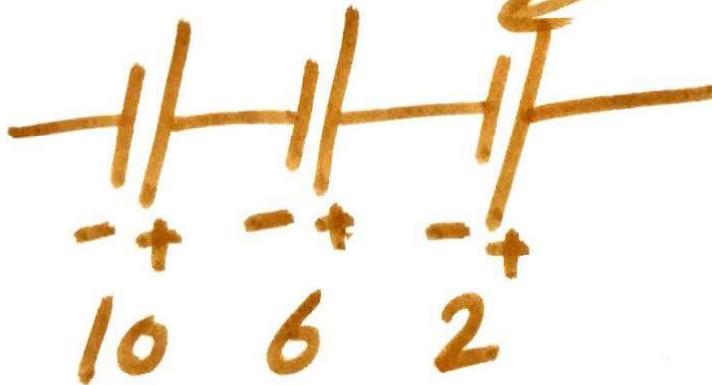

$$+10 + 6 + 2 = +18$$

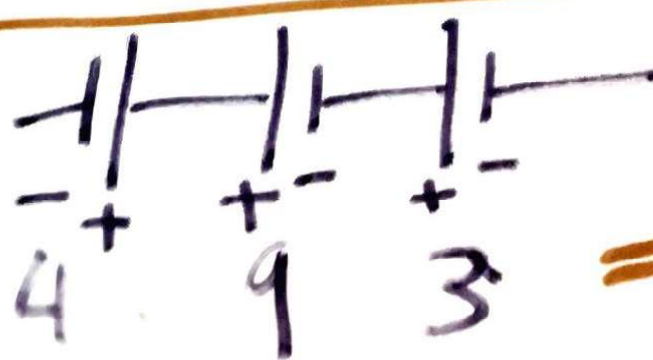

$$= +4 - 9 - 3 = -8$$

VOLTAGE DIVIDER RULE

$$R_T = R_1 + R_2$$

~~$E =$~~

$$E = V_1 + V_2$$

$$E = IR_1 + IR_2$$

$$E = I(R_1 + R_2)$$
$$\boxed{E = I R_T}$$

$$I = \frac{E}{R_T}$$


$$V_1 = I R_1$$

$$\boxed{V_1 = \frac{E}{R_T} \times R_1}$$


$$= \frac{E R_1}{R_T}$$

$$V_2 = \frac{E R_2}{R_T}$$

$$V_x = \frac{E R_x}{R_T}$$

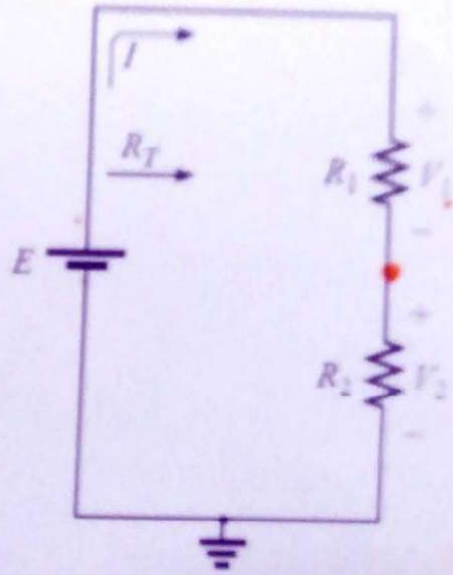

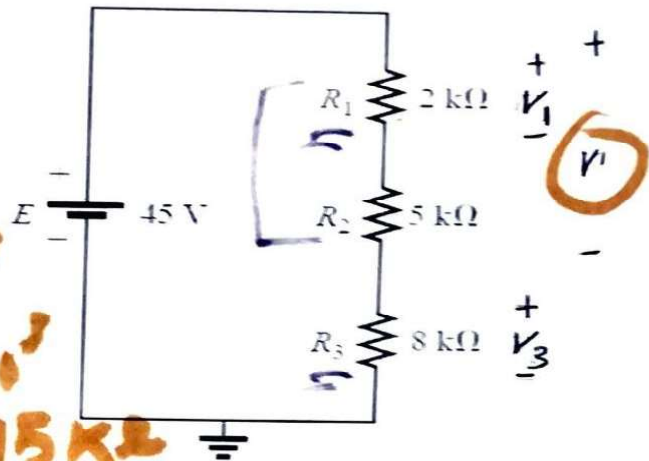EXAMPLE Using the voltage divider rule, determine the voltages V_1 , V' and V_3 for the series circuit of Fig.



$$R_T = 2 \times 10^3 + 5 \times 10^3 + 8 \times 10^3$$

$$V_x = \frac{E R_x}{R_T} = \frac{45 \times 2 \times 10^3}{15 \times 10^3}$$

$$V_1 = \frac{E R_1}{R_T} = \frac{45 \times 2 \times 10^3}{15 \times 10^3} = 6V$$

$$V_3 = \frac{E R_3}{R_T} = \frac{45 \times 8 \times 10^3}{15 \times 10^3} = 24V$$

~~$$R' = 2 \times 10^3$$~~

$$R' = R_1 + R_2 = 2 \times 10^3 + 5 \times 10^3 = 7k \Omega$$




$$V' = \frac{E \times R'}{R_T} = \frac{45 \times 7 \times 10^3}{15 \times 10^3} = 21V$$

$$E = V_1 + V_2 + V_3$$


$$= V_1 + V_3$$

$$= 21 + 24 = \cancel{51} 45V$$

Voltage Sources and Ground

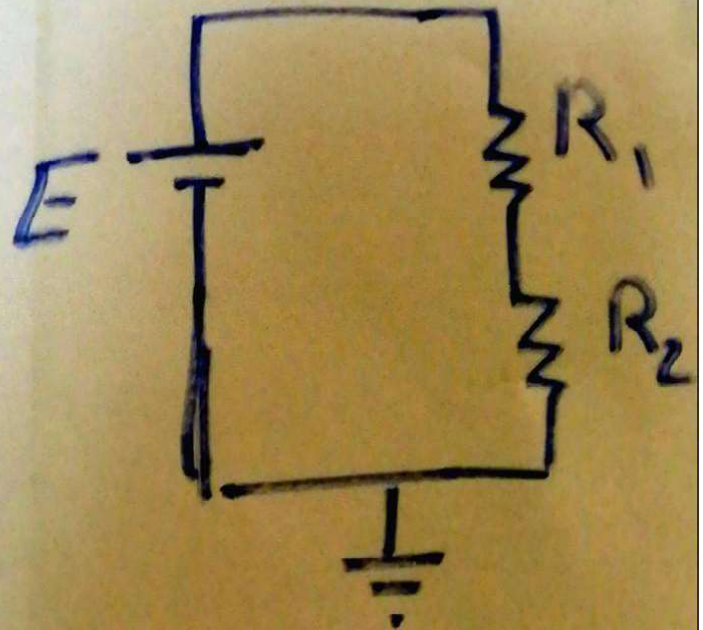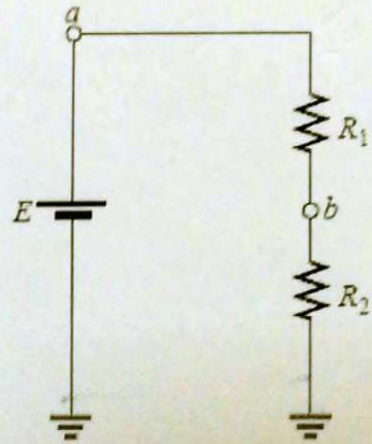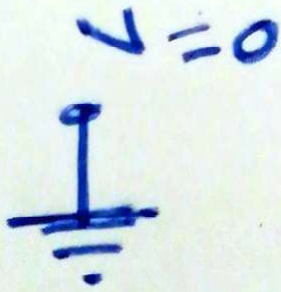

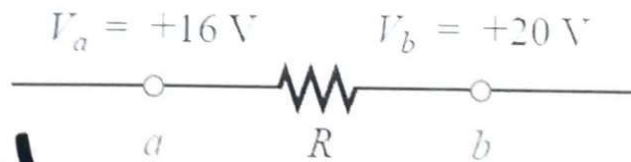EXAMPLE 5.14 Find the voltage V_{ab} for the conditions of Fig. 5.38.



V_{ba}

$$V_{ab} = V_a - V_b = 16 - 20 = -4\text{ V}$$

$$V_{ba} = V_b - V_a = 20 - 16 = +4\text{ V}$$


EXAMPLE 5.15 Find the voltage V_a for the configuration of Fig. 5.39.

~~$V_{ab} = 20 - (-15)$~~


$$V_{ab} = V_a - V_b$$


$$V_{ab} = 20 - (-15)$$

$$V_{ab} = 20 + 15 = 35\text{ V}$$


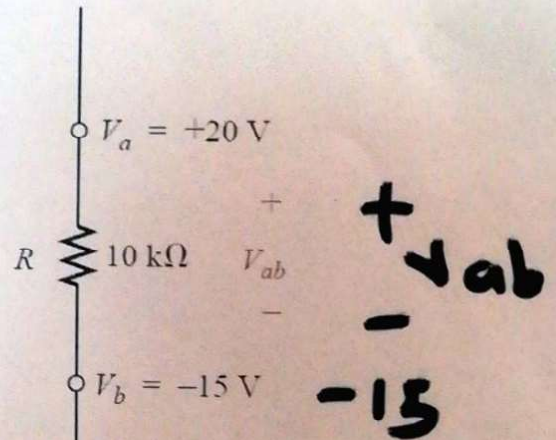

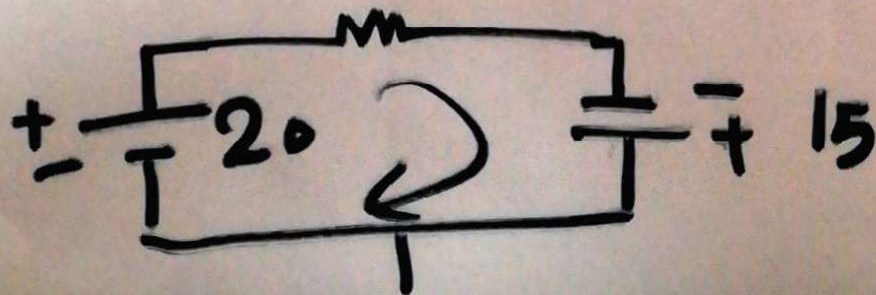
$$V_{ba} = V_b - V_a = -15 - 20 = -35\text{ V}$$



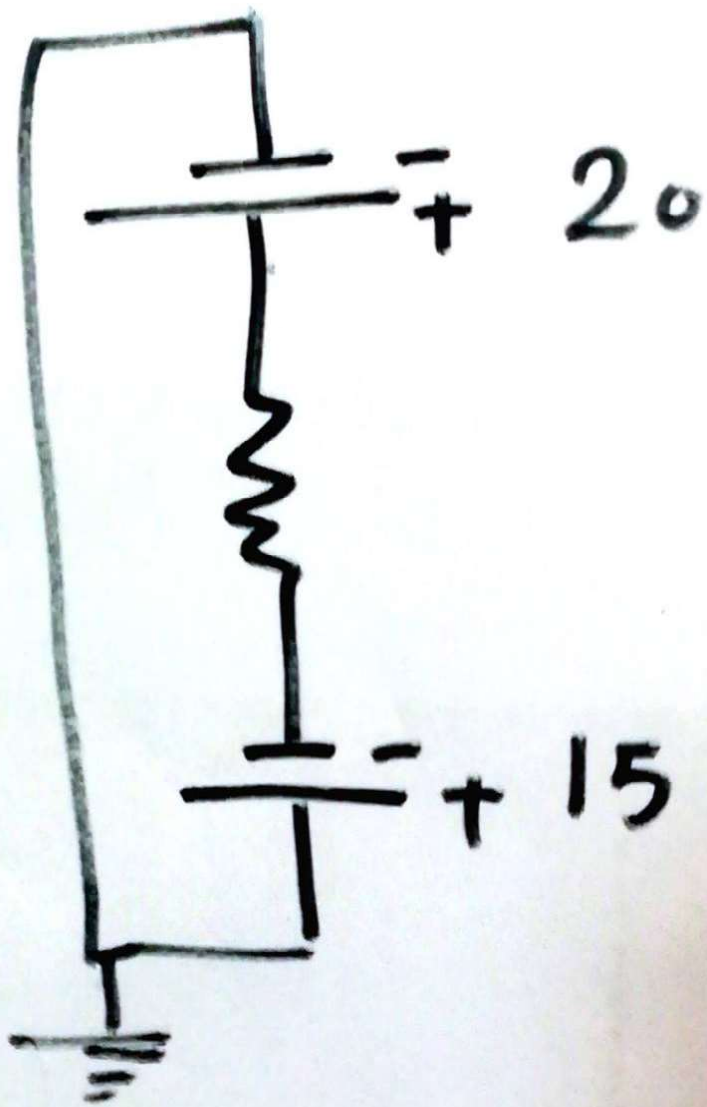

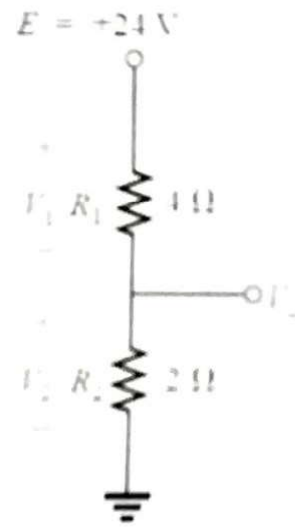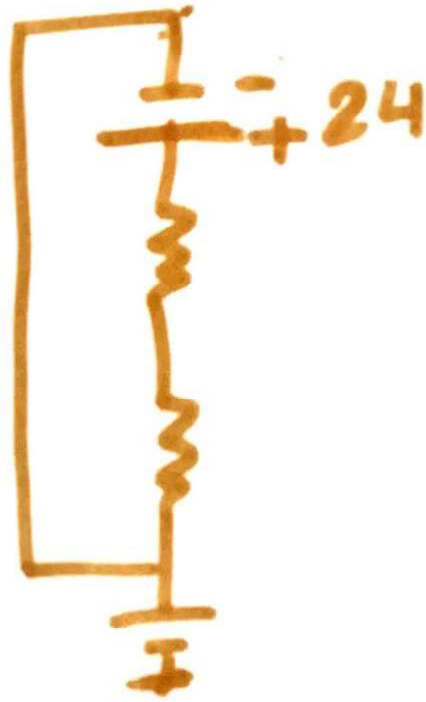EXAMPLE Using the voltage divider rule, determine the voltages V_1 and V_2 of Fig.





$$R_T = R_1 + R_2 = 4 + 2 = 6$$


$$V_1 = \frac{E R_1}{R_T} = \frac{24 \times 4}{6} = 16V$$

$$V_2 = \frac{E R_2}{R_T} = \frac{24 \times 2}{6} = 8V$$

KVL $E = V_1 + V_2$
 $= 16 + 8 = 24$

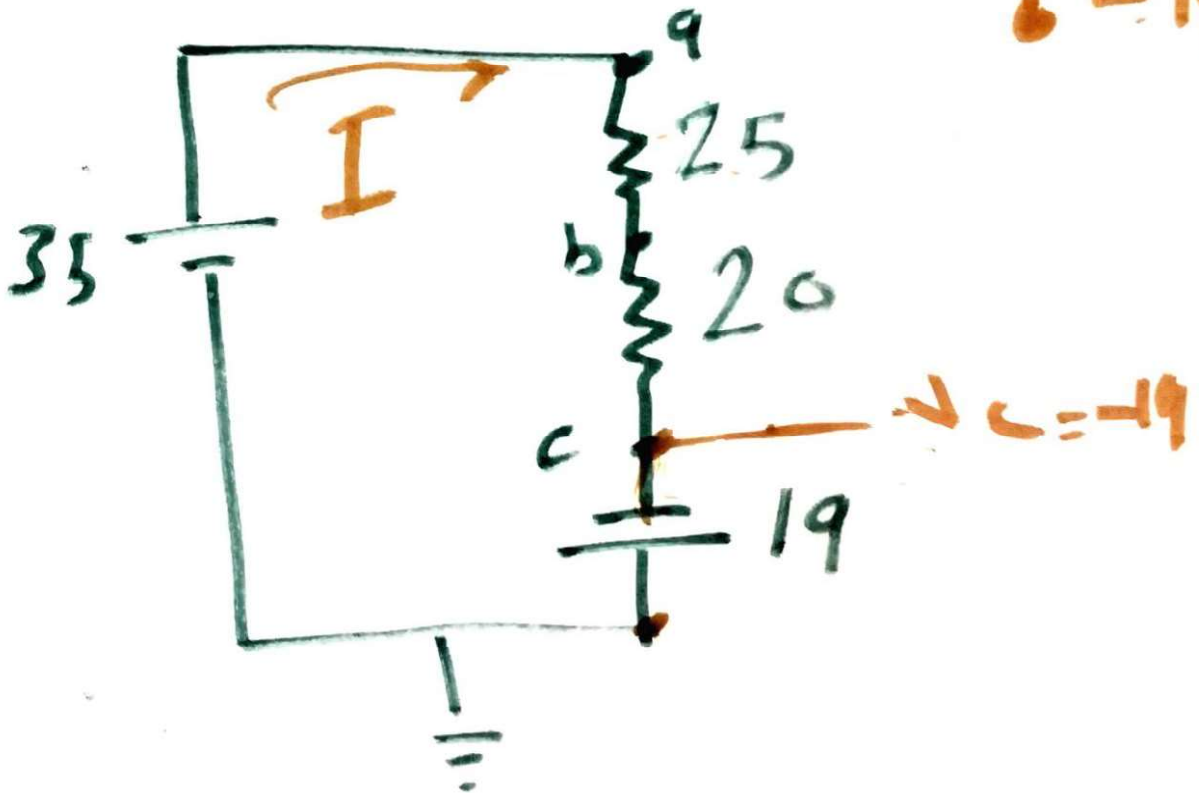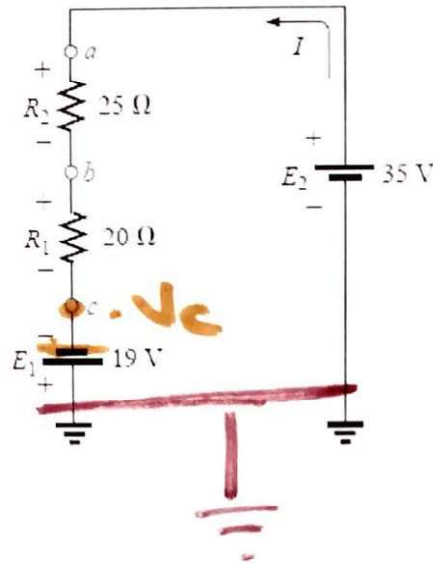EXAMPLE Determine V_{ab} , V_{cb} , and V_c for the network of Fig.



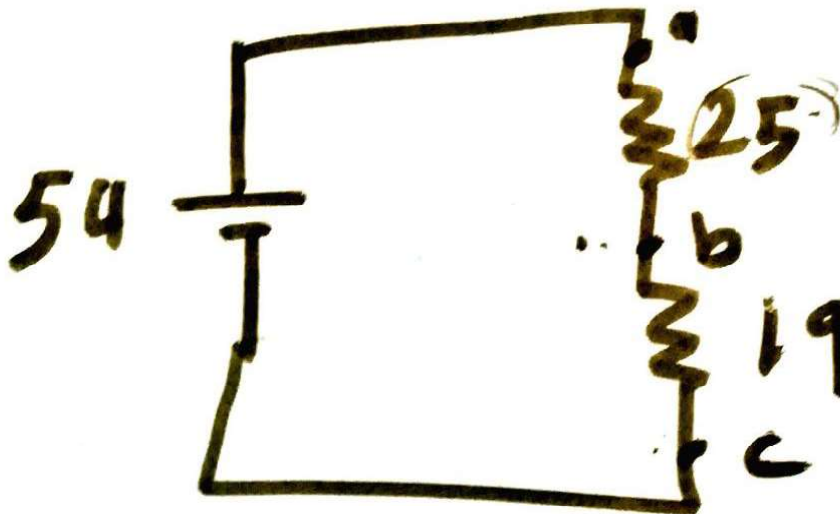

$$V_{ab} = V_{25} = \frac{E \times R_{25}}{R_T} = \frac{54 \times 25}{44}$$

$$V_{cb} = -V_{bc} = 30V$$

$$V_{bc} = -\frac{E \cdot R_{19}}{R_T}$$

$$= -\frac{54 \times 19}{44} = -24$$

$$V_c = -19 - 0 = -19$$

$$I = \frac{54}{45} = 1.2$$

$$V_{25} = V_{ab} = IR_1 = 1.2 \times 25 = 30^{\text{V}}$$

$$V_{cb} = -V_{bc} = -IR_{20} = 1.2 \times 20 \\ = -24\text{V}$$


$$V_c = -19$$

No.

Example


EXAMPLE 5.2 Determine R_T , I , and V_2 for the circuit of Fig. 5.8.

1

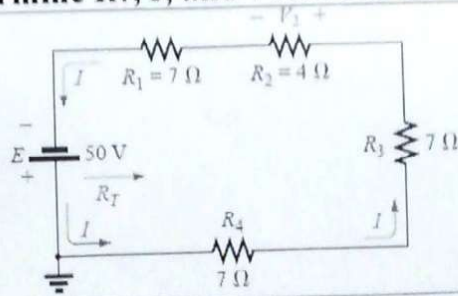


EXAMPLE 5.3 Given R_T and I , calculate R_1 and E for the circuit of

2

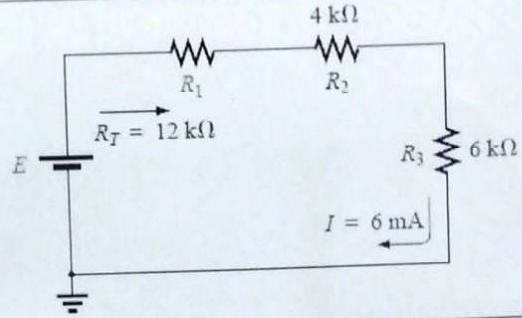

EXAMPLE 5.4 Determine the unknown voltages for the networks of Fig. 5.14.


3

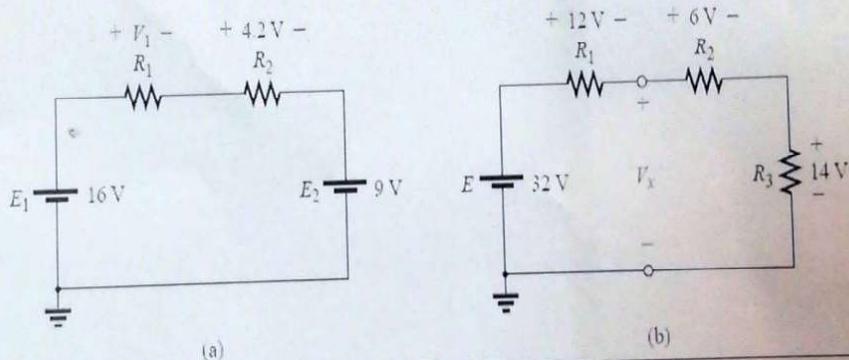

EXAMPLE 5.7 For the circuit of Fig. 5.17:


- Find R_T .
- Find I .
- Find V_1 and V_2 .
- Find the power to the $4\ \Omega$ and $6\ \Omega$ resistors.
- Find the power delivered by the battery, and compare it to that dissipated by the $4\ \Omega$ and $6\ \Omega$ resistors combined.
- Verify Kirchhoff's voltage law (clockwise direction).

3

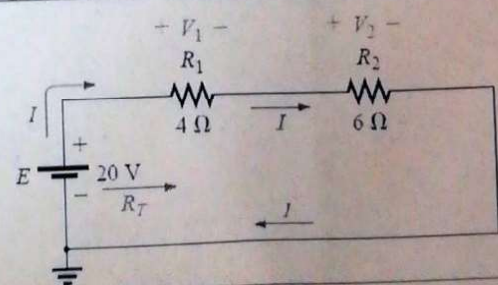


EXAMPLE 5.9 Determine I and the voltage across the 7Ω resistor for the network of Fig.

4

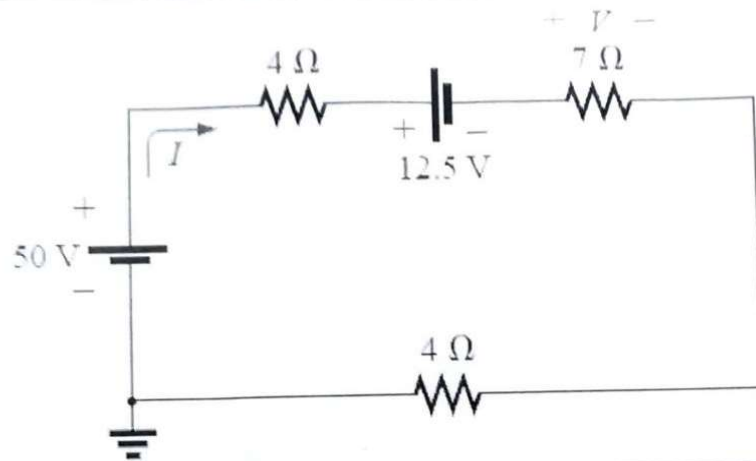

EXAMPLE 5.10 Determine the voltage V_1 for the network of Fig. 5.27.

5

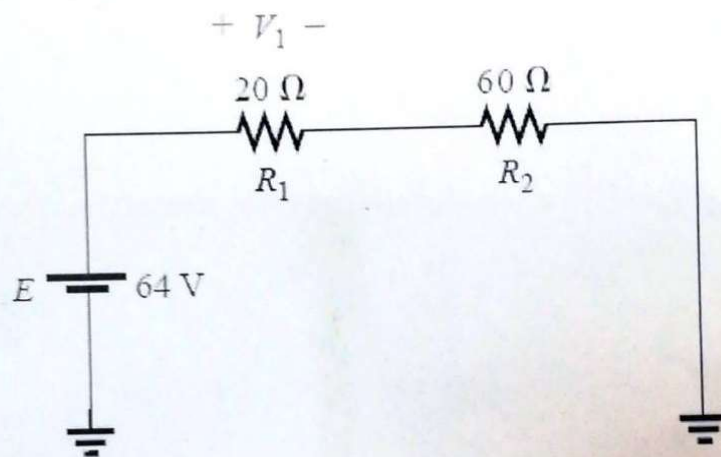

EXAMPLE 5.20 For the network of Fig. 5.50:

- Calculate V_{ab} .
- Determine V_b .
- Calculate V_c .

8


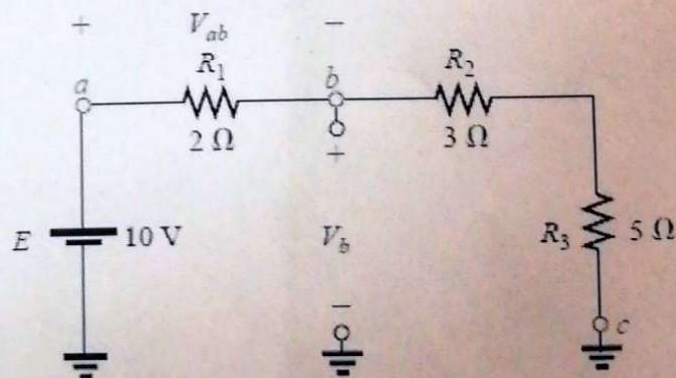


FIG. 5.50

Parallel Circuits

KVL

KCL

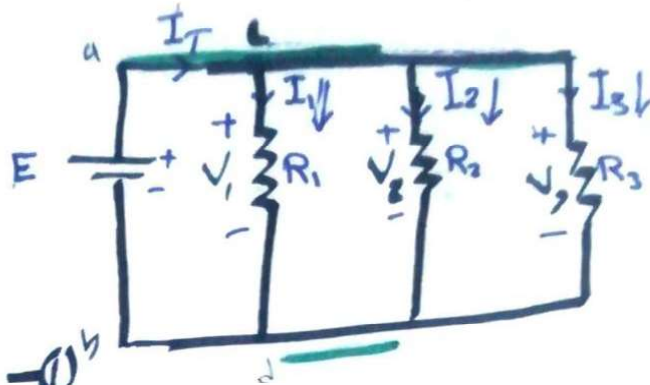

$$I_T = I_1 + I_2 + I_3 \quad \text{--- (1)}$$

$$V = IR \Rightarrow I = \frac{V}{R} \quad \text{--- (2)}$$

$$\frac{E}{R_T} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$


$$E = V_1 = V_2 = V_3 = V$$

$$\frac{V}{R_T} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{V}{R_T} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
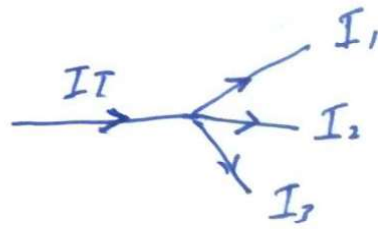
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$



$$G = \frac{1}{R}$$

$$G_T = G_1 + G_2 + G_3$$

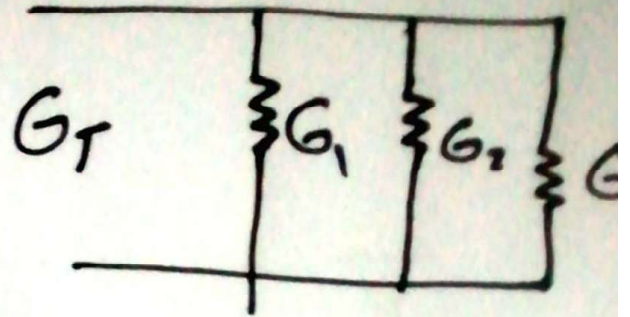

Special cases

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

* Case 1 ::

$$R_1 = R_2 = R_3 = \dots = R_N = R$$

$$\frac{1}{R_T} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R}$$

$$\frac{1}{R_T} = N \times \frac{1}{R}$$

$$\frac{1}{R_T} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{1+1+1}{R} = \frac{3}{R}$$


* Case 2 ::

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{R_2 + R_1}{R_1 R_2}$$




$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

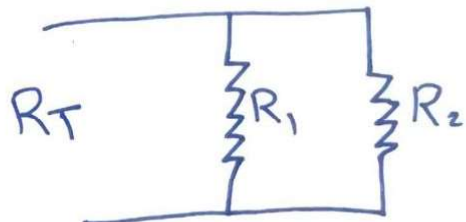

Case 3 ::
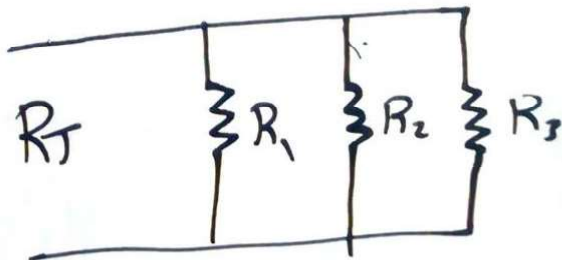
$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$



H.W

Example ∴ Determine the total resistance for the network shown.




$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5}$$

$$\frac{1}{R_T} = 0.95$$

$$R_T = \frac{1}{0.95} = 1.053 \Omega$$
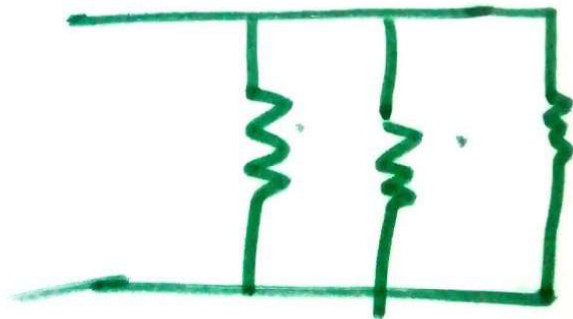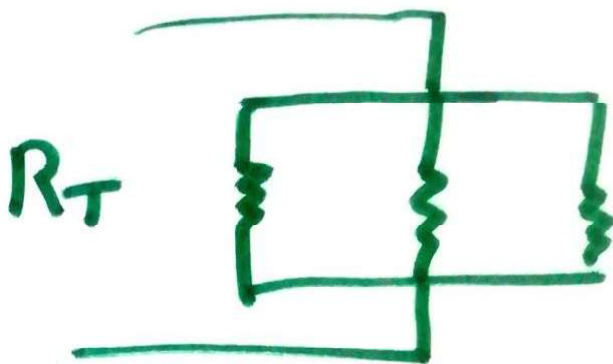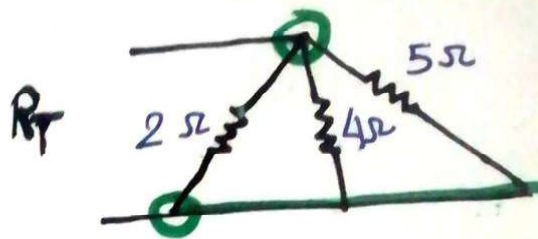
$$R_T = \frac{2 \times 4 \times 5}{2 \times 4 + 2 \times 5 + 4 \times 5}$$



Example: For the parallel network shown:


a- Calculate R_T .

b- Determine I_T .

c- Calculate I_1 and I_2 .

d- Determine the power to each resistive load.

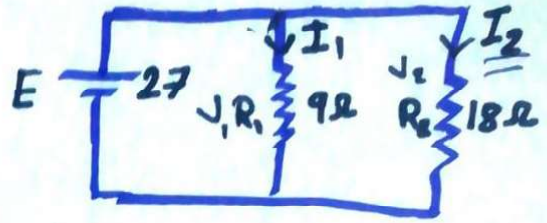e- Determine the power delivered by the source and compare it with total power dissipated by the resistive elements.



Solution


1. (a)

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{9 \times 18}{9 + 18} = 6 \Omega$$

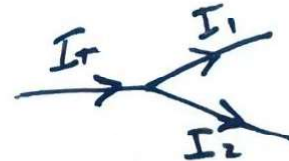(b) $I_T = ?$

$$V = IR \Rightarrow I = \frac{V}{R} \Rightarrow I_T = \frac{E}{R_T}$$

$$I_T = \frac{27}{6} = \underline{\underline{4.5 A}}$$



(c) I_1 & I_2 ?

$$E = V_1 = V_2$$

$$I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{27}{9} = \underline{\underline{3 A}}$$

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{27}{18} = 1.5 A$$

$$I_T = I_1 + I_2 \\ = 3 + 1.5 = 4.5 A$$

$$\textcircled{d} P = IV$$

$$P_1 = I_1 V_1 = I_1 * E = 3 * 27 = \underline{\underline{81 \text{ W}}}$$

$$P_2 = I_2 V_2 = I_2 * E = 1.5 * 27 = \underline{\underline{40.5 \text{ W}}}$$

$$\textcircled{e} P_T = IV = I_T E = 4.5 * 27 = \underline{\underline{121.5 \text{ W}}}$$

$$\cancel{P_T} P_1 + P_2 = 81 + 40.5 = \underline{\underline{121.5}}$$

Current Divider Rule


$$V = I_T R_T \Rightarrow I = \frac{V}{R_T}$$

$$R_T = \frac{R_1 * R_2}{R_1 + R_2} \quad \text{--- (1)}$$

$$I_1 = \frac{V}{R_1} = \frac{I R_T}{R_1} \quad \text{--- (2)}$$

$$I_1 = \frac{I \frac{R_1 * R_2}{R_1 + R_2}}{R_1} = \frac{I R_2}{R_1 + R_2}$$

$$I_2 = \frac{I R_1}{R_1 + R_2}$$

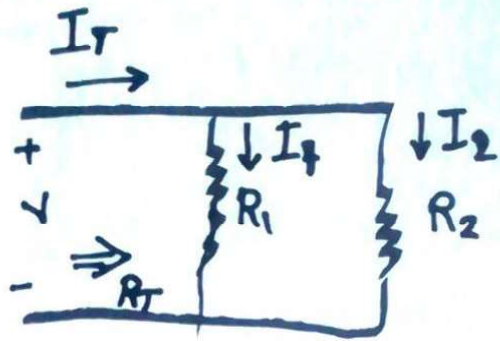


Example: Determine the current I_2 for the network

$$R_T = \frac{R_1 * R_2}{R_1 + R_2}$$


$$I_2 = \frac{6 * 4 * 10^3}{4 * 10^3 + 8 * 10^3} = \underline{\underline{2A}}$$

$$I_1 = \frac{I_T * R_2}{R_1 + R_2} = \frac{6 * 8 * 10^3}{4 * 10^3 + 8 * 10^3} = \underline{\underline{4A}}$$

$$I_1 + I_2 = 4 + 2 = 6A$$

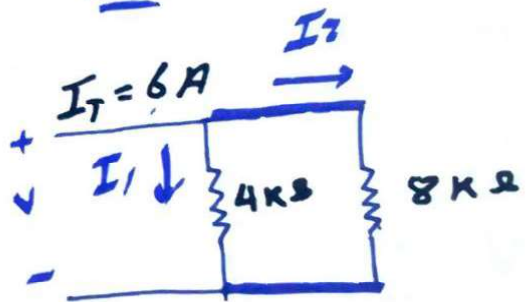

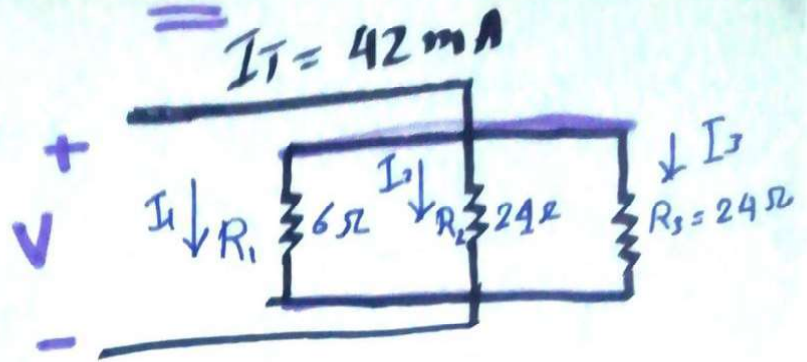Example: Find the current I_1 for the network



$$I_1 = \frac{V}{R_1} \quad \text{--- ①}$$

$$V = I_T R_T \quad \text{--- ②}$$

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \quad \text{--- ③}$$

$$I_1 = \frac{I_T R_T}{R_1} = \frac{I_T \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}}{R_1}$$

$$I_1 = \frac{I_T R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} = \frac{42 \times 10^{-3} \times 24 \times 24}{6 \times 24 + 24 \times 24 + 24 \times 6} =$$


$$0.028 \text{ A} = 28 \text{ mA}$$

$$\text{① } R_T = 4 \Omega$$

$$\text{② } V = I_T R_T = 42 \times 10^{-3} \times 4 = 0.168 \text{ V}$$



$$\text{③ } I_1 = \frac{V}{R_1} = \frac{0.168}{6} = 0.028 \text{ A} = 28 \times 10^{-3} \text{ A} = 28 \text{ mA}$$

Voltage Source in Parallel

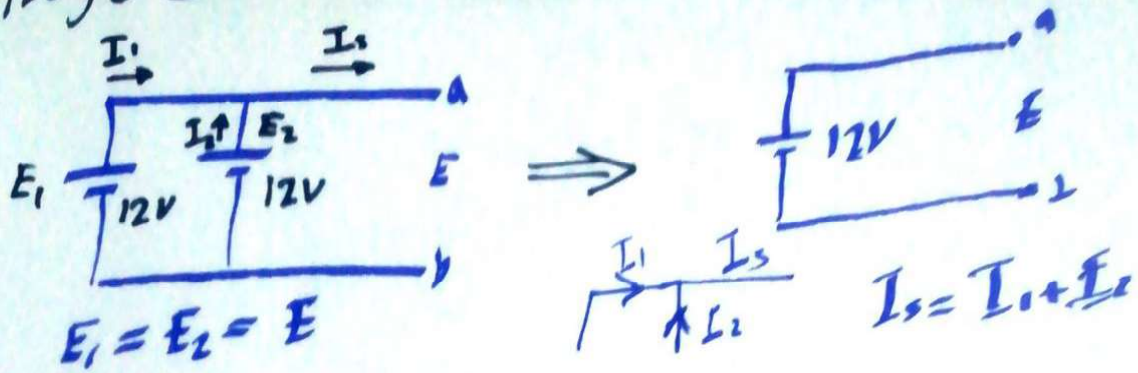



Open and short circuits

* Open circuit (o.c)

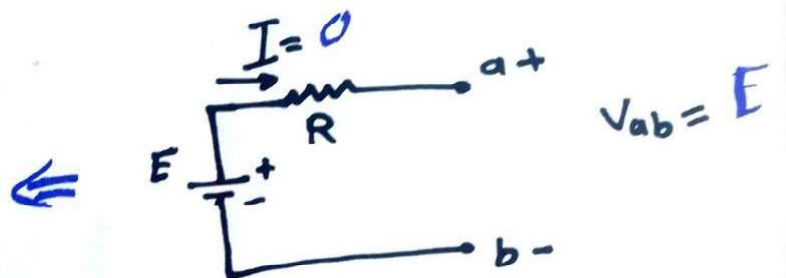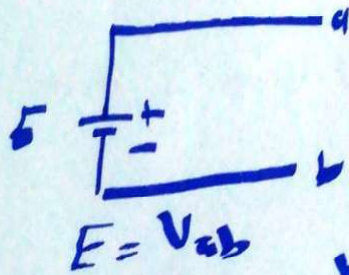

$V_{open\ circuit} = V_{o.c} = E = V_{ab}$


* Short circuit (s.c)

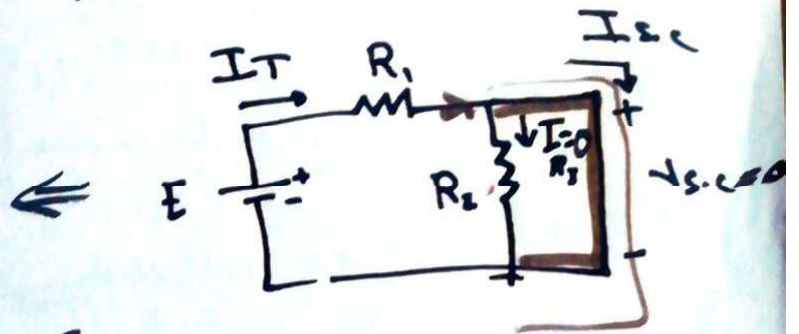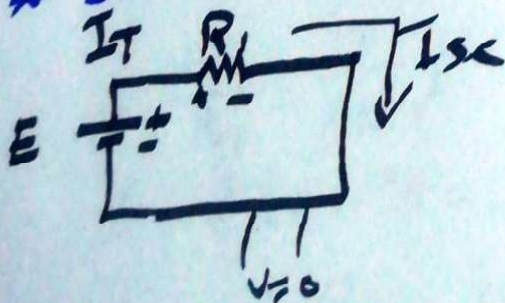

$I_{s.c} = \frac{E}{R_1} = I_T = I$

Example:- (a) For the network shown, determine V_{ab}

$\rightarrow I = ?$

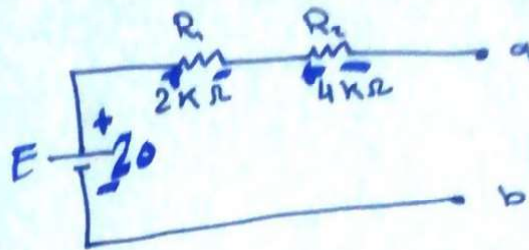


Solution:-

$V_{ab} = E = 20$

$I = 0$

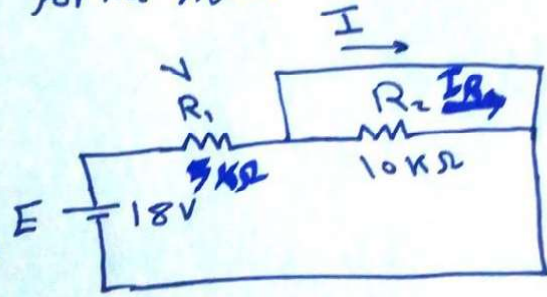(b) Calculate I and V for the network shown, I_{R_2}



$R_T = R_1 + R_2 = 5 \times 10^3 + 0$

Solution ∴ $R_T = R_1 = 5 \times 10^3$ $V = ?$ $I = ?$


$I = \frac{E}{R_T} = \frac{18}{5 \times 10^3} = 3.6 \mu A$

$I = 3.6 \times 10^{-6} A = 3.6 \mu A$

$V_{R_2} = I R = 3.6 \times 10^{-6} \times 5 \times 10^3 = 18 \mu V$
 $V_{R_1} = 18 V$

$I_{R_2} = 0$

Example = $V_{ab} = ?$

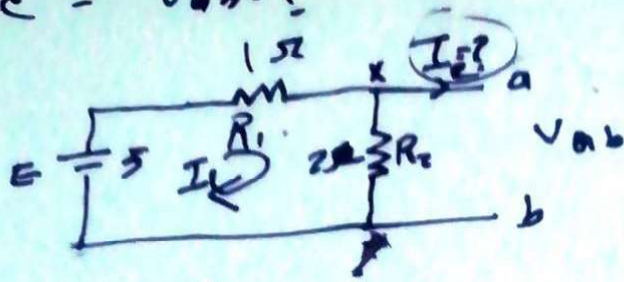

$$V_{ab} = V_{R_2}$$

$$V = IR \Rightarrow I = \frac{V}{R} \Rightarrow I_T = \frac{E}{R_T}$$

$$R_T = R_1 + R_2 = 1 + 2 = 3 \Omega$$




$$I_T = \frac{5}{3} = 1.666 \text{ A}$$

$$V_{R_2} = I_T R_2 = 1.666 \times 2 = 3.333 \text{ V}$$


$$\therefore V_{ab} = V_{R_2} = 3.333 \text{ V}$$

$$I_2 = I_{out} = 0$$


Example:

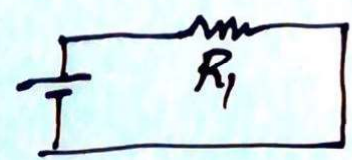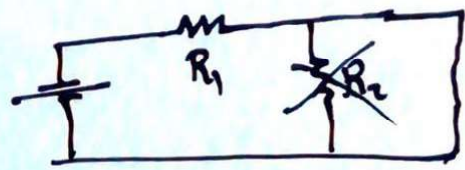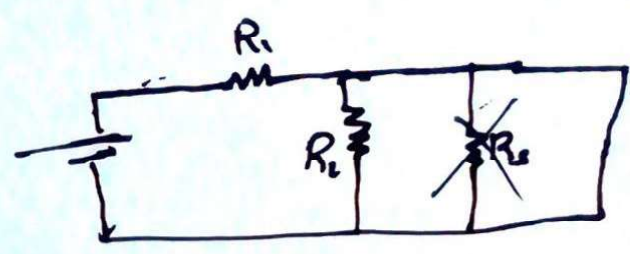




H.W

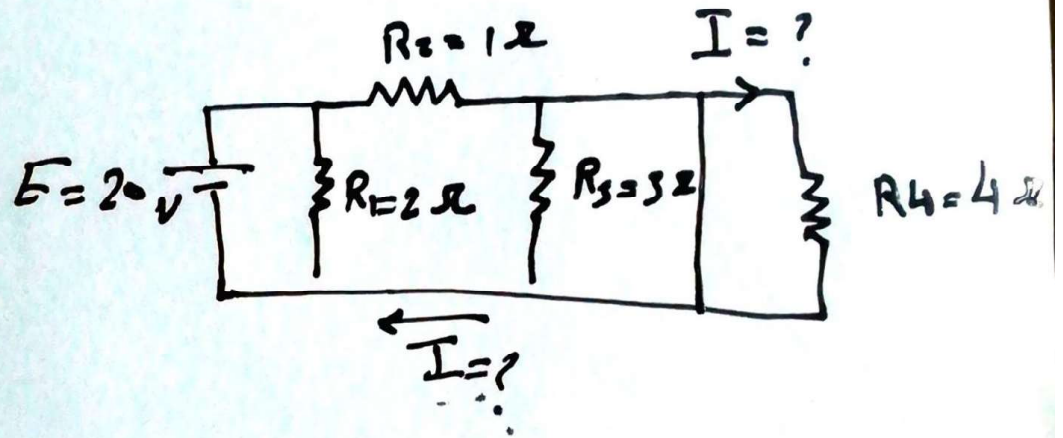

Series and Parallel circuits




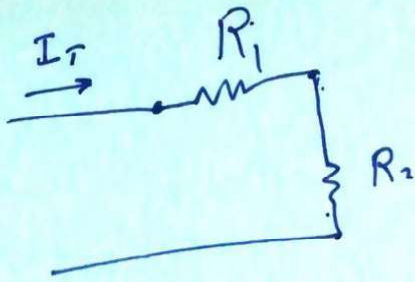



$$I_T = I_{R_1} = I_{R_2}$$

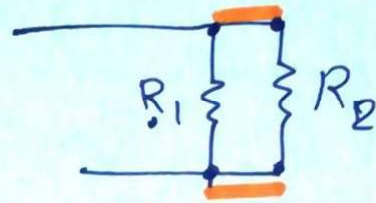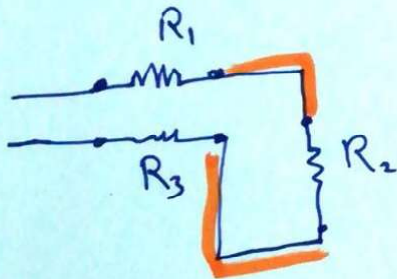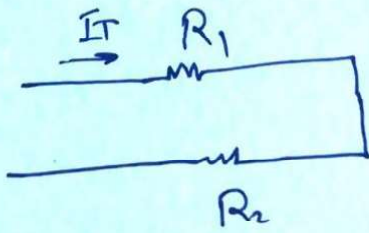



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_T = \frac{R_1 * R_2}{R_1 + R_2}$$

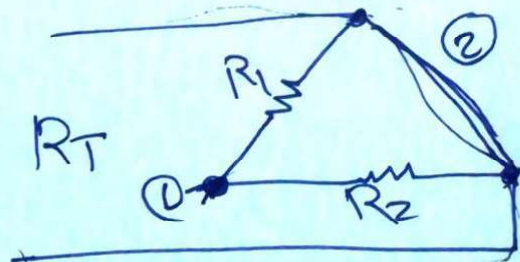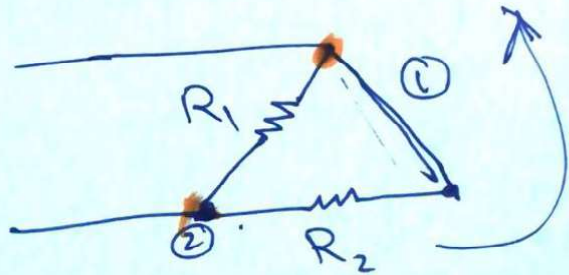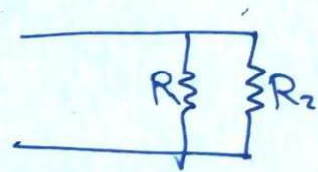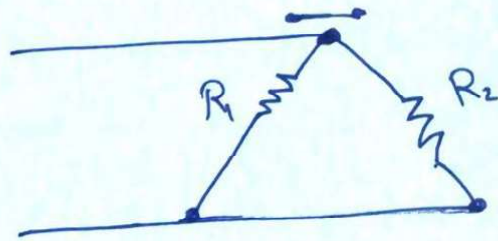


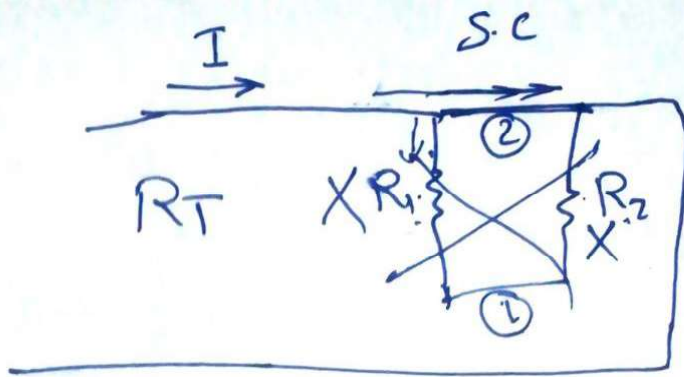


$$R_T = 0$$

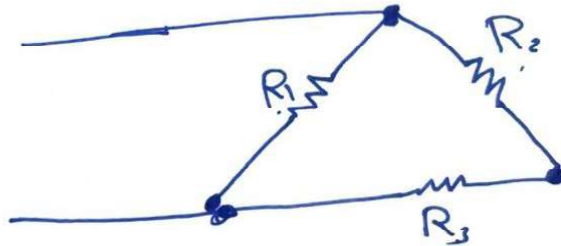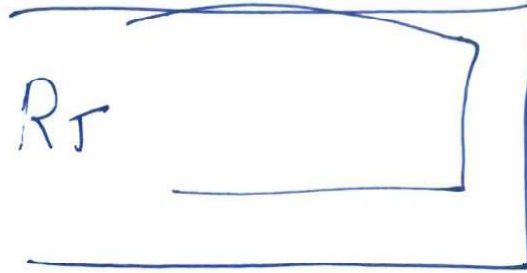


$$R_X = R_1 + R_2$$

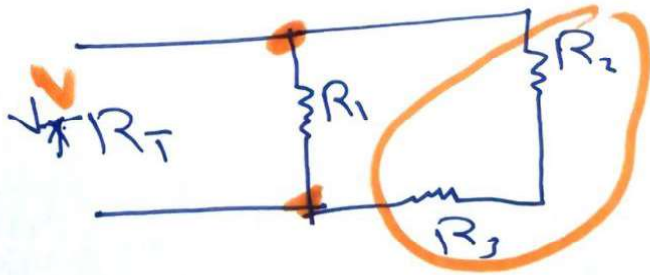

$$R_T = \frac{R_1 R_X}{R_1 + R_X}$$

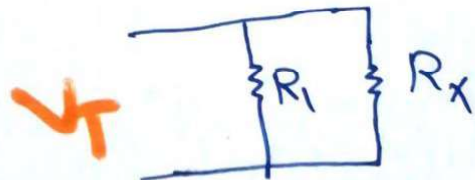


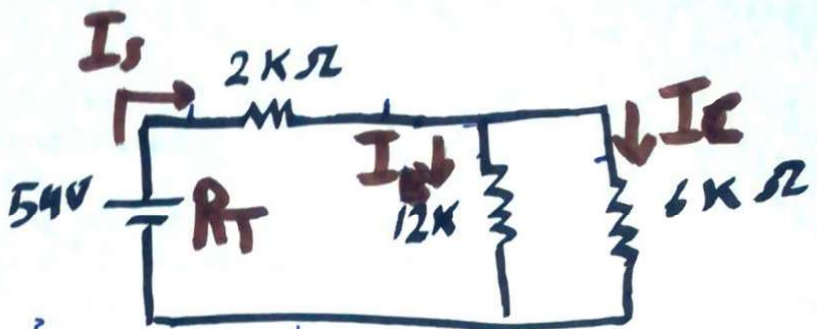Example 1: Calculate the indicated current.




$$6k // 12k = \frac{12 \times 10^3 \times 6 \times 10^3}{12 \times 10^3 + 6 \times 10^3} = 4000 = 4k\Omega$$
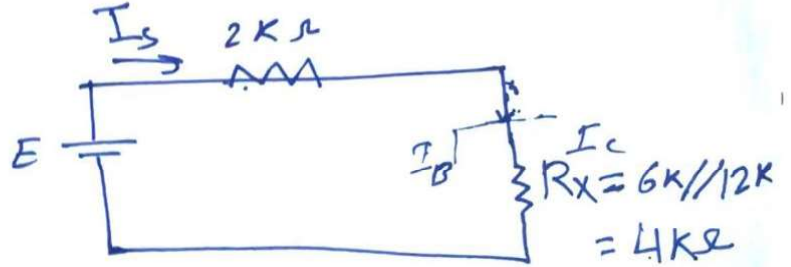
$$R_T = 2 \times 10^3 + 4 \times 10^3 = 6k\Omega$$




$$V = IR$$
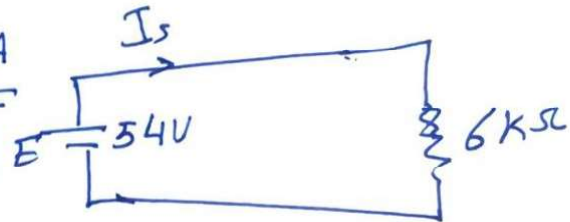
$$I_s = I_T = \frac{E}{R_T} = \frac{54}{6 \times 10^3} = 9mA$$




$$V_{R_X} = 9 \times 10^{-3} \times 4 \times 10^3 = 36V$$
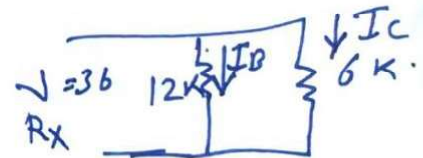
$$I_B = \frac{V_{12k}}{R_{12k}} = \frac{36}{12 \times 10^3} = 3mA$$




$$I_C = \frac{V_{6k}}{R_{6k}} = \frac{36}{6 \times 10^3} = 6mA$$

$$I_T = 3 \times 10^{-3} + 6 \times 10^{-3} = 9mA = I_s$$

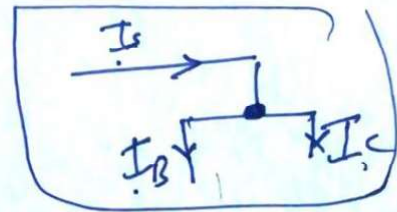

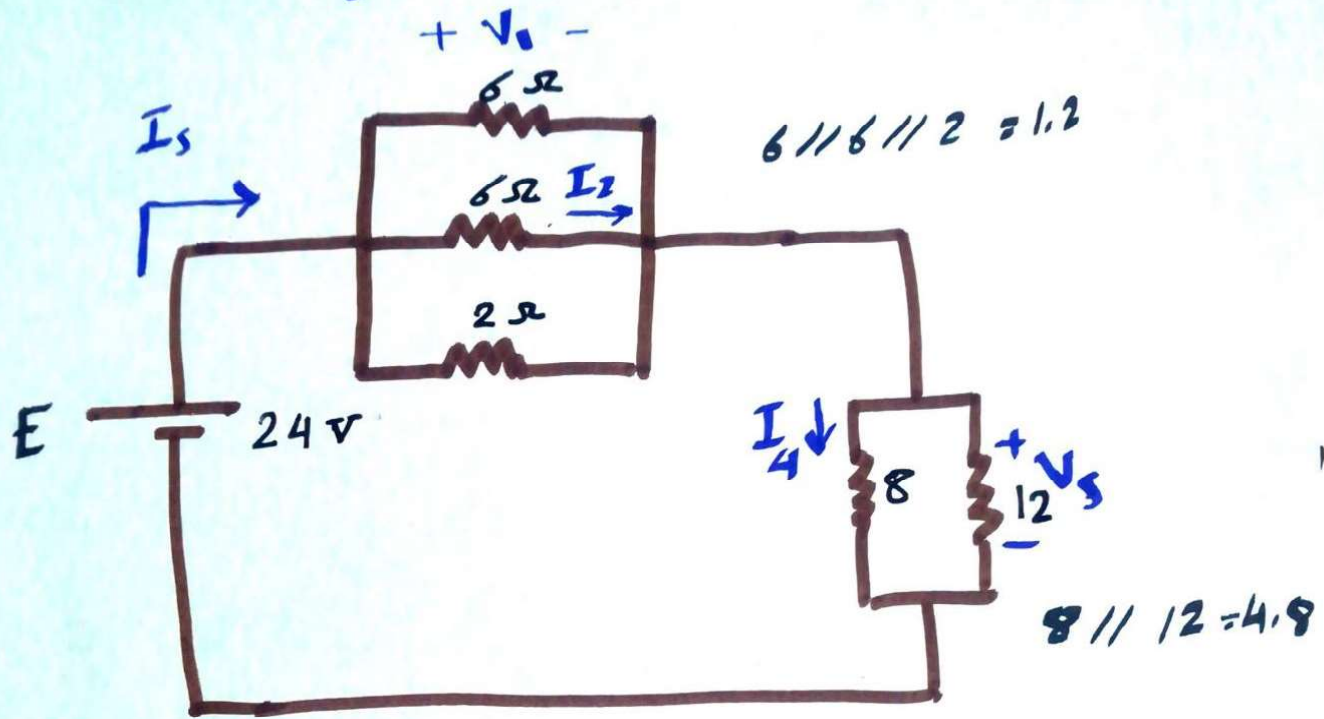
Example 3. Find the indicated current and the voltage for the network.



$$V = IR \quad \therefore I = \frac{V}{R_T}$$

$$R = \frac{R_1 R_2}{R_1 + R_2} = \frac{8 \times 12}{8 + 12} = 4.8 \Omega$$
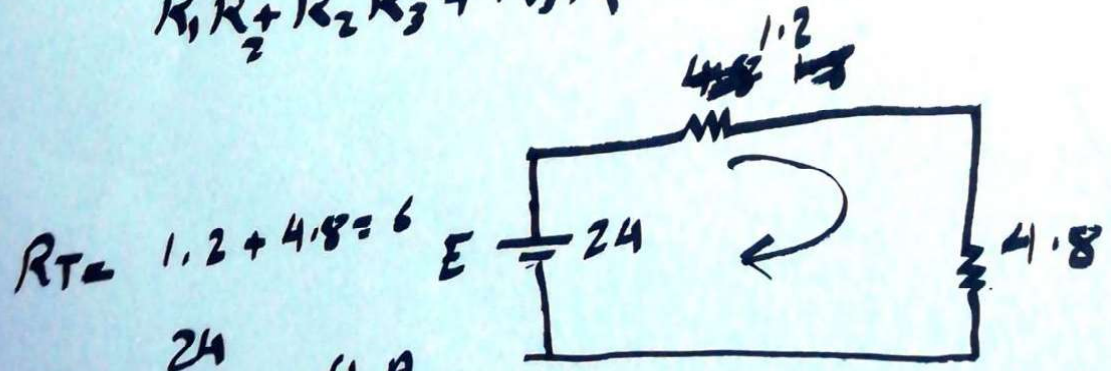
$$R = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} = \frac{6 \times 6 \times 2}{6 \times 6 + 6 \times 2 + 2 \times 6} = 1.2 \Omega$$



$$R_T = 1.2 + 4.8 = 6$$

$$I_T = \frac{24}{6} = 4 \text{ A}$$

$$V = 4.2 \text{ V}$$

$$R_T = 1.2$$



$$V_{1.2\Omega} = IR = 4 \times 1.2 = 4.8 \text{ V}$$


$$V_{4.8} = IR = 4 \times 4.8 = 19.2 \text{ V}$$

$$V_1 = V_{1.2} = 4.2 \text{ V}$$

$$I_2 = ? \quad R = 6$$

$$V = 4.2$$
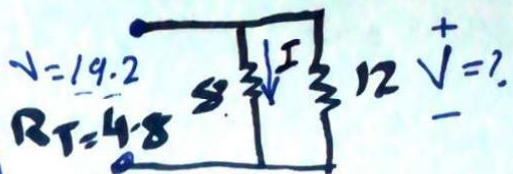
$$I_2 = \frac{V}{R} = \frac{4.2}{6} = 0.7 \text{ A}$$



$$V = 19.2$$

$$R_T = 48$$

$$= 4.8 + 19.2 = 24$$

$$V_{12} = V_8 = V_{1.2} = 19.2 \text{ V}$$

$$I_4 = ?$$

$$R = 8 \quad V = 19.2 \text{ V}$$

$$I = \frac{V}{R} = \frac{19.2}{8} = 2.4 \text{ A}$$


OR

$$I_2 = \frac{4 \times 4.8}{8} = 2.4$$

$$= \frac{I_T \times R_T}{R_8}$$

$$I_T = \frac{19.2}{4.8} = 4$$

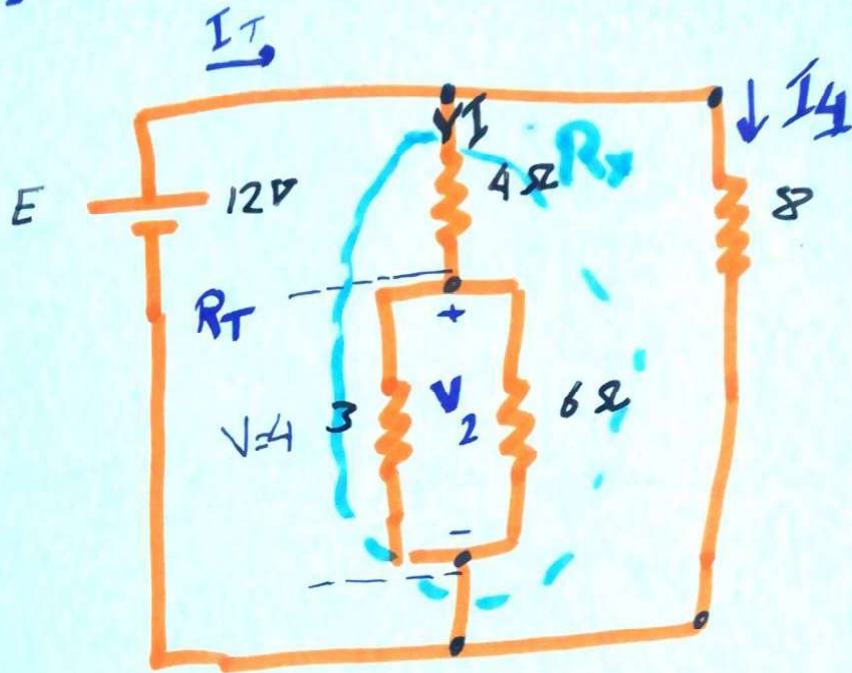EXAMPLE ④ Find the current I_4 and the Voltage V_2 for the network. R_T




$I_4 = ?$

$R = 8$

$V_{R_x} = 12V$



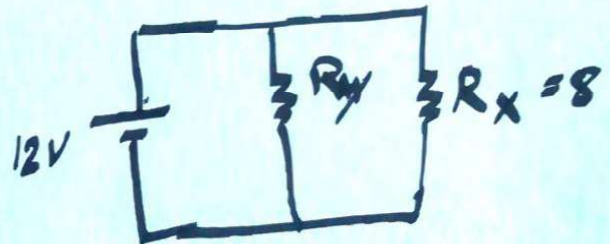
$I_4 = \frac{V}{R} = \frac{12}{8} = 1.5A$




$I = \frac{V}{R} = \frac{12}{6} = 2A$

$V_2 = I \times R = 2 \times 2 = 4V$


$V_2 = 4V$

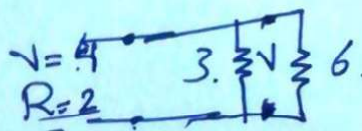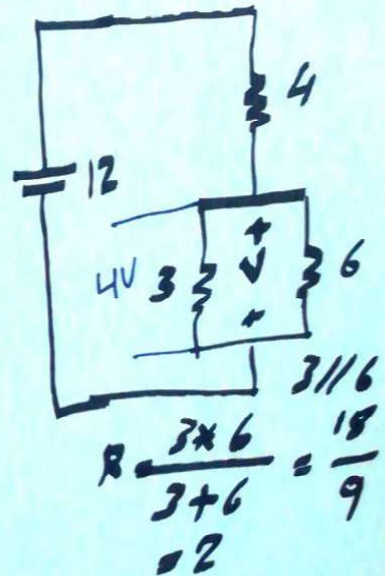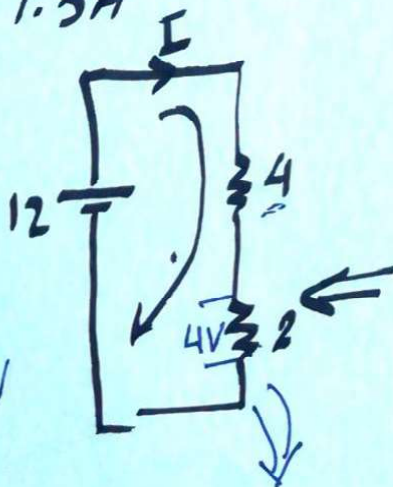

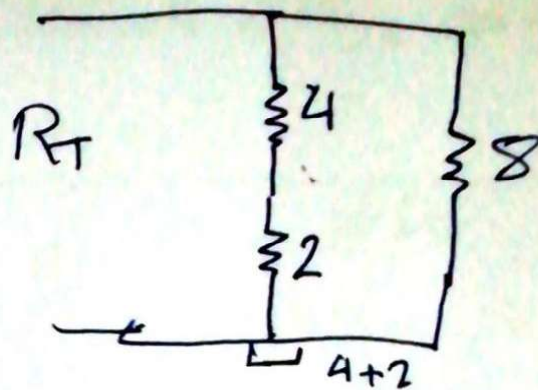


$$R_T = \frac{6 \times 8}{6 + 8} = 3.4$$

$$I = \frac{E}{R} = \frac{12}{3.4} = 3.5A$$

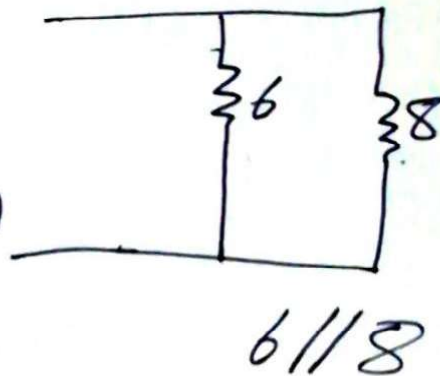

Example 3: Calculate the indicated voltage and current.



5

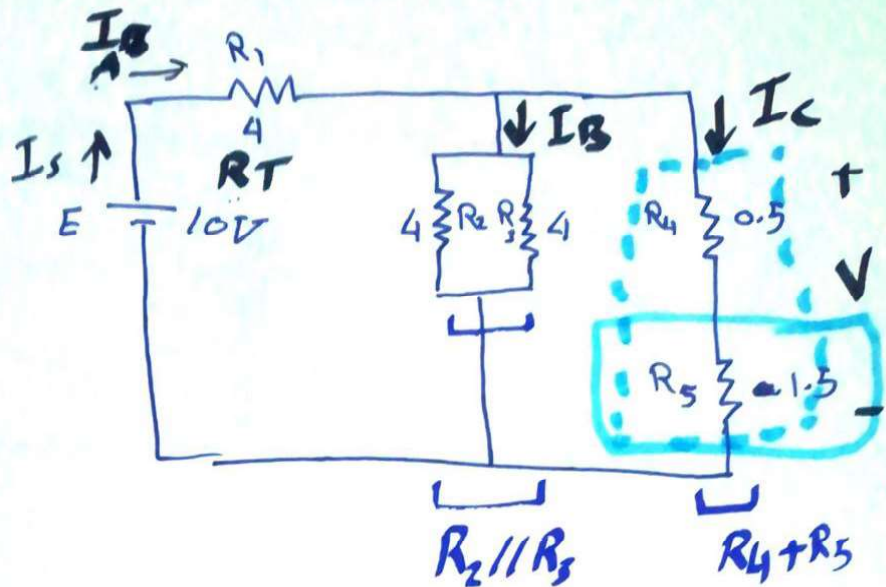

$V = 2V$

H.W

$V_{1.5} = ?$

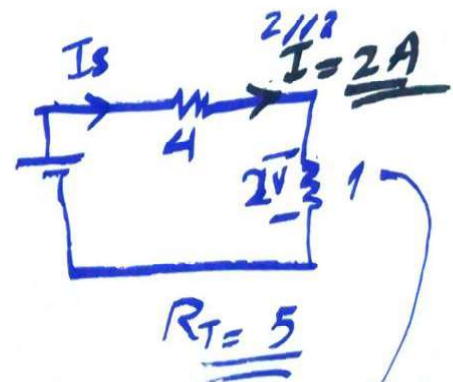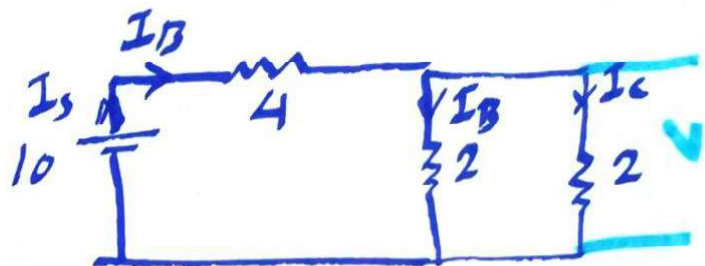

① $R_T = 5$

② $I_s = \frac{V}{R_T} = \frac{10}{5} = \underline{2A}$


③ $I_A = I_s = \underline{2A}$

$V_{1\Omega} = I * R = 2 * 1 = 2$



$I_B = \frac{V}{R} = \frac{2}{2} = 1$ KCL

$I_C = \frac{V}{R} = \frac{2}{2} = 1$




$I = I_B + I_C = 1 + 1 = 2A$

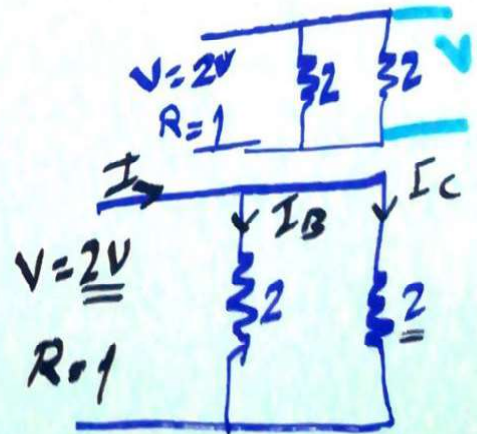

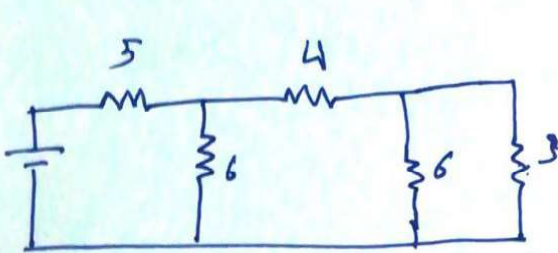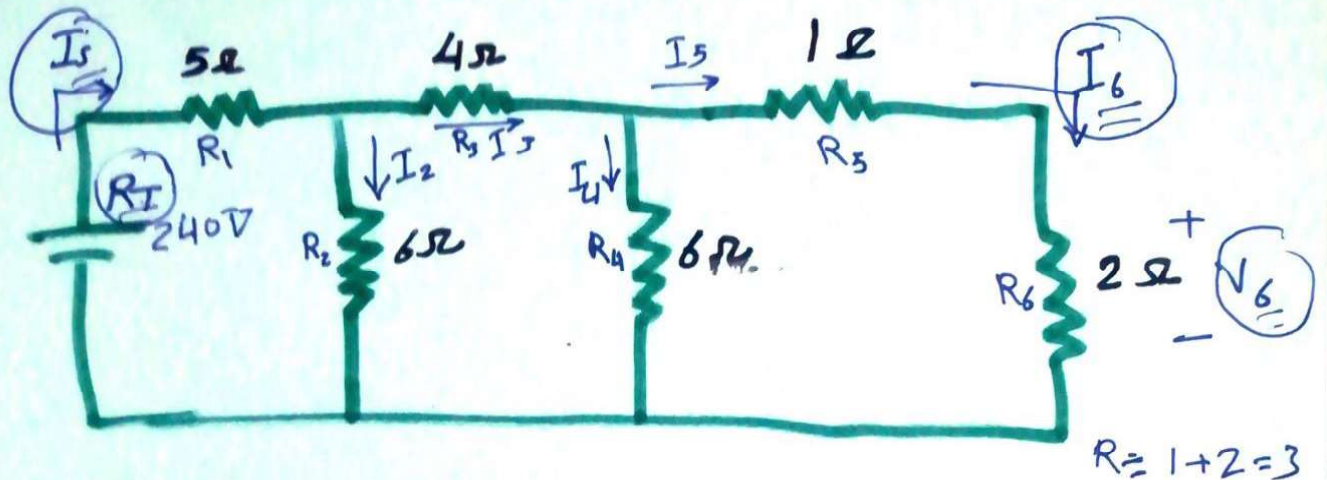
Example 2: Calculate the indicated current and the voltages.


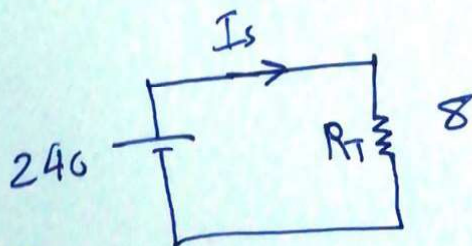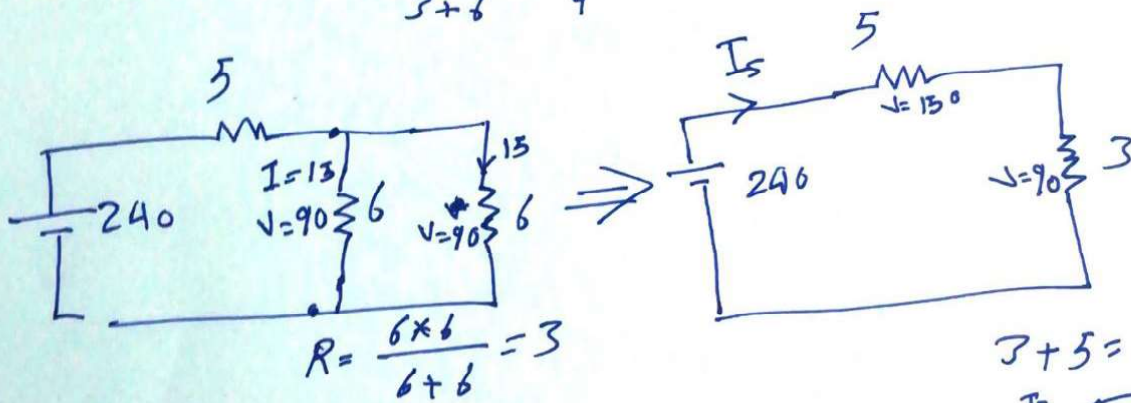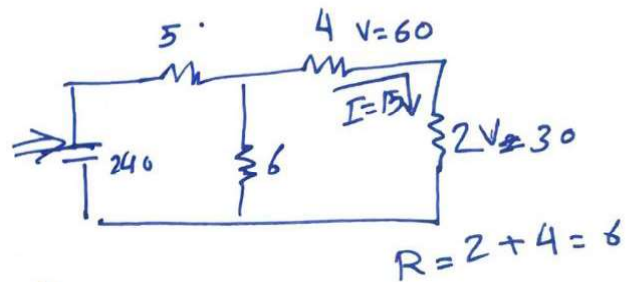
$$\frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2$$


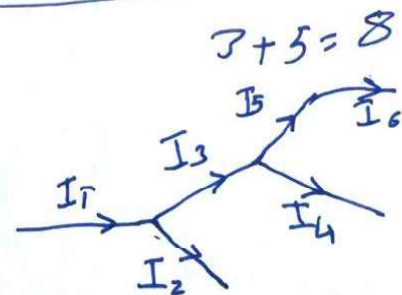
$$I_5 = \frac{E}{R_T} = \frac{240}{8} = 30 \text{ A}$$



$$V_3 = I \times R = 30 \times 5 = 150$$


$$V = 30 \times 3 = 90V$$

$$I_6 = \frac{90}{6} = 15A$$

$$I = \frac{90}{6} = 15A$$

$$V_4 = 15 \times 4 = 60V$$


$$V_2 = 15 \times 2 = 30$$

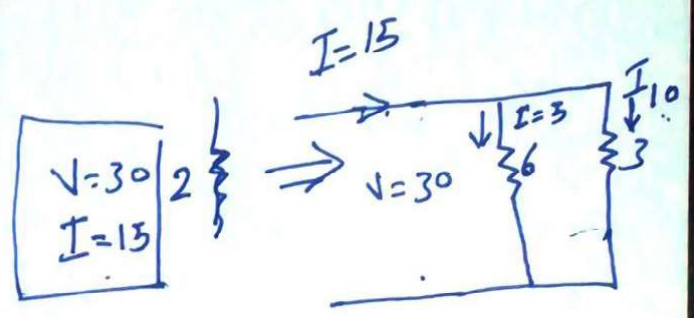

$$I_6 = \frac{V}{R} = \frac{30}{6} = 5A$$

$$I_3 = \frac{V}{R} = \frac{30}{3} = 10A$$
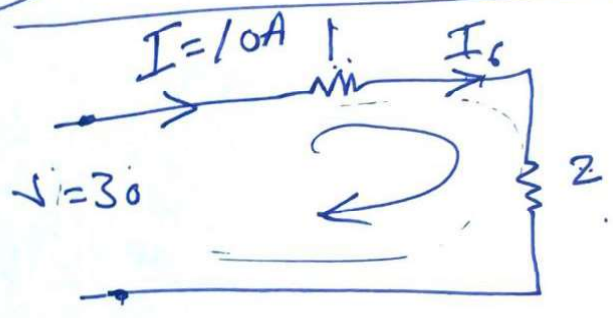
$$\begin{matrix} I = 10A \\ V = 30 \end{matrix} \left. \vphantom{\begin{matrix} I = 10A \\ V = 30 \end{matrix}} \right\} 3 \Omega$$



$$V = IR = 10 \times 1 = 10V$$


$$V_{2\Omega} = IR = 10 \times 2 = 20V$$

$$V_T = 10 + 20 = 30V$$



$$I_6 = 10A$$

$$V_6 = 20V$$



Delta - star transformation

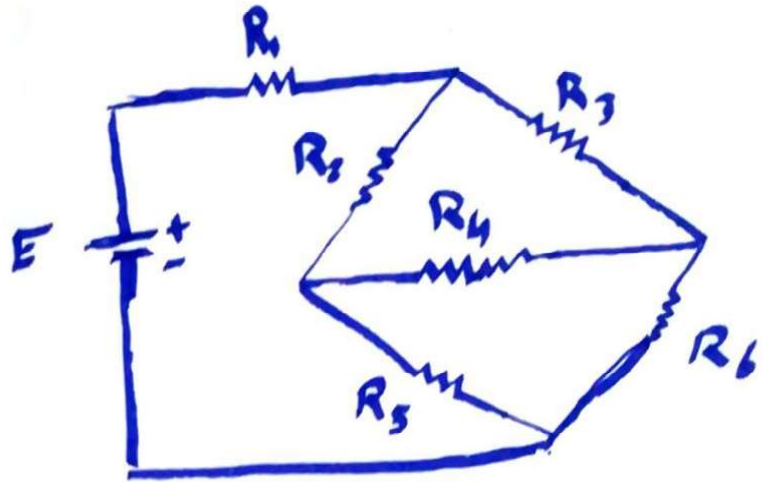


~~Wavy~~ star (Y or star) connection

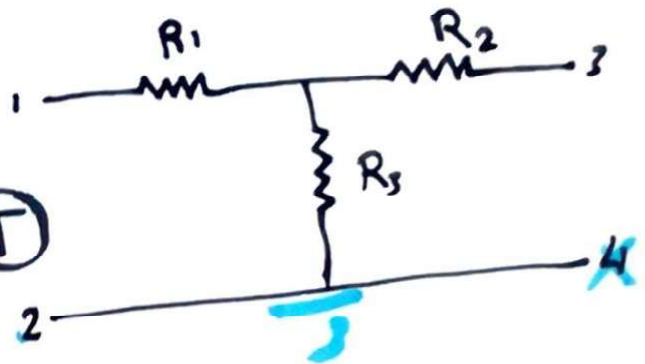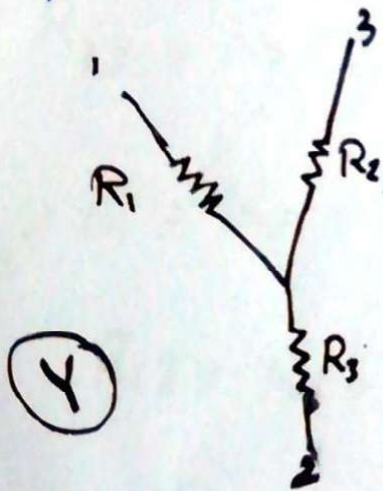


* Delta (Δ or π) connect

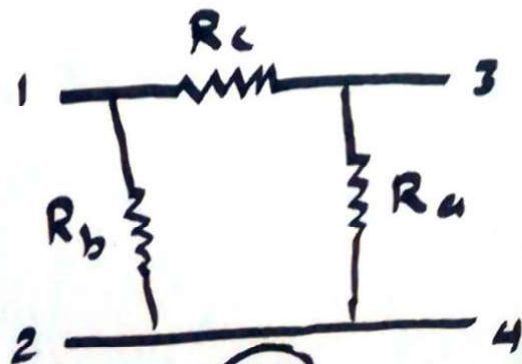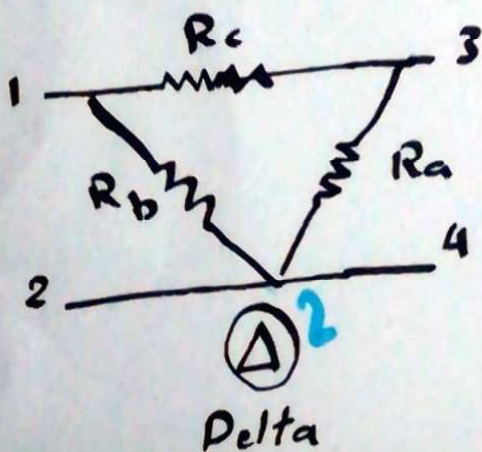
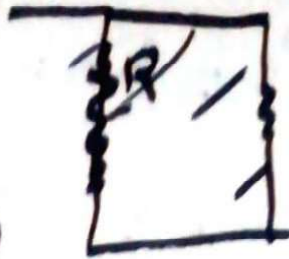
$$R_{12} = \frac{R_b (R_c + R_a)}{R_b + (R_c + R_a)} \quad \text{--- (1)}$$


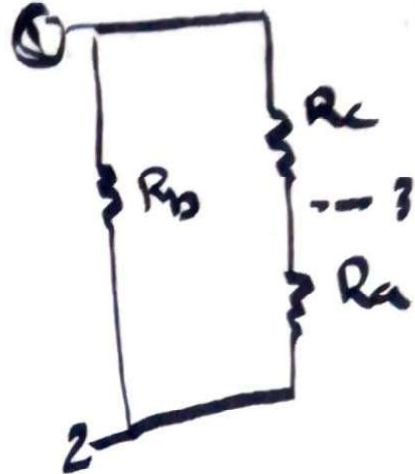
$$R_{13} = \frac{R_c (R_a + R_b)}{R_c + R_b + R_a} \quad \text{--- (2)}$$



$$R_{23} = \frac{R_a (R_c + R_b)}{R_a + R_b + R_c} \quad \text{--- (3)}$$

$$R_{12} = R_1 + R_3 \quad \text{--- (4)}$$


$$R_{13} = R_1 + R_2 \quad \text{--- (5)}$$

$$R_{23} = R_2 + R_3 \quad \text{--- (6)}$$

$$R_{12} = R_1 + R_3 = \frac{R_b (R_c + R_a)}{R_b + R_c + R_a} \quad \text{--- (1)}$$

$$R_{13} = R_1 + R_2 = \frac{R_c (R_a + R_b)}{R_c + R_b + R_a} \quad \text{--- (2)}$$
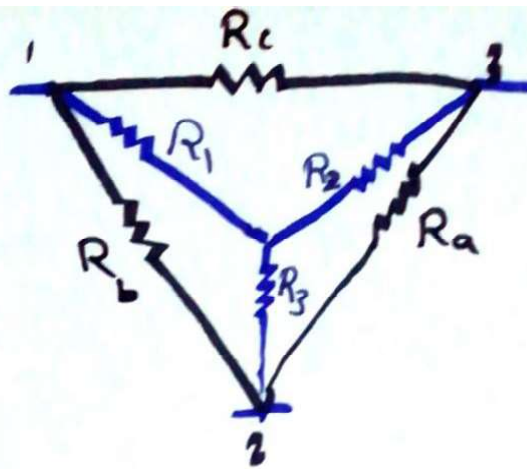
$$R_{23} = R_2 + R_3 = \frac{R_a (R_c + R_b)}{R_a + R_b + R_c} \quad \text{--- (3)}$$



⊙ Δ to ⊙ Y transformation

$$R_1 = \frac{R_c \times R_b}{R_a + R_b + R_c}$$



$$R_2 = \frac{R_c \times R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a \times R_b}{R_a + R_b + R_c}$$

$$R_c = R_b = R_a = R_\Delta$$

$$R_1 = R_2 = R_3 = R_Y$$

$$R_Y = \frac{R_\Delta}{3}$$

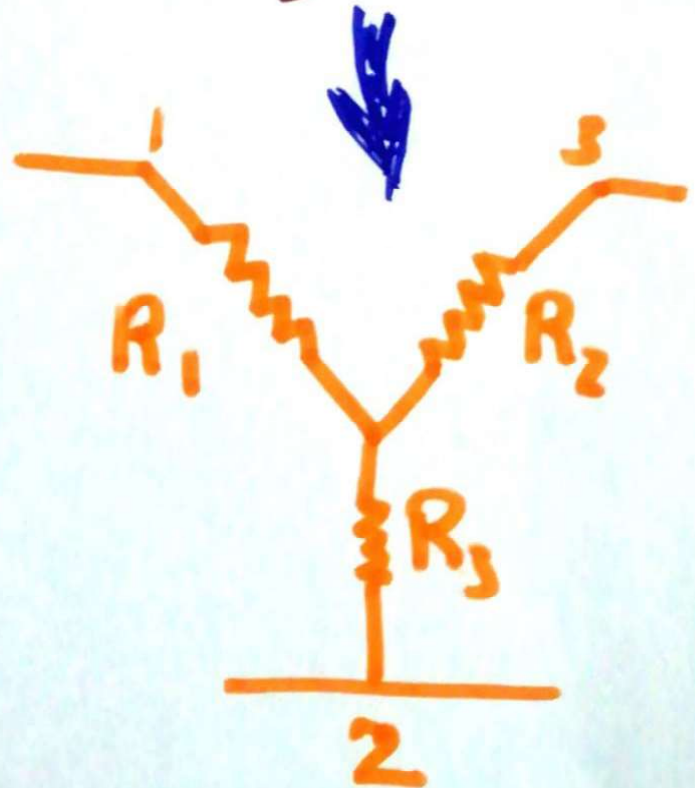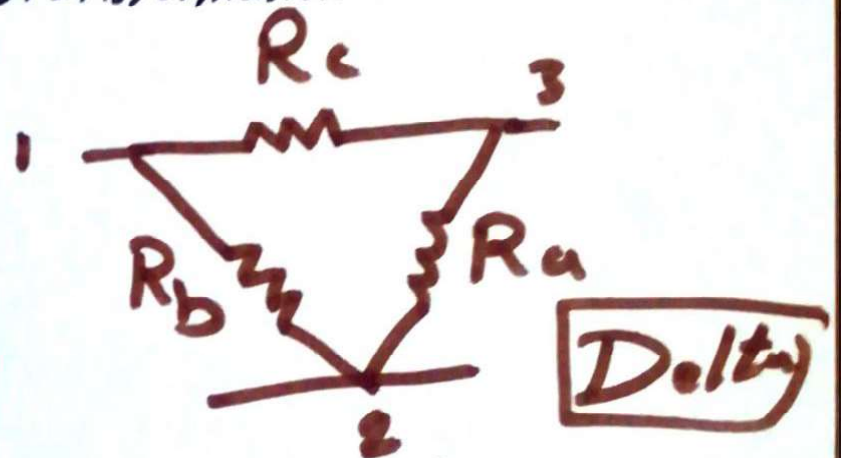

Wye to Delta Transformation

(Y)

(Δ)

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$




$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


$$R_1 = R_2 = R_3 = R_Y$$

$$R_a = R_b = R_c = R_\Delta$$

$$R_\Delta = 3R_Y$$

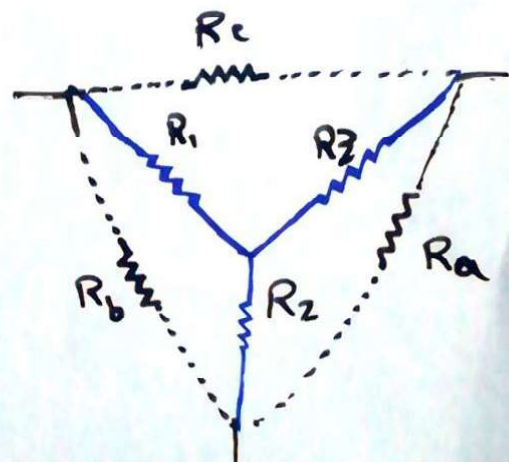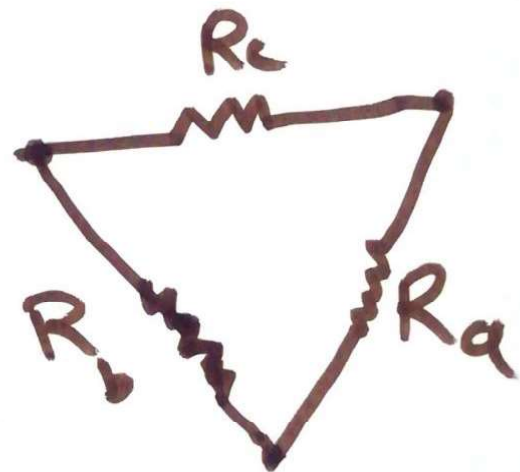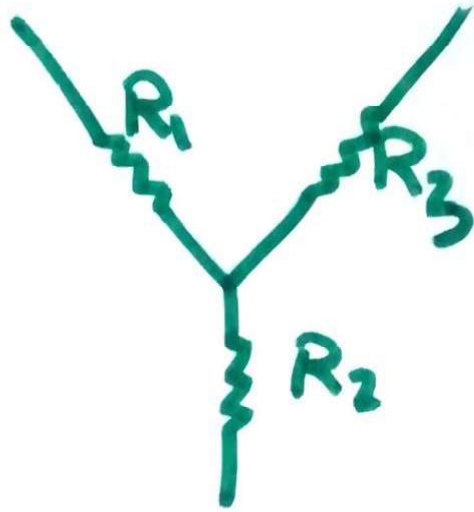

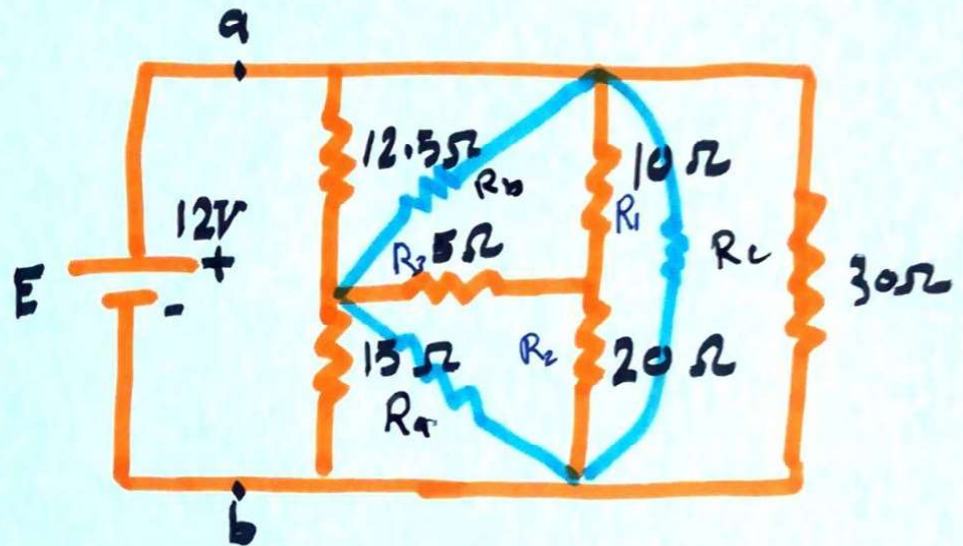Example is obtain the equivalent resistance R_{ab} for the circuit shown and use it to find the current I .





Solution:

$$R_a = \frac{R_1 R_3 + R_2 R_3 + R_3 R_1}{R_1} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10} = 35$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{20} = 17.5$$
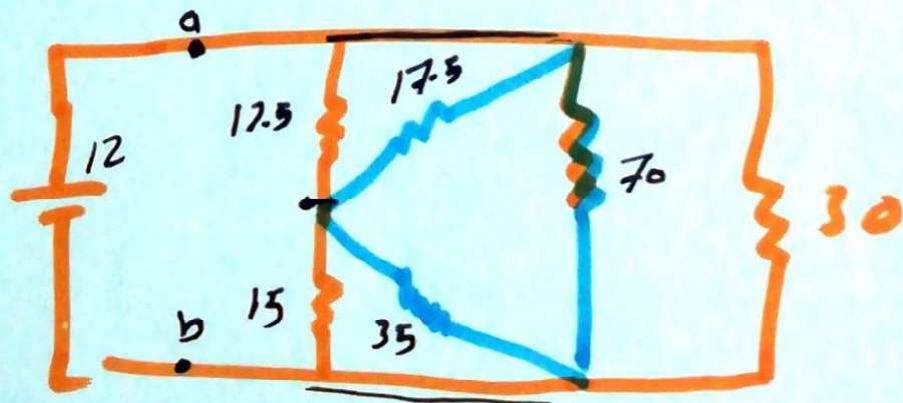
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{5} = 70$$




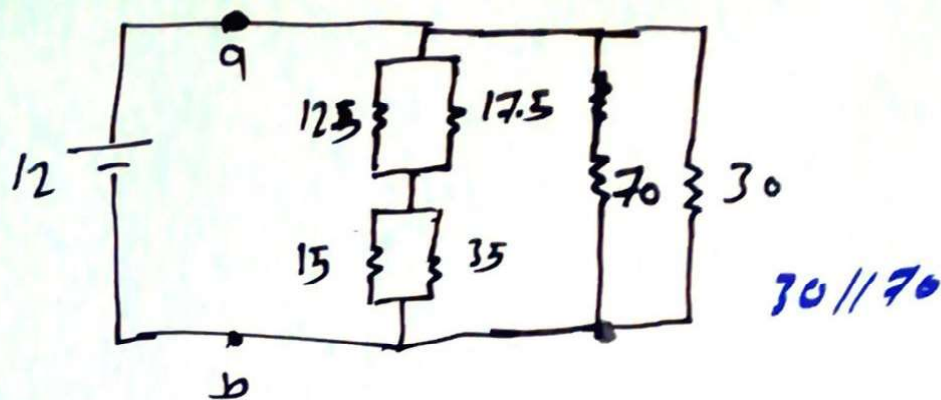

$$30 // 70 = \frac{30 \times 70}{30 + 70} = 21 \Omega$$



$$17.5 // 12.5 = \frac{17.5 \times 12.5}{17.5 + 12.5} = 7.3 \Omega$$
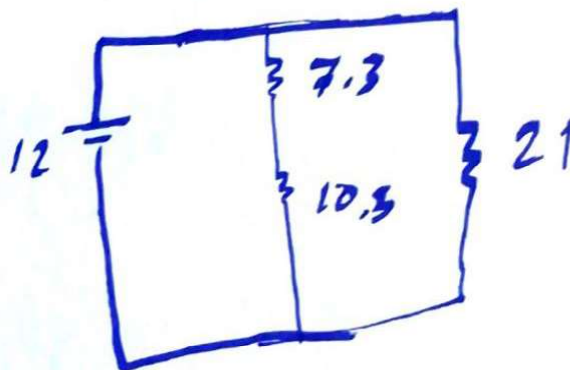
$$15 // 35 = \frac{15 \times 35}{15 + 35} = 10.5 \Omega$$



$$R_{ab} = 17.5 // 21 = \frac{17.5 \times 21}{17.5 + 21} = 9.63 \Omega$$
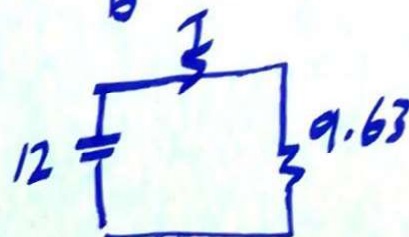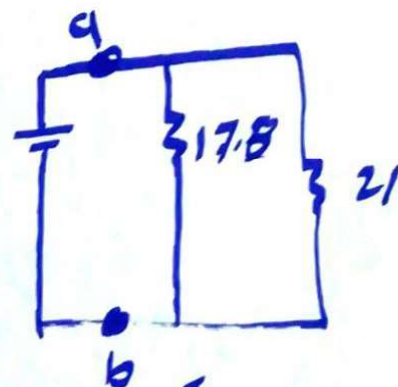
$$I_T = \frac{E}{R_T} = \frac{12}{9.63} = 1.246 \text{ A}$$



Example =- ~~Three~~ Three resistors are connected in series across a 12V battery. The first resistor has a value of 1Ω , the second has a voltage drop of 4V, and the third has a power 12W. Calculate the value of the circuit current.

Solution :-

$$P_{R_3} = 12 \quad R_1 = 1\Omega$$

$$P_3 = I^2 R_3 = 12 \quad \text{--- (1)}$$

$$V_2 = IR_2 = 4V$$

$$I = \frac{4}{R_2} \quad \text{--- (2)}$$

$$\left(\frac{4}{R_2}\right)^2 R_3 = 12 \Rightarrow R_3 = \frac{12}{16} R_2^2 \Rightarrow R_3 = \frac{3}{4} R_2^2$$

$$\text{KVL} \cdot E = V_1 + V_2 + V_3$$


$$E = IR_1 + IR_2 + IR_3$$

$$12 = I \left(1 + R_2 + \frac{3}{4} R_2^2\right) \Rightarrow 12 = \frac{4}{R_2} \left(1 + R_2 + \frac{3}{4} R_2^2\right)$$

$$\frac{12R_2}{4} = 1 + R_2 + \frac{3}{4} R_2^2$$

$$3R_2 = 1 + R_2 + \frac{3}{4} R_2^2 \Rightarrow \left(\frac{3}{4} R_2^2 - 2R_2 + 1 = 0\right)$$
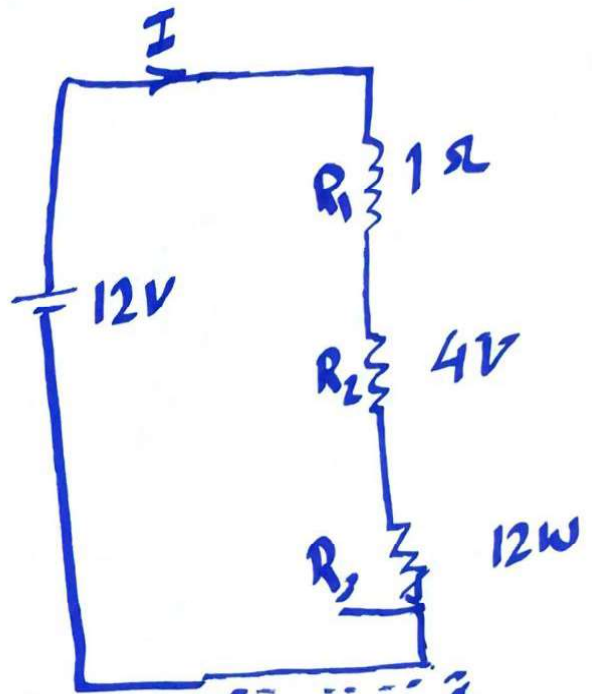
$$\underbrace{3R_2^2}_{(a)} - \underbrace{8R_2}_{(b)} + \underbrace{4}_{(c)} = 0$$



$$R_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{8 \pm \sqrt{64 - 48}}{2 \times 3} =$$

OR

$$R_2 = 2 \Omega$$

$$R_2 = \frac{2}{3} \Omega$$

$$R_3 = \frac{3}{4} R_2$$

$$R_3 = 3$$

$$R_3 = \frac{1}{3}$$

$$\textcircled{1} I = \frac{V}{R_T} = \frac{12}{1+2+3} = \frac{12}{6} = 2 \text{ A}$$

$$\textcircled{2} I = \frac{V}{R_T} = \frac{12}{1 + \frac{2}{3} + \frac{1}{3}} = 6 \text{ A}$$

Solution (2)

$$P_3 = 12 \text{ W}$$

$$3 = IV_3$$

$$V_2 = 4$$

$$R_1 = 1$$

$$E = 12 \text{ V}$$

$$E = V_1 + V_2 + V_3$$

$$12 = IR_1 + 4 + \frac{12}{I}$$

$$P_3 = IV_3$$

$$V_3 = \frac{P_3}{I} = \frac{12}{I}$$

$$8 = \frac{I}{I} + \frac{12}{I}$$

$$\frac{I+12}{I} = 8 \Rightarrow \frac{I^2 + 12}{I} = 8$$

$$\Rightarrow I^2 + 12 = 8I$$

$$I^2 - 8I + 12 = 0$$



$$a = 1 \quad b = -8 \quad c = 12$$

$$I = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{8 \pm \sqrt{64 - 48}}{2} =$$


$$I = 6A$$

$$I = 2A'$$

Calculate R_{ab}

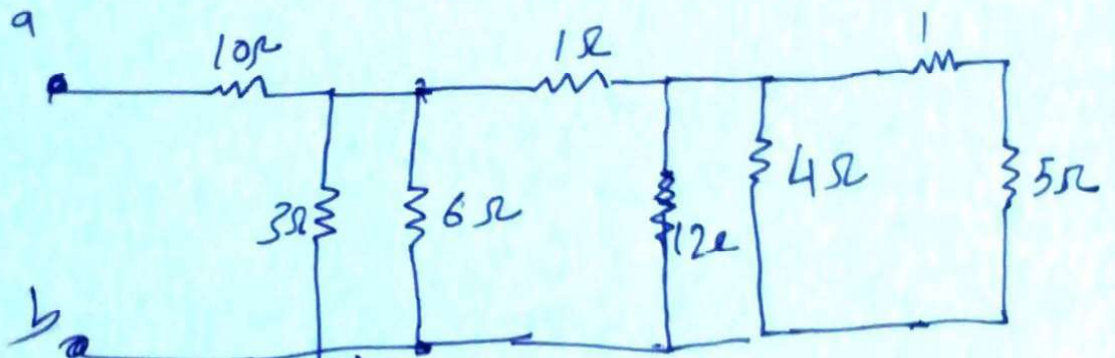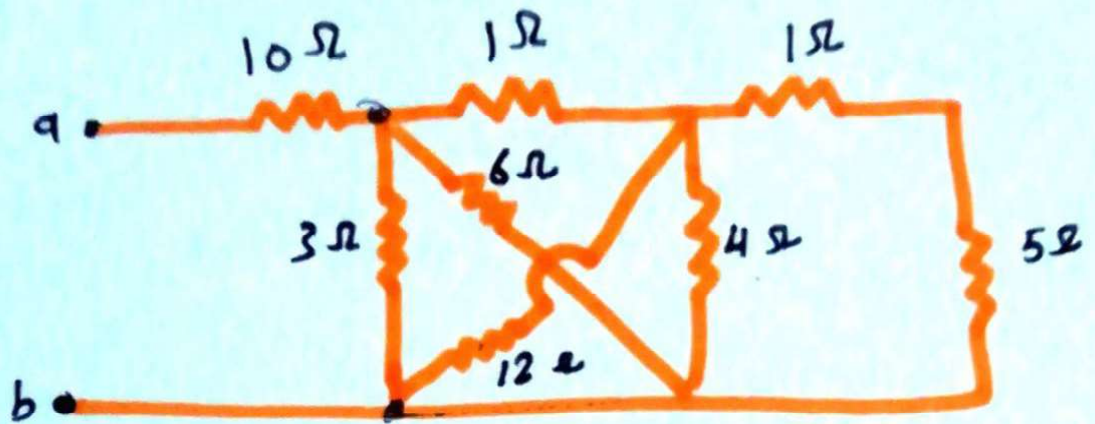

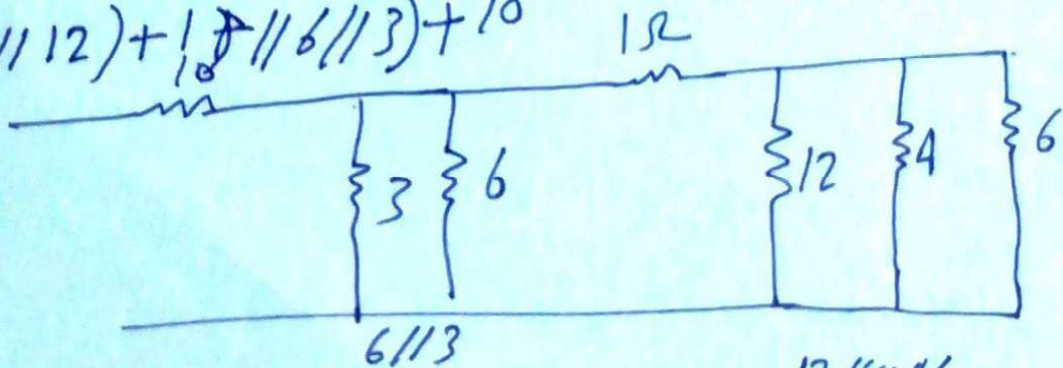
$$\left(\frac{1}{\frac{1}{3} + \frac{1}{6}} + 1 + \frac{1}{\frac{1}{12} + \frac{1}{4}} \right) + 5$$




$$R = \frac{R_1 R_2 R_3}{R_2 R_1 + R_2 R_3 + R_3 R_1} = \frac{12 \times 4 \times 6}{12 \times 4 + 4 \times 6 + 6 \times 12} = 2$$
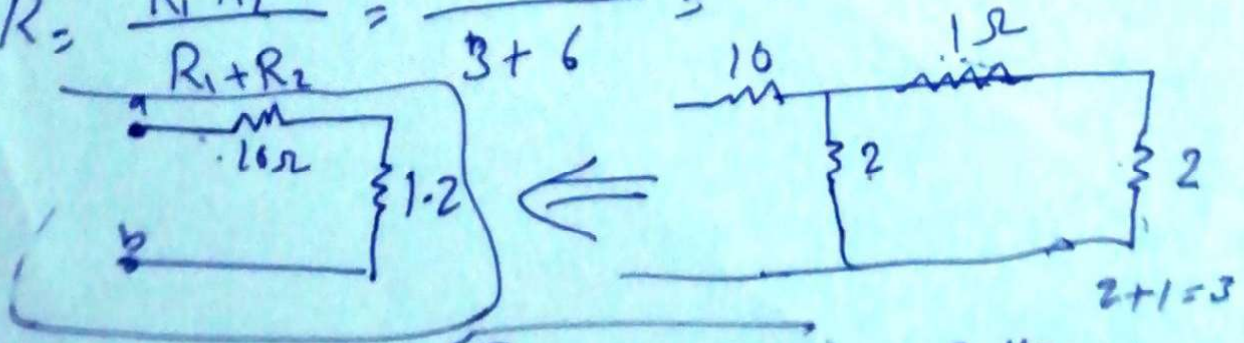
$$R = \frac{R_1 R_2}{R_1 + R_2} = \frac{3 \times 6}{3 + 6} = 2$$



$$R_{ab} = 11.2 \Omega$$

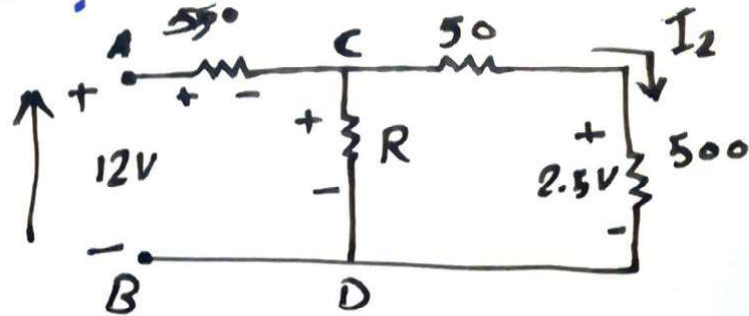Example 20: What is the value of the unknown resistor R in the circuit shown, if the voltage drop across the $500\ \Omega$ resistor is 2.5 V ? All resistors are in Ohms.



Solution:

$$I_2 = \frac{V_{500}}{R} = \frac{2.5}{500} = 5 \times 10^{-3} = 5\text{ mA}$$

$$V_{50} = R_{50} \times I_2 = 50 \times 5 \times 10^{-3} = 0.25\text{ V}$$

$$V_R = V_{50} + V_{500} = 0.25 + 2.5$$

$$V_R = 2.75\text{ V}$$

$$V_{CD} = 2.75$$



$$E = V_{50} + V_{CD} \Rightarrow 12 = V_{50} + 2.75$$

$$V_{50} = 12 - 2.75 = 9.25\text{ V}$$


$$I_{500} = I_T = \frac{V_{500}}{R_{500}} = \frac{9.25}{500} = 0.0168\text{ A}$$

$$I_T = I_1 + I_2 \Rightarrow 0.0168 = I_1 + 5 \times 10^{-3}$$
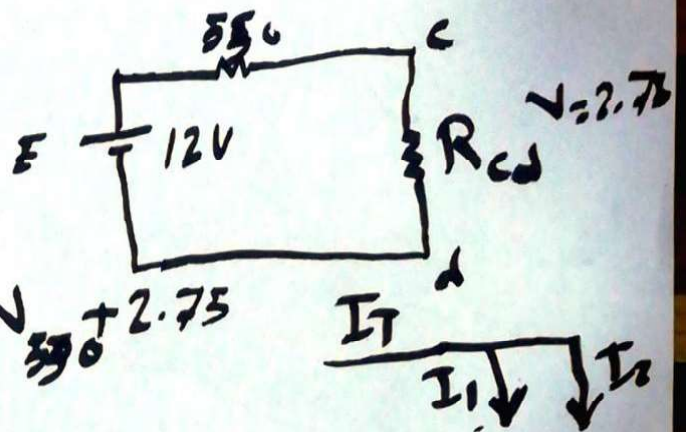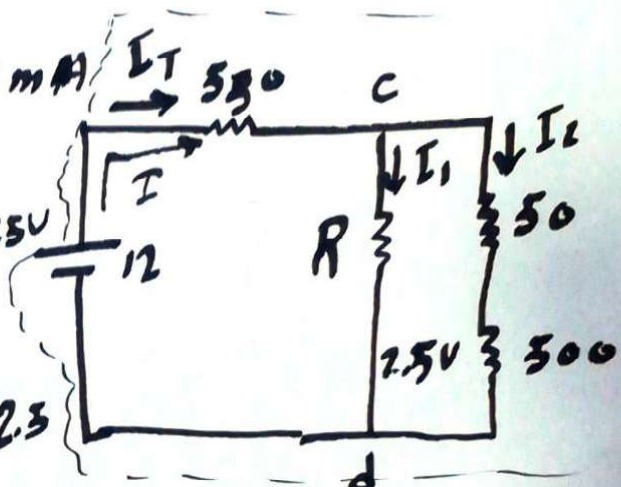
$$I_1 = 0.0118\text{ A} \quad R = \frac{V}{I_1} = \frac{2.75}{0.0118} = 233\ \Omega$$



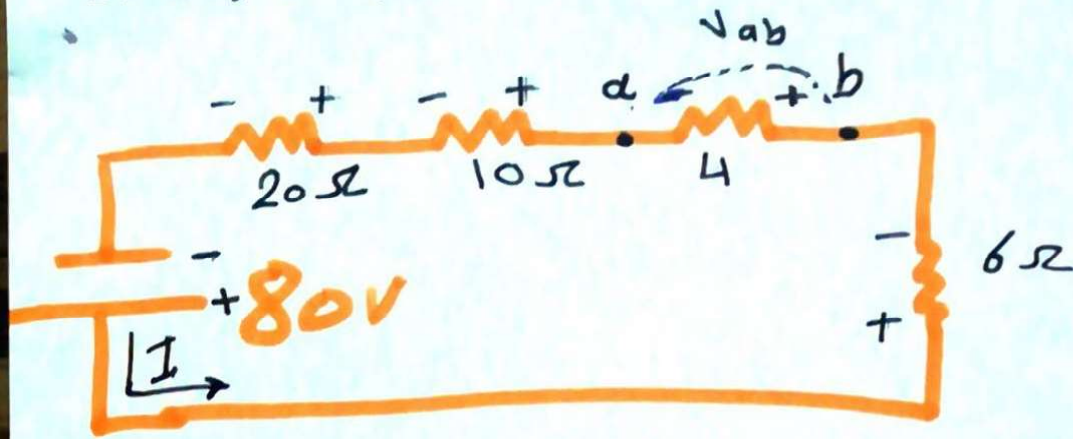Example: For the networks shown, find (V_{ab})




$$V_{ab} = \frac{E \cdot R_4}{R_T} = \frac{80 \times 4}{40} = 8V$$

$$V_{ab} = -\frac{80 \times 4}{40} = -8V$$

$$V_{ab} = V_a - V_b$$



$$V_{ba} = -V_{ab}$$
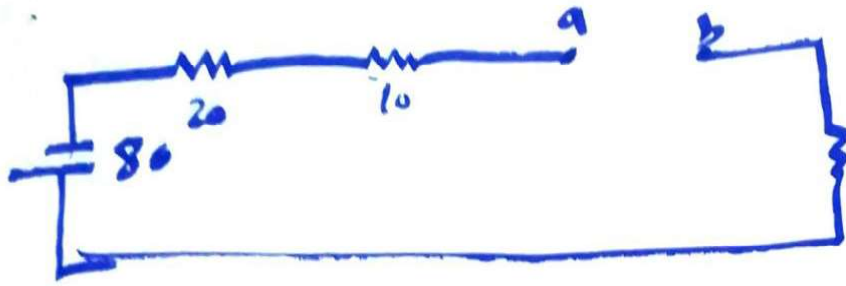
$$V_{ba} = V_b - V_a = -V_{ab} = -(-8) = 8$$




$V_{ab} = ?$


$V_{ab} = E = -80$

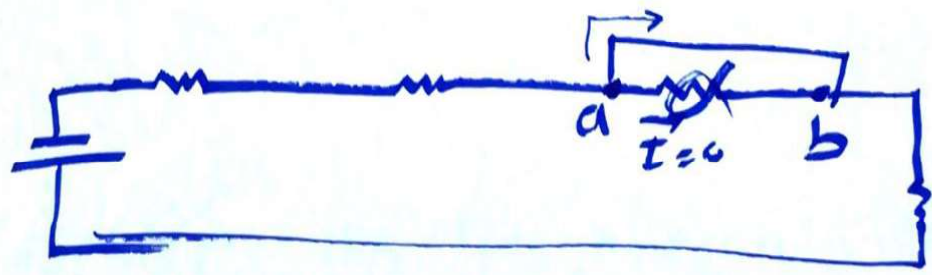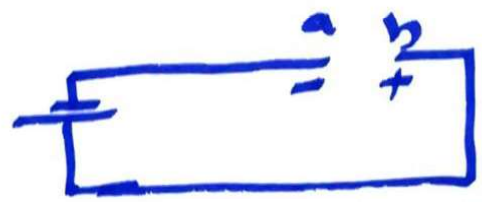


$V_{ab} = 0$

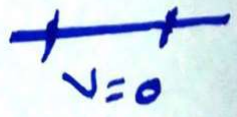

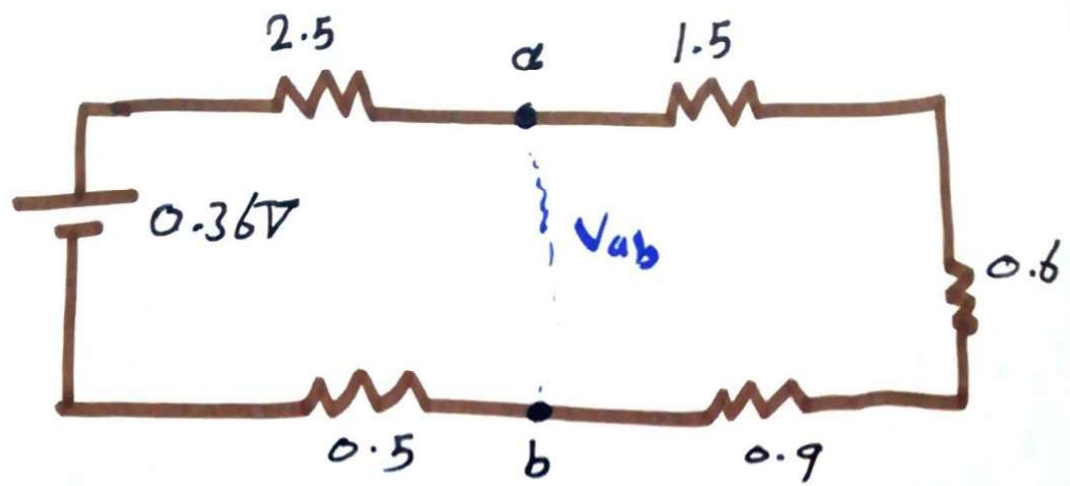Example 2: For the network shown, find V_{ab}



$$V_{ab} = \frac{E R_{ab}}{R_T}$$

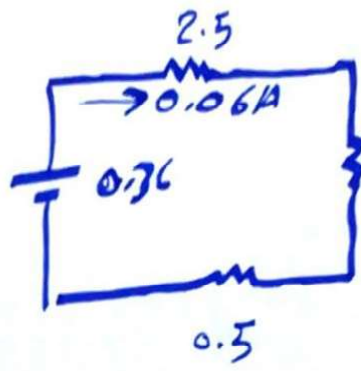

$$R_{ab} = 1.5 + 0.6 + 0.9$$

$$V_a = \frac{0.36 \times 3}{2.5 + 0.5 + 3}$$

$$V_{ab} = \cancel{1.73} \times 1.8 = 0.18 \text{ V}$$

$$I = \frac{V}{R_T} = \frac{0.36}{6} = 0.06 \text{ A}$$

$$V_{ab} = V_{1.5} + V_{0.6} + V_{0.9} = 0.06 \times 1.5 + 0.06 \times 0.6 + 0.9 \times 0.06 =$$


$$V_{ab} = 0.18$$

$$E = V_{2.5} + V_{0.5} + V_{ab}$$

$$0.36 = 0.06 \times 2.5 + 0.06 \times 0.5 + V_{ab}$$

$$V_{ab} = 0.36 - 0.18 = 0.18 \text{ V}$$

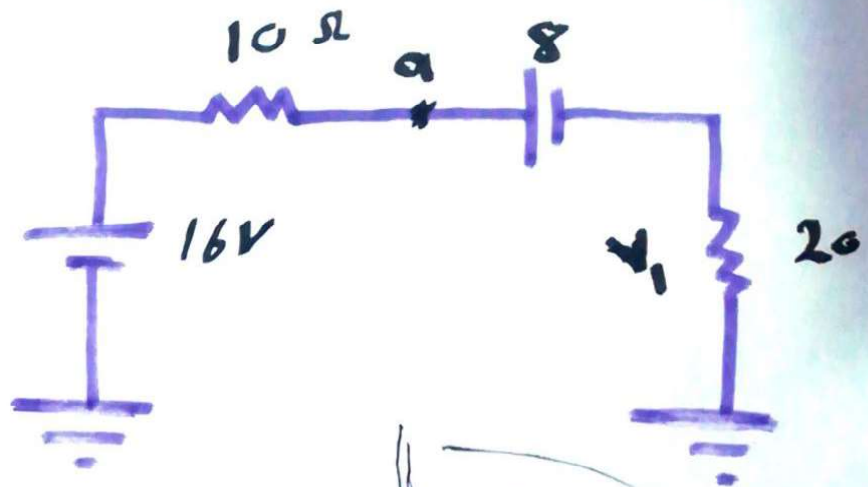Example: Determine the voltage V_a and V_1 for the network shown.



Solution:

$$V_a = V_a - 0$$

$$V = V_{10} + V_a$$


$$16 = I(10) + V_a \quad \text{--- (1)}$$

$$I = \frac{E}{R_T} = \frac{8}{30} \quad \text{--- (2)}$$

$$16 = \frac{8}{30} * 10 + V_a$$

$$V_a = 16 - \frac{8}{3} = \frac{40}{3}$$

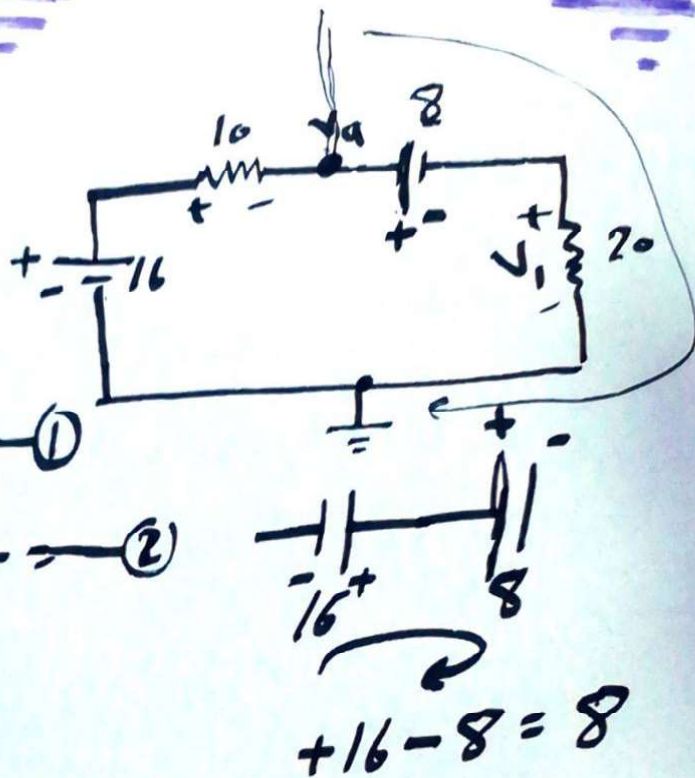
$$V_1 = IR = \frac{8}{30} * 20 = \frac{16}{3} \text{ V}$$



OR

$$V_a = V_{8V} + V_{20}$$

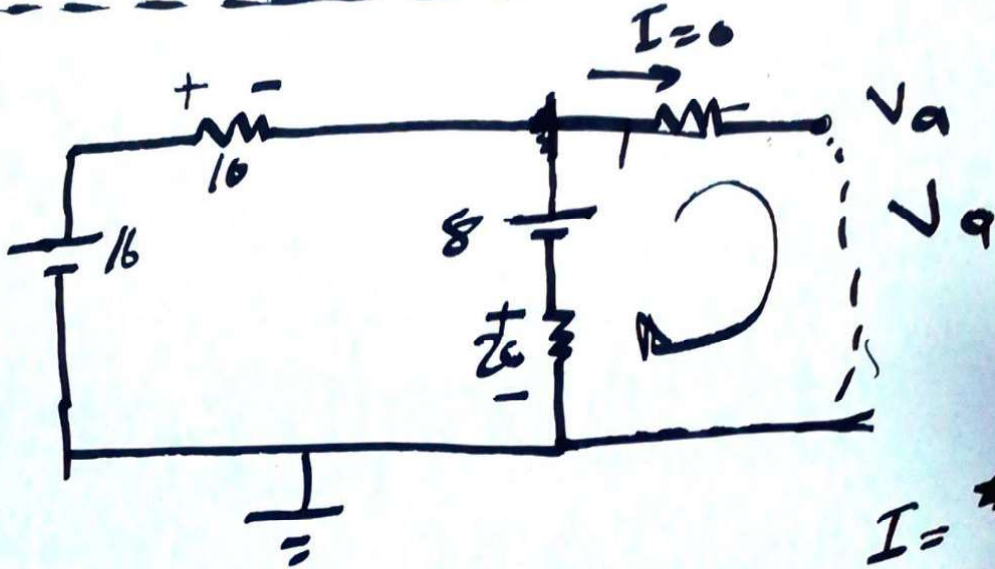
$$V_a = 8 + IR_{20} = 8 + \frac{8}{30} \cdot 20 = \frac{40}{3} V$$




$$V_a = V_a - 0 = V_a$$

$$\begin{aligned} V_a = 8 + V_{20} &= 8 + I \cdot 20 \\ &= 8 + \frac{8}{30} \cdot 20 = \frac{40}{3} \end{aligned}$$

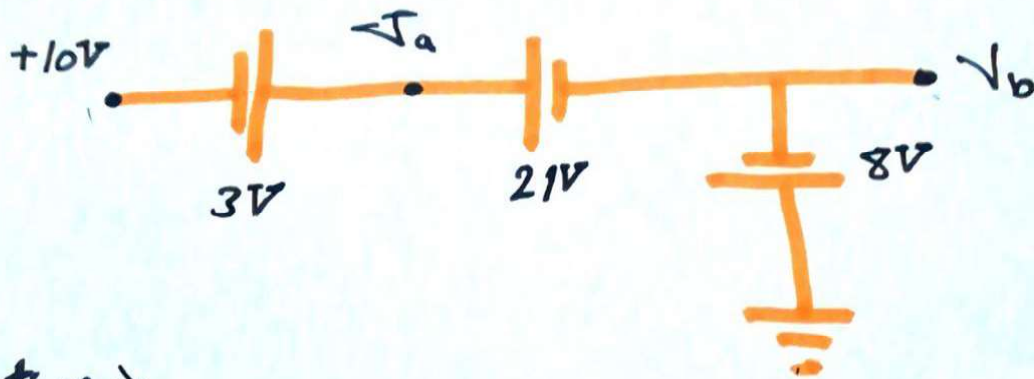Example: Determine the Voltage V_{ab} for the network shown.



Solution:

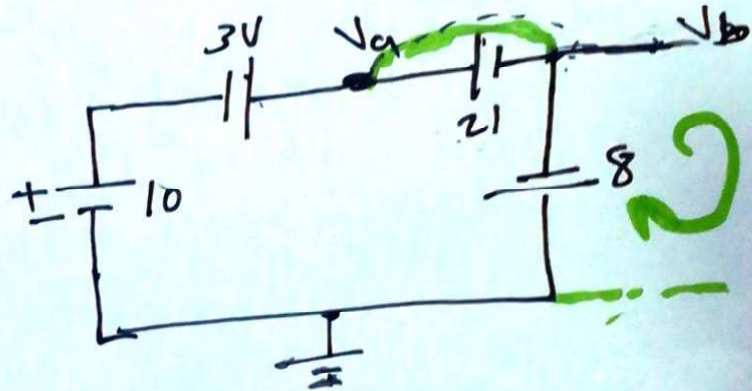

$$V_{ab} = V_a - V_b$$

$$V_{ab} = 21$$


$$V_a = V_a - 0$$

$$V_a = 21 - 8 = 13$$

$$V_b = V_b - 0 = -8$$

$$V_{ab} = V_a - V_b = 13 - (-8) = 21 \text{ V}$$

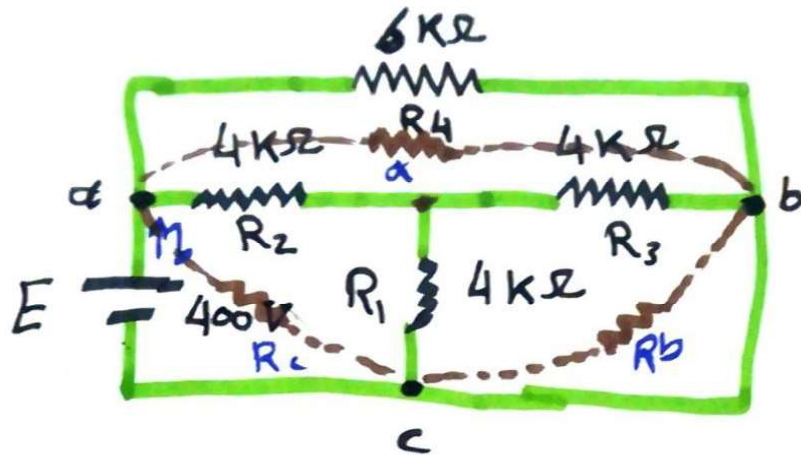Example is for the network, find the current I .



Solution:

$$V = IR_T$$

$$I = \frac{V}{R_T}$$

$$R_x = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_0 = 3 R_y$$

$$R_a = R_b = R_c = R_\Delta = 3 R_y = 3 \times 4 \times 10^3 = 12 \text{ k}\Omega$$

$$R_T = 12 \text{ k}\Omega // 12 \text{ k}\Omega // 6 \text{ k}\Omega$$




$$\frac{1}{R_T} = \frac{1}{12 \times 10^3} + \frac{1}{6 \times 10^3} + \frac{1}{12 \times 10^3}$$

$$R_T = 3 \text{ k}\Omega$$


$$I = \frac{400}{3 \times 10^3} = \frac{2}{15}$$

$$= 0.1333 \text{ A}$$


$$= 133.333 \text{ mA}$$

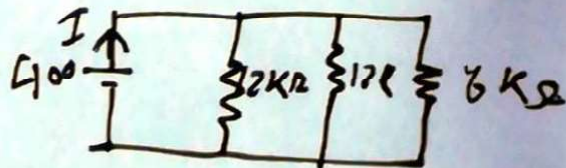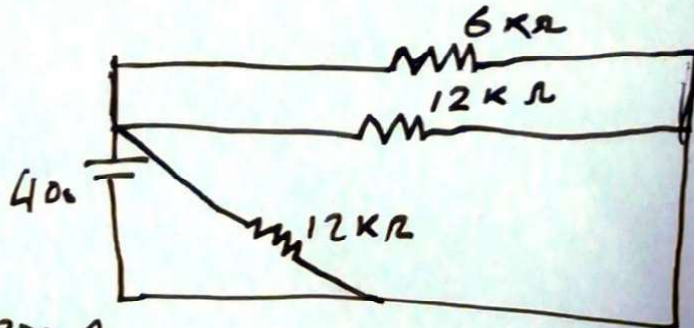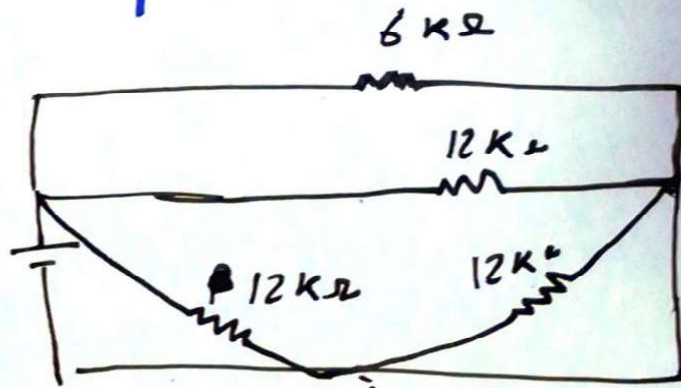

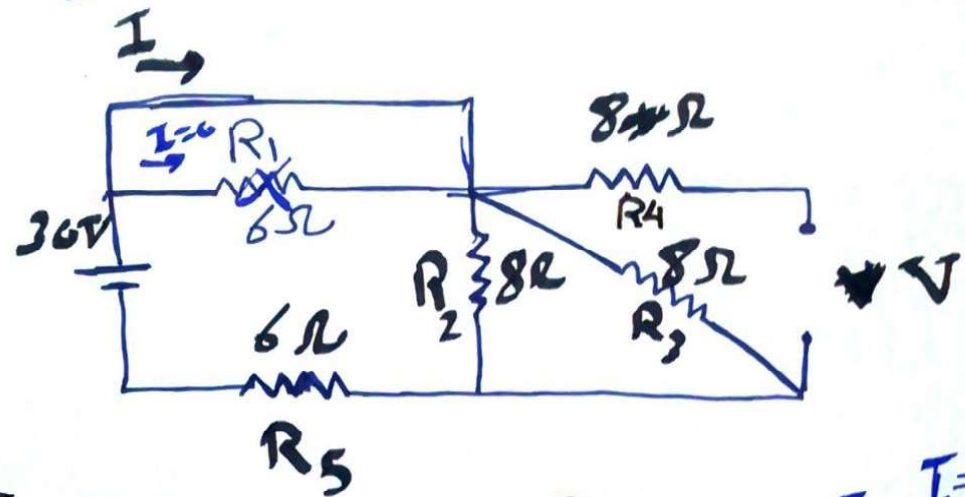Example: For the circuit shown, calculate I and V.



Solution:-


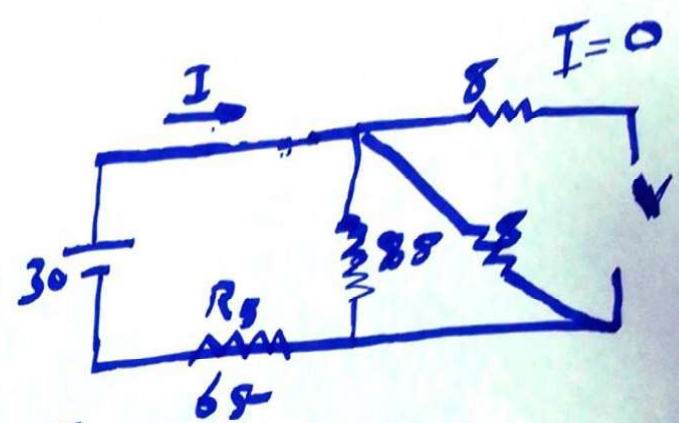


$$I = \frac{E}{R_T} =$$

$$R_T = 4 + 6 = 10 \Omega$$

$$I = \frac{30}{10} = 3 A$$
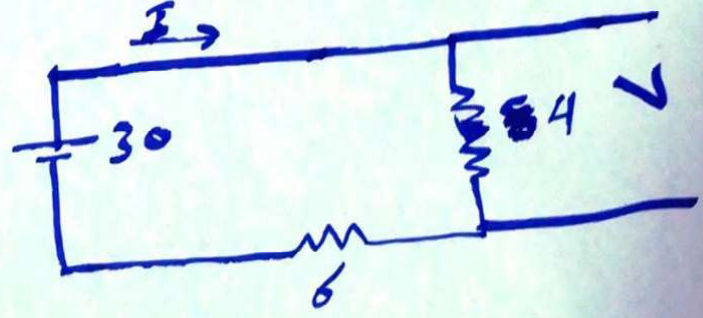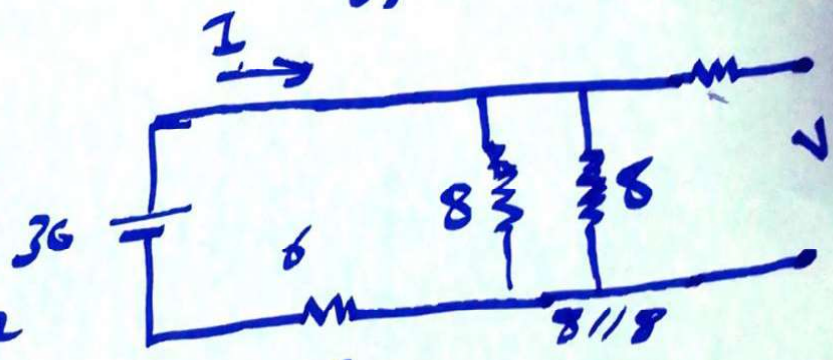
$$V = V_{4\Omega} = \frac{30 \times 4}{10} = 12 V$$



Techniques of circuit Analysis

$$a_1x + b_1y = c_1$$

$$a_1, b_1, a_2, c_1, c_2 = \text{num}$$

$$a_2x + b_2y = c_2$$

$$x = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} c_1 & b_1 \\ c_2 & b_2 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}} =$$

$$\Delta_1 = \begin{vmatrix} c_1 & b_1 \\ c_2 & b_2 \end{vmatrix} = c_1 b_2 - b_1 c_2$$

$$\Delta = \begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix} = a_1 b_2 - a_2 b_1$$

$$y = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} a_1 & c_1 \\ a_2 & c_2 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}}$$

$$\Delta_2 = \begin{vmatrix} a_1 & c_1 \\ a_2 & c_2 \end{vmatrix} = a_1 c_2 - a_2 c_1$$

$$\Delta = a_1 b_2 - a_2 b_1$$

Third order

$$a_1x + b_1y + c_1z = d_1$$

$$a_2x + b_2y + c_2z = d_2$$

$$a_3x + b_3y + c_3z = d_3$$

$$x = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} d_1 & b_1 & c_1 \\ d_2 & b_2 & c_2 \\ d_3 & b_3 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix}}$$

$$y = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} a_1 & d_1 & c_1 \\ a_2 & d_2 & c_2 \\ a_3 & d_3 & c_3 \end{vmatrix}}{\Delta}$$

$$z = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} a_1 & b_1 & d_1 \\ a_2 & b_2 & d_2 \\ a_3 & b_3 & d_3 \end{vmatrix}}{\Delta}$$

$$\Delta_1 = \begin{vmatrix} d_1 & b_1 & c_1 & d_1 & b_1 \\ d_2 & b_2 & c_2 & d_2 & b_2 \\ d_3 & b_3 & c_3 & d_3 & b_3 \end{vmatrix}$$

$$= [d_1 b_2 c_3 + b_1 c_2 d_3 + c_1 d_2 b_3] - [c_1 b_2 d_3 + d_1 c_2 b_3 + b_1 d_2 c_3]$$

$$\Delta = \begin{vmatrix} a_1 & b_1 & c_1 & a_1 & b_1 \\ a_2 & b_2 & c_2 & a_2 & b_2 \\ a_3 & b_3 & c_3 & a_3 & b_3 \end{vmatrix}$$

$$= [a_1 b_2 c_3 + b_1 c_2 a_3 + c_1 a_2 b_3] - [c_1 b_2 a_3 + a_1 c_2 b_3 + b_1 a_2 c_3]$$

Example 18 Find x & y .

$$-x + 2y = 3$$

$$3x - 2y = -2$$

$$x = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 3 & 2 \\ -2 & -2 \end{vmatrix}}{\begin{vmatrix} -1 & 2 \\ 3 & -2 \end{vmatrix}} = \frac{3 \times (-2) - 2 \times (-2)}{(-1) \times (-2) - 2 \times 3}$$
$$= \frac{-2}{-4} = \boxed{\frac{1}{2}}$$

$$y = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} -1 & 3 \\ 3 & -2 \end{vmatrix}}{\begin{vmatrix} -1 & -2 \\ 3 & -2 \end{vmatrix}} = \frac{(-1) \times (-2) - 3 \times 3}{-4}$$
$$= \frac{-7}{-4} = \boxed{\frac{7}{4}}$$

$$-x + 2y = 3$$

$$-\frac{1}{2} + 2 \times \frac{7}{4} = -\frac{1}{2} + \frac{7}{2} = \frac{-1+7}{2} = \frac{6}{2} = 3$$

Example: Find x, y and z

$$x - 2z = -1$$

$$3y + z = 2$$

$$x + 2y + 3z = 0$$

$$x + 0y - 2z = -1$$

$$\Rightarrow 0x + 3y + z = 2$$

$$x + 2y + 3z = 0$$


$$x = \frac{\Delta_1}{\Delta}$$

$$x = \frac{\begin{vmatrix} -1 & 0 & -2 & -1 & 0 \\ 2 & 3 & 1 & 2 & 3 \\ 0 & 2 & 3 & 0 & 2 \\ 1 & 0 & -2 & 1 & 0 \\ 0 & 3 & 1 & 0 & 3 \\ 1 & 2 & 3 & 1 & 2 \end{vmatrix}}{\begin{vmatrix} 1 & 0 & -2 & 1 & 0 \\ 0 & 3 & 1 & 0 & 3 \\ 1 & 2 & 3 & 1 & 2 \end{vmatrix}}$$

$$= \frac{(-1 \times 3 \times 3) + (0 \times 1 \times 0) + (-2 \times 2 \times 2) - (-2 \times 3 \times 0) - (-1 \times 1 \times 2) - (0 \times 2 \times 3)}{(1 \times 3 \times 3) + (0 \times 1 \times 1) + (-2 \times 0 \times 2) - (-2 \times 3 \times 1) - (1 \times 1 \times 2) - (0 \times 0 \times 3)}$$

$$x = \frac{-9 + (-8) - (-2)}{(9) - (-6) - (2)} = \frac{-15}{13} =$$


$$y = \frac{\Delta_2}{\Delta}$$

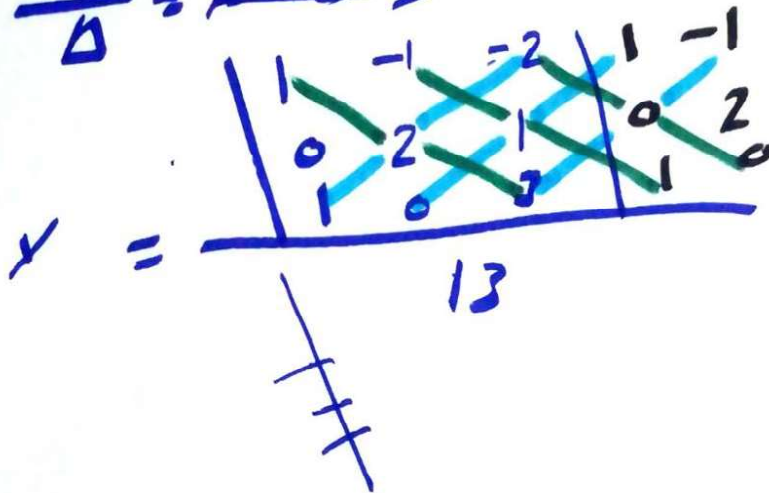

$$\Delta = 13$$

$$= \frac{(1 \times 2 \times 3) + (-1 \times 1 \times 1) + (-2 \times 0 \times 0) - (-2 \times 2 \times 1) - (1 \times 1 \times 0) - (-1 \times 0 \times 0)}{13}$$
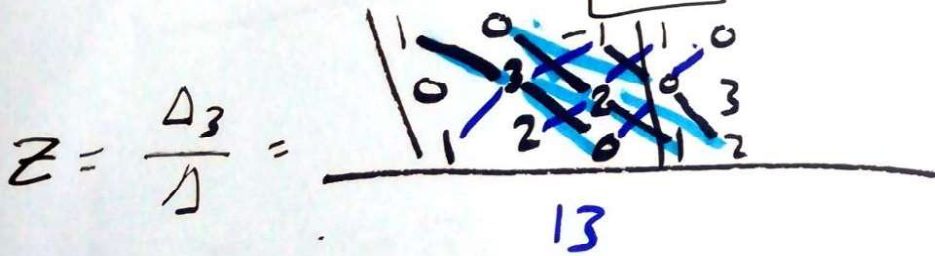
$$y = \frac{6 - 1 + 4}{13} = \frac{9}{13}$$



$$z = \frac{(1 \times 3 \times 0) + (0 \times 2 \times 1) + (-1 \times 0 \times 2) - (-1 \times 3 \times 1) - (1 \times 2 \times 2) - (0 \times 0 \times 0)}{13}$$


$$\frac{+3 - 4}{13} = \frac{-1}{13}$$

$$x = -\frac{15}{13} \quad y = \frac{9}{13} \quad z = \frac{-1}{13}$$

Source Transformation


$$V \rightarrow I$$

$$I = \frac{E}{R_s}$$

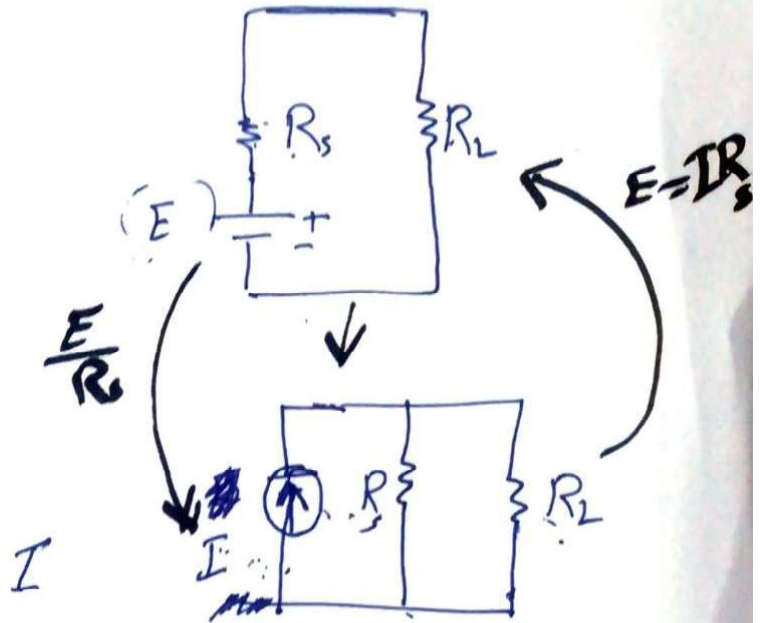


$$\underline{I \rightarrow V}$$

$$E = I R_s$$

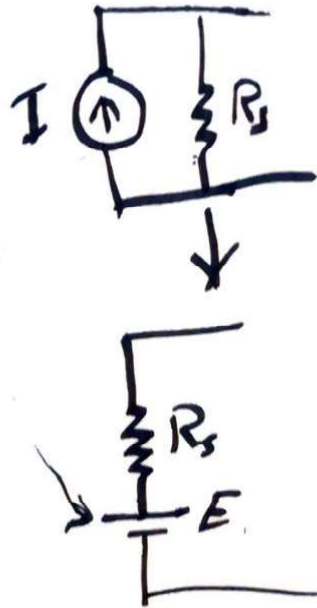


Example: Calculate the current through the load for each switch source.

$$I = \frac{E}{R_T} = \frac{6}{6} = 1A$$

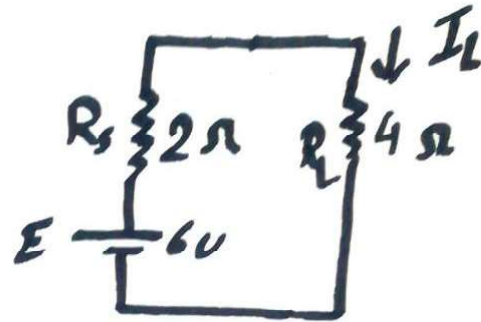


$$I_L = \frac{I \times R_1}{R_1 + R_2} = \frac{3 \times 2}{6} = \frac{6}{6} = 1A$$

$$I = \frac{E}{R_1} = \frac{6}{2} = 3$$

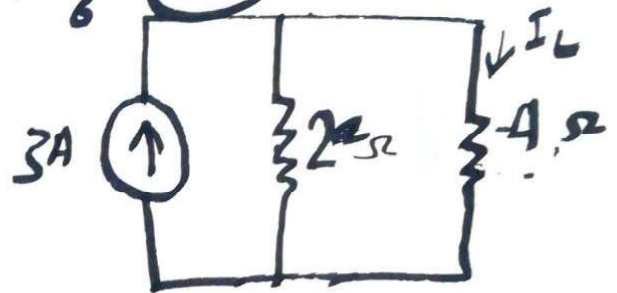


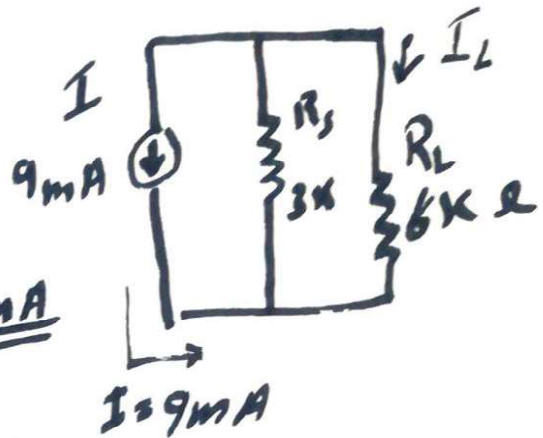Example: determine I_L for the circuit.

$$I_L = \frac{I \times R_s}{R_s + R_L}$$
$$I = \frac{9 \times 10^{-3} \times 3 \times 10^3}{3 \times 10^3 + 6 \times 10^3} = \frac{27}{9 \times 10^3} = \underline{\underline{3 \text{ mA}}}$$



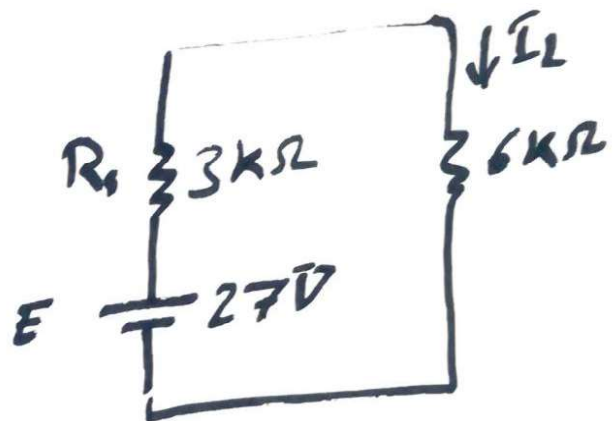
$$* I_L = \frac{27}{9 \text{ k}\Omega} = \underline{\underline{3 \text{ mA}}}$$




$$E = I \times R_s =$$
$$9 \times 10^{-3} \times 3 \times 10^3 =$$
$$E = 27 \text{ V}$$


Loop (Mesh) Current Method

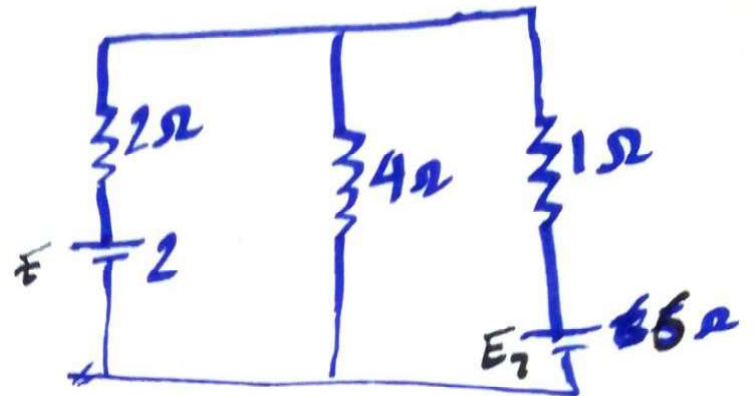

Step 1:

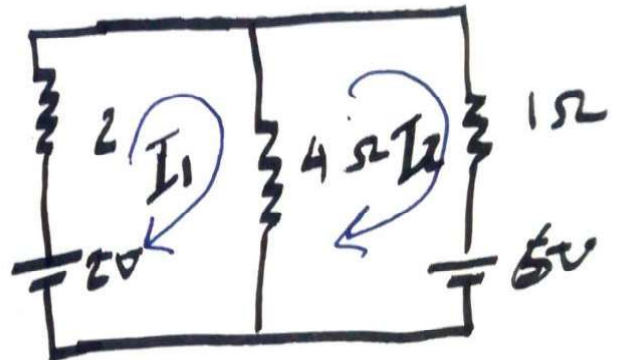

Step 2:

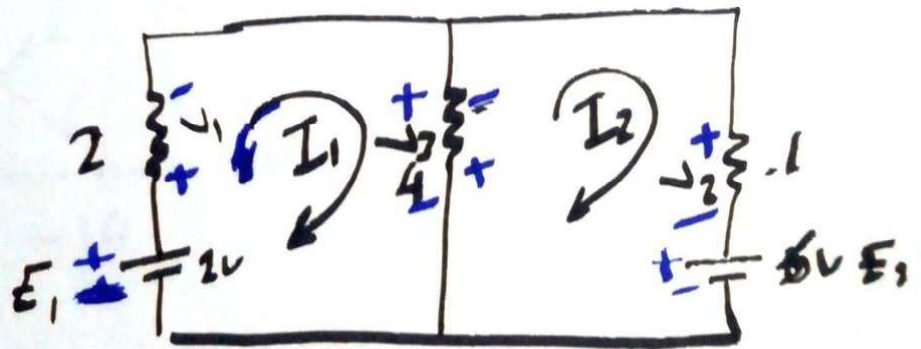

Step 3: KVL

Loop 1

$$V = IR$$

$$E_1 - V_1 - V_3 = 0 \Rightarrow 2 - 2I_1 - 4(I_1 - I_2) = 0$$

$$2 - 2I_1 - 4I_1 + 4I_2 = 0 \Rightarrow (-6I_1 + 4I_2 = -2) \times (-1)$$

$$6I_1 - 4I_2 = 2 \quad \text{--- (1)}$$

Loop (2)

$$-E_2 - V_2 - V_3 = 0$$

$$-5 - I_2 - 4(I_2 - I_1) = 0$$

$$-5 - \underline{I_2} - \underline{4I_2} + 4I_1 = 0$$

$$4I_1 - 5I_2 = 5 \quad \text{--- (1)}$$

$$6I_1 - 4I_2 = 2$$

$$4I_1 - 5I_2 = 6$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 2 & -4 \\ 6 & -5 \end{vmatrix}}{\begin{vmatrix} 6 & -4 \\ 4 & -5 \end{vmatrix}} = \frac{(2 \times -5) - (-4 \times 6)}{(6 \times -5) - (-4 \times 4)}$$

$$= \frac{-10 + 24}{-30 + 16} = \frac{14}{-14} = -1$$



$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 6 & 2 \\ 4 & 6 \end{vmatrix}}{\begin{vmatrix} 6 & -4 \\ 4 & -5 \end{vmatrix}} = \frac{6 \times 6 - 4 \times 2}{-14} = \frac{36 - 8}{-14} = \frac{28}{-14} = -2$$

$$I_1 = -1$$

$$I_2 = -2$$

$$I_3 = I_1 - I_2 = -1 - (-2) = 1 \text{ A}$$

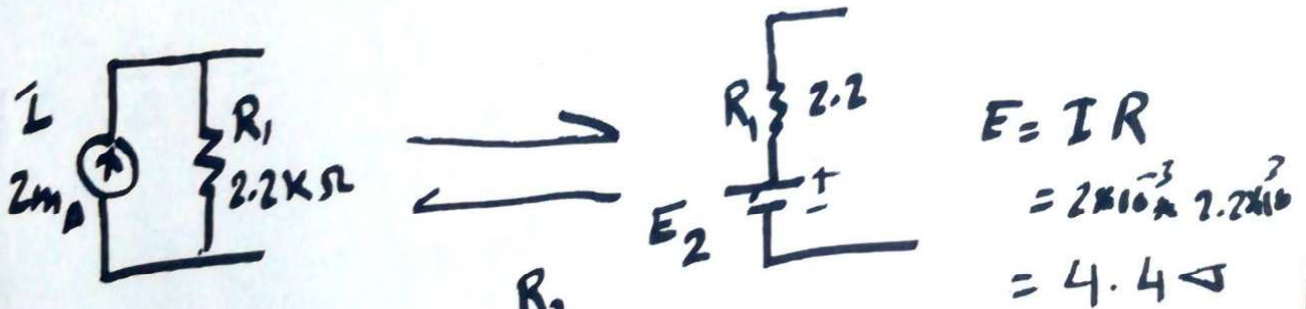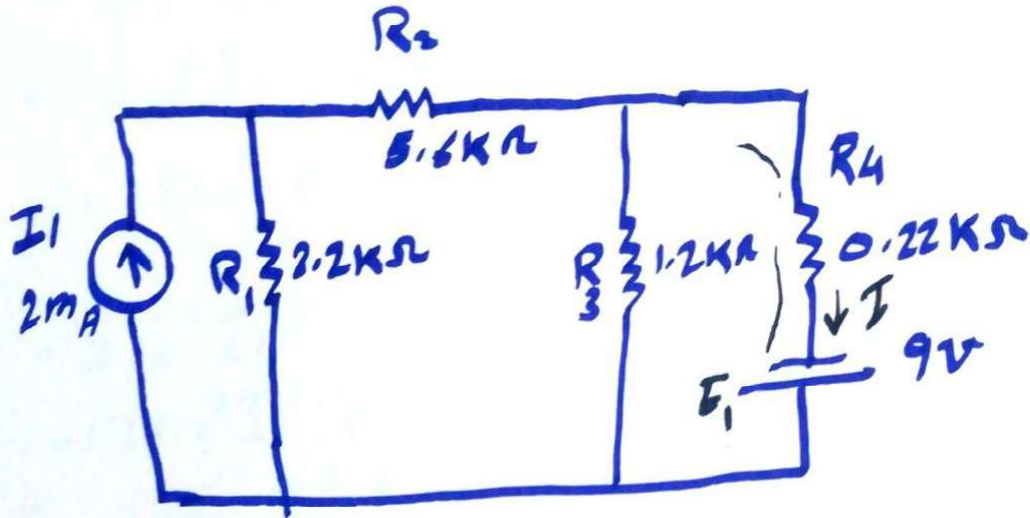Example: Using the mesh analysis, determine the current through 9V for the network.



Loop ①: KVL

$$+E_2 - V_1 - V_2 - V_3 = 0$$

$$4.4 - 2.2 \times 10^3 I_1 - 5.6 \times 10^3 I_2 - 1.2 \times 10^3 (I_1 - I_2) = 0$$

$$(-9 \times 10^3 I_1 + 1.2 \times 10^3 I_2 = -4.4) \quad \text{--- } 1$$

$$9 \times 10^3 I_1 - 1.2 \times 10^3 I_2 = 4.4 \quad \text{--- } \textcircled{1}$$

Loop ②:

$$+E_1 - V_3 - V_4 = 0$$

$$9 - 1.2 \times 10^3 (\bar{I}_2 - \bar{I}_1) - 0.72 \times 10^3 I_2 = 0$$

$$(+ 1.2 \times 10^3 \bar{I}_1 - 1.42 \times 10^3 I_2 = -9) \times -1$$

$$-1.2 \times 10^3 \bar{I}_1 + 1.42 \times 10^3 I_2 = 9 \quad \text{--- ②}$$

$$9 \times 10^3 \bar{I}_1 - 1.2 \times 10^3 I_2 = 4.4$$


$$-1.2 \times 10^3 \bar{I}_1 + 1.42 \times 10^3 I_2 = 9$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 4.4 & -1.2 \times 10^3 \\ 9 & 1.42 \times 10^3 \end{vmatrix}}{\begin{vmatrix} 9 \times 10^3 & -1.2 \times 10^3 \\ -1.2 \times 10^3 & 1.42 \times 10^3 \end{vmatrix}}$$

$$I_1 = \frac{4.4 \times 1.42 \times 10^3 + 1.2 \times 10^3 \times 9}{9 \times 10^3 \times 1.42 \times 10^3 - 1.2 \times 10^3 \times 1.2 \times 10^3} = \frac{17048}{11340000}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 9 \times 10^3 & 4.4 \\ -1.2 \times 10^3 & -9 \end{vmatrix}}{11340000} = \frac{86280}{11340000} = 7.608 \text{ mA}$$

Example

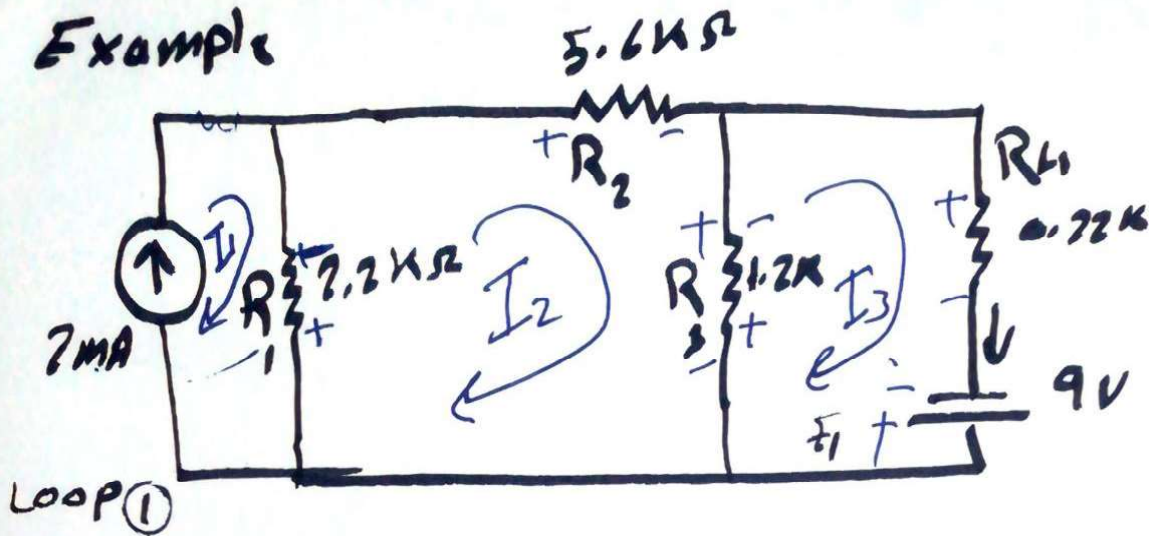

Loop 1
 $I_1 = 2 \text{ mA}$

Loop 2

$$-V_1 - V_2 - V_3 = 0$$

$$-2.2 \times 10^3 (I_2 - I_1) - 5.6 \times 10^3 I_2 - 1.2 \times 10^3 (I_2 - I_3) = 0$$

$$-2.2 \times 10^3 I_2 + 2.2 \times 10^3 I_1 - 5.6 \times 10^3 I_2 - 1.2 \times 10^3 I_2 + 1.2 \times 10^3 I_3 = 0$$

$$4.4 - 9 \times 10^3 I_2 + 1.2 I_3 = 0$$

$$\left(\begin{array}{l} -9 \times 10^3 I_2 + 1.2 I_3 = -4.4 \\ 9 \times 10^3 I_2 - 1.2 I_3 = 4.4 \end{array} \right) \times -1$$

Loop 3

$$+E_4 - V_3 - V_4 = 0$$

$$9 - 1.2 \times 10^3 (I_3 - I_2) - 0.22 \times 10^3 I_3 = 0$$

$$+1.2 \times 10^3 I_2 - 1.42 \times 10^3 I_3 = -9$$

$$-1.2 \times 10^3 I_2 + 1.42 \times 10^3 I_3 = 9$$


$$-1.2 \times 10^3 I_2 + 1.42 \times 10^3 I_3 = 9 \quad \text{--- (2)}$$

$$9 \times 10^3 I_2 - 1.2 I_3 = 4.4$$

$$-1.2 \times 10^3 I_2 + 1.42 \times 10^7 = 9$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 9 \times 10^3 & 4.4 \\ -1.2 \times 10^3 & 9 \end{vmatrix}}{\begin{vmatrix} 9 \times 10^3 & -1.2 \times 10^3 \\ -1.2 \times 10^3 & 1.42 \times 10^7 \end{vmatrix}} = \frac{86280}{11340000}$$

Example: Find the current through the 10Ω resistor of the network shown.

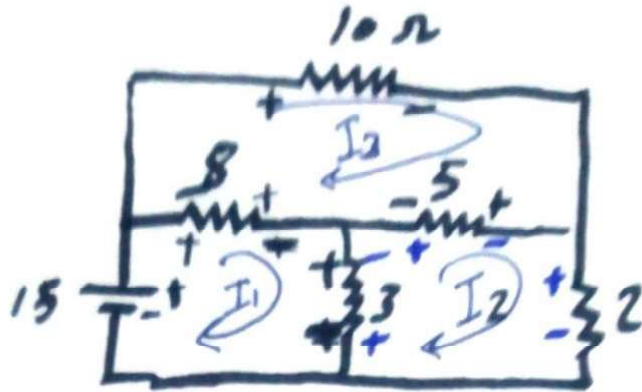

Loop 1:

~~$R=V$~~

$$15 - 8(I_1 - I_3) - 3(I_1 - I_2) = 0$$

$$(-11I_1 + 3I_2 + 8I_3 = -15) \times -1$$

$$11I_1 - 3I_2 - 8I_3 = 15 \quad \text{--- (1)}$$

Loop 2:

$$-3(I_2 - I_1) - 5(I_2 - I_3) - 2I_2 = 0$$

$$(3I_1 - 10I_2 + 5I_3 = 0) \times -1$$

$$-3I_1 + 10I_2 - 5I_3 = 0 \quad \text{--- (2)}$$

Loop 3:

$$-8(I_3 - I_1) - 10I_3 - 5(I_3 - I_2) = 0$$

$$(8I_1 + 5I_2 - 23I_3 = 0) \times -1$$

$$-8I_1 - 5I_2 + 23I_3 = 0 \quad \text{--- (3)}$$

$$11I_1 - 3I_2 - 8I_3 = 15$$

$$-3I_1 + 10I_2 - 5I_3 = 0$$

$$-8I_1 - 5I_2 + 23I_3 = 0$$

$I_3 =$


$$\begin{array}{ccc|ccc} 11 & -3 & 15 & 11 & -3 & \\ -3 & 10 & 0 & -3 & 10 & \\ -8 & -5 & 0 & -8 & -5 & \end{array}$$

$$= 1.22 \text{ A}$$

$$\begin{array}{ccc|ccc} 11 & -3 & -8 & 11 & -3 & \\ -3 & 10 & -5 & -3 & 10 & \\ -8 & -5 & 23 & -8 & -5 & \end{array}$$

$$= \frac{[(11 \times 10 \times 0) + (-3 \times 0 \times -8) + (15 \times -3 \times -5)] - [(15 \times 10 \times -8) + (11 \times 0 \times -5) + (-3 \times -8 \times 0)]}{\dots}$$

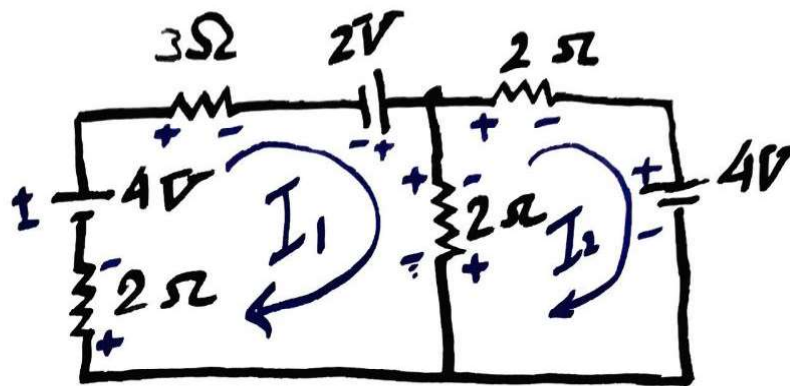Example: For the circuit shown, find the current in the $3\ \Omega$ resistor using (a) Loop method (b) nodal method



Solution:

(a) Loop current method $V = IR$

Loop 1:

$$4 - I_1 \cdot 3 + 2 - 2(I_1 - I_2) - 2I_1 = 0$$

$$(-I_1(3+2+2) + 2I_2 = -6) \quad * -1$$

$$7I_1 - 2I_2 = 6 \quad \text{--- (1)}$$

Loop 2:

$$-4 - 2(I_2 - I_1) - 2I_2 = 0$$

$$(2I_1 - 4I_2 = 4) \quad * -1$$


$$-2I_1 + 4I_2 = -4 \quad \text{--- (2)}$$

$$I_1 = \frac{\begin{vmatrix} 6 & -2 \\ -4 & 4 \end{vmatrix}}{\begin{vmatrix} 7 & -2 \\ -2 & 4 \end{vmatrix}} = \frac{2}{3} \text{ A}$$

$$I_1 = \frac{3}{2} \text{ A}$$


② Nodal voltage method

$I_{3\Omega} = ?$

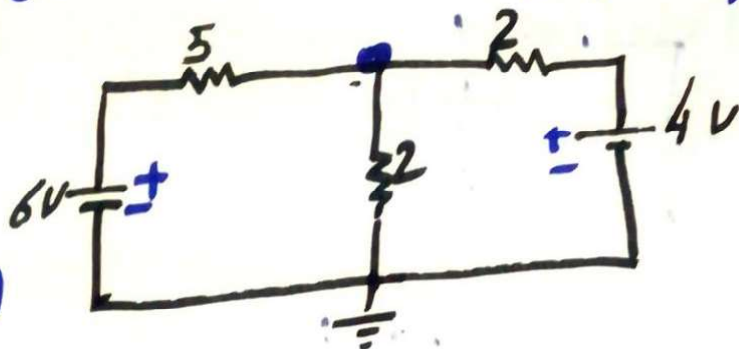

$$I_1 = \frac{V}{R} = \frac{6}{5} A$$


$$I_2 = \frac{V}{R} = \frac{4}{2} = 2A$$

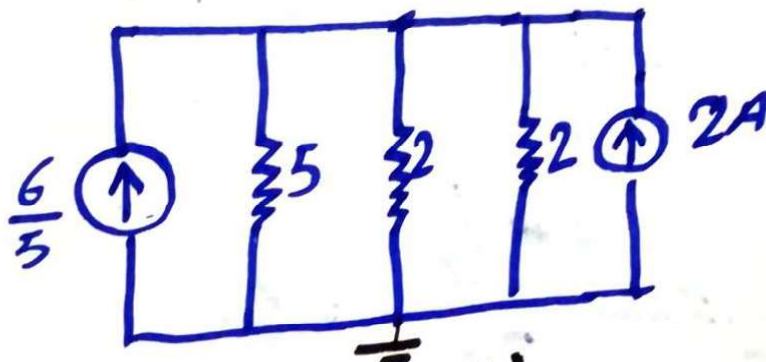

$$I_T + \frac{6}{5} + 2 = +\frac{16}{5}$$

$$I = \frac{V}{R}$$
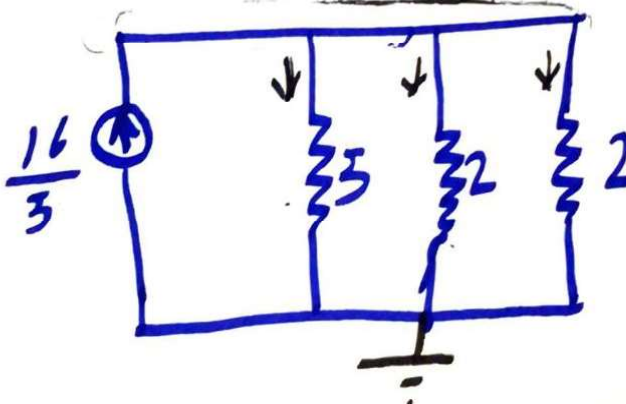
$$\frac{16}{5} = \frac{V_1}{5} + \frac{V_1}{2} + \frac{V_1}{2}$$





$$\frac{16}{5} = V_1 \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2} \right)$$



$$V_1 = \frac{8}{3}$$

$$V_3 = \frac{10}{3}$$

2+3

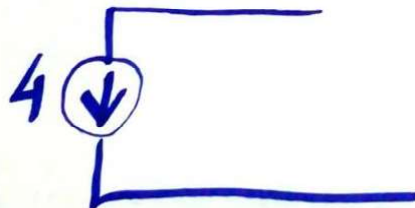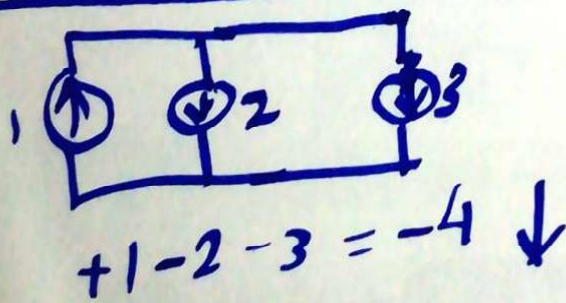
$$I = \frac{V_3}{5\Omega} = \frac{\frac{10}{3}}{5} = \frac{2}{3}$$



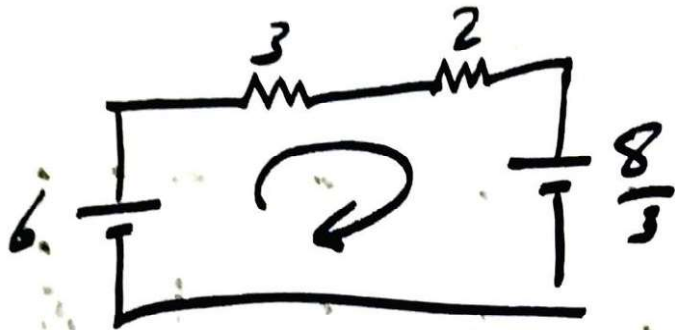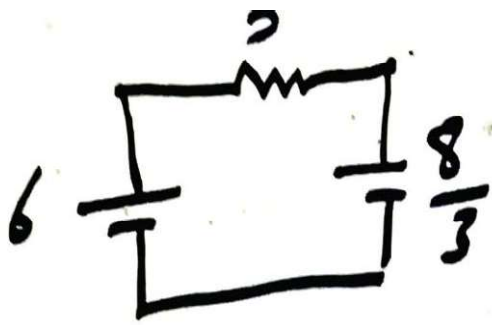

$$I_{3\Omega} = \frac{6 - \frac{8}{3}}{2+3} = \frac{2}{3}$$

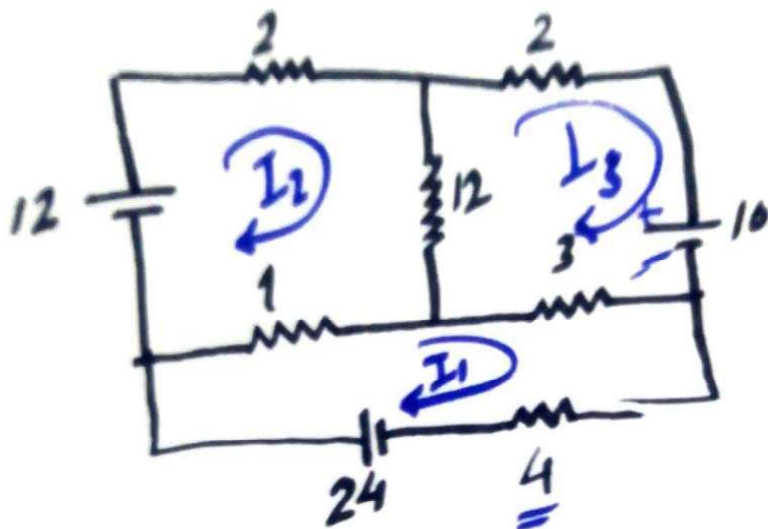Example: Determine the current in the 4 Ω resistor for the circuit shown, using loop current method. All resistor value in ohms.



Solution:

Loop 1:

$$24 - 4I_1 - (I_1 - I_2) - 3(I_1 - I_3) = 0$$

$$(-8I_1 + I_2 + 3I_3 = -24) \times -1$$

$$8I_1 - I_2 - 3I_3 = 24 \quad \text{--- (1)}$$

Loop 2:

$$12 - 2I_2 - (I_2 - I_1) - 12(I_2 - I_3) = 0$$

$$(I_1 - 15I_2 + 12I_3 = 12) \times -1$$

$$-I_1 + 15I_2 - 12I_3 = 12 \quad \text{--- (2)}$$

Loop 3:

$$-10 - 12(I_3 - I_2) - 3(I_3 - I_1) - 2I_3 = 0$$

$$(+3I_1 + 12I_2 - 17I_3 = 10) \times -1$$

$$-3I_1 - 12I_2 + 17I_3 = -10 \quad \text{--- (3)}$$

$$8I_1 - I_2 - 3I_3 = 24$$

$$-I_1 + 15I_2 - 12I_3 = 12$$

$$-3I_1 - 12I_2 + 15I_3 = -10$$

$$I = \left(\begin{array}{ccc|c} 24 & -1 & -3 & \\ 12 & 15 & -12 & \\ -10 & -12 & 15 & \end{array} \right) = 4.111 \text{ A}$$


$$\left(\begin{array}{ccc|c} 8 & -1 & -3 & \\ -1 & 15 & -12 & \\ -3 & -12 & 15 & \end{array} \right)$$

$$I_2 = 2.7 \text{ A}$$

$$I_3 = 2.05 \text{ A}$$

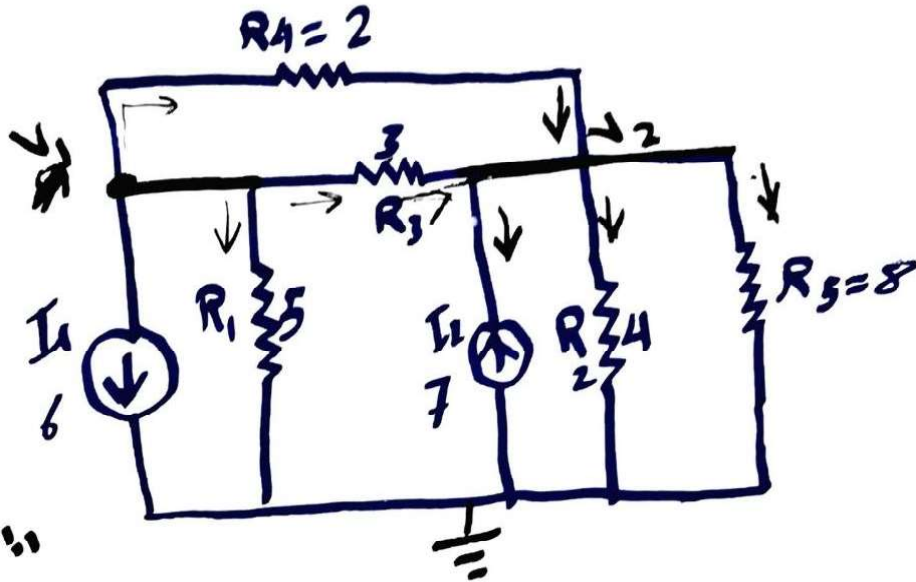xii. Write the nodal equation for the circuit shown and solve for the nodal voltage.

① Determine the magnitude and polarity of the voltage across each resistor.



Solution:

①

$$-6 = \frac{V_1}{5} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3}$$

$$-6 = V_1 \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{3} \right) - V_2 \left(\frac{1}{2} + \frac{1}{3} \right)$$

$$-6 = V_1 \frac{31}{30} - V_2 \frac{5}{6} \quad \text{--- ①}$$

②

$$\frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3} = -7 + \frac{V_2}{4} + \frac{V_2}{8}$$

$$V_1 \left(\frac{1}{2} + \frac{1}{3} \right) - V_2 \left(\frac{1}{2} + \frac{1}{3} + \frac{1}{4} + \frac{1}{8} \right) = -7$$

$$V_1 \frac{5}{6} - V_2 \frac{29}{24} = -7 \quad \text{--- ②}$$

$$V_1 \frac{31}{30} - V_2 \frac{5}{6} = -6$$

$$V_1 \frac{5}{6} - V_2 \frac{29}{24} = -7$$

$$V_1 = \frac{\begin{vmatrix} -6 & -\frac{5}{6} \\ -7 & -\frac{29}{24} \end{vmatrix}}{\begin{vmatrix} \frac{31}{30} & -\frac{5}{6} \\ \frac{5}{6} & -\frac{29}{24} \end{vmatrix}} = -2.556 \text{ V}$$


$$V_2 = \frac{\begin{vmatrix} \frac{31}{30} & -6 \\ \frac{5}{6} & -7 \end{vmatrix}}{\begin{vmatrix} \frac{31}{30} & -\frac{5}{6} \\ \frac{5}{6} & -\frac{29}{24} \end{vmatrix}} = \underline{\underline{4.03 \text{ V}}}$$

$$V_{R_1} = V_1 = -2.556 \text{ V}$$

$$V_{R_2} = V_{R_5} = 4.03 \text{ V}$$

$$V_{R_3} = V_{R_4} = V_1 - V_2 = (-2.556 - 4.03) \\ = +6.586 \text{ V}$$

another
Solution

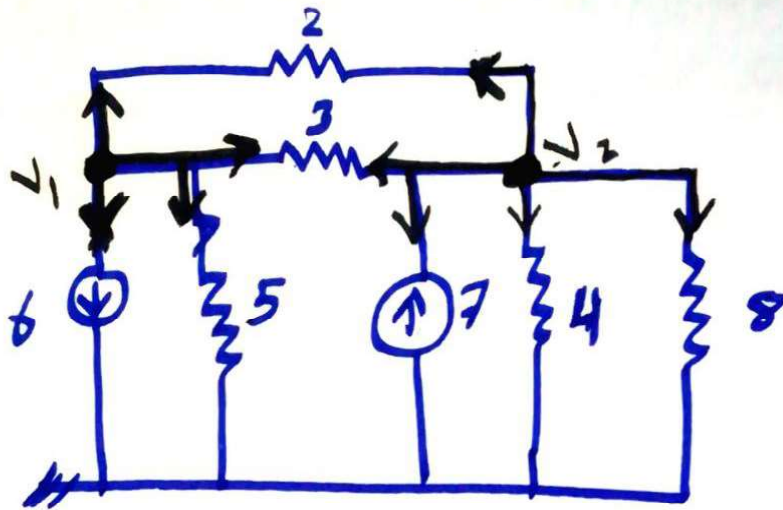

$$V_1$$

$$6 + \frac{V_1}{5} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3} = 0$$

$$V_1 \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{3} \right) - V_2 \left(\frac{1}{2} + \frac{1}{3} \right) = -6$$

$$\frac{31}{30} V_1 - \frac{5}{6} V_2 = -6 \quad \text{--- (1)}$$

$$V_2$$


$$-7 + \frac{V_2}{4} + \frac{V_2}{8} + \frac{V_2 - V_1}{2} + \frac{V_2 - V_1}{3} = 0$$

$$-V_1 \left(\frac{1}{2} + \frac{1}{3} \right) + V_2 \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{2} + \frac{1}{3} \right) = 7$$


$$\left(-\frac{5}{6} V_1 + \frac{29}{24} V_2 = 7 \right) * -1$$

$$\frac{5}{6} V_1 - \frac{29}{24} V_2 = -7 \quad \text{--- (2)}$$

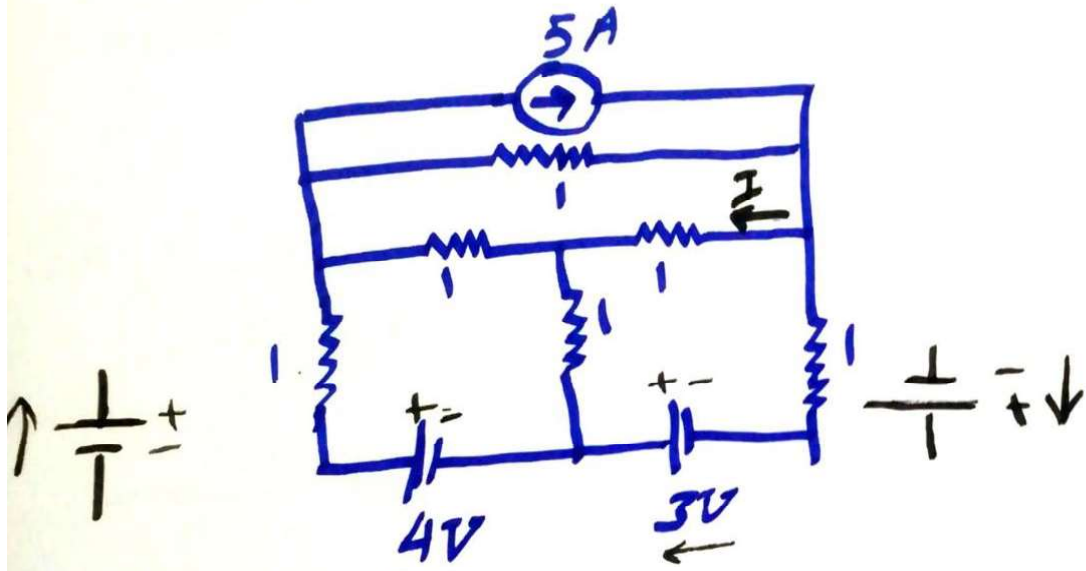Example: Using the nodal voltage method, find the current I in the circuit shown. All resistors are in ohms.


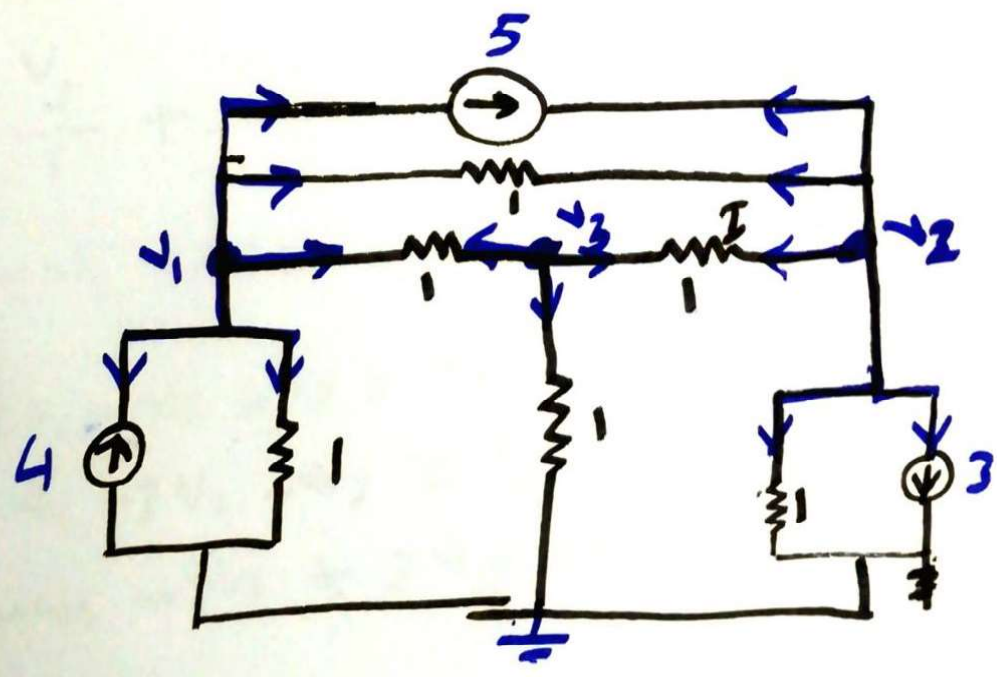
$$I_1 = \frac{V}{R} = \frac{4}{1} = 4A \quad I_2 = \frac{V}{R} = \frac{3}{1} = 3A$$



$$\frac{V_2 - V_3}{R} =$$

$$\frac{v_1}{1} - 4 + \frac{v_1 - v_2}{1} + \frac{4 - v_3}{1} + 5 = 0$$

$$v_1(1 + 1 + 1) - v_2 - v_3 = -1$$

$$3v_1 - v_2 - v_3 = -1 \quad \text{--- (1)}$$

$$\textcircled{2} \quad \frac{v_2 - v_3}{1} + \frac{v_2 - v_1}{1} - 5 + \frac{v_2}{1} + 3 = 0$$

$$-v_1 + v_2(1 + 1 + 1) - v_3 = 2$$

$$-v_1 + 3v_2 - v_3 = 2 \quad \text{--- (2)}$$

$$\textcircled{3} \quad \frac{v_3}{1} + \frac{v_3 - v_1}{1} + \frac{v_3 - v_2}{1} = 0$$

$$-v_1 - v_2 + 3v_3 = 0 \quad \text{--- (3)}$$

$$3v_1 - v_2 - v_3 = -1$$

$$-v_1 + 3v_2 - v_3 = 2$$

$$-v_1 - v_2 + 3v_3 = 0$$

$$V_1 = 0$$


$$V_2 = \frac{\begin{vmatrix} 3 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & 0 & 3 \end{vmatrix}}{\begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix}} = \frac{3}{4} \text{ V}$$

$$V_3 = \frac{1}{4} \text{ V}$$

$$V_{1\Omega} = V_2 - V_3 = \frac{3}{4} - \frac{1}{4} = \frac{2}{4} = \frac{1}{2} \text{ V}$$


$$I = \frac{V_{1\Omega}}{R} = \frac{\frac{1}{2}}{1} = \frac{1}{2} \text{ A} = 0.5 \text{ A}$$

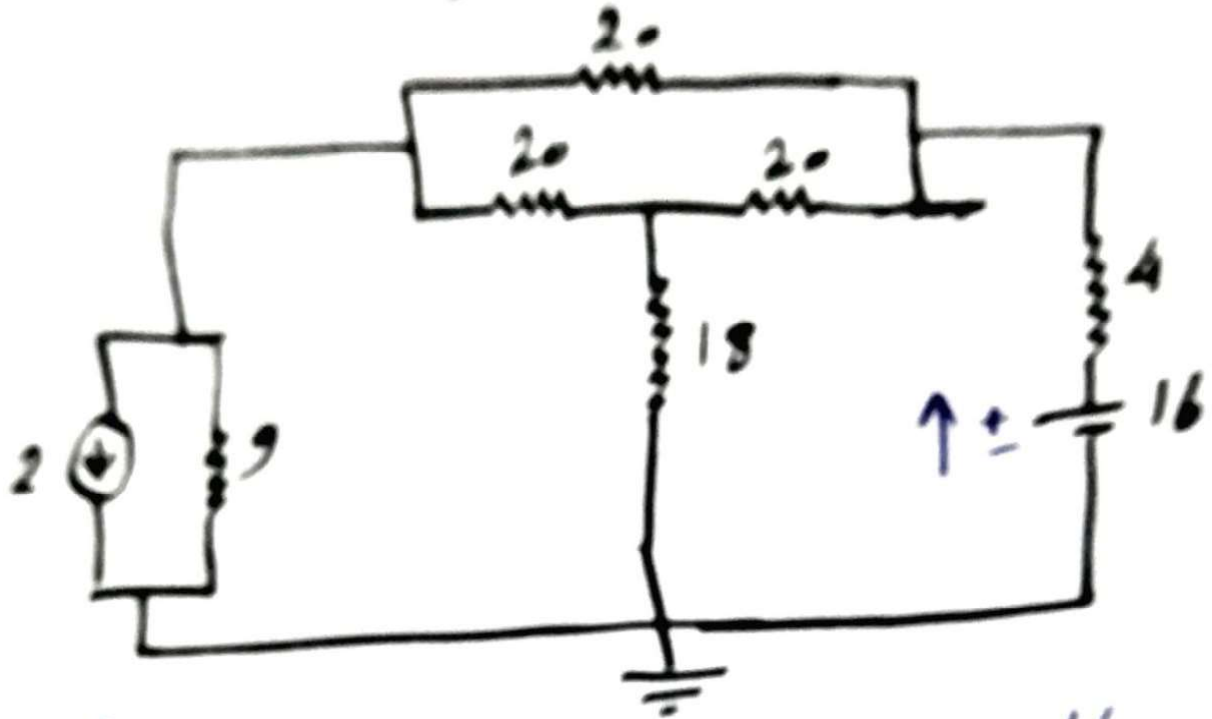Example For the network shown in Fig below
 Write the equations and Solve for the
 Node voltage.



$V \rightarrow I$ R series -
 $I \rightarrow V$ R parallel

$$I = \frac{V}{R} = \frac{16}{4} = 4A$$

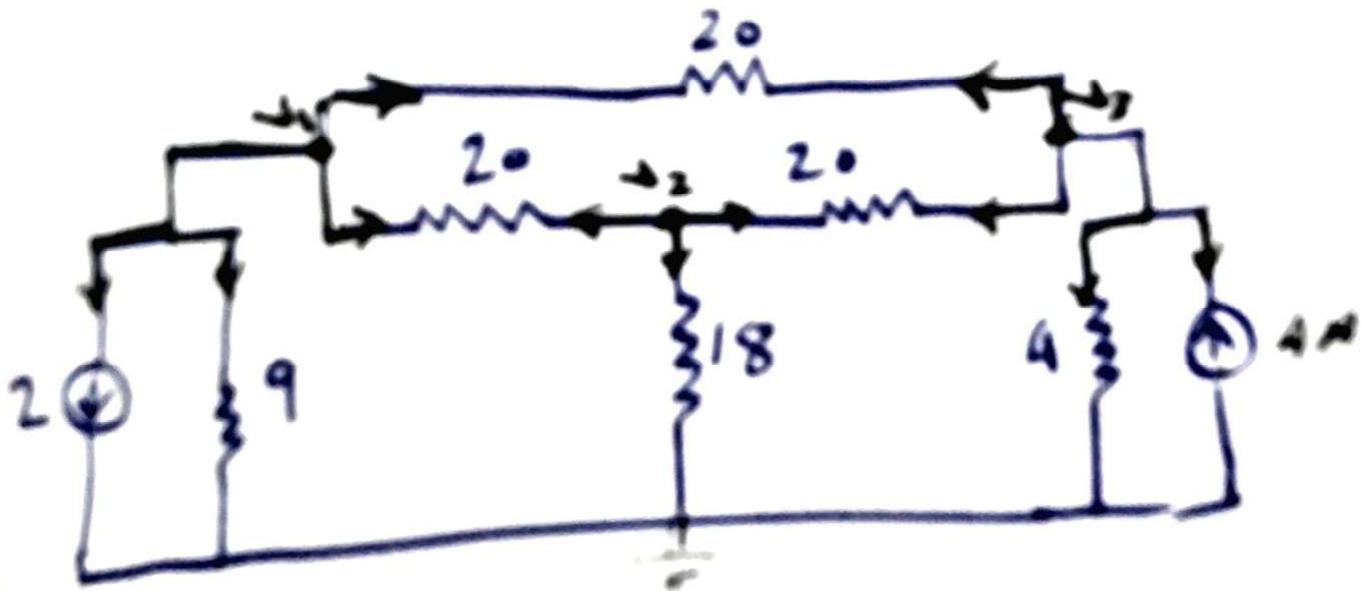

$$\textcircled{1} \quad 2 + \frac{v_1}{9} + \frac{v_1 - v_3}{20} + \frac{v_1 - v_2}{20} = 0$$

$$v_1 \left(\frac{1}{9} + \frac{1}{20} + \frac{1}{20} \right) - \frac{1}{20} v_2 - \frac{1}{20} v_3 = 0 - 2$$

$$\frac{19}{90} v_1 - \frac{1}{20} v_2 - \frac{1}{20} v_3 = -2 \quad \textcircled{1}$$

$\textcircled{2}$

$$\frac{v_2 - v_1}{20} + \frac{v_2}{18} + \frac{v_2 - v_3}{20} = 0$$

$$-\frac{v_1}{20} + v_2 \left(\frac{1}{20} + \frac{1}{18} + \frac{1}{20} \right) - \frac{v_3}{20} = 0$$

$$-\frac{v_1}{20} + \frac{7}{45} v_2 - \frac{v_3}{20} = 0 \quad \textcircled{2}$$

$\textcircled{3}$

$$\frac{v_3 - v_1}{20} + \frac{v_3 - v_2}{20} + \frac{v_3}{4} = 4 = 0$$

$$-\frac{v_1}{20} - \frac{v_2}{20} + v_3 \left(\frac{1}{20} + \frac{1}{20} + \frac{1}{4} \right) = 0 - 4$$

$$-\frac{v_1}{20} - \frac{v_2}{20} + \frac{7}{20} v_3 = 4 \quad \textcircled{3}$$

$$\frac{19}{20} v_1 - \frac{1}{20} v_2 - \frac{1}{20} v_3 = -2$$

$$-\frac{v_1}{20} + \frac{7}{45} v_2 - \frac{v_3}{20} = 0$$


$$-\frac{v_1}{20} - \frac{v_2}{20} + \frac{7v_3}{20} = 4$$

$$v_1 = -6.64 \text{ V}$$

$$v_2 = 1.29 \text{ V}$$

$$v_3 = 10.66 \text{ V}$$

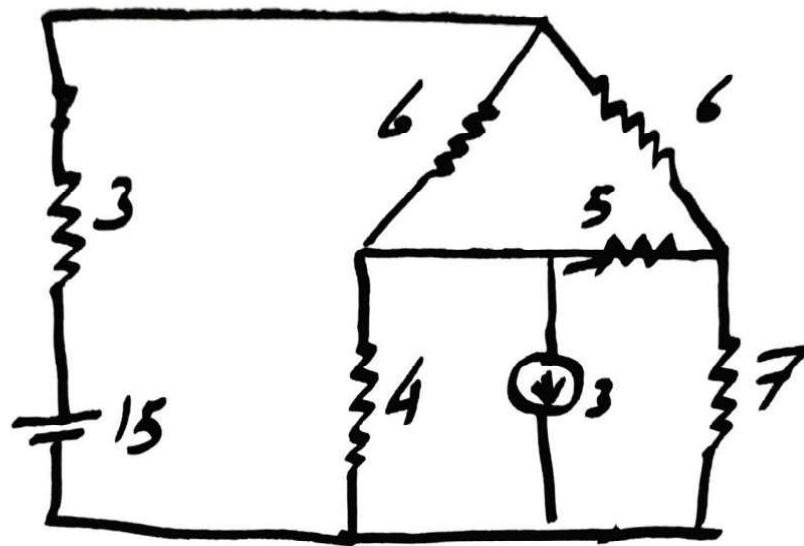
Example 1: For the circuit shown, write the nodal equation and solve for the nodal voltage




+1

1
2
3
4
5

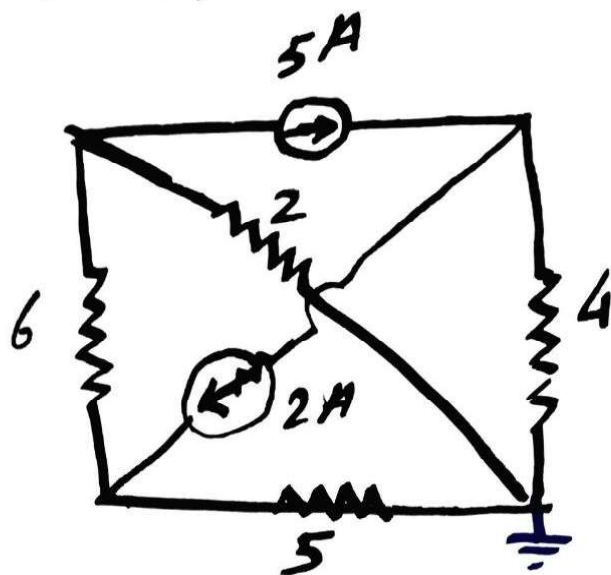Example: For the network write the nodal equation and solve for the nodal voltage.



Solution:

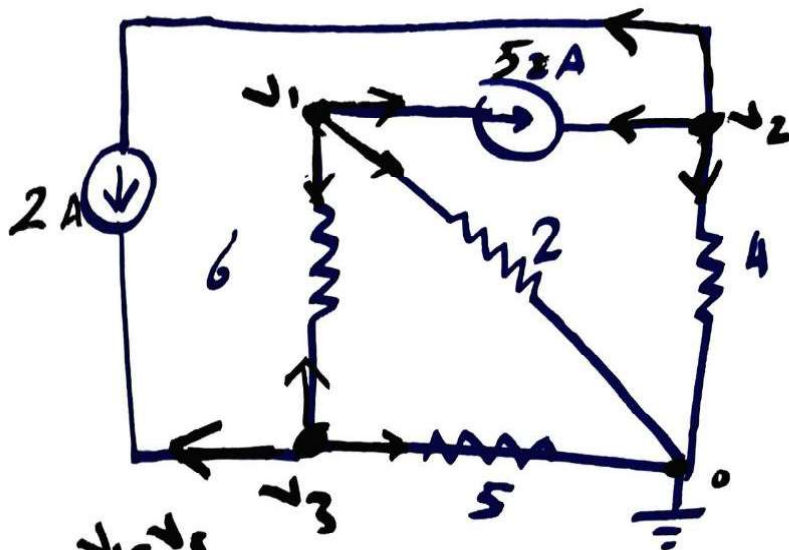

①

$$5 + \frac{v_1}{2} + \frac{v_1 - v_3}{6} = 0$$

$$\frac{v_1}{2} \left(\frac{1}{2} + \frac{1}{6} \right) - \frac{v_3}{6} = -5$$

②

$$2 + (-5) + \frac{v_2}{4} = 0$$


$$\frac{v_2}{4} = 3 \Rightarrow \underline{\underline{v_2 = 12}}$$

③

$$\frac{v_3 - v_1}{6} + (-2) + \frac{v_3}{5} = 0$$

$$\underline{\underline{-\frac{v_1}{6} + v_3 \left(\frac{1}{6} + \frac{1}{5} \right) = 2}}$$

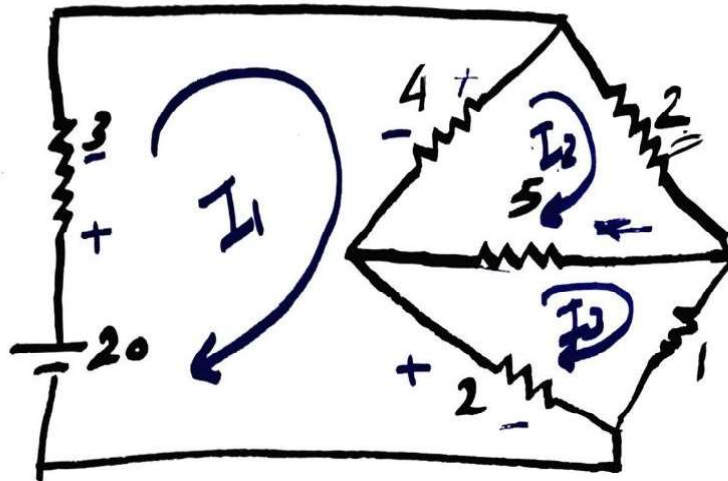Example: For the bridge network shown, using the Loop current method find the current in R_5 .



Solution:

Loop 1:

$$20 - 3I_1 - 4(I_1 - I_2) - 2(I_1 - I_3) = 0$$

$$(-3 - 4 - 2)I_1 + 4I_2 + 2I_3 = -20$$

$$9I_1 - 4I_2 - 2I_3 = 20 \quad \text{--- (1)}$$

Loop 2:

$$-4(I_2 - I_1) - 2(I_2) - 5(I_2 - I_3) = 0$$

$$(+4I_1 - 11I_2 + 5I_3 = 0) \quad \text{--- (2)}$$

$$-4I_1 + 11I_2 - 5I_3 = 0 \quad \text{--- (2)}$$

Loop 3:

$$-2(I_3 - I_1) - 5(I_3 - I_2) - 1I_3 = 0$$

$$-2I_1 - 5I_2 + 8I_3 = 0 \quad \text{--- (3)}$$

$$9I_1 - 4I_2 - 2I_3 = 20$$

$$-4I_1 + 11I_2 - 5I_3 = 0$$

$$-2I_1 - 5I_2 + 8I_3 = 0$$

$$I_1 = 4$$

$$I_2 = \frac{\begin{vmatrix} 9 & 20 & -2 \\ -4 & 0 & -5 \\ -2 & 0 & 8 \end{vmatrix}}{\begin{vmatrix} 9 & -4 & -2 \\ -4 & 11 & -5 \\ -2 & -5 & 8 \end{vmatrix}} = \frac{8}{3} = 2.66 \text{ A}$$

$$I_3 = \frac{8}{3} = 2.66 \text{ A}$$

$$I_5 = I_2 - I_3 = \frac{8}{3} - \frac{8}{3} = 0 \text{ A}$$


Nodal = ??

+1 1


+1 2

+1 3

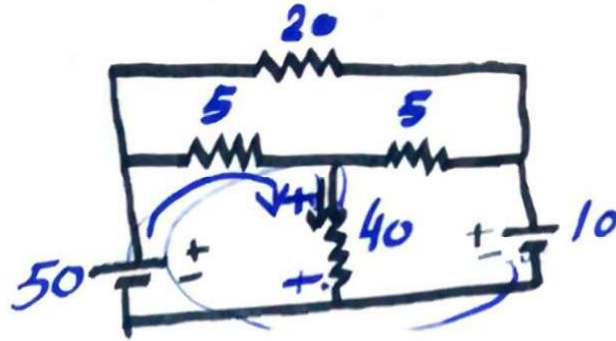
Example. Use the superposition theorem.
Find the current in the 40 Ω






Solution:

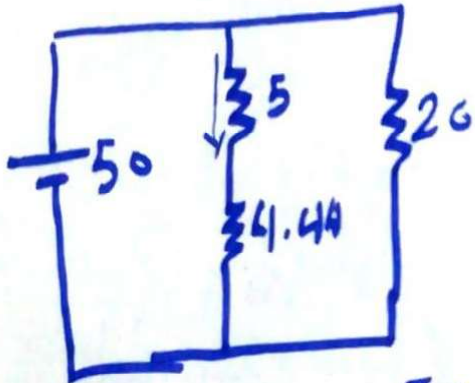
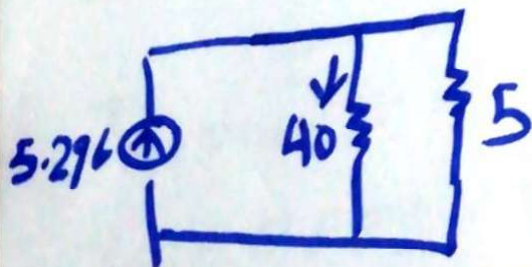
$$I = \frac{V}{R} = \frac{50}{5 + 4.44} = 5.296 \text{ A}$$




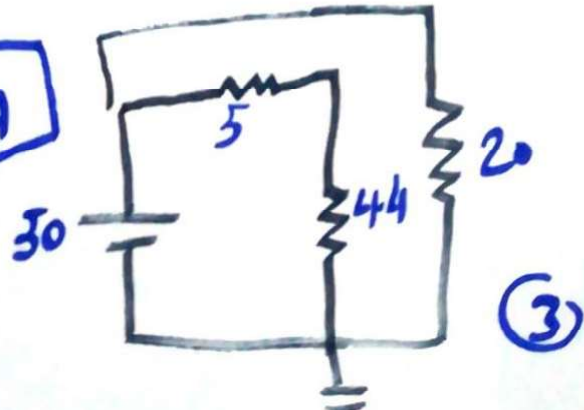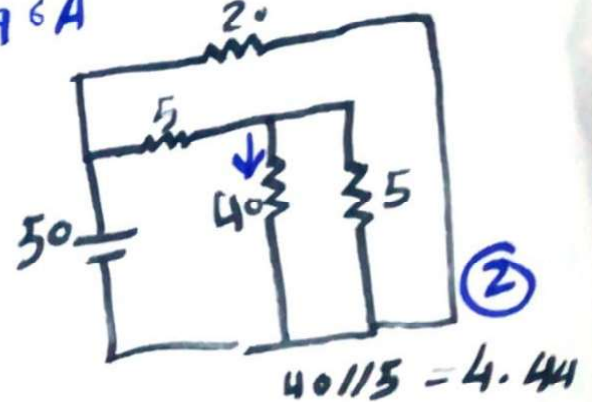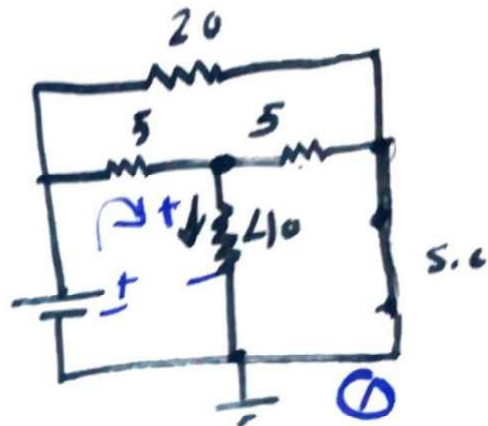
$$\bar{I}_{40} = \frac{5.296 \times 5}{5 + 40} = 0.589 \text{ A}$$




$$I = \frac{V}{R_T} = \frac{10}{5 + 4.44}$$

$$I = 1.059 \text{ A}$$

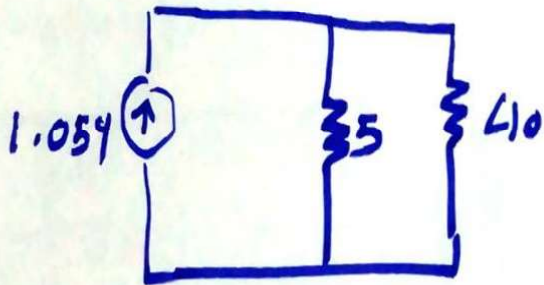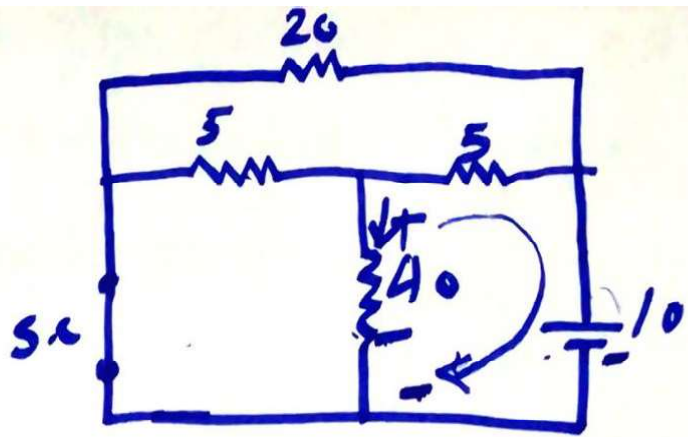

$$\bar{I}_{40} = 1.059 \times \frac{5}{5 + 40}$$

$$\bar{I}_{40} = 0.118 \text{ A}$$

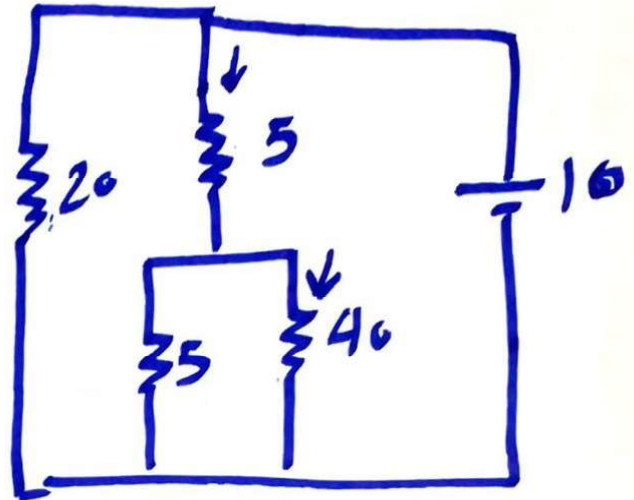


$$5 / 40 = 4.44$$



$$I_{40} = \bar{I}_4 + \bar{\bar{I}}_4 = \bar{I}_4 - (-\bar{I}_4) = \bar{I}_4 + \bar{\bar{I}}_4$$

$$I_{40} = 0.589 + 0.118 = 0.707 \text{ A}$$

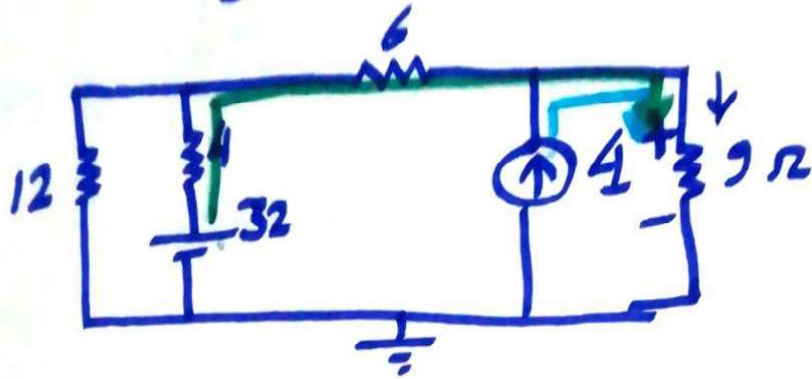Example :: Find the current in the 9Ω using superposition theorem.




Solution ::

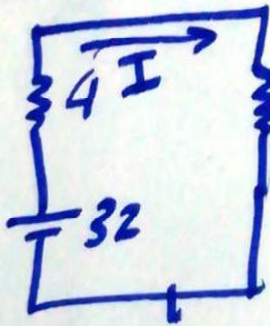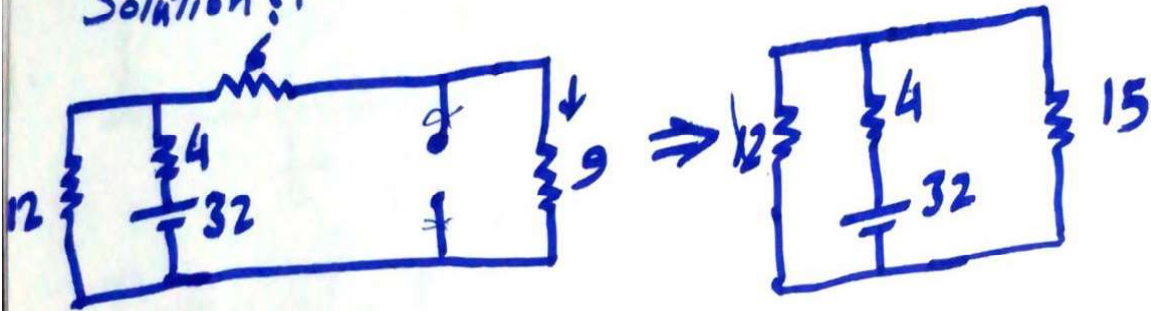

$$15 // 12 = \frac{20}{3}$$



$$I = \frac{V}{R_T} = \frac{32}{4 + \frac{20}{3}} = 3A$$
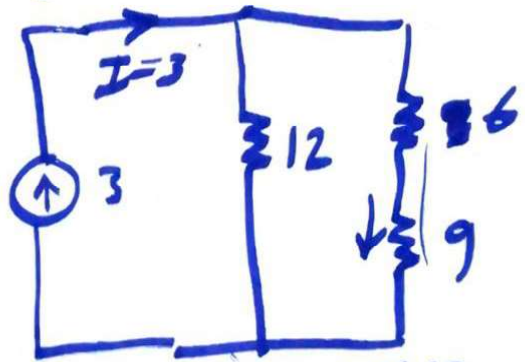
$$\bar{I}_9 = \frac{3 \times 12}{12 + (6 + 9)} = \frac{4}{3} A$$



$$(9 + 6) // 12 = \frac{20}{3}$$




②

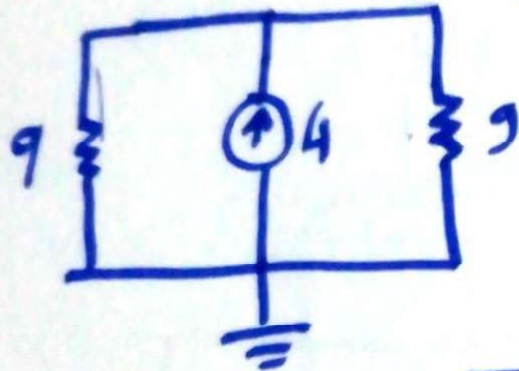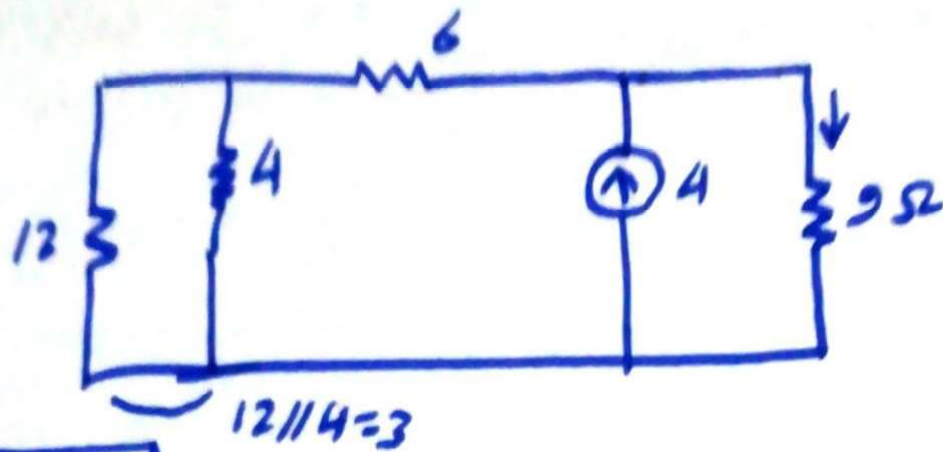

$$\bar{I}_9 = \frac{4 \times 9}{9+9} = 2 \text{ A}$$

$$I_{9\Omega} = +\bar{I}_9 + \bar{I}_9 = \frac{4}{3} + 2 = \frac{10}{3} \text{ A}$$

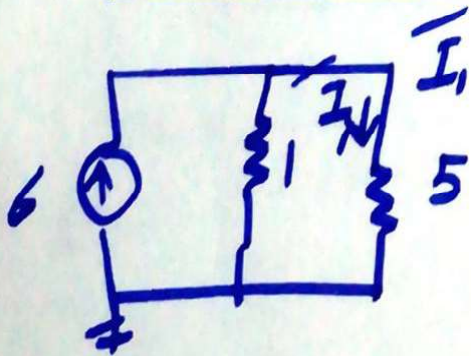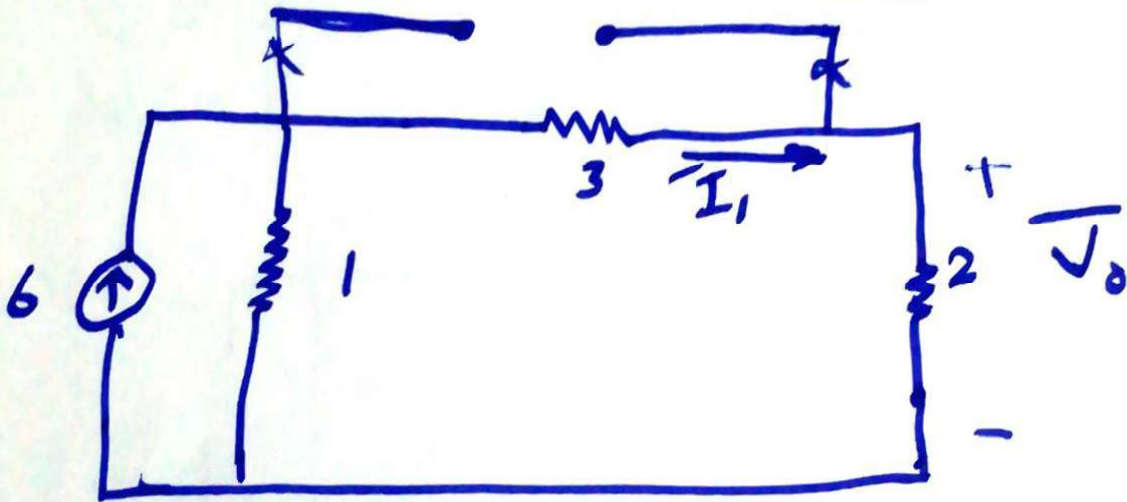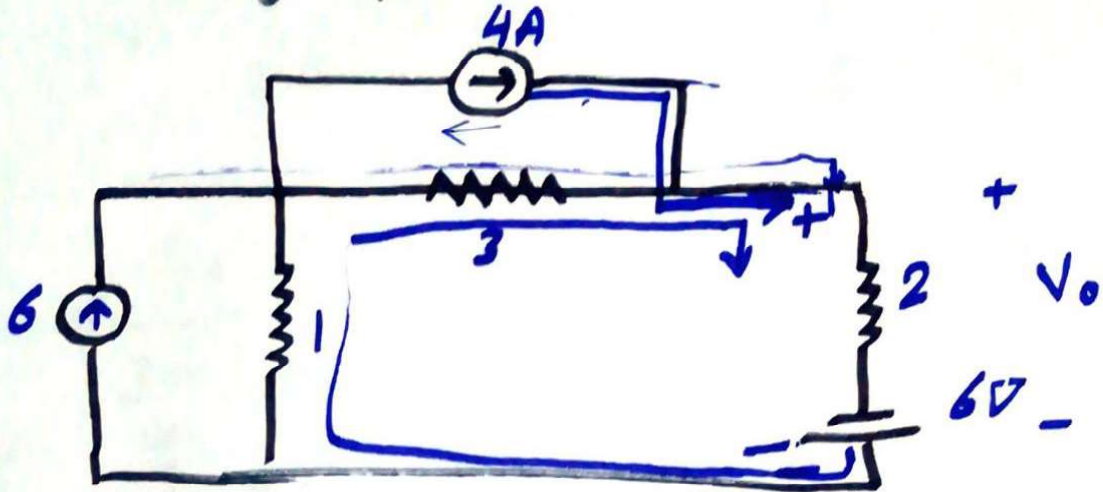
Example: find the Value of the Output Voltage V_o using Superposition.



$$\bar{I}_1 = \frac{6 \times 1}{1+5}$$


$$\bar{I}_1 = \frac{6 \times 1}{1+2+3} = 1A$$
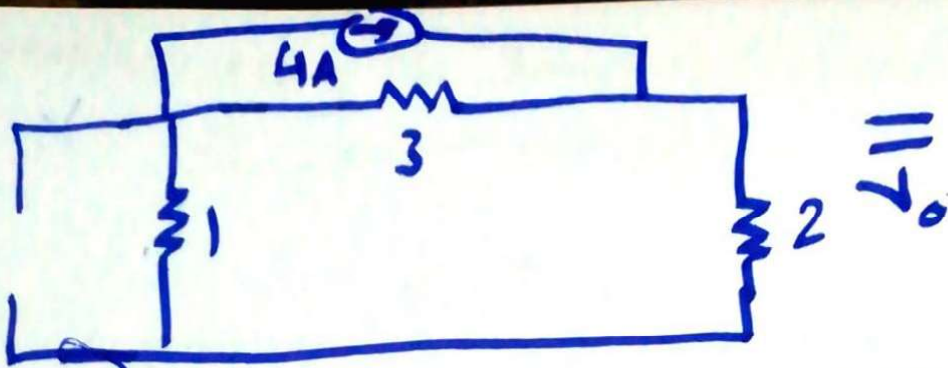
$$V_o = \bar{I}_1 \times 2 = 1 \times 2 = \underline{\underline{2V}}$$




$$\bar{I}_1 = \frac{4 \times 3}{3+1+2} = 2A$$
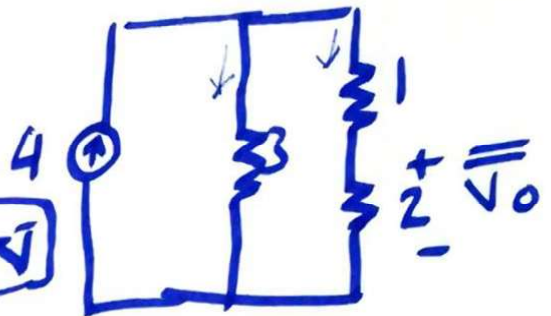
$$\bar{V}_o = \bar{I}_1 \times 2 = 2 \times 2 = 4V$$



~~~~~

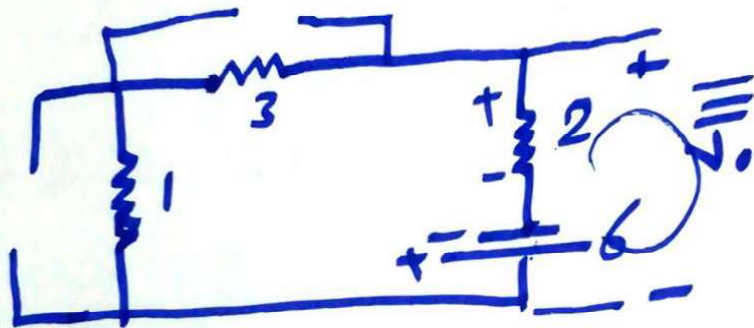

$$V_{2\Omega} = \frac{6 \times 2}{1+3+2} = 2V$$

$$\bar{V}_o = 2 - 6 = -4$$

$$\bar{V}_o = -4$$



$$\bar{V}_o = 2V$$

$$\bar{V}_o = 4V$$


$$V_o = +\bar{V}_o + \bar{V}_o + \bar{V}_o$$

$$V_o = 2V + 4V + (-4) = 2V$$

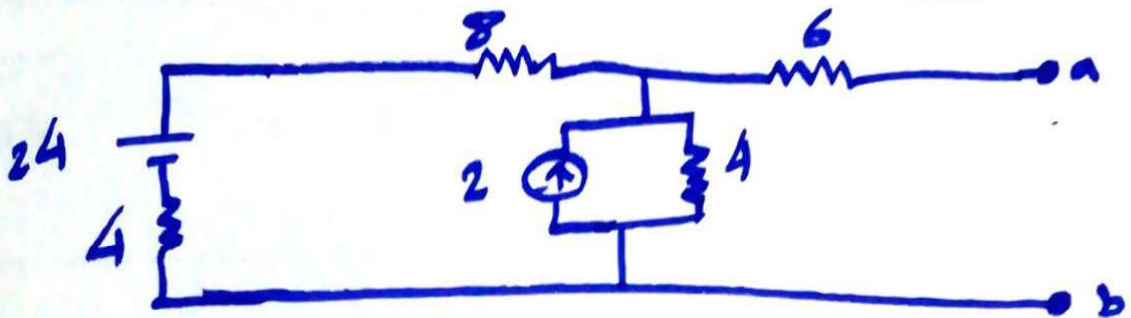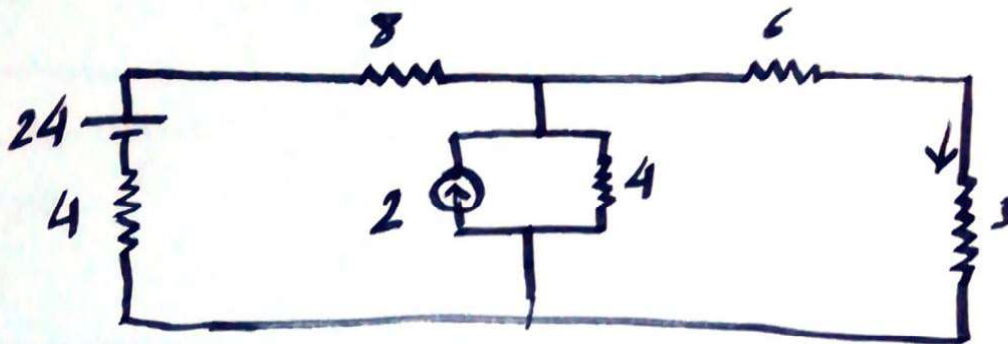Example 2. Using the Thevenin's theorem to find the current in the  $3\Omega$ .



$$E = IR = 2 \times 4 = 8V$$


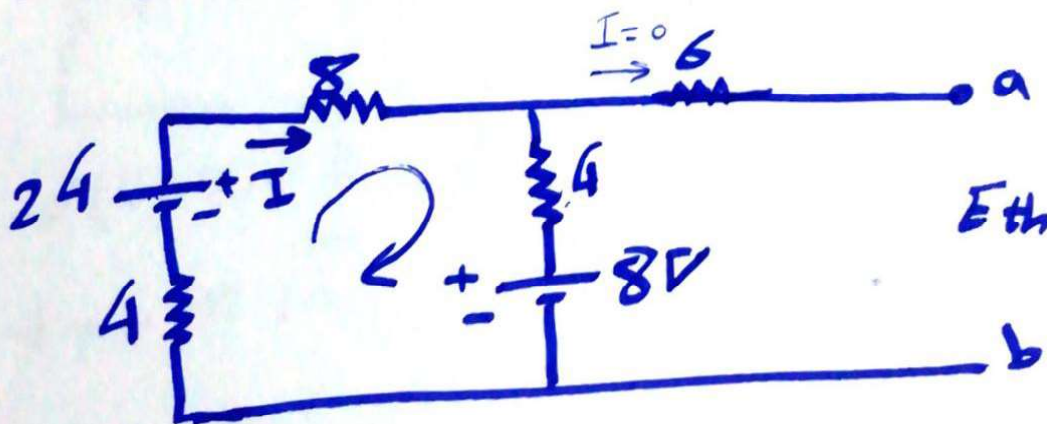


$E_{th}$


$$I = \frac{24 - 8}{8 + 4 + 4} = 1A$$

$$V_{4\Omega} = 1 \times 4 = 4V$$

$$E_{th} = 8 + 4 = 12V$$

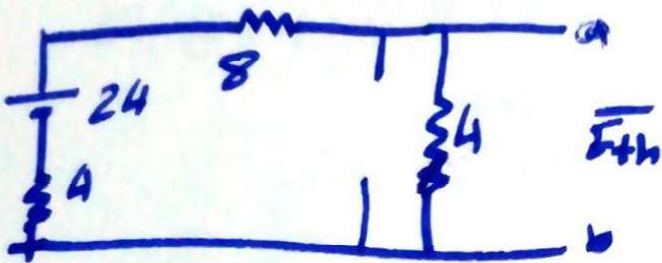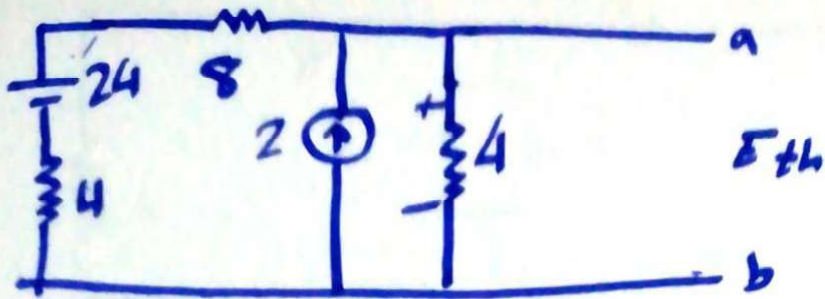

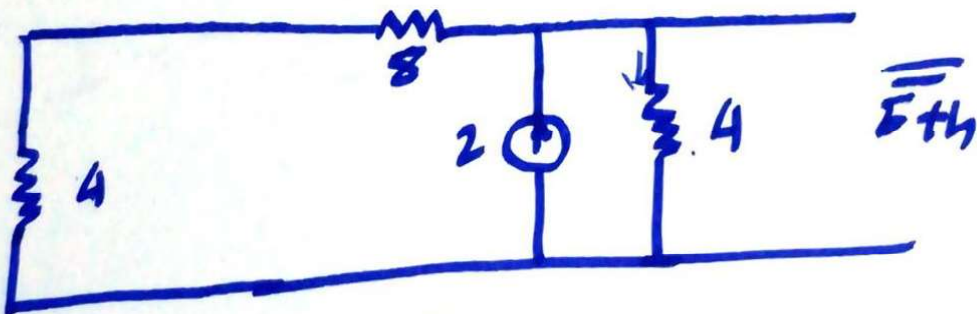
$$\overline{E}_{th} = \sqrt{4\Omega} = \frac{24 \times 4}{8+4+4} = 6 \text{ V}$$




$$R_T = (4+8) // 4 = 3 \Omega$$

$$V_T = \overline{E}_{th} = I R_T = 2 \times 3 = 6 \text{ V}$$
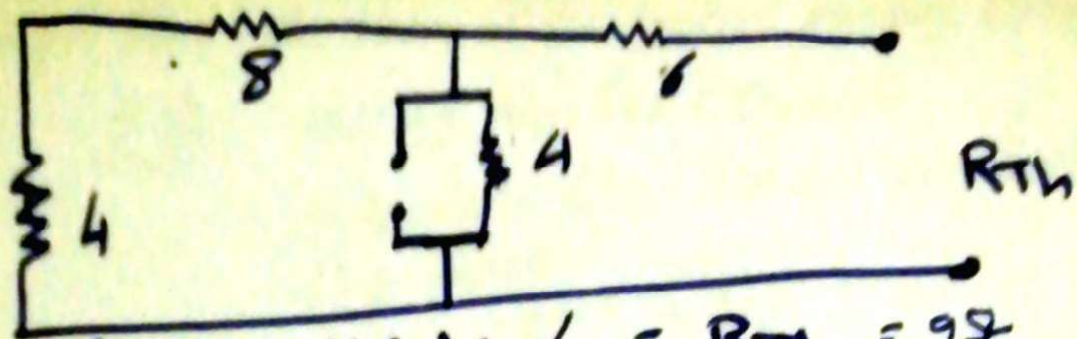
$$E_{th} = +\overline{E}_{th} + \overline{E}_{th} = 6 + 6 = 12 \text{ V}$$





$$((8+4) // 4) + 6 = R_{Th} = 9\Omega$$

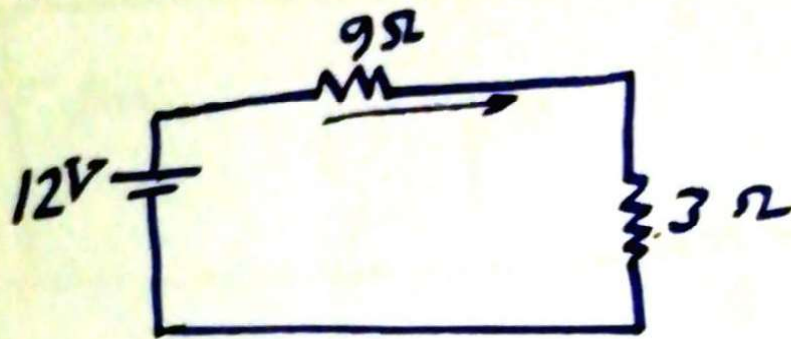

$$I = \frac{E_{Th}}{R_T} = \frac{12}{9+3} = \frac{12}{12} = 1A$$

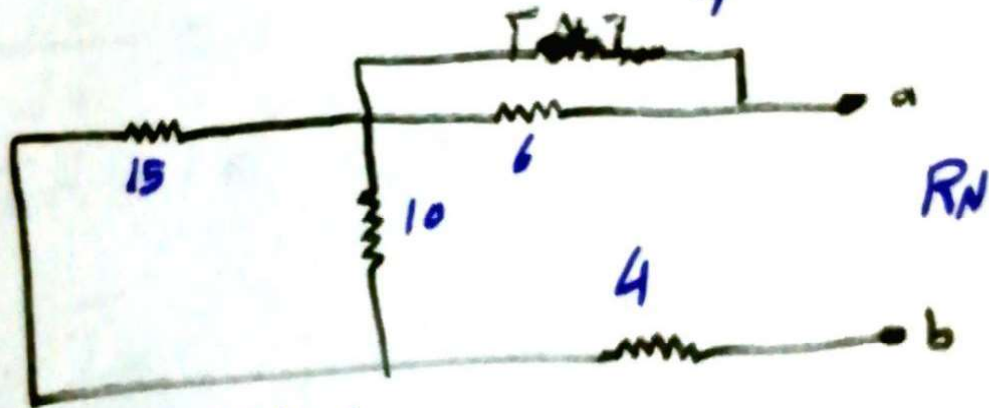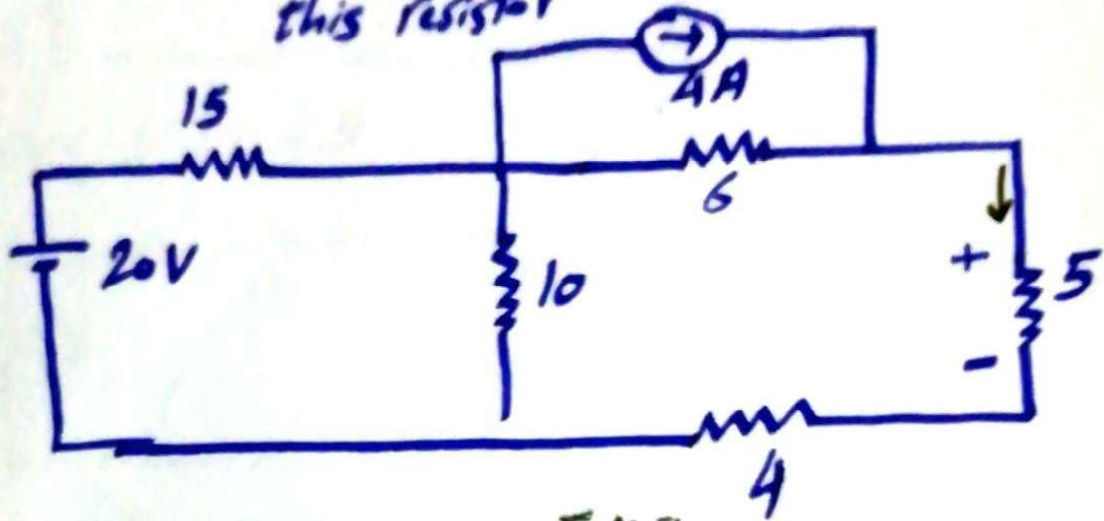
Example: Find the value of the current passing through 5Ω using Norton's theorem. Calculate the power absorbed by this resistor.




$$(15 \parallel 10) = 6$$


$$R_N = (15 \parallel 10) + 4 + 6 = 16\Omega$$

$\bar{I}_N$

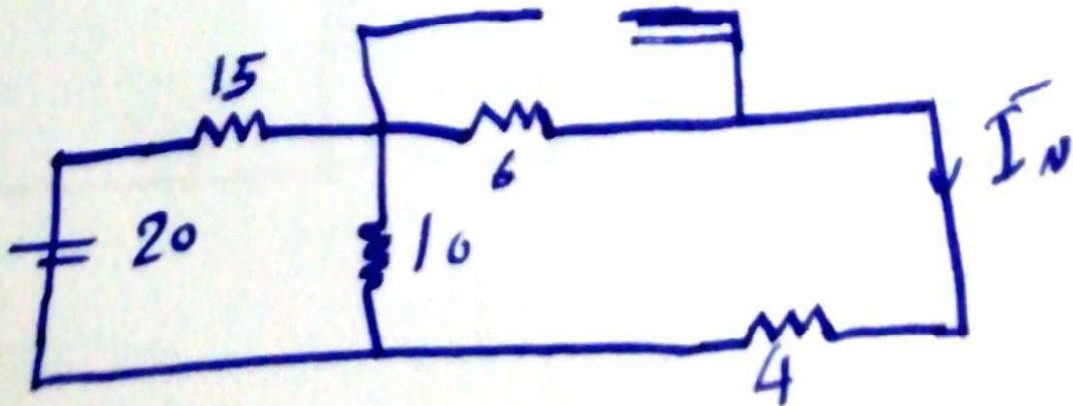

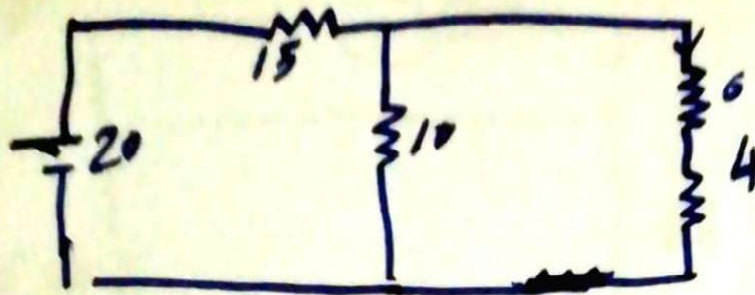


$$(6+4) \parallel 10 = 5$$

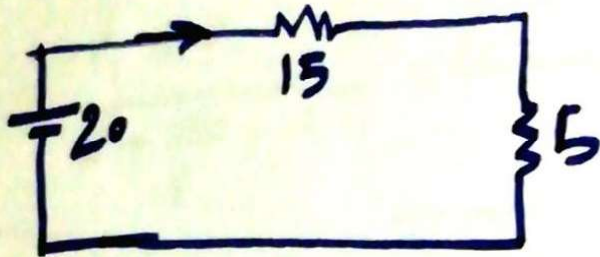


$$I = \frac{20}{20} = 1$$

$$V_{5\Omega} = IR = 1 \times 5 = 5V$$
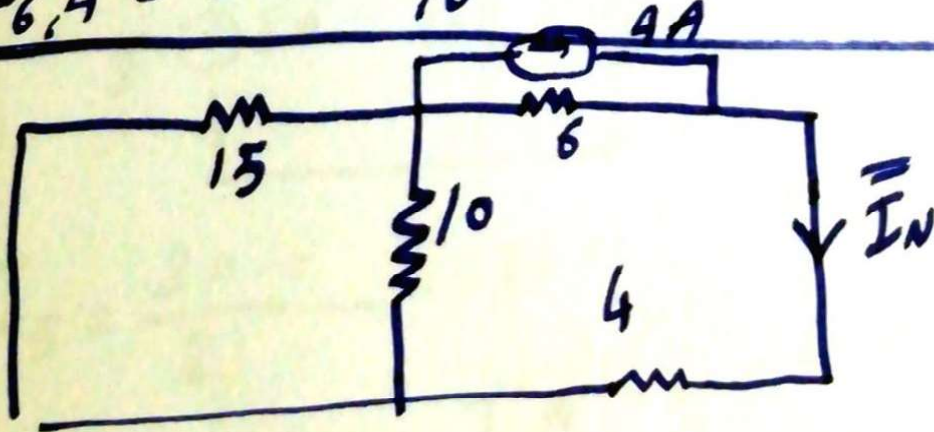
$$I_{6,4} = \bar{I}_N = \frac{5}{10} = \frac{1}{2} = \boxed{0.5A}$$



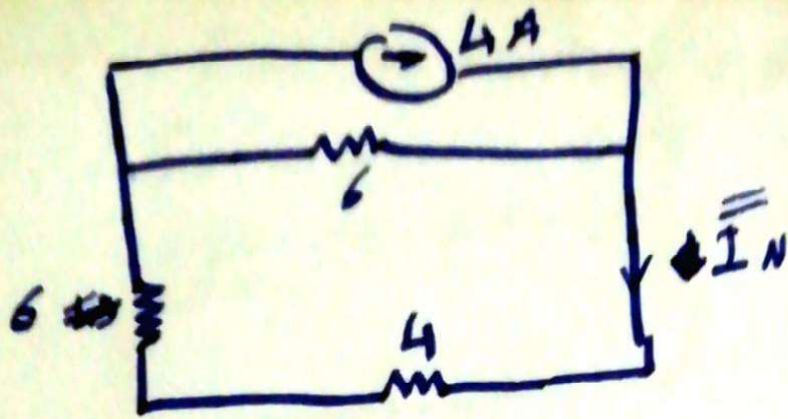


$$\bar{I}_N = \frac{4 \times 6}{6 + \cancel{6} + 4} = \cancel{\frac{3}{2}} = 1.5 \text{ A}$$

$$\bar{I}_N = 0.5 \text{ A}$$

$$\bar{I}_N = 1.5 \text{ A}$$
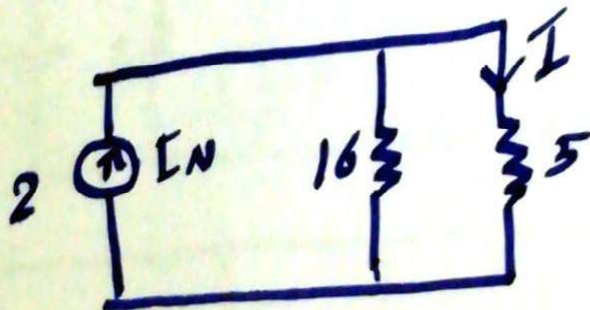
$$I_N = \bar{I}_N + \bar{I}_N = 0.5 + 1.5 = 2 \text{ A}$$






$$I_5 = \frac{2 \times 16}{21} = 1.52 \text{ A}$$





$$P = V \times I = I^2 \times R = (1.52)^2 \times 5 = 11.6$$




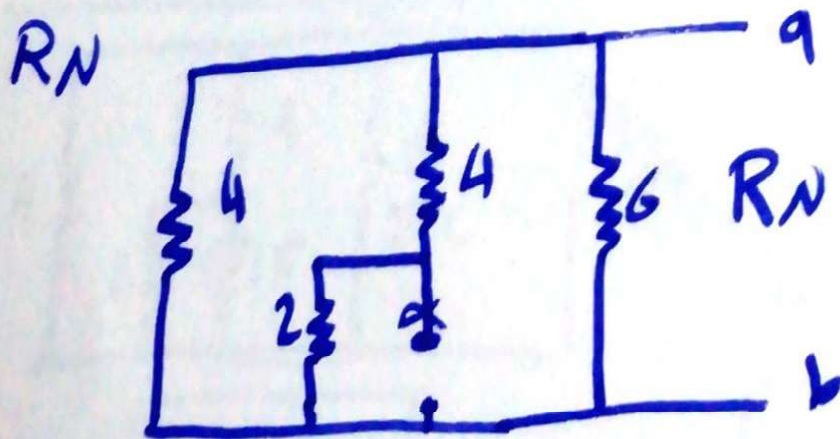
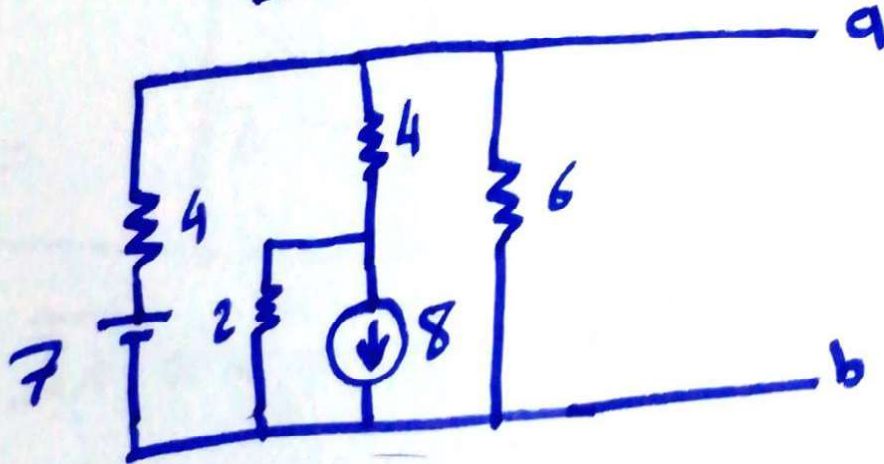
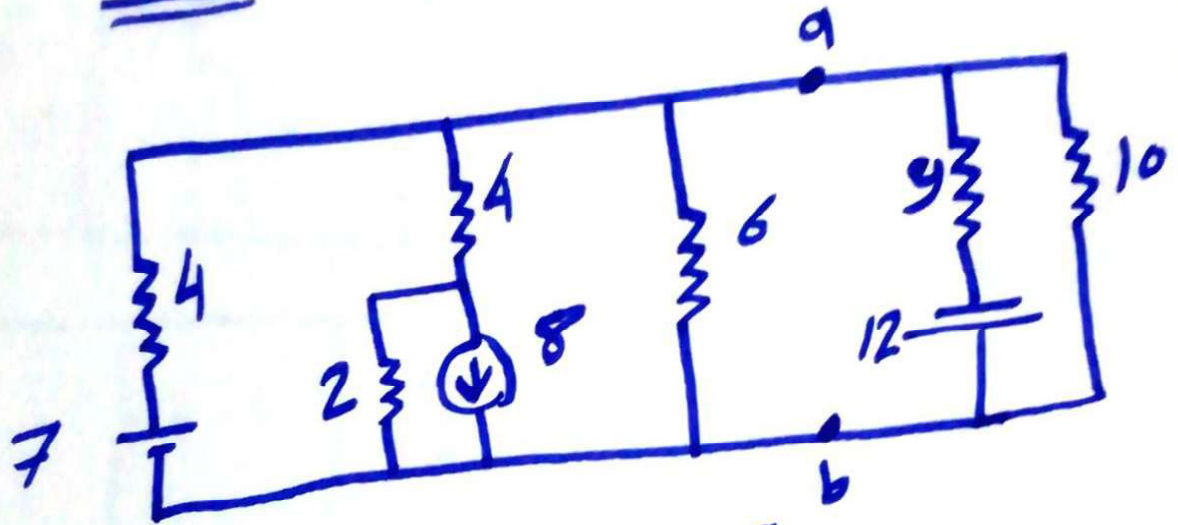
Example: Find the Norton equivalent circuit for the portion of the network to the left of (a-b) in the circuit shown.


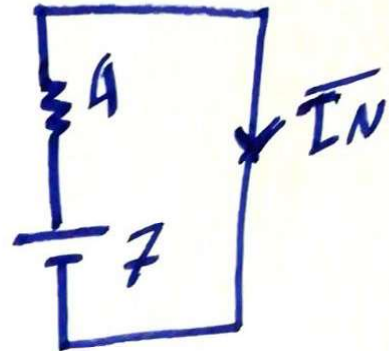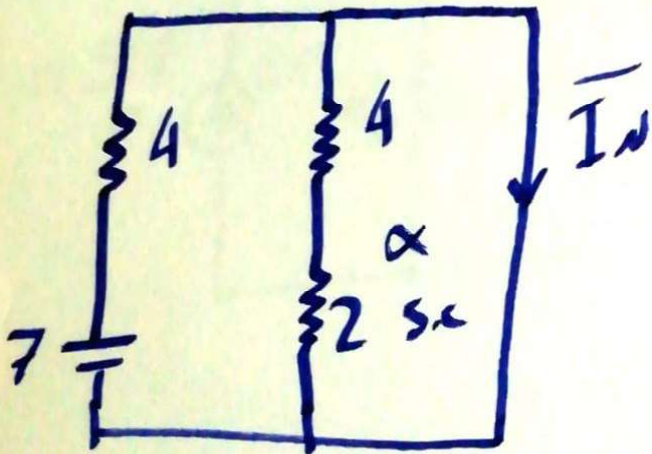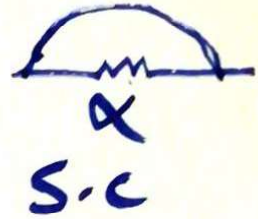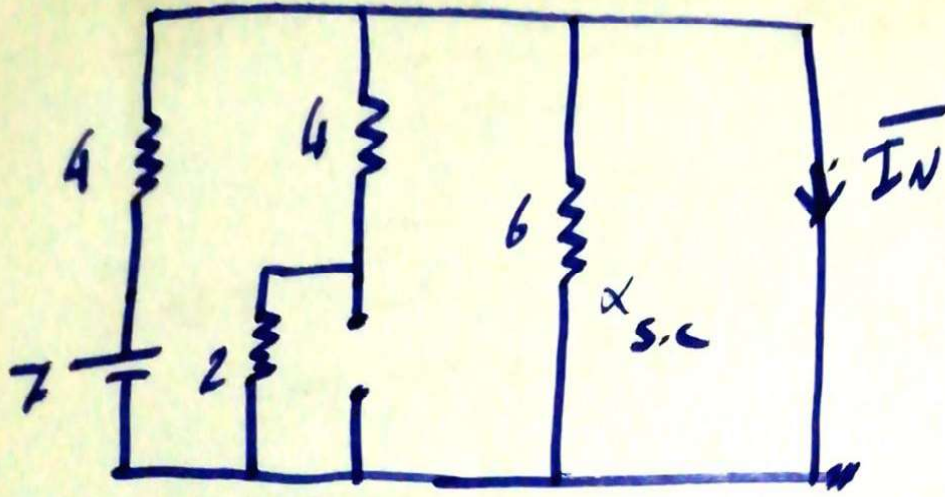
$$R_N = 4 \parallel (4+2) \parallel 6 = 1.714 \Omega$$



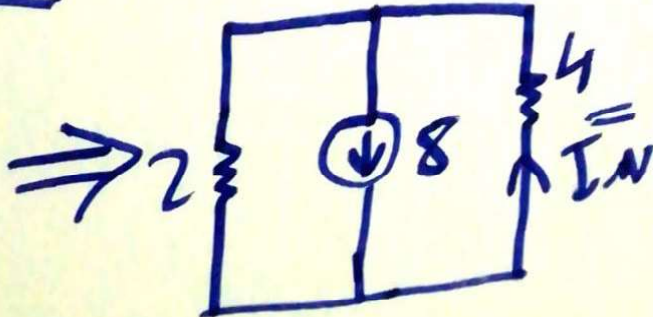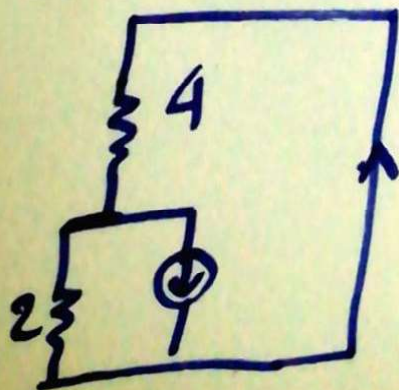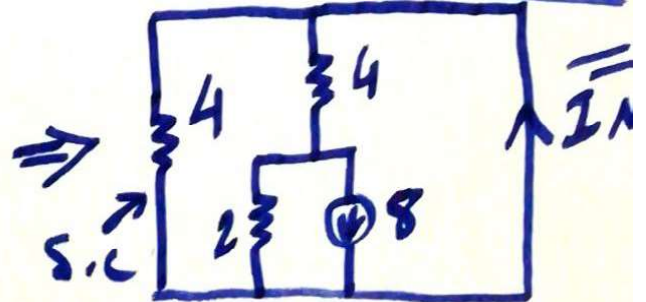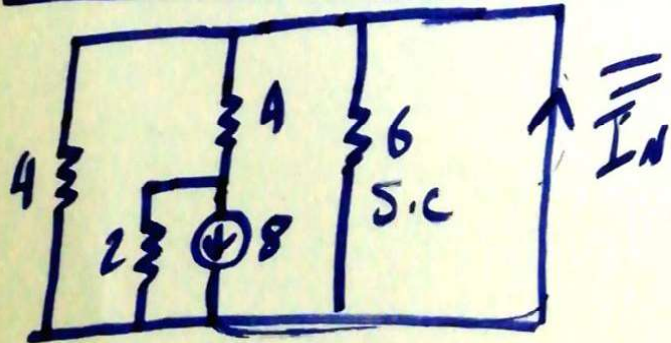
$$\bar{I}_N = \frac{7}{4} = 1.75 \text{ A}$$




$$\bar{I}_N = \frac{8 \times 2}{2 + 4} = 2.667 \text{ A}$$

$$I_N = -\bar{I}_N + \bar{I}_N$$
$$= -1.75 + 2.667 = 0.917 \text{ A}$$

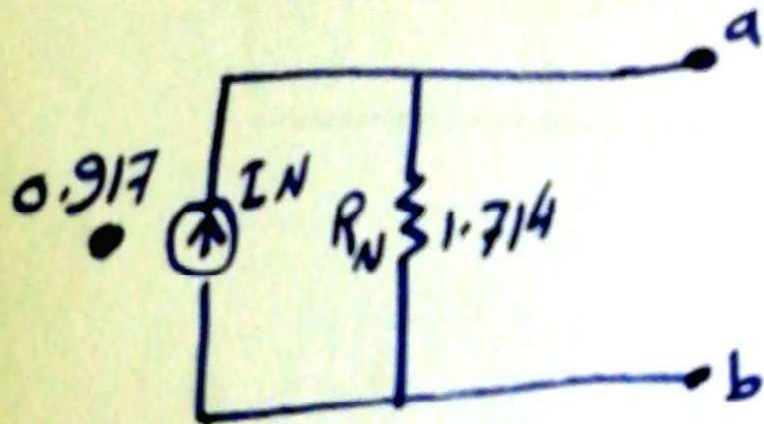

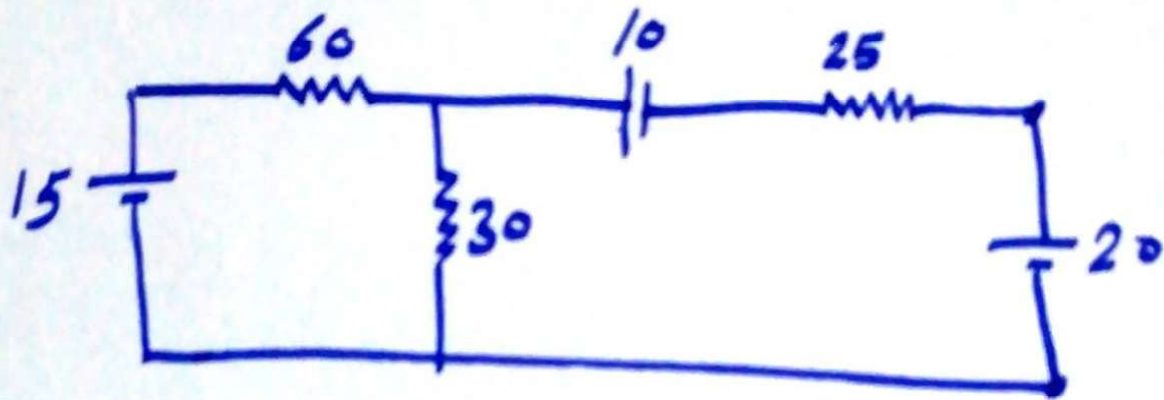Example 1: For the circuit, find the current through the 20V voltage source using Thevenin's theorem.



H.W

# Series and Parallel AC circuits

## 1- Series circuits


### 1.1 AC through R and L

$V =$  the rms value of voltage

$$\bar{V}_{rms} = \frac{V}{\sqrt{2}}$$

$I =$  The rms value of the current

$$\bar{I}_{rms} = \frac{I}{\sqrt{2}}$$

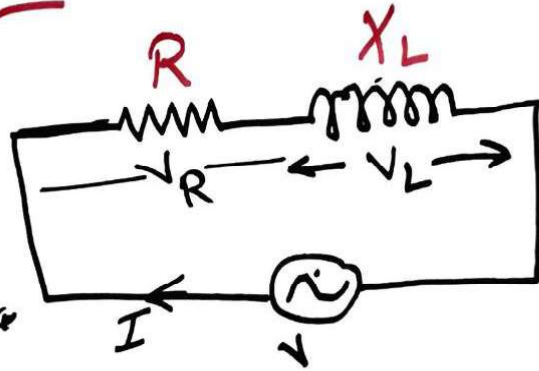


$$V_R = IR$$

$$V_L = IX_L$$

\* (V in phase I)  $\phi = 0$

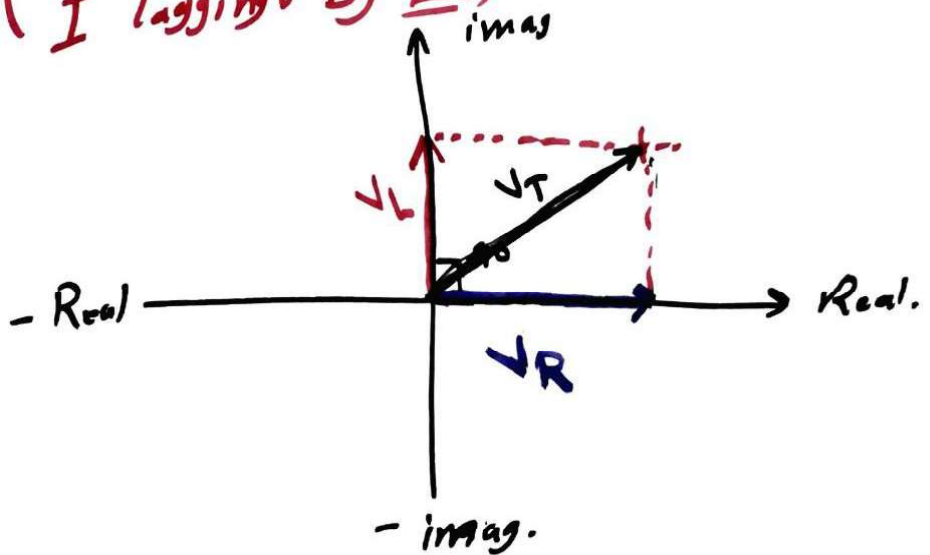(V leading I by  $90^\circ$ )  
(I lagging V by  $90^\circ$ )



$$V_{\text{eff}}^2 = V_R^2 + V_L^2$$

$$V = \sqrt{V_R^2 + V_L^2}$$

$$V = \sqrt{(IR)^2 + (IX_L)^2}$$

$$V = \sqrt{I^2(R^2 + X_L^2)}$$

$$V = I \sqrt{R^2 + X_L^2} \quad **$$

$$I = \frac{V}{\sqrt{R^2 + X_L^2}}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$I = \frac{V}{Z}$$


$$V = IZ$$

$\phi$  phase

$$\tan \phi = \frac{\text{مقابل}}{\text{مجاور}} = \frac{V_L}{V_R} = \frac{IX_L}{IR} = \frac{X_L}{R}$$

$$\frac{\phi}{\tan^{-1}} = \frac{X_L}{R} \Rightarrow$$

$$\phi = \tan^{-1} \frac{X_L}{R}$$

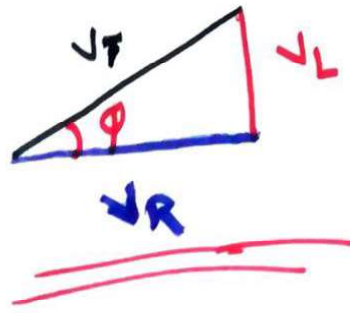

$$X = R + yi$$

$$\bar{X} = \sqrt{R^2 + y^2}$$

$$\phi = \tan^{-1} \frac{y}{R}$$

$$X = \bar{X} \angle \phi$$

$$R \angle 0$$

$$X_L \angle 90$$

$$\bar{Z} = \underline{R \angle 0} + X_L \angle 90$$

$$\bar{Z} = R + jX_L$$

$$R \cos \phi = R$$

$$R \sin \phi = 0i$$


$$R + j0$$

$$X_L \cos 90 = 0$$

$$jX_L \sin 90 = jX_L$$

$$0 + jX_L$$

Impedance diagram

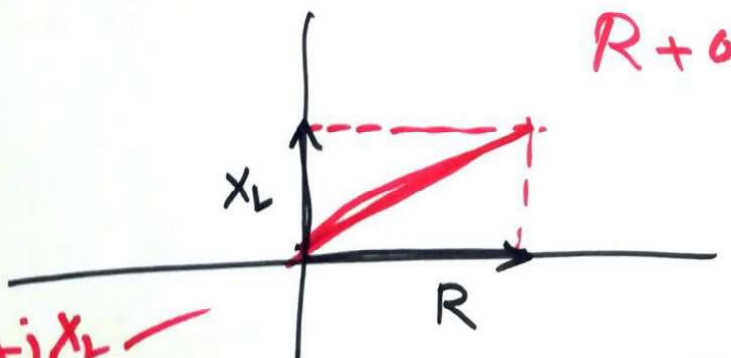


$$\bar{Z} = R + jX_L$$


$$\bar{Z} = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1} \frac{X_L}{R}$$

$$\bar{Z} = Z \angle \phi$$

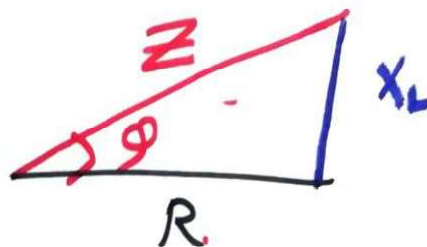

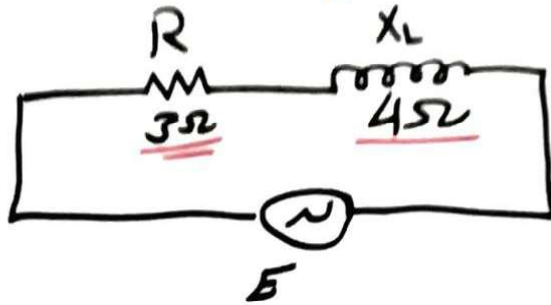Example :: for the circuit shown, determine the total  $\bar{Z}_T$  impedance and draw the impedance diagram



Solution ::

$$\bar{Z}_T = R + jX_L$$

$$\bar{Z}_T = 3 + j4$$

Vector form


$4 \angle 90^\circ$

$$Z = \sqrt{3^2 + 4^2} = 5$$

$$\phi = \tan^{-1}\left(\frac{4}{3}\right) = 53.13^\circ$$

$$\bar{Z}_T = 5 \angle 53.13$$

Polar form

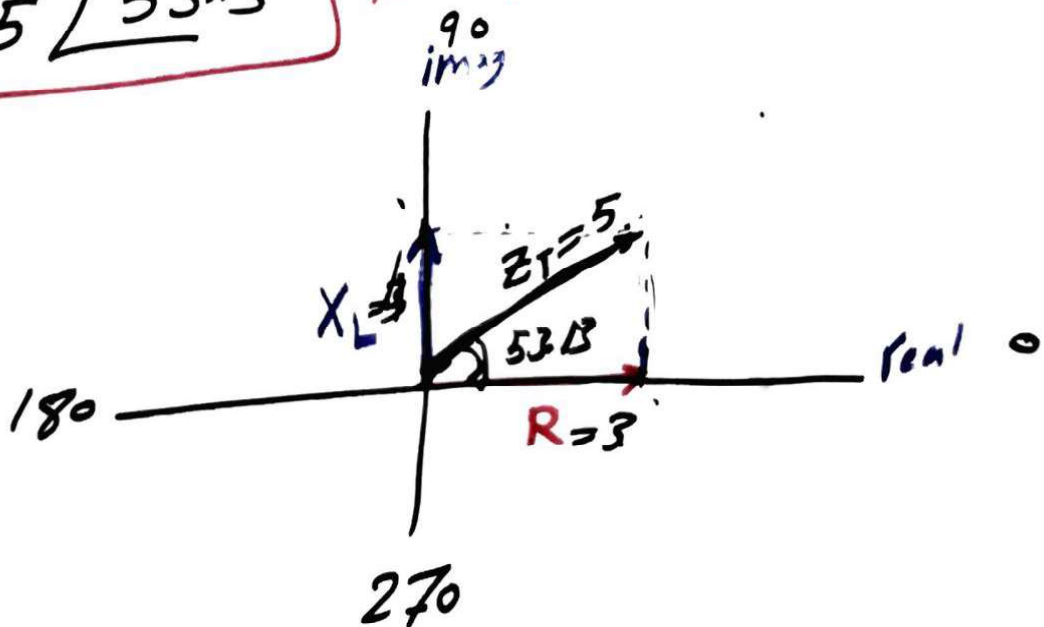





# Power factor (P<sub>f</sub>)

I leading V -||-  
I lagging V -||-

\*  $P_f = \cos \phi$

\*  $P_f = \frac{R}{Z_T}$

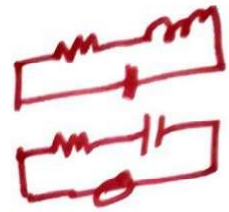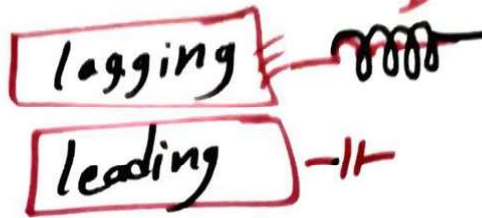

## \* The Apparent Power (S)

$S = V \cdot I = (IZ)I = I^2 Z \quad \text{(VA)}$


$S = \sqrt{Q^2 + P^2} = \sqrt{(I^2 R)^2 + (I^2 X_L)^2}$

## \* The Active Power (P)

$P = \frac{I^2 R}{\text{W}} = \sqrt{I} \cos \phi = S \cos \phi$
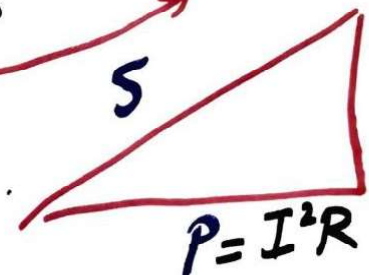
## \* The Reactive Power (Q)

$Q = I^2 X_L = \frac{VI \sin \phi}{\text{VAR}} = S \sin \phi$




## \* The quality factor of the coil

$Q_{\text{factor}} = \frac{1}{P_f} = \frac{1}{\cos \phi} = \frac{Z_T}{R}$

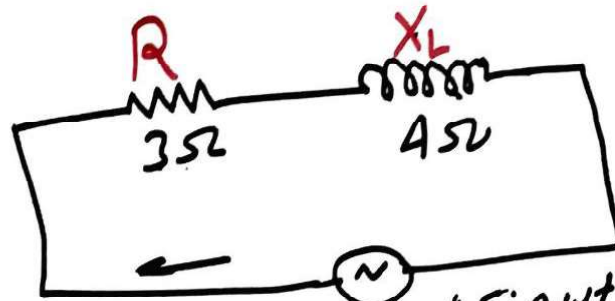**Example:** For the circuit shown, draw the phasor diagram of the voltage across each element and applied voltage and determine -

- The power factor
- The active power **and reactive power**
- The apparent power



$$v = 141.4 \sin(\omega t + 0) \times \sin(\omega t + \phi)$$

Solution

$$V = \frac{141.4}{\sqrt{2}} = 100 \angle 0 \Rightarrow 100 + j0$$

$$\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2$$

$$\bar{Z}_T = 3 + j4 \Leftrightarrow \bar{Z}_T = 5 \angle 53.13^\circ$$

~~$$I = \frac{V}{Z_T} = \frac{100 \angle 0}{5 \angle 53.13} = \frac{100}{3 + j4}$$~~

$$I = \frac{100}{5} \angle 0 - 53.13 = 20 \angle -53.13$$

$$V_R = IR \Rightarrow 20 \angle -53.13 \times 3 \angle 0$$

$$V_R = 60 \angle -53.13$$

$$V_L = I X_L = 20 \angle -53.13 \times 4 \angle 90$$
~~$$= 80 \angle$$~~

$$= (20 \times 4) \angle -53.13 + 90$$

$$V_L = 80 \angle 36.87$$

~~$$V_T = V_L + V_R$$~~

$$V_T = V_R + V_L$$

$$V_T = 60 \angle -53.13 + 80 \angle 36.87$$

$$V_T = \underline{36} - \underline{j48} + \underline{64} + \underline{j48}$$

$$V_T = 100 + 0$$



$$V_T = 100 \angle 0$$

$$V_R = 60 \angle -53.13$$

$$V_L = 80 \angle 36.87$$

$$V_T = 100 \angle 0$$


Phasor diagram  
Voltage

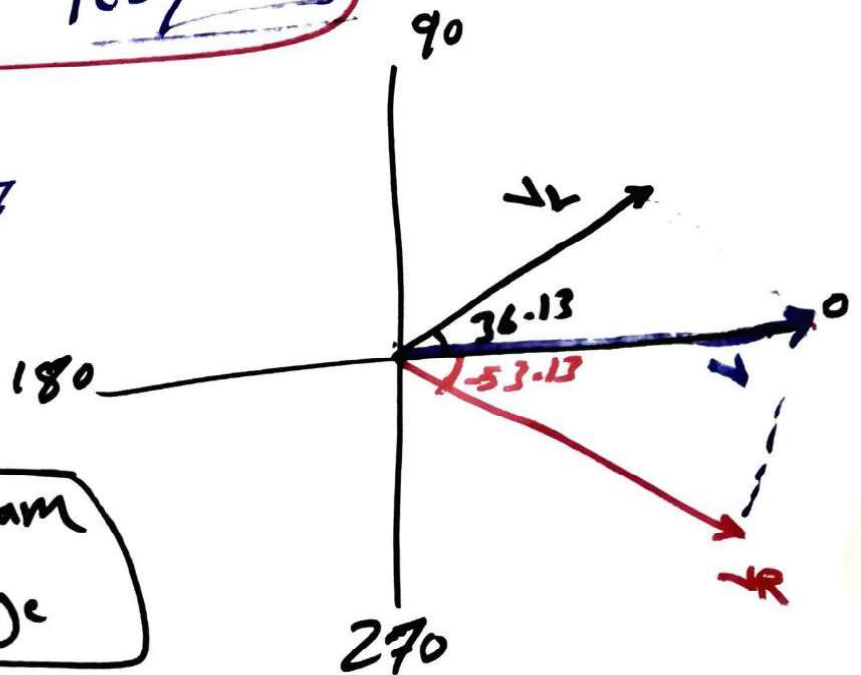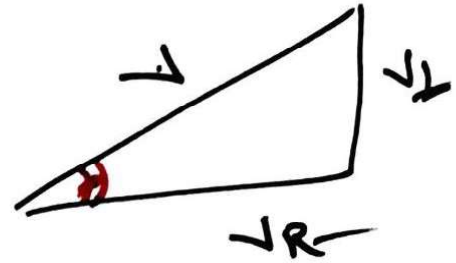

$$R = 3 \Omega$$

$$X_L = 4 \Omega$$

$$Z_T = 5 \angle 53.13$$

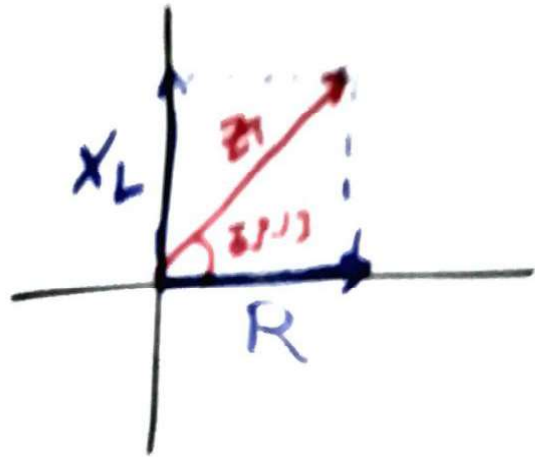

Power factor

$$\phi = -53.13$$

$$P_F = \cos(-53.13) = 0.6 \text{ lagging}$$

$$P = I^2 R = IV \cos \phi$$

$$I = 20 \angle -53.13$$

$$V = 100 \angle 0$$

$$\phi = -53.13$$

$$R = 3 \Omega$$

$$P = (20)^2 \times 3 = 1200 \text{ W}$$

$$P = IV \cos \phi = 20 \times 100 \times \cos 53.13 = 1200 \text{ W}$$

~~$Q = I^2 X_L = I^2 Z$~~   $X_L = 4 \Omega$

$$Q = I^2 X_L = IV \sin \phi$$

$$Q = (20)^2 \times 4 = 1600 \text{ VAR}$$


$$Q = IV \sin \phi = 20 \times 100 \sin 53.13 = 1600 \text{ VAR}$$

$$1.6 \text{ KVAR}$$

$$S = \sqrt{P^2 + Q^2} = 1968 \text{ VA}$$

$$S = IV = 20 \times 100 = 2000 \text{ VA}$$

# AC Through R and C

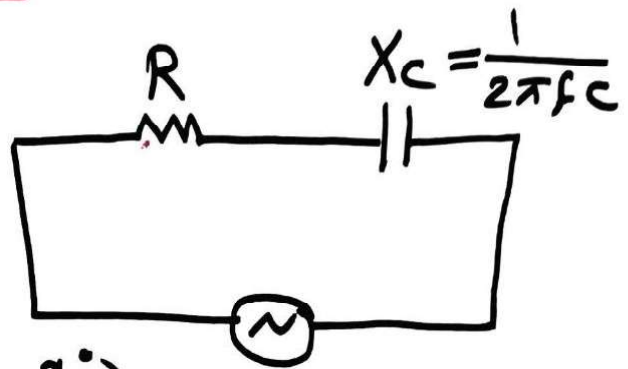

$$V_R = IR \quad \checkmark \text{ in phase } I$$

$$V_C = IX_C \left( \begin{array}{l} \checkmark \text{ lagging } I \text{ by } 90^\circ \\ I \text{ leading } \checkmark \text{ by } 90^\circ \end{array} \right)$$

$|A| \cdot \sin \omega t$

$$V = \sqrt{V_R^2 + V_C^2}$$

$$V = I \sqrt{R^2 + X_C^2}$$




$$V = I Z_T$$

$$Z_T = \sqrt{R^2 + X_C^2}$$


$$\tan \phi = \frac{\text{مقاوم}}{\text{مجاور}} = \frac{X_C}{R}$$

$$\phi = \tan^{-1} \frac{X_C}{R}$$
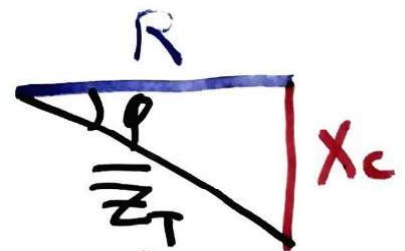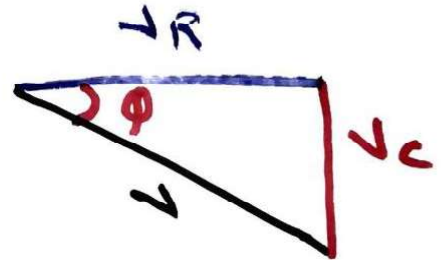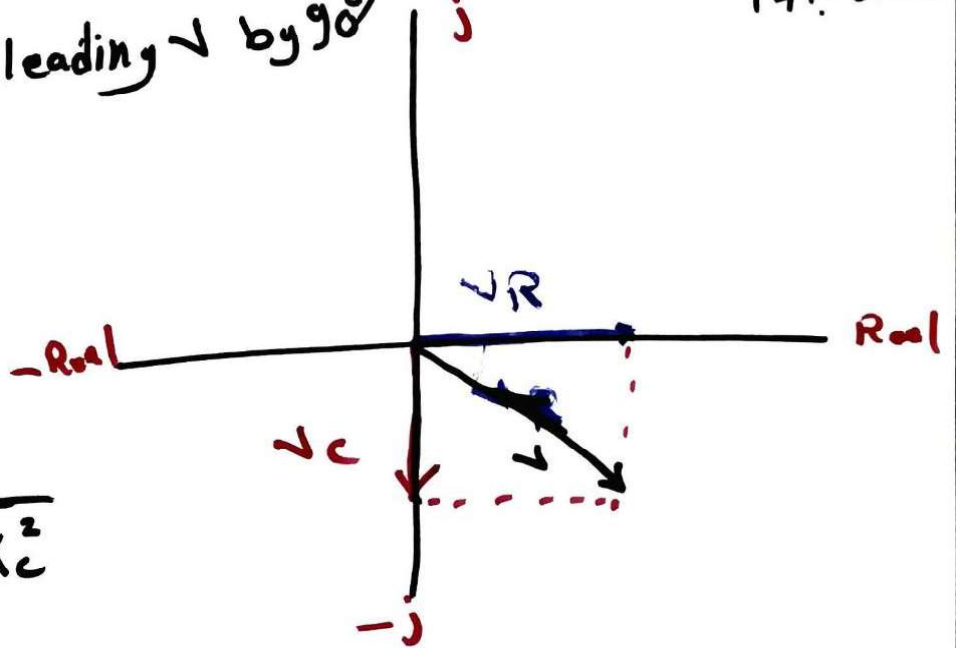
$$P_f = \cos \phi = \frac{V_R}{V} = \frac{R}{Z_T} \quad \text{leading}$$



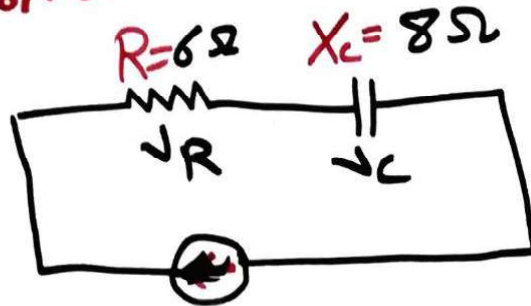Example: For the circuit shown, draw the phasor diagram. voltage



$$I = 5 \angle 53.13$$

Solution ①


$$I = 5 \angle 53.13 = 3 + 4i$$

$$Z_T = R - jX_c = 6 - j8$$

$$V_R = IR = (3 + 4i)(6) = 18 + 24i$$

$$V_C = IX_c = (3 + 4i)(-8i) = -24i + 32 = 32 - 24i$$

$$V = IZ = (3 + 4i)(6 - j8) = 50$$

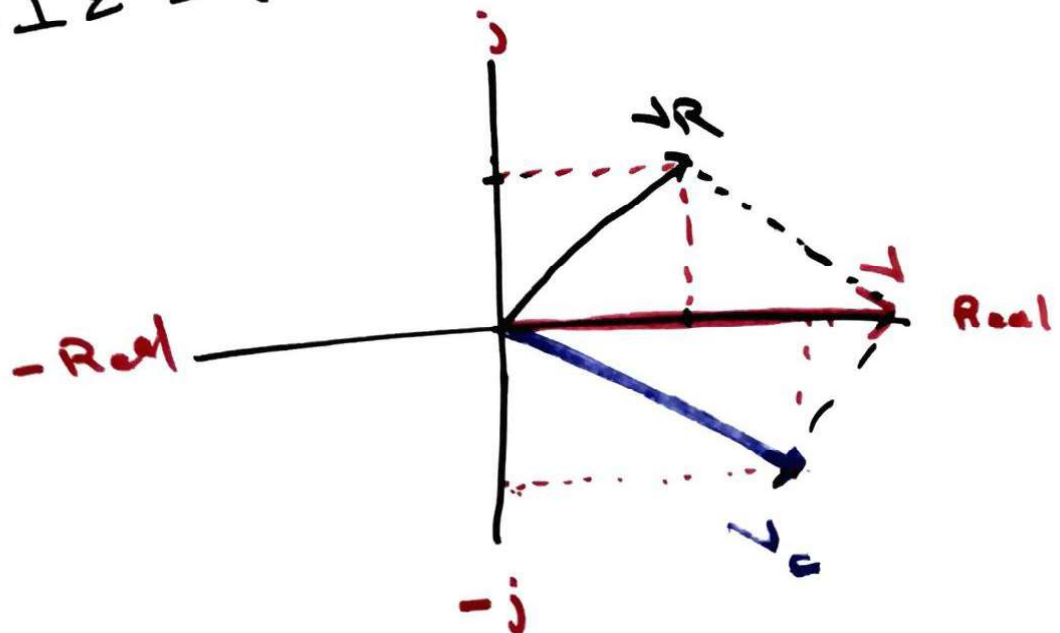

## Solution ②

$$I = 5 \angle 53.13$$

$$Z_T = 6 - 8i = \sqrt{6^2 + 8^2} \angle \tan^{-1} \frac{-8}{6}$$

$$Z_T = 10 \angle -53.13$$

$$\begin{aligned} R &\angle 0 \\ X_C &\angle -90 \\ X_L &\angle 90 \end{aligned}$$

$$V_R = IR = 5 \angle 53.13 * 6 \angle 0$$


$$V_R = 30 \angle 53.13$$

$$V_C = IX_C = 5 \angle 53.13 * 8 \angle -90$$

$$V_C = 40 \angle -36.87$$


$$V = E = IZ = 5 \angle 53.13 * 10 \angle -53.13$$

$$V = 50 \angle 0$$

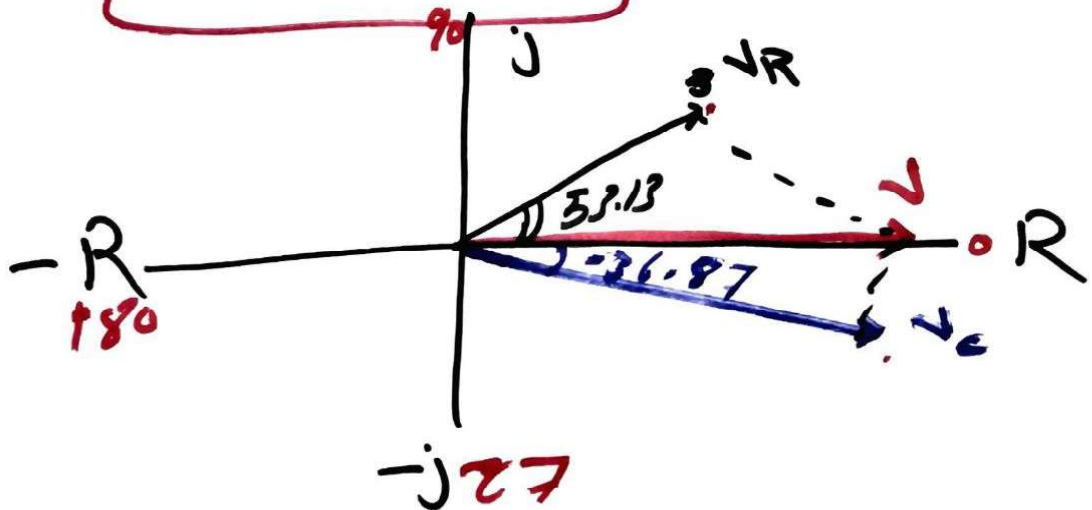



### 3- AC Through RLC Series circuit

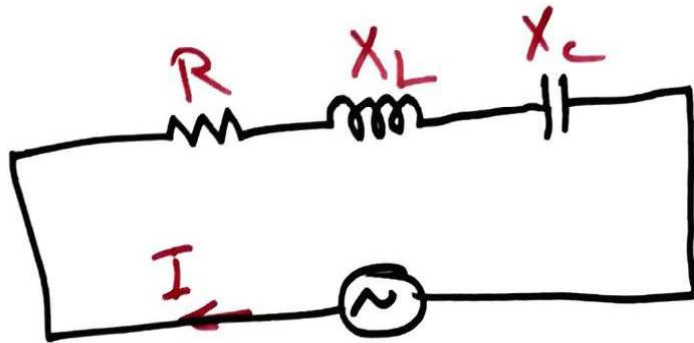

$$Z = R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ$$

$$Z = R + jX_L - jX_C$$



$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$$\bar{E} = Z I$$

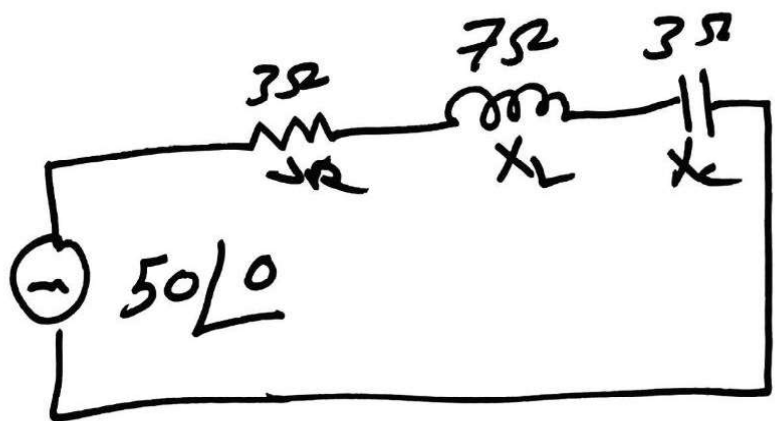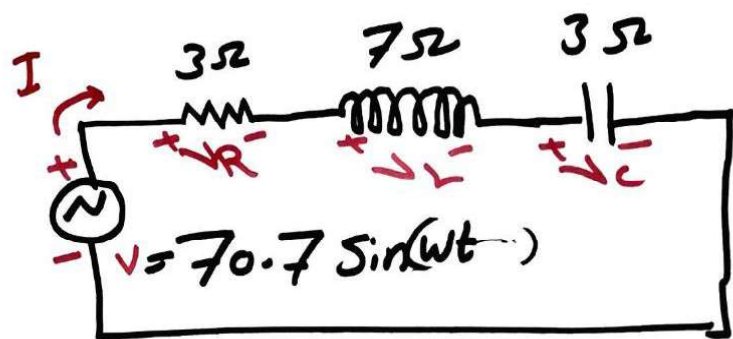Example. For the circuit shown. determine

- 1-  $\bar{Z}_T$ , and draw the impedance diagram
- 2-  $\bar{I}$ ,  $\bar{V}_R$ ,  $\bar{V}_L$ ,  $\bar{V}_C$  in the phasor domain and draw the phasor diagram.
- 3-  $i$ ,  $v_R$ ,  $v_L$ ,  $v_C$  in time domain
- 4- the power factor of the circuit
- 5- the active power, reactive power and apparent power.



$$\textcircled{1} Z_T = R + jX_L - jX_C$$

$$Z_T = 3 + j7 - j3 \quad (3\angle 0^\circ + 7\angle 90^\circ + 3\angle 270^\circ)$$

$$Z_T = 3 + j4 \quad \text{As } X_L - X_C = 7 - 3 = 4j$$

$$Z_T = \sqrt{3^2 + 4^2} \angle \tan^{-1} \frac{4}{3}$$



$$\underline{Z_T = 5 \angle 53.13}$$

$$Z = \sqrt{3^2 + (7-3)^2}$$

$$Z = 5$$


$$\phi = \tan^{-1} \frac{7-3}{4} = 53.13$$

$$Z_T = 5 \angle 53.13$$

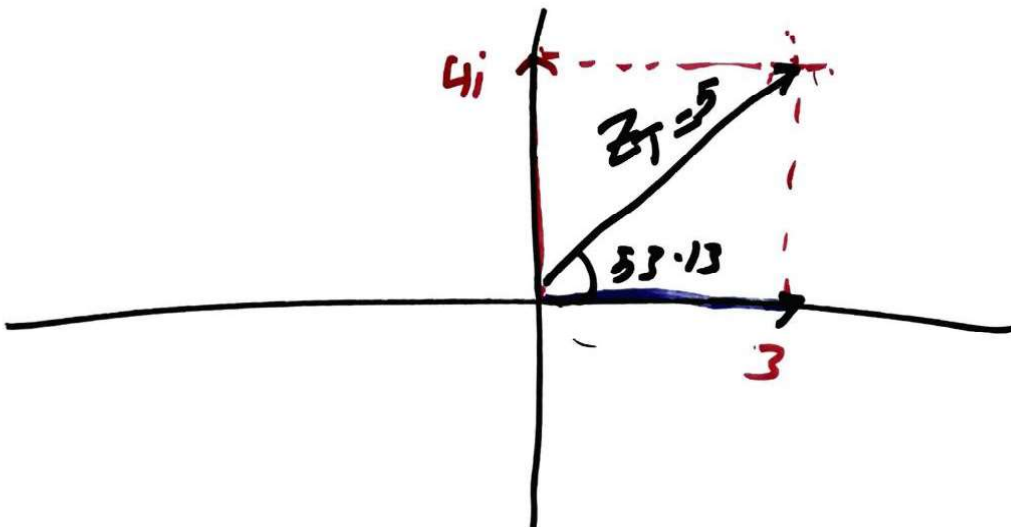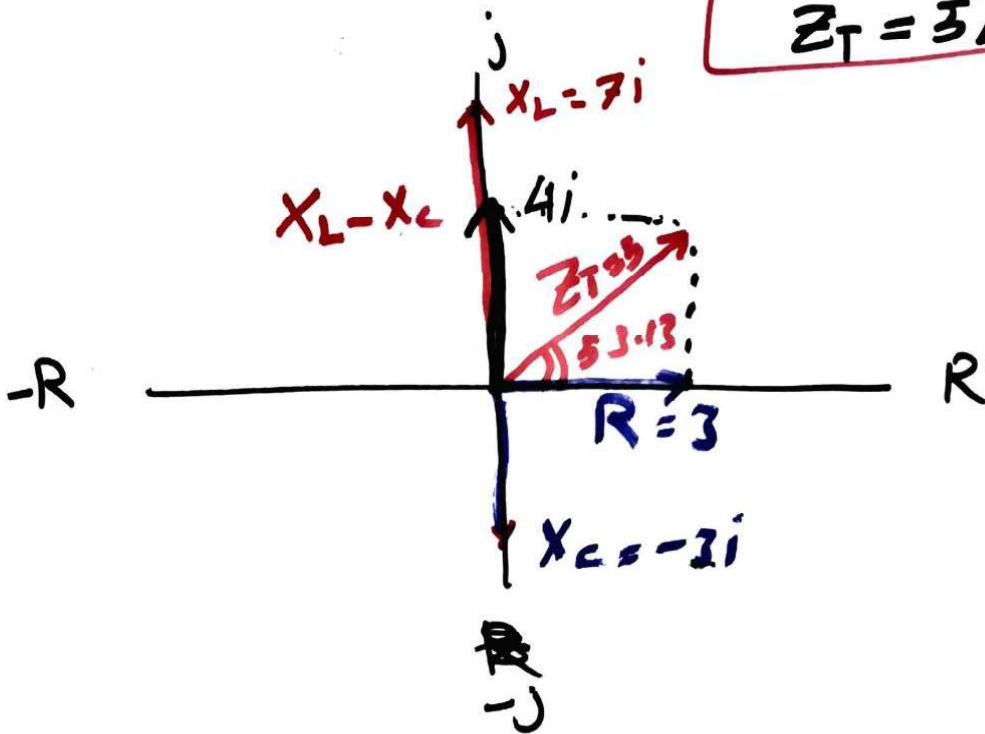

$$Z_T = 3 \angle 0^\circ + j7 \angle 90^\circ + 3 \angle -90^\circ$$

$$Z_T = 5 \angle +53.13^\circ$$

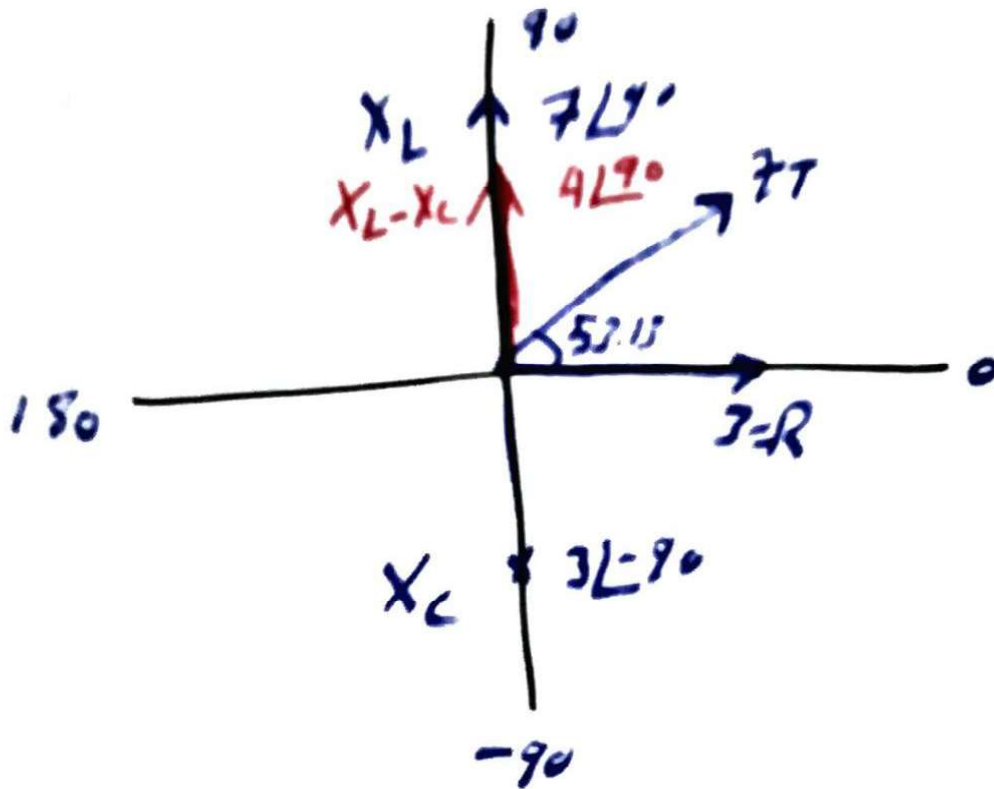

$$\textcircled{2} Z_T = \cancel{5 \angle 53.13} \quad 5 \angle 53.13$$

$$E \text{ rms} = \frac{70.7}{\sqrt{2}} = 50 \angle 0$$

$$I = \frac{V}{Z} = \frac{50 \angle 0}{5 \angle 53.13} = 10 \angle -53.13$$

$$V_R = I R = 10 \angle -53.13 \times 3 \angle 0$$


$$V_R = 30 \angle -53.13$$

$$V_L = I X_L = 10 \angle -53.13 \times 7 \angle 90$$

$$V_L = 70 \angle 36.87$$

$$V_C = I X_C = 10 \angle -53.13 \times 3 \angle -90$$

$$V_C = 30 \angle -143.13$$

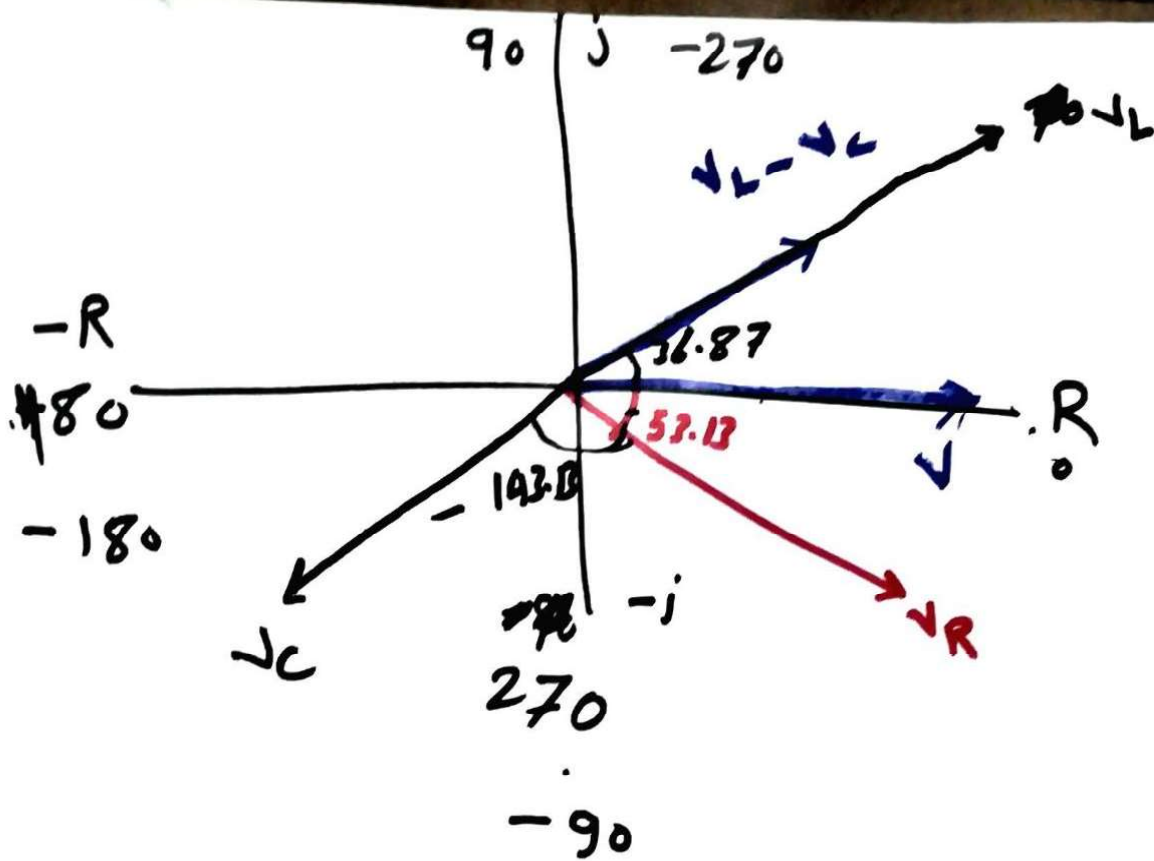

$$\textcircled{3} \quad I = 10 \angle -53.13$$

$$i = 10 \sqrt{2} \sin(\omega t - 53.13)$$

$$\textcircled{i} = 14.14 \sin(\omega t - 53.13)$$

$$V_R = 30 \angle -53.13$$

$$v_R = 30 \sqrt{2} \sin(\omega t - 53.13)$$

$$v_R = 42.42 \sin(\omega t - 53.13)$$

$$V_L = 70 \angle 36.87$$

$$V_L = 70\sqrt{2} \sin(\omega t + 36.87)$$

$$V_L = 98.98 \sin(\omega t + 36.87)$$

$$V_C = 30 \angle -143.13$$

$$V_C = 30\sqrt{2} \sin(\omega t - 143.13)$$

$$V_C = 42.42 \sin(\omega t - 143.13)$$

$$\textcircled{4} \quad P_F = \cos \phi = \cos 53.13 \\ = 0.6 \text{ lagging}$$

#### ④ active power

$$P = I^2 R$$

$$I = 10 \angle -53.13$$

$$R = 3 \angle 0$$

$$P = \sqrt{I} \cos \phi$$
$$= 50 \times 10 \cos 53.13 = 300$$

$$P = 100 \times 3 = 300 \text{ W}$$


#### Reactive Power

$$Q = I^2 (X_L - X_C) = 10^2 \times 4 = 400 \text{ VAR}$$

$$Q = I \sqrt{L} \sin \phi = 50 \times 10 \sin(53.13) = 400$$

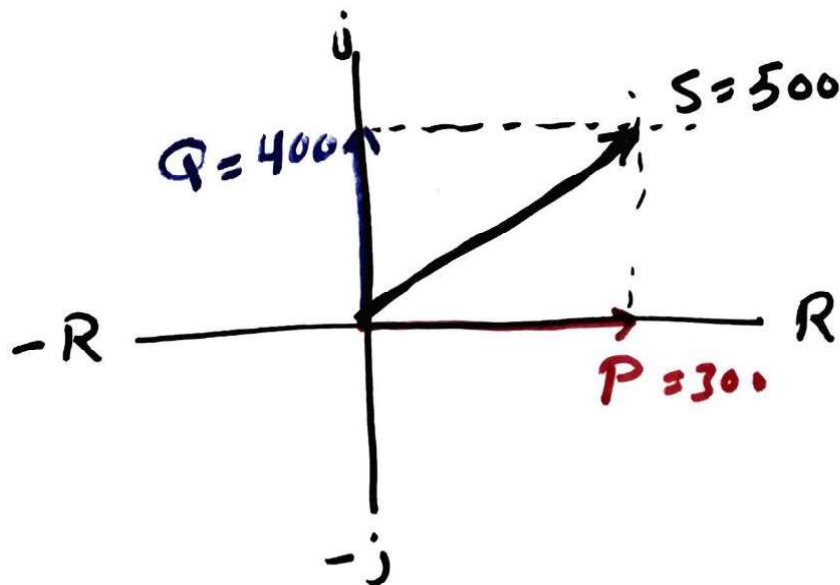
#### apparent power =

$$S = I V = 10 \times 50 = 500 \text{ VA}$$





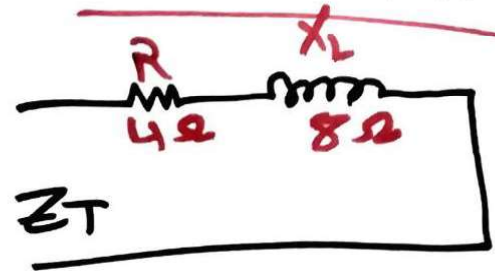
Example ∴ Draw the impedance diagram for the circuit shown and find the total total impedance.



Solution


$$\bar{Z}_T = 4 + j8 = 4\angle 0^\circ + 8\angle 90^\circ$$
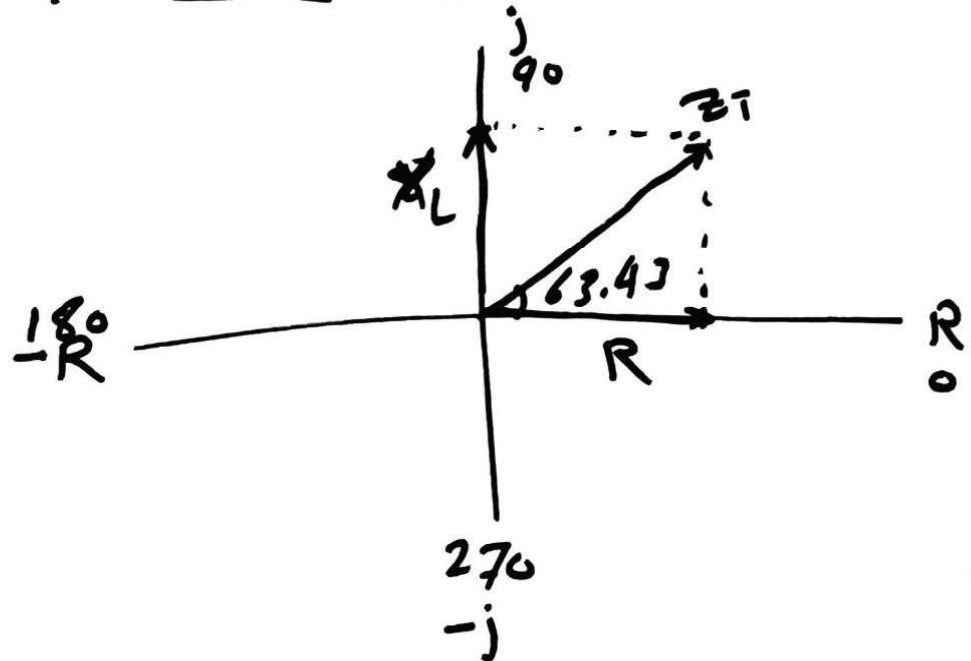
$$\bar{Z}_T = 8.944\angle 63.43^\circ \Omega$$



Example :- Determine the input impedance to the series network shown.

Solution

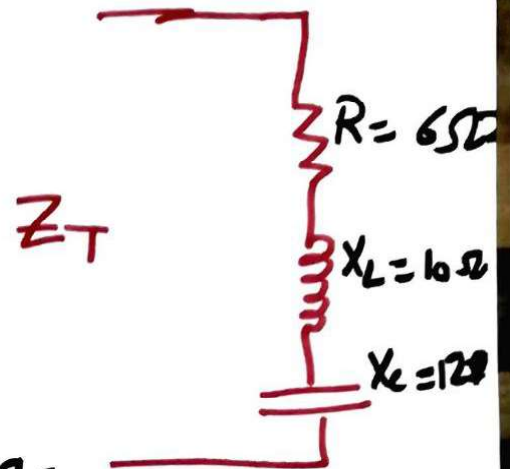

$$\begin{aligned} Z_T &= 6 + j10 - j12 \\ &= 6\angle 0^\circ + 10\angle 90^\circ + 12\angle -90^\circ \\ &= 6 + j(10 - 12) \end{aligned}$$

$$Z_T = 6 - j2$$

$$Z_T = 6.325 \angle -18.43^\circ$$

P.F.  $\begin{cases} \text{lagging} \\ \text{leading} \end{cases} \quad ??$

$$P.F. = \cos \phi = \frac{R}{Z}$$

Example: A 60 Hz sinusoidal voltage  $v = 141 \sin \omega t$  a series R-L circuit. The ~~voltage value~~ value of the resistance and the inductance are 3 and 0.0106 H respectively.

- Compute the RMS value of the current in the circuit and its phase angle with respect to the voltage.
- Write the expression for the instantaneous current in the circuit.
- Find the average power ~~and~~.
- Calculate the P.F of circuit.


Solution :-

$$f = 60 \text{ Hz}$$

$$v = 141 \sin \omega t$$

$$V = 100 \angle 0$$

$$V = \frac{141}{\sqrt{2}} = 100$$

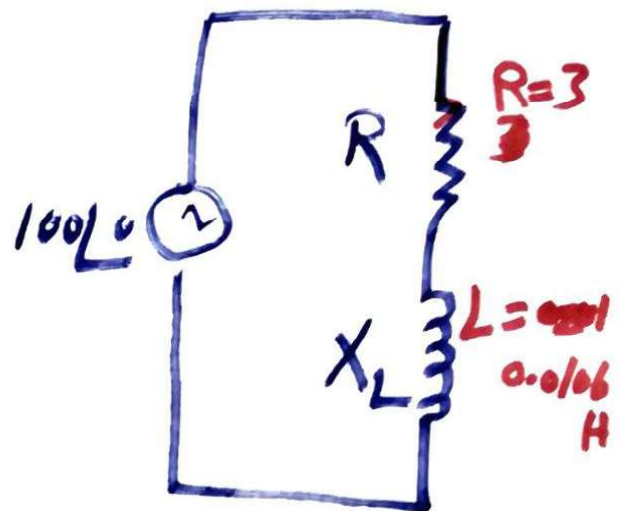

$$\textcircled{a} \quad I = ?$$

$$R = 3$$

$$L = 0.0106 \text{ H}$$

$$Z_T = R + jX_L$$

$$X_L = 2\pi fL = 2\pi * 60 * 0.0106 = 4 \Omega$$

$$Z_T = 3 + j4$$

$$Z = 5 \angle 53.13$$

$$I = \frac{V}{Z} = \frac{100 \angle 0}{5 \angle 53.13} = 20 \angle -53.13$$

I lagging voltage

$$\textcircled{b} \quad i = 20 * \sqrt{2} \sin(\omega t + (-53.13))$$

$$i = 28.28 \sin(\omega t - 53.13)$$

$\textcircled{c}$  average power = Active Power

$$P = I^2 R = 20^2 * 3 = 1200 \text{ W}$$

$$\textcircled{d} \quad \text{P.F} = \cos \phi = \cos(53.13) = 0.6 \text{ lagging}$$

Example: A two elements series circuit is connected across an A.C circuit having source  $e = \sqrt{2}(200) \sin(\omega t + 20)$ . The current circuit is found to be  $i = \sqrt{2}(10) \cos(341t - 25)$ . Determine the parameters of the circuit.

Solution

\* Two ~~elements~~ elements

$$e = \sqrt{2}(200) \sin(\omega t + 20)$$

$$i = \sqrt{2}(10) \cos(341t - 25)$$

$$E = \frac{(200)\sqrt{2}}{\sqrt{2}} = 200$$

$$\phi = 20$$

$$E = 200 \angle 20$$

$$i = \sqrt{2}(10) \cos(341t - 25) = \sqrt{2}10 \sin(\overset{\omega t}{\underbrace{341t - 25 + 90}_{+65}})$$

$$I = \frac{10(\sqrt{2})}{\sqrt{2}} = 10$$

$$\phi = +65$$

$$I = 10 \angle 65$$

$$Z_T = \frac{V}{I} = \frac{200 \angle 20}{10 \angle 65} = 20 \angle -45$$

$$Z_T = 20 \angle -45 = \underline{14.14 \overset{R}{-} j14.14 \overset{X_C}{}}$$

$$R = 14.14$$

$$X_C = 14.14$$

R & C

$$X_C = \frac{1}{2\pi fC}$$

$$14.14 = \frac{1}{\omega C}$$

$$14.14 = \frac{1}{314 * C}$$

$$C = \frac{1}{314 * 14.14} = \cancel{2.07} 2.25 * 10^{-4} \text{ F}$$

$$R = 14.14 \Omega$$

$$C = 2.25 * 10^{-4} \text{ F}$$

$$\omega = \frac{314}{314} = 2\pi$$