



University: *Tikrit*
College: *Petroleum Processes Engineering*
Department: *Petroleum Systems Control Engineering*
Subject: *Electrical Engineering Fundamentals*
Assistant Lecturer: *Waladdin Mezher Shaher*
2023-2024



Electrical Engineering Fundamentals

First class

AC & DC

University: Tikrit
College: Petroleum Processes Engineering
Department: Petroleum Systems Control Engineering
Assistant Lecturer: Waladdin Mezher Shaher
2024-2025

Electrical Engineering Fundamentals

EEI

① Basic Concepts & Basic Laws

1.1 Basic Concepts

1.1.1 System of Units

The basic SI units

Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd

The SI prefixes

Multiplier	Prefix	Symbol
10^{18}	exa	E
10^{15}	peta	P
10^{12}	tera	T
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10	deca	da
10^{-1}	deci	d
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f
10^{-18}	atto	a

Examples

$$10 \text{ MHz} \Rightarrow 10 \times 10^6 \text{ Hz}$$

$$2 \text{ mA} = 2 \times 10^{-3} = 0.002 \text{ A}$$

$$5 \mu\text{s} = 5 \times 10^{-6} \text{ s}$$

1.1.2 Charge and Current


EE1

The electric charge is an electrical property of the atomic particles of which matter consists, measured in coulombs (C). The charge of an electron is $(-1.602 \times 10^{-19} \text{ C})$.


Electric Current

is the rate of change of charge, measured in amperes (A). The current (I) is defined mathematically as:

$$i = \frac{dq}{dt}$$

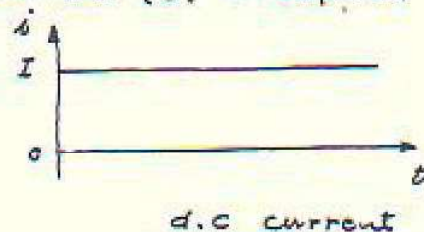

$$\therefore q = \int_{t_1}^{t_2} i dt$$

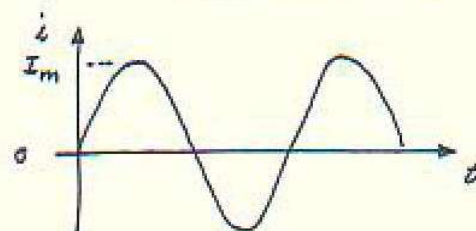

- * A direct current (dc) is current that remains constant with time. The symbol (I) is usually used to represent such a constant current.
- * An alternating current (ac) is a current that is varying sinusoidally with time. A time varying current is represented by the symbol (i).

Example

Determine the total charge entering a terminal between $t = 1 \text{ s}$ and $t = 2 \text{ s}$, if the current passing the terminal is $i = (3t^2 - t) \text{ A}$.


Solution

$$\begin{aligned} q &= \int_{t_1}^{t_2} i dt \\ &= \int_1^2 (3t^2 - t) dt = \left(t^3 - \frac{t^2}{2} \right) \Big|_1^2 \\ &= (8 - 2) - \left(1 - \frac{1}{2} \right) = \underline{\underline{5.5 \text{ C}}} \end{aligned}$$

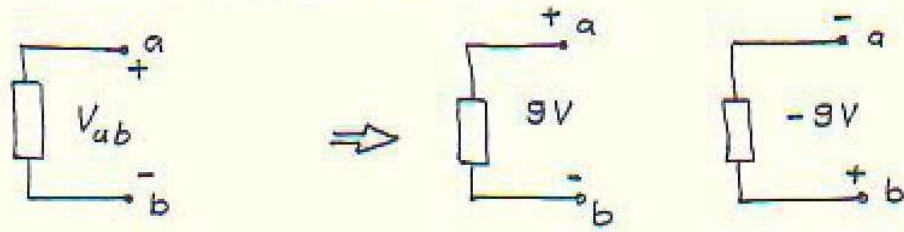1.1.3 Voltage

EE1

 : The voltage (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).



Polarity of Voltage
 V_{ab}

* For the voltage $V_{ab} \Rightarrow$ This means that the potential of point a is higher than that of point b

$$V_{ab} = V_a - V_b$$

1.1.4 Power and Energy

* Power: is the time rate of expending or absorbing energy, measured in watts (W)

$$\Rightarrow p = \frac{dw}{dt}$$

where p is the power in watts (W), w is the energy in joules (J), and t is the time in seconds (s)

$$\text{We have; } p = \frac{dw}{dt} \Rightarrow p = \frac{dw}{dt} \cdot \frac{dq}{dq}$$

$$\Rightarrow p = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i$$

$$\therefore p = vi$$

* The energy absorbed or supplied by an element

from time t_0 to time t is :

EEI

$$w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$$

Energy is the capacity to do work, measured in joules (J)

* The electric power utility companies measure energy in watt-hour (Wh), where

$$1 \text{ Wh} = 3,600 \text{ J}$$

Example

: How much energy does a 100 W electric bulb consume in 2 hours?

Solution

$$w = pt = 100 \times 2 = 200 \text{ Wh}$$

or


$$\begin{aligned} w &= pt = (100 \text{ W})(2 \times 60 \times 60) \\ &= 720000 \text{ J} \\ &= 720 \text{ kJ} \end{aligned}$$

which is the same result (if you convert from joules to watts or vice-versa).

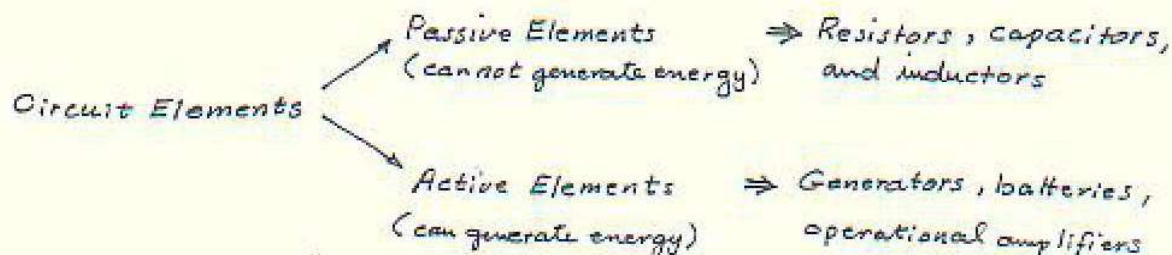1.1.5 Circuit Elements

: An electric circuit is an interconnection of electrical elements.

* Circuit analysis is the process of determining voltages across (or the currents through) the elements of the circuit.



- * The most important active elements are voltage or current EE1 sources that generally deliver power to the circuit connected to them.

Voltage (or current) sources $\left\{ \begin{array}{l} \text{Independent sources} \\ \text{Dependent sources} \end{array} \right.$

- * An ideal independent source is an active element that provides a specified voltage or current that is completely independent of other circuit variables.
- * Dependent sources (or controlled sources) are active elements in which the source quantity is controlled by another voltage or current. (It will be discussed later).

1.2 Basic Laws:


1.2.1 Ohm's Law

(1826): Ohm's Law states that the voltage V across a resistor is directly proportional to the current I flowing through the resistor.

$$V \propto I$$

$$\Rightarrow V = IR$$

$$\Rightarrow V = IR$$

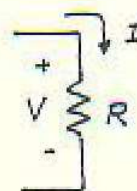


where R is the resistance. The resistance R denotes the ability of an element to resist the flow of electric current, it is measured in ohms (Ω).

For any material, the resistance R depends on its physical dimensions as follows:

$$R = \rho \frac{l}{A}$$

where ρ is the resistivity of the material.

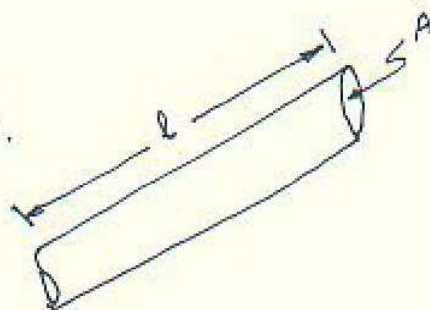- \Rightarrow Good conductors have low resistivities (such as copper, aluminum, etc..)
- \Rightarrow Insulators have high resistivities (such as mica, paper, etc...)



المعلومات


Resistivities of Common Materials

EE1


Material	Resistivity ($\Omega \cdot m$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	"
Aluminum	2.80×10^{-8}	"
Gold	2.45×10^{-8}	"
Carbon	4.00×10^{-5}	Semiconductor
Germanium	47.0×10^{-2}	"
Silicon	6.40×10^{-2}	"
Paper	10^{10}	Insulator
Mica	5×10^{11}	"
Glass	10^{12}	"
Teflon	3×10^{12}	"

* The resistance of a short circuit element is approaching zero

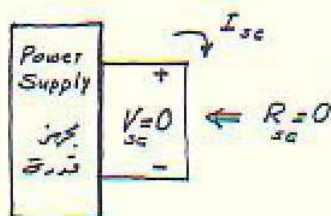* The resistance of an open circuit is approaching infinity.



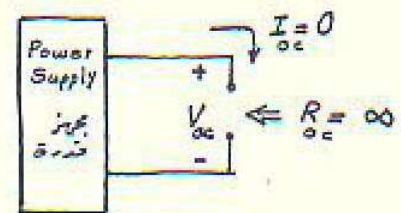Short circuit with $R_{sc} = 0$
 $V_{sc} = 0$



Open circuit with $R_{oc} = \infty$
 $I_{oc} = 0$

* Conductance (G)

A useful quantity in circuit analysis is the reciprocal of resistance (R), is called the conductance (G);

$$G = \frac{1}{R} = \frac{i}{v}$$

The conductance can be explained as the ability of an element to conduct electric current, it is measured in mhos (\mathcal{M}) or in siemens (S).

$$\therefore i = Gv$$

and:


$$p = vi = i^2 R = \frac{v^2}{R} \quad \text{watts (W)}$$

OR

$$p = vi = v^2 G = \frac{i^2}{G}$$

Example

 : In the circuit shown, calculate the current I , the conductance G , and the power P

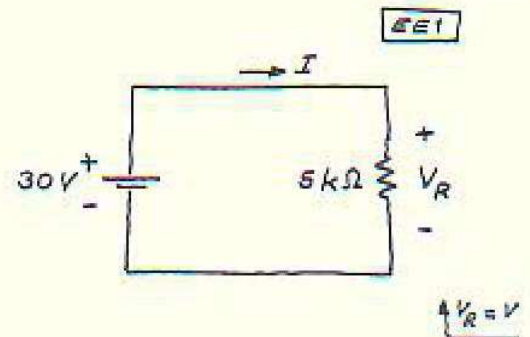Solution

- the current $I = \frac{V_R}{R} = \frac{30}{5 \times 10^3} = 6 \times 10^{-3} = \underline{6 \text{ mA}}$

- the conductance $G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \times 10^{-3} = 0.2 \text{ mS}$

- the power $P = V_R I = 30 (6 \times 10^{-3}) = \underline{180 \text{ mW}}$

or

$$P = I^2 R = (6 \times 10^{-3})^2 (5 \times 10^3) = \underline{180 \text{ mW}}$$

or

$$P = V_R^2 G = (30)^2 (0.2 \times 10^{-3}) = \underline{180 \text{ mW}}$$

1.2.2 Nodes, branches and loops


* A branch represents a single element in the electric circuit, such as a voltage source or a resistor etc...

* A node represents the point of connection between two or more branches.

* A loop is any closed path in a circuit.

Example

 : For the circuit shown, determine the number of branches, nodes and the independent loops.

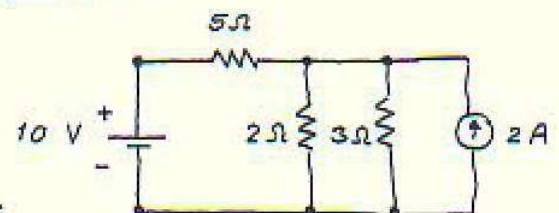Solution

 Since there are 5 elements


$$\Rightarrow \text{Number of branches} = \underline{5} \quad 10\text{V}, 5\Omega, 2\Omega, 3\Omega, \text{ and } 2\text{A}$$

$$\text{Number of nodes} = \underline{3} \quad (\text{as shown in the figure}).$$

3 nodes

تمرینہ حل کیا جا

⇒ There are 3 nodes :
a, b and c

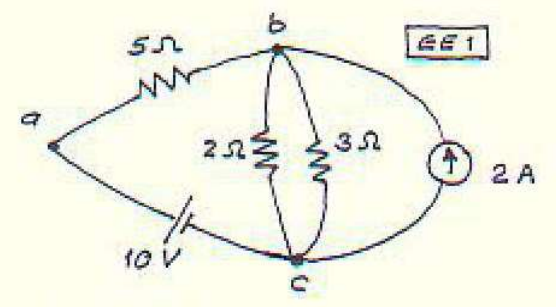


* The number of the independent loops = 3

⇒ loop 1 or loop abc :
contains (10V, 5Ω, 2Ω)

⇒ loop 2 or loop bcb :
contains (2Ω, 3Ω)

⇒ loop 3 or loop bcb :
contains (3Ω, 2A)

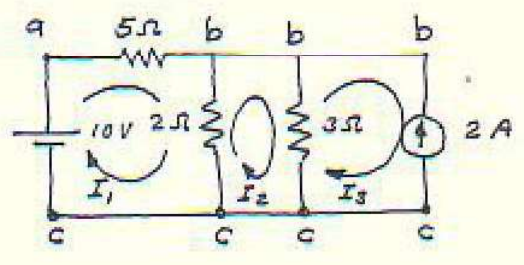

Notes

— : There are more than 3 (dependent) loops in this example, we had only calculated the INDEPENDENT loops which are only 3.

IN GENERAL; Any circuit with b branches, n nodes and l independent loops, the following fundamental theorem of network topology:

$$b = l + n - 1$$

* Two or more elements are in SERIES if they are cascaded sequentially and consequently carry the SAME current.

* Two or more elements are in PARALLEL if they are connected to the same two nodes and have consequently the same VOLTAGE across them.

1.2.3 Kirchoff's Laws (1847)

* Kirchoff's current law (KCL); states that the algebraic sum of all current entering a node is zero or: The sum of currents entering a node is equal to the sum of currents leaving that node.

$$\sum_{n=1}^N I_n = 0$$


or

$$\sum_{m=1}^M I_{mi} = \sum_{n=1}^N I_{no}$$

where I_{mi} are the currents entering the node and I_{no} are the currents leaving the node.

Example

For the network shown, calculate the total current I_T

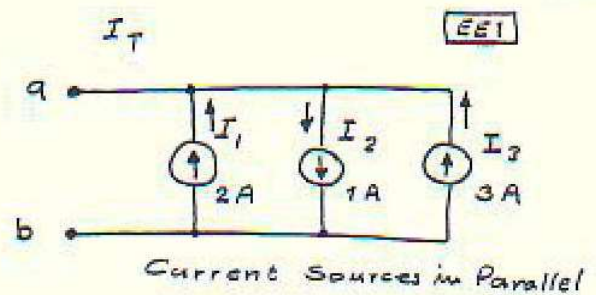
Solution

According to KCL;

$$I_T = I_1 - I_2 + I_3$$

$$= 2 - 1 + 3 = \underline{\underline{5A}}$$

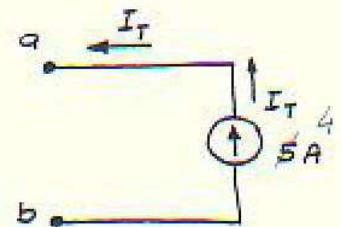∴ The equivalent circuit for the network can be as shown ⇒



* Kirchoff's Voltage Law (KVL); states that the algebraic sum of all voltages around a closed path (or loop) is zero.
تأثير كيرشوف للجهد


∴ Mathematically KVL states that:

$$\sum_{m=1}^M V_m = 0$$

where M is the number of voltages in the loop (or the number of branches in the loop), and V_m is the m th voltage.

Example

For the circuit shown, find the voltages V_1 and V_2

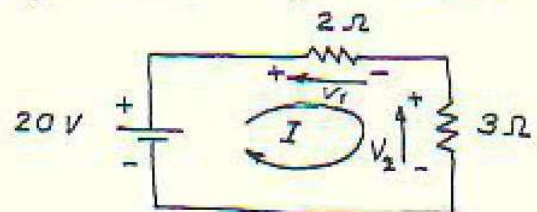Solution

$$V_1 = 2I$$

$$V_2 = 3I$$

From KVL:

$$\sum V = 0 \Rightarrow 20 - V_1 - V_2 = 0 \Rightarrow 20 = 3I + 2I$$

$$\Rightarrow 5I = 20 \Rightarrow I = 4A$$


$$\therefore V_1 = 2I = \underline{\underline{8V}} \quad \text{and} \quad V_2 = 3I = \underline{\underline{12V}}$$

Tutorial Sheet No 1

Basic Concepts & Basic Laws

T.S.I

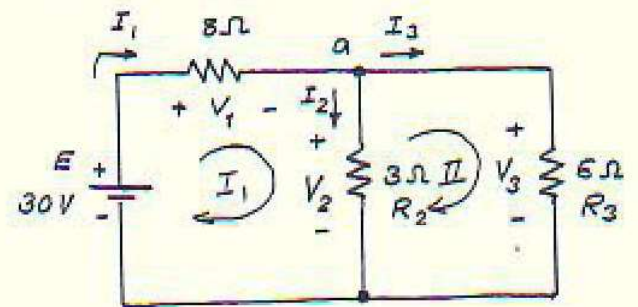Example Using Kirchoff's laws. find the currents and voltages in the circuit shown.



Solution

ملاحظة: المطلوب في المثال إيجاد كل من I1, I2, I3, V1, V2 و V3 باستخدام قوانين كيرشوف

* Using Ohm's law:

V1 = I1R1 = 8I1
V2 = I2R2 = 3I2
V3 = I3R3 = 6I3

* Applying KCL at node a:

I1 = I2 + I3 => I1 - I2 - I3 = 0 Eq(1)

* Applying KVL to loop 1:

E - V1 - V2 = 0 => 30 - V1 - V2 = 0
=> 30 - 8I1 - 3I2 = 0
I1 = (30 - 3I2) / 8 Eq(2)

* Applying KVL to loop 2:

V2 - V3 = 0 => V2 = V3
6I3 = 3I2
I3 = I2 / 2 Eq(3)

=> From Eq(1), Eq(2) & Eq(3)

(30 - 3I2) / 8 - I2 - I2 / 2 = 0 => I2 = 2 A

and I1 = (30 - 3(2)) / 8 = 3 A

I3 = I2 / 2 = 1 A

$$\Rightarrow \therefore V_1 = 8I_1 \Rightarrow \therefore V_1 = 8(3) = 24 \text{ V} \quad \boxed{\text{T51}}$$

$$\text{Similarly } V_2 = 3I_2 = 3(2) = 6 \text{ V}$$

$$\text{and } V_3 = 6I_3 = 6(1) = 6 \text{ V}$$

لنتأكد من صحة الحل :

$$I_1 = I_2 + I_3$$

$$3 = 2 + 1 \Rightarrow \underline{\underline{3 = 3}}$$

كذلك فان تطبيع تارة كرتونة للثولسية على الماء المظلمه يتم النتيجه ما يأتي :

$$E = V_1 + V_2$$


$$\therefore 30 = 24 + 6$$

$$\therefore 30 = 30$$

∴ الحل صحيح

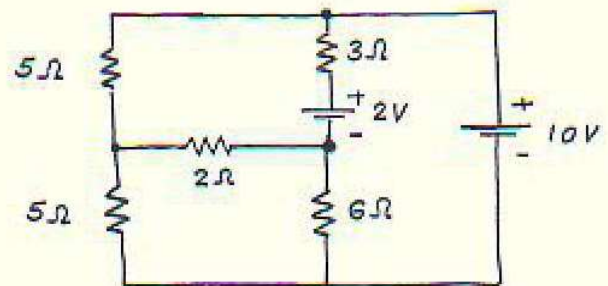Example

Determine the number of branches, nodes and independent loops in the circuit shown.



Solution

* There are 7 element \Rightarrow no. of branches = 7
 $\Rightarrow \underline{\underline{b = 7}}$


a, b, c, d, e \Leftarrow * There are 5 nodes as shown in the figure :
 $\Rightarrow n = 5$

I, II, III \Leftarrow * There are 3 independent loops :
 $\Rightarrow l = 3$

$\therefore b = l + n - 1$ is satisfied

since $7 = 3 + 5 - 1$


$$\Rightarrow 7 = 7$$

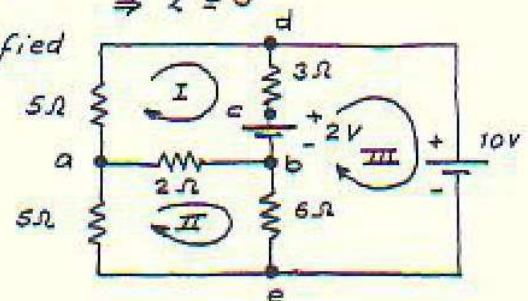

Practice Problem

T51

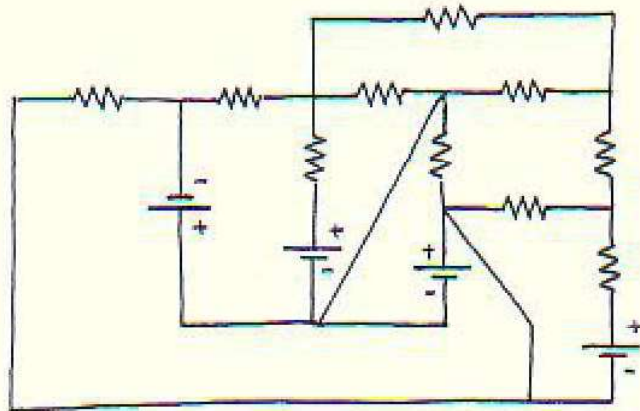Identify all nodes, branches and independent loops in the circuit shown in the figure.



Answer


no. of nodes = 8 $n = 8$
 no. of branches = 14 $b = 14$
 no. of independent loops = 7 $l = 7$

Check. Does this satisfy the fundamental theorem of network topology?

$$b = l + n - 1 = 7 + 8 - 1 = 14 \quad \underline{\text{YES}}$$

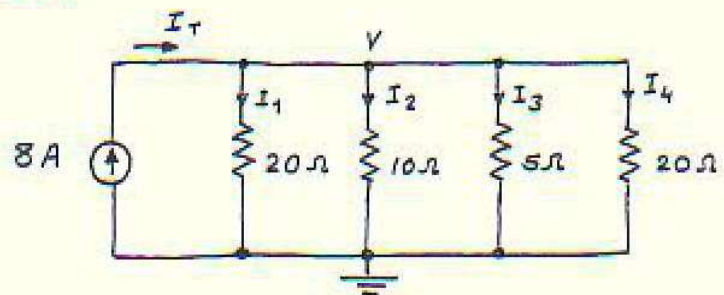Example

Determine all currents and voltages in the circuit of the figure shown.



Solution

KCL \Rightarrow
 $I_T = I_1 + I_2 + I_3 + I_4 \Rightarrow 8 = I_1 + I_2 + I_3 + I_4$

Ohm's law

$$\begin{aligned} V &= 20 I_1 & \Rightarrow I_1 &= V/20 \\ &= 10 I_2 & I_2 &= V/10 \\ &= 5 I_3 & I_3 &= V/5 \\ &= 20 I_4 & I_4 &= V/20 \end{aligned}$$

Substituting in the current equation;

$$\Rightarrow 8 = \frac{V}{20} + \frac{V}{10} + \frac{V}{5} + \frac{V}{20}$$

$$\therefore 160 = V + 2V + 4V + V$$

$$160 = 8V$$

$$\therefore \underline{V = 20 \text{ Volts}}$$

$$\therefore I_1 = \frac{V}{20} = \frac{20}{20} = 1 \text{ A}$$

$$I_2 = \frac{V}{10} = \frac{20}{10} = 2 \text{ A}$$

$$I_3 = \frac{V}{5} = \frac{20}{5} = 4 \text{ A}$$

$$I_4 = \frac{V}{20} = \frac{20}{20} = 1 \text{ A}$$

Check

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$8 = 1 + 2 + 4 + 1$$

$$8 = 8 \quad \checkmark$$


2. Circuit Transformations

2.1 Series Circuits

Two elements are in series if they have only one point in common that is not connected to other current carrying elements of the network.

For the series ckt. shown, using KVL we have:
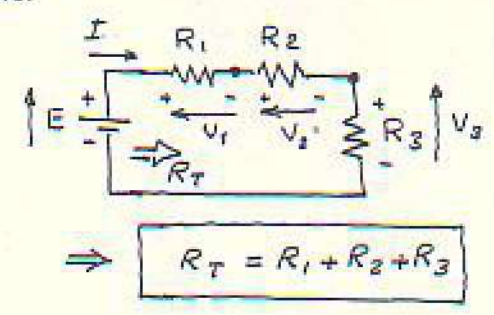
$$\begin{aligned}
 E &= V_1 + V_2 + V_3 \\
 &= IR_1 + IR_2 + IR_3 \\
 &= I(R_1 + R_2 + R_3) \\
 &= IR_T
 \end{aligned}$$




$$\therefore I = \frac{E}{R_T}$$

In general, for a series ckt. consisting N resistors, then the total resistance of such a ckt. R_T is given as

$$R_T = R_1 + R_2 + R_3 + \dots + R_N$$

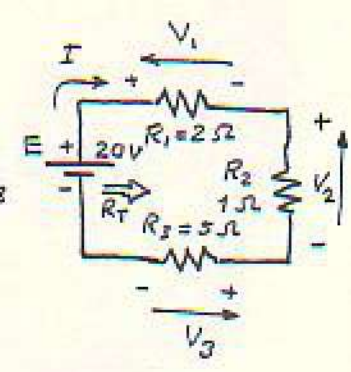Example

- For the ckt. shown;
- Find the total resistance
 - Calculate the current I
 - Determine the voltages V_1 , V_2 and V_3



Solution

- $$R_T = R_1 + R_2 + R_3 = 2 + 1 + 5 = 8 \Omega$$
- $$I = \frac{E}{R_T} = \frac{20}{8} = 2.5 \text{ A}$$
- $$\begin{aligned}
 V_1 &= IR_1 = (2.5)(2) = 5 \text{ V} \\
 V_2 &= IR_2 = (2.5)(1) = 2.5 \text{ V} \\
 V_3 &= IR_3 = (2.5)(5) = 12.5 \text{ V}
 \end{aligned}$$


ملاحظة

$$\begin{aligned}
 V_1 + V_2 + V_3 &= E \\
 5 + 2.5 + 12.5 &= 20 \text{ V} \\
 \therefore 20 \text{ V} &= 20 \text{ V}
 \end{aligned}$$

2.1.1 Voltage Sources in Series

The net voltage will be the algebraic sum of all sources that are connected in series.

Example

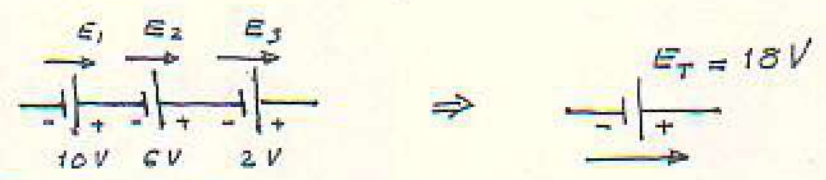

$$\begin{aligned}
 E_T &= E_1 + E_2 + E_3 \\
 &= 10 + 6 + 2 = 18 \text{ V}
 \end{aligned}$$

ملاحظة: عند دمج مصادر الجهد المتساوية في التوالي نلاحظ ذلك مخالف لقانون كيرشوف للتساوي.

2.1.2 Voltage Divider Rule

EE2


Consider the series ckt. shown.

we have:

$$R_T = R_1 + R_2$$

and
$$I = \frac{E}{R_T}$$
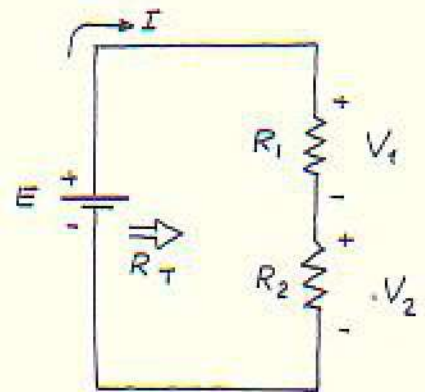
$$V_1 = IR_1 = \left(\frac{E}{R_T}\right) \cdot R_1 = \frac{E \cdot R_1}{R_T}$$



Similarly;

$$V_2 = IR_2 = \left(\frac{E}{R_T}\right) \cdot R_2 = \frac{E \cdot R_2}{R_T}$$

Hence, we can write:

$$V_x = \frac{E \cdot R_x}{R_T}$$
 ← Voltage divider rule

This means that "the voltage divider rule" can be understood to state that:

The voltage across a resistor in a series circuit is equal to the value of that resistor times the the total applied voltage across the series elements divided by the total resistance of the series elements.


Example

Determine the voltages V_1 , V_3 , and V' for the ckt. shown.

Solution

Using the voltage divider rule:
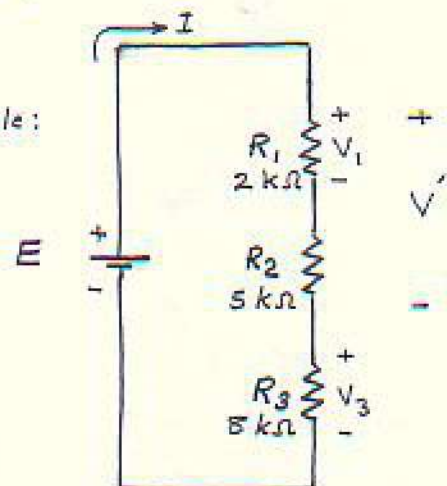
$$V_1 = \frac{E \cdot R_1}{R_T} = \frac{(45) \cdot (2 \times 10^3)}{(2+5+8) \times 10^3} = 6V$$
$$V_3 = \frac{E \cdot R_3}{R_T} = \frac{(45)(8 \times 10^3)}{(2+5+8) \times 10^3} = 24V$$



$$V' = \frac{E \cdot R'}{R_T}$$

$$= \frac{(45) \cdot (7 \times 10^3)}{(2 + 5 + 8) \times 10^3}$$

$$= \underline{21 V}$$

$$R' = (2 + 5) \times 10^3 \Omega$$

$$= 7 \times 10^3 \Omega$$

EE2

دو طرفه انا :

$$E = V_3 + V'$$

$$45 V = 24 V + 21 V$$

$$45 V = 45 V$$

دو طرفه انا نوده الجهد بان طرفيا اي عنصر به عناصر دائرة الترانزستور تتواجد مع مقاومة ذلك العنصر ، ابي ان المقاومة الكبيرة يقابلها نوده جهده كبير والمقاومة الصغيرة يقابلها نوده جهده صغير ، وفي جميع الاحوال يجب ان يكون مجموع نودوه الجهد مساويا الى فولتية المصدر .

NOTATION

ground potential



It is common, for safety purposes and as a reference to ground electrical and electronic systems. The symbol for the ground connection is :



with its defined potential level (zero volts). As a consequence, the ckt. might need to be redrawn in the ordinary form so as to be analyzed.

Example


For the ckt. shown, with ground potentials connected for the source and to elements; this ckt. can be redrawn to make it easy analyzing it.

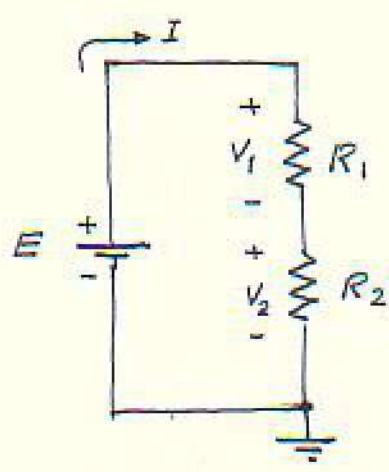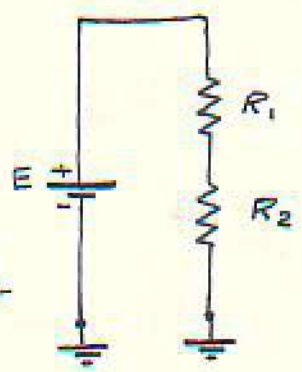

EE2

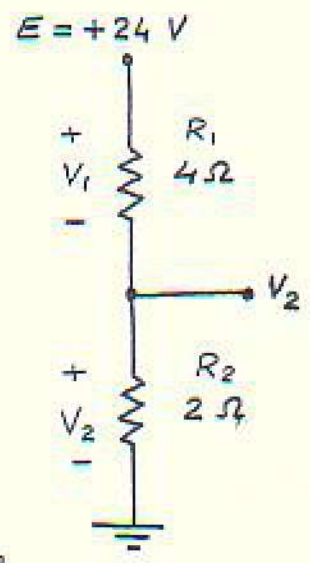Example

: Using the voltage divider rule, determine the voltages V_1 and V_2 for the ckt shown:




Solution

: Redrawing the ckt. with the standard battery symbol, then the ckt. will be as shown below:

$$\therefore V_1 = \frac{R_1 E}{R_T} = \frac{(4) \cdot (24)}{4 + 2} = 16\text{ V}$$


and
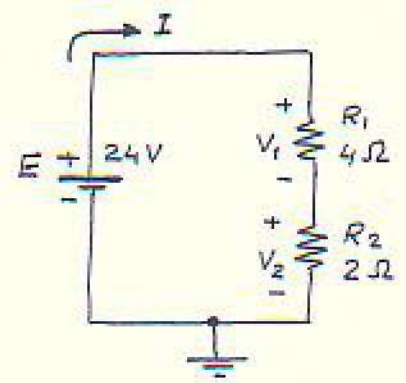
$$V_2 = \frac{R_2 E}{R_T} = \frac{(2) \cdot (24)}{4 + 2} = 8\text{ V}$$



Example

: For the ckt. shown, determine V_{ab} , V_{cb} and V_b .

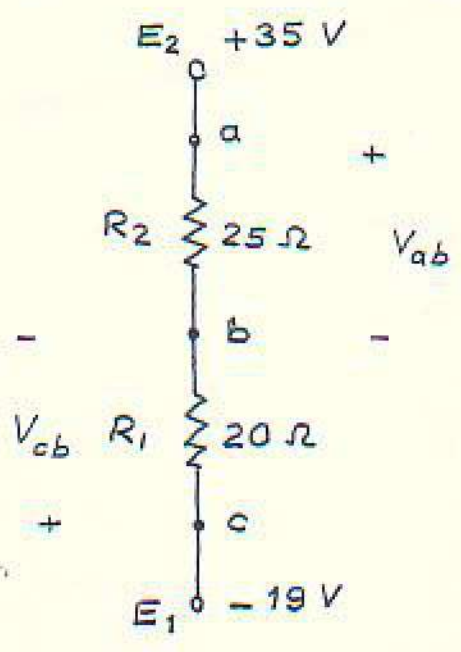

EE2

Solution


The cct. is redrawn as shown;

$$\therefore I = \frac{E_1 + E_2}{R_T} = \frac{19 + 35}{20 + 25} = 1.2 \text{ A}$$

$$V_{ab} = IR_2 = (1.2)(25) = 30 \text{ V}$$

$$\text{and } V_{cb} = -V_{bc} = -IR_1 = -(1.2)(20) = -24 \text{ V}$$

$$V_c = -E_1 = -19 \text{ V}$$

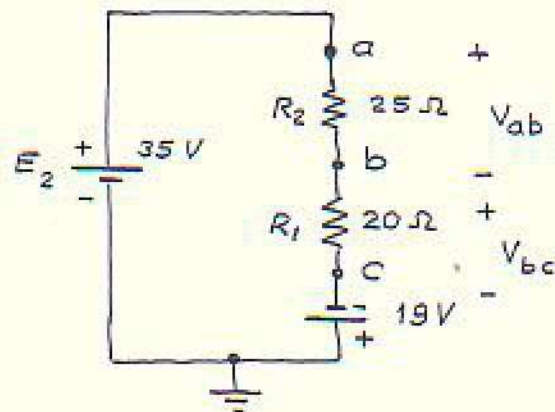

ملاحظة ١ / يمكنه الحل باستخدام voltage divider rule مع ملاحظة ان $V_{cb} = -V_{bc}$

ملاحظة ٢ / ان V_{ab} تعني منه جهد النقطة \$a\$ عن النقطة \$b\$ فاذا كانت V_{ab} موجبة فان معناها ان V_a اكبر من V_b

ملاحظة ٣ / ان V_a تعني جهد النقطة \$a\$ بالنسبة الى الارض.

2.2 Parallel Circuits

EE2

: Two branches or elements or networks are in parallel if they have two points in common.

For the parallel cct. shown ; using KCL, we have:

$$I = I_1 + I_2 + I_3$$


$$= \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

since $V_1 = V_2 = V_3 = E = V$

$$\therefore I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\therefore \frac{V}{R_T} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$
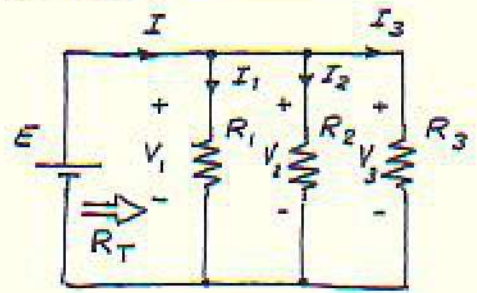
$$\therefore \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$E = V_1 = V_2 = V_3$$

$$I = \frac{E}{R_T} = \frac{V}{R_T}$$

In general, for N resistors connected in parallel, then:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

Notation

Conductance G


For parallel networks, it is common to use the idea of conductance in the cct. analysis. The conductance (G) is defined as:

$$G = \frac{1}{R} \quad \text{Siemens (S)}$$

So, we can write the total conductance G_T for the parallel cct shown, as:

$$G_T = G_1 + G_2 + G_3$$

$$\Rightarrow R_T = \frac{1}{G_T}$$

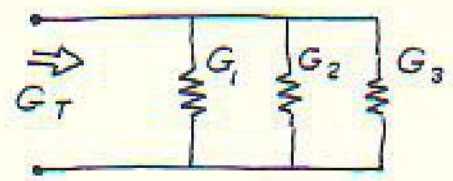

NOTE that, the total resistance R_T of parallel resistors is always less than the value of the smallest resistor.

Special Cases

EE2

The general relation for the total resistance of parallel resistors is:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

* Case 1

For equal resistors in parallel, ie, when

$$R_1 = R_2 = R_3 \dots R_N = R$$

then;
$$\frac{1}{R_T} = \underbrace{\frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R}}_N$$

$$\therefore \frac{1}{R_T} = N \left(\frac{1}{R} \right) \Rightarrow \boxed{R_T = \frac{R}{N}}$$

* Case 2

For two resistors in parallel, then R_T is given as:

$$\boxed{R_T = \frac{R_1 R_2}{R_1 + R_2}}$$

This means that, the total resistance of the two parallel resistors is the product of the two divided by their sum.


* Case 3

For three resistors in parallel, then R_T is given as:

$$\boxed{R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}}$$

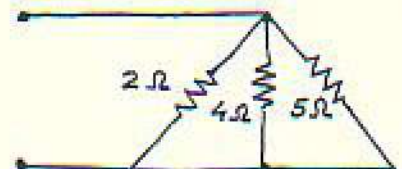Example


Determine the total resistance for the network shown:



Solution

Redraw the ckt. to be as shown;
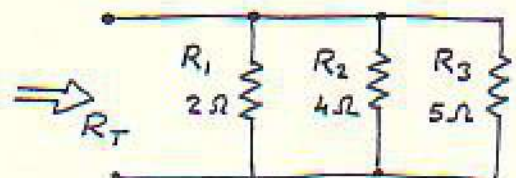
$$\begin{aligned} \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{2} + \frac{1}{4} + \frac{1}{5} \\ &= 0.5 + 0.25 + 0.2 \\ &= 0.95 \end{aligned}$$




$$\Rightarrow \therefore R_T = \frac{1}{0.95} = \underline{1.053 \Omega}$$

Example

For the parallel network shown;

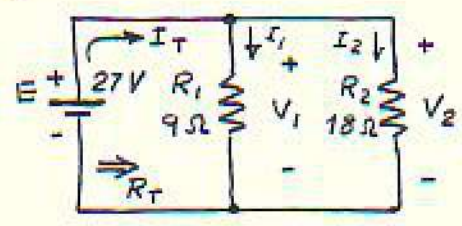- a. Calculate R_T
- b. Determine I_T
- c. Calculate I_1 and I_2
- d. Determine the power to each resistive load.
- e. Determine the power delivered by the source and compare it with the total power dissipated by the resistive elements.



Solution

a. $R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(9)(18)}{9 + 18} = \frac{162}{27} = \underline{6 \Omega}$

b. $I_T = \frac{E}{R_T} = \frac{27}{6} = \underline{4.5 A}$

c. $I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{27}{9} = \underline{3 A}$

and

$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{27}{18} = \underline{1.5 A}$

ملاحظة: $I_T = I_1 + I_2$

d. $P_1 = I_1 V_1 = E I_1 = (27)(3) = \underline{81 W}$

$P_2 = I_2 V_2 = E I_2 = (27)(1.5) = \underline{40.5 W}$

e. $P_s = E I_T = (27)(4.5) = 121.5 W$

$P_s = P_1 + P_2 = 81 + 40.5 = 121.5 W$

* لاحظ ان مجموع القدرة المستهلكة في المقاومتين R_1 و R_2 يساوي القدرة التي يخرجها المصدر E


2.2.1 Current Divider Rule

Consider the parallel ckt. shown;

We have; $I = \frac{V}{R_T} \Rightarrow V = I R_T$

and $R_T = \frac{R_1 R_2}{R_1 + R_2}$

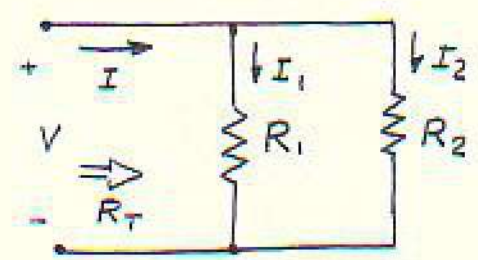but $I_1 = \frac{V}{R_1} = \frac{I R_T}{R_1} = I \cdot \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{R_1}$



$\therefore I_1 = I \cdot \frac{R_2}{R_1 + R_2}$


Similarly, for I_2 , we have:

$$I_2 = \frac{V}{R_2} = \frac{I R_T}{R_2} = I \cdot \frac{R_1 R_2}{R_1 + R_2} \quad \boxed{EE1}$$

$$\therefore I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

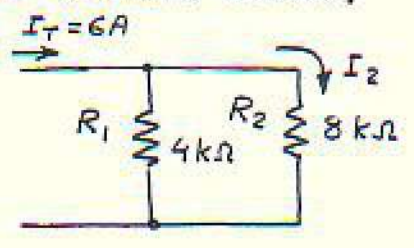Example

: Determine the current I_2 for the network shown;




solution:
$$I_2 = I_T \cdot \frac{R_1}{R_1 + R_2}$$

$$= 6 \frac{4 \times 10^3}{(4 + 8) \times 10^3} = 6 \cdot \frac{4}{12} = \underline{2 \text{ A}}$$

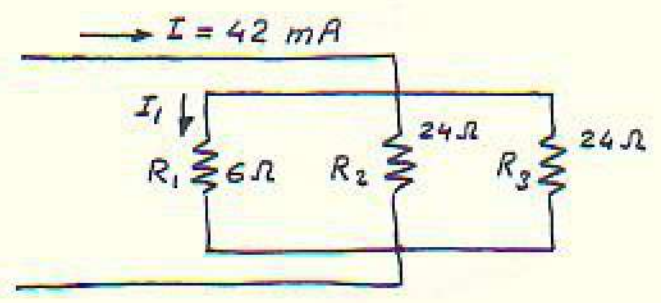Example

: Find the current I_1 for the network shown;



Solution:

$$I_1 = I \cdot \frac{R_T}{R_1}$$

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

or

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6} + \frac{1}{24} + \frac{1}{24}$$

$$\Rightarrow R_T = 4 \Omega$$

$$\therefore I_1 = 42 \times 10^{-3} \frac{4}{6}$$

$$= 28 \times 10^{-3} = \underline{28 \text{ mA}}$$

2.2.2 Voltage Sources in Parallel :

EE2



$E_1 = E_2 = E$ and $I_s = I_1 + I_2$

To increase the current rating of the source, two or more batteries in parallel of the same terminal voltage would be used.

2.3 Open and Short Circuits


: We often need to apply the open and short circuits in the analysis of electric networks.

* Open Circuit

: An open circuit is simply two isolated terminals not connected by an element of any kind.

Consider the circuit shown; with open circuit terminals a and b.

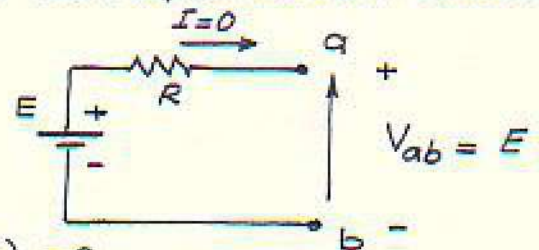$V_{open\ circuit} = V_{OC} = V_{ab} = E$



since I (in the open circuit) = 0


In general

: An open circuit CAN HAVE a potential difference (voltage) across its terminals but the current is always ZERO.

* Short Circuit

: A short circuit is a direct connection of zero ohms across an element or combination of elements.

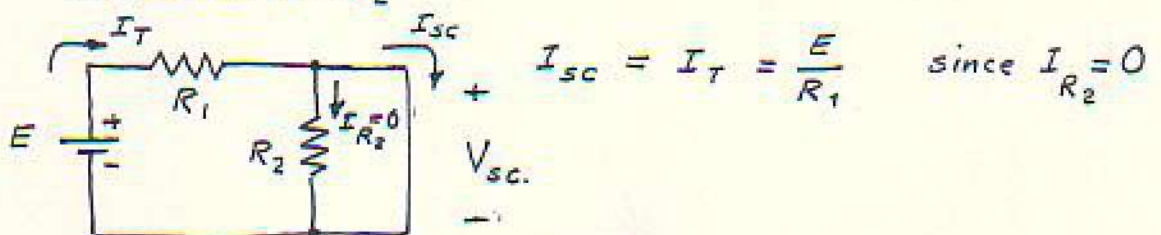Consider the circuit shown, with a short circuit across the resistor R_2



$I_{sc} = I_T = \frac{E}{R_1}$ since $I_{R_2} = 0$

$V_{short\ ckt.} = V_{sc} = \underline{\underline{0}}$


EE2

In general

: A short circuit CAN CARRY a current of any level but the potential difference (voltage) across its terminals is always ZERO.

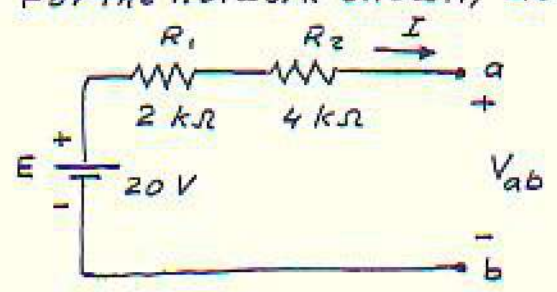Examples

(a). For the network shown, determine V_{ab} .




Solution: - We have an open ckt across the terminal a and b, the

$I = 0 \Rightarrow V_1 = 0$ and $V_2 = 0$

- Applying KVL $\Rightarrow V_{ab} = E = 20V$

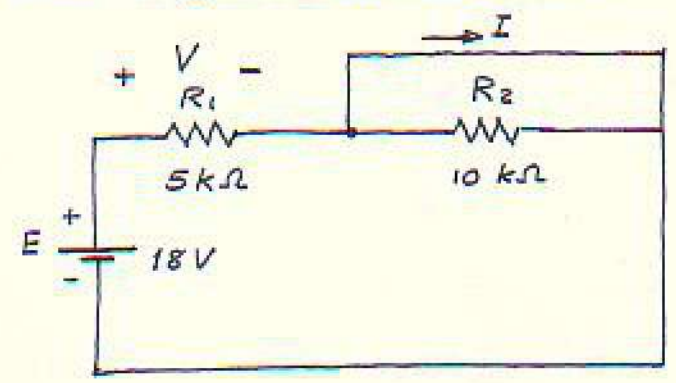(b). Calculate I and V for the network shown;



Solution: - We have a short ckt. across R_2


\Rightarrow No current through R_2

$\Rightarrow I = \frac{E}{R_T} = \frac{E}{R_1 + 0} = \frac{18}{5k\Omega}$

$= \underline{3.6 \text{ mA}}$

$\therefore V = I R_1 = E = \underline{18V}$

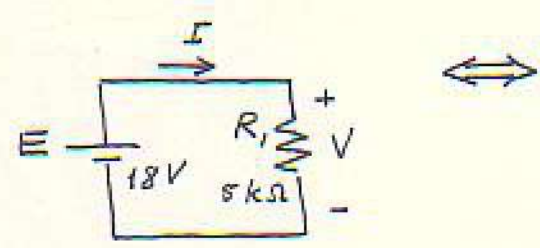
Note: the ckt can be redrawn to be as shown



Wye - Delta Transformation


EE2

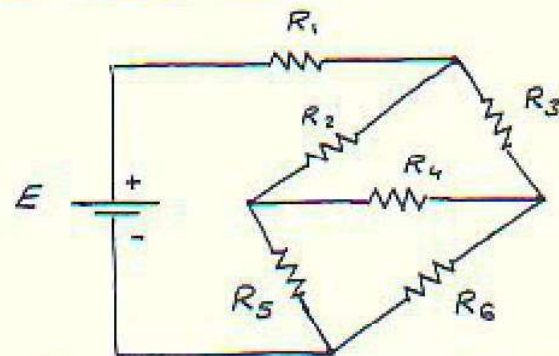There are some cases often arises in circuit analysis, when the resistors are neither in parallel nor in series. For example, consider the circuit shown:




In this circuit, $R_1, R_2, R_3 \dots R_6$ are neither in series nor in parallel

Wye (Y or star) connection

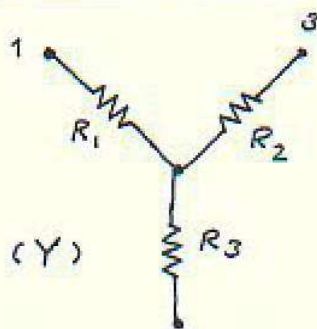

Y or star circuit connection


Equivalent

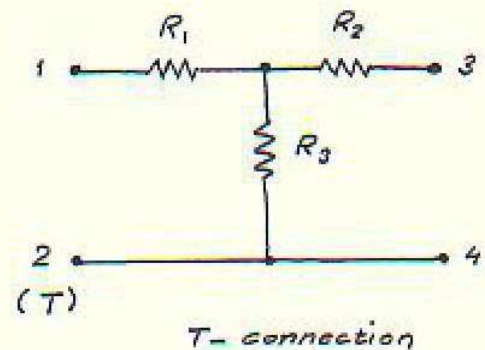

T-connection


Y and T connections

Delta (Δ or π) circuit connection

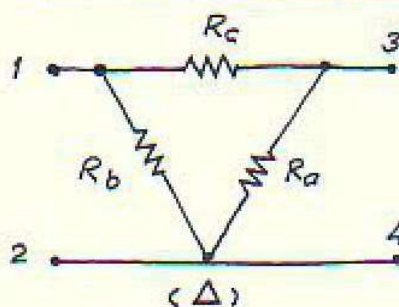

Delta circuit connection

Equivalent

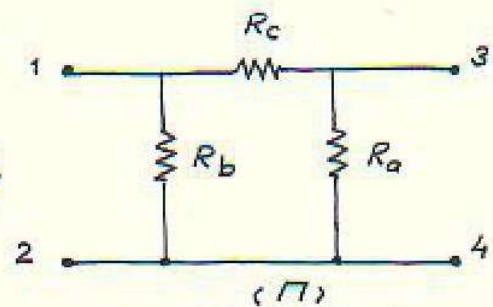

Π-connection

Delta circuit connection & its equivalent Π-connection

Δ Y

* Delta to Wye Transformation

EE2



- We have Δ and want to get its equivalent star circuit

- Consider the Δ circuit shown; to be transformed into its equivalent star shown below:

$$R_{12} = \frac{R_b (R_a + R_c)}{R_a + R_b + R_c}$$

$$R_{13} = \frac{R_c (R_a + R_b)}{R_a + R_b + R_c}$$
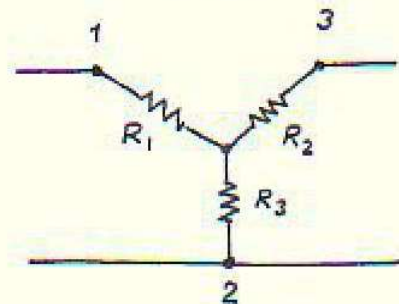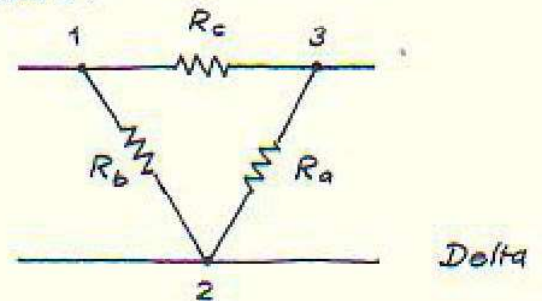
$$R_{23} = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c}$$



$$R_{12} = R_1 + R_3$$

$$R_{13} = R_1 + R_2$$

$$R_{23} = R_2 + R_3$$

$$\therefore R_1 + R_3 = \frac{R_b (R_a + R_c)}{R_a + R_b + R_c} \quad \dots (1)$$

and

$$R_1 + R_2 = \frac{R_c (R_b + R_c)}{R_a + R_b + R_c} \quad \dots (2)$$

$$R_2 + R_3 = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} \quad \dots (3)$$

Subtraction Eq.(3) from Eq.(1) and adding the resulting equation to Eq.(1) results in:

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

Similarly;

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

and;

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

IN GENERAL

Each resistor in the Y network is the product of the resistors in the two adjacent Δ branches, divided by the sum of the three resistors

* Wye to Delta Transformation

- We have Y connected circuit and want to get its equivalent Δ .
- Consider the Y circuit shown, its equivalent Δ is shown below;

Using the previous sets of equations, then we have:


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

and

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

IN GENERAL

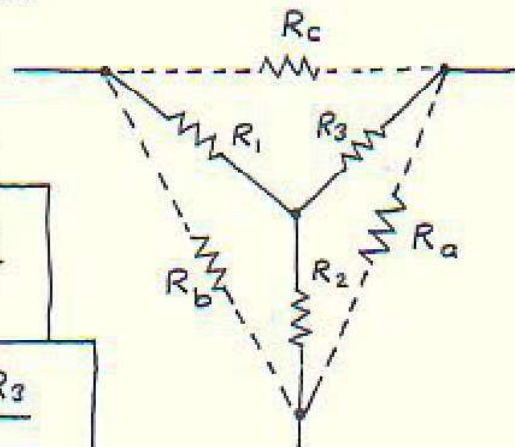

Each resistor in the Δ network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor.

Notes

_____:

- * The Y and Δ networks are said to be balanced when:

$$R_1 = R_2 = R_3 = R_Y$$

and

$$R_a = R_b = R_c = R_\Delta$$

- * Under balance condition, the conversion equations become:


$$R_Y = \frac{R_\Delta}{3}$$

or

$$R_\Delta = 3R_Y$$

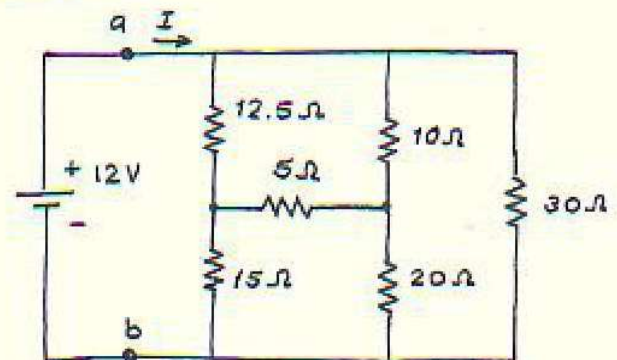Example

_____ Obtain the equivalent resistance R_{ab} for the circuit shown and use it to find the current I




Solution

- * We can't use the relations of series connected or parallel connected resistors to obtain R_{ab} .
- * We try to use Δ -Y transformations or Y- Δ to get R_{ab} .

* If we transform the Y consisting of :

$$\begin{aligned} R_1 &= 10 \Omega \\ R_2 &= 20 \Omega \\ \text{and } R_3 &= 5 \Omega \end{aligned}$$

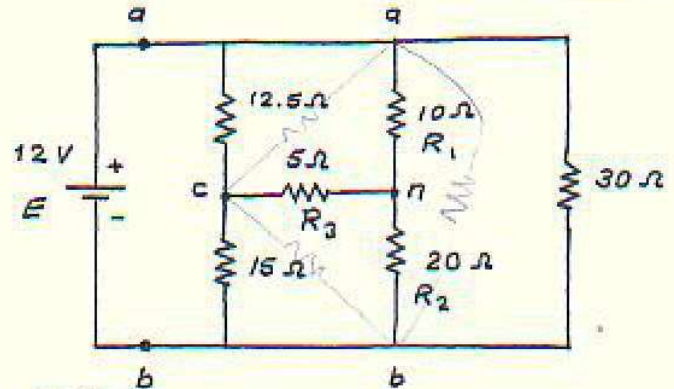\therefore the equivalent Δ circuit contains :



$$\begin{aligned} R_a &= \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1} \\ &= \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10} = \frac{350}{10} \\ &= 35 \Omega \end{aligned}$$

Similarly;

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2} = \frac{350}{20} = 17.5 \Omega$$

and:

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3} = \frac{350}{5} = 70 \Omega$$

$$\therefore R_{ab} = (7.3 + 10.5) \parallel 30$$



$$= \frac{17.8 \times 21}{17.8 + 21}$$

$$\Rightarrow R_{ab} = 9.632 \Omega$$

$$\therefore I = \frac{E}{R_{eq}} = \frac{E}{R_{ab}}$$

$$= \frac{12}{9.632}$$

$$\Rightarrow I = 1.246 \text{ A}$$

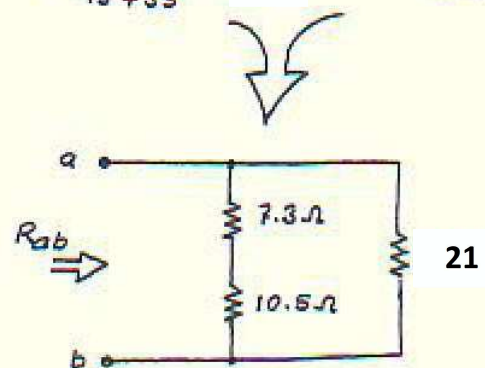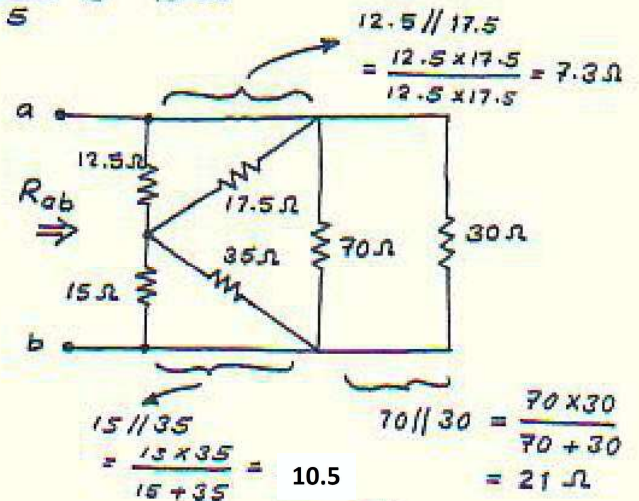

ملاحظة: جميع أسئلة الكتاب والدروس المرفقة فيه مطلوبة

Example 1

Three resistors are connected in series across a 12 V battery. The first resistor has a value of 1Ω , the second has a voltage drop of 4 V, and the third has a power dissipation of 12 W.

Calculate the value of the circuit current.

Solution

We have

$$P_3 = I^2 R_3 = 12 \text{ W} \quad \text{--- (1)}$$

and

$$V_2 = I R_2 = 4 \text{ V} \quad \text{--- (2)}$$


From (2)

$$\therefore I = \frac{4}{R_2}$$

From (1) & (2)

$$\left(\frac{4}{R_2}\right)^2 R_3 = 12$$

$$\therefore R_3 = \frac{3}{4} R_2^2$$

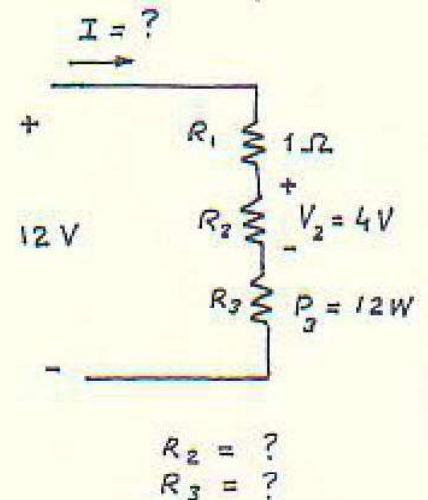

From the circuit shown, we have:

$$12 = I (R_1 + R_2 + R_3) = I (1 + R_2 + R_3)$$

Substituting for I and R_3 , we have:

$$12 = \frac{4}{R_2} \left(1 + R_2 + \frac{3}{4} R_2^2\right)$$

$$\therefore 3R_2^2 - 8R_2 + 4 = 0$$

$$\therefore R_2 = \frac{8 \pm \sqrt{64 - 48}}{6} = 2\Omega \quad \text{or} \quad \frac{2}{3}\Omega$$

$$\therefore R_3 = \frac{3}{4} R_2^2 \Rightarrow R_3 = 3\Omega \quad \text{or} \quad \frac{1}{3}\Omega$$


$$\therefore I = \frac{12}{R_1 + R_2 + R_3} = \frac{12}{1 + 2 + 3} = \underline{2 \text{ A}}$$

or

$$I = \frac{12}{1 + \left(\frac{2}{3}\right) + \left(\frac{1}{3}\right)} = \underline{6 \text{ A}}$$

Practice Problem

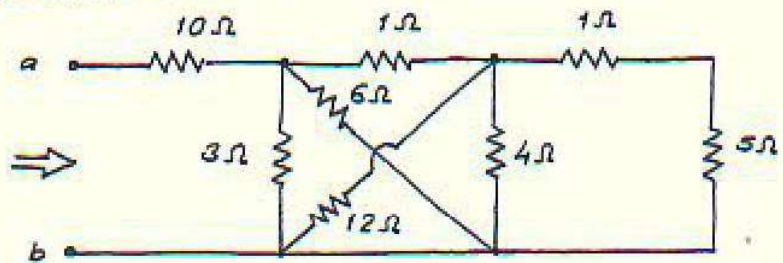_____ : Calculate the equivalent resistance R_{ab} in the circuit shown.




Answer

_____ : $R_{ab} = 11.2 \Omega$

Practice Problem

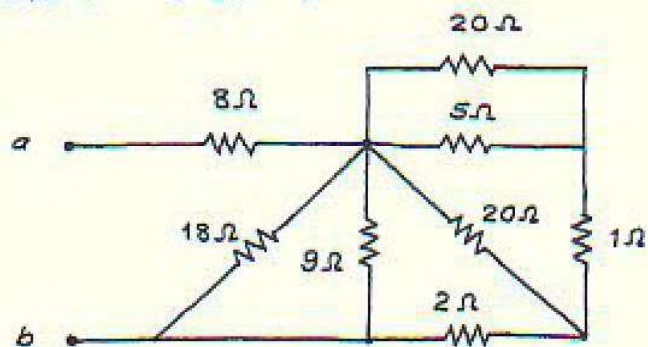_____ : Find R_{ab} for the circuit shown:



Answer

_____ : $R_{ab} = 11 \Omega$

Practice Problem


_____ : Find V_1 and V_2 in the circuit shown. Also calculate I_1 and I_2 and the power dissipated in the 12Ω and 40Ω resistors.

Answer

$V_1 = 5V$, $V_2 = 10V$

$I_1 = 416.7 \text{ mA}$, $I_2 = 250 \text{ mA}$

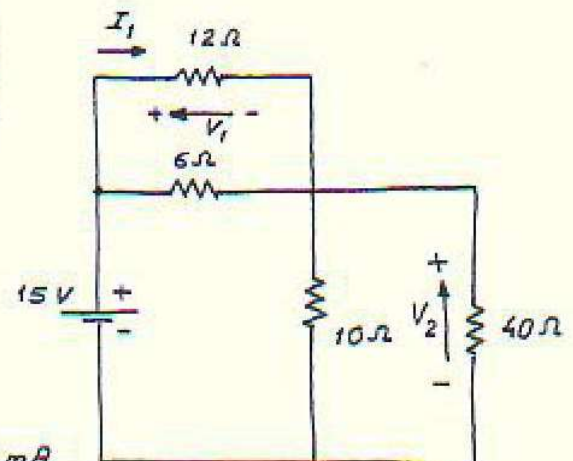$P_1 = 2.083 \text{ W}$, $P_2 = 2.5 \text{ W}$



3. Techniques of Circuit Analysis

EE3

3.1 Determinants

Consider the two simultaneous equations

$$a_1x + b_1y = C_1$$

and

$$a_2x + b_2y = C_2$$

where x and y are the unknown variables, and a_1, a_2, b_1, b_2, C_1 and C_2 are constants.

Using the determinants, the following formats are obtained for each of the variables; x and y :

$$x = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} C_1 & b_1 \\ C_2 & b_2 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}}$$

$$\text{where; } \Delta_1 = C_1 b_2 - C_2 b_1$$

$$\Delta = a_1 b_2 - a_2 b_1$$

$$y = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} a_1 & C_1 \\ a_2 & C_2 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}}$$

$$\text{where; } \Delta_2 = a_1 C_2 - a_2 C_1$$

Δ, Δ_1 and Δ_2 are called second order determinants, since it contains two rows and two columns.

Third order determinants are used to solve three simultaneous linear equations. Consider, the following three simultaneous equations:

$$a_1x + b_1y + c_1z = d_1$$

$$a_2x + b_2y + c_2z = d_2$$

$$a_3x + b_3y + c_3z = d_3$$


The unknown variables, x, y , and z are determined as follows:

$$x_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} d_1 & b_1 & c_1 \\ d_2 & b_2 & c_2 \\ d_3 & b_3 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix}}$$

$$y = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} a_1 & d_1 & c_1 \\ a_2 & d_2 & c_2 \\ a_3 & d_3 & c_3 \end{vmatrix}}{\Delta}$$

$$z = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} a_1 & b_1 & d_1 \\ a_2 & b_2 & d_2 \\ a_3 & b_3 & d_3 \end{vmatrix}}{\Delta}$$

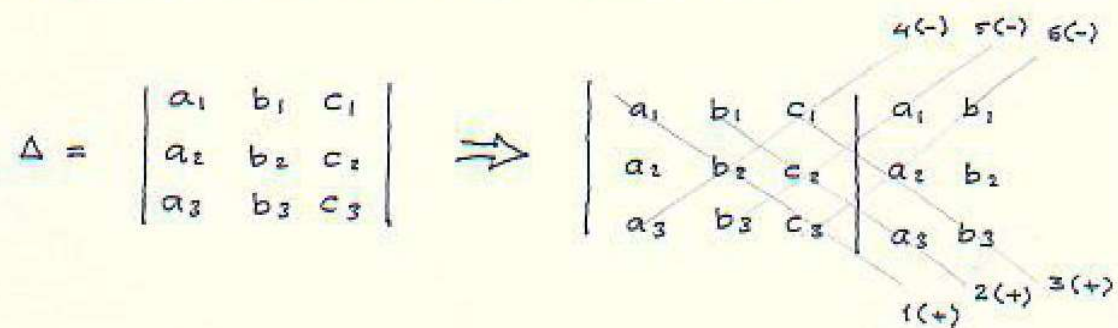The third order determinant can be evaluated as:



$$\Rightarrow \Delta = \overset{1(+)}{a_1 b_2 c_3} + \overset{2(+)}{b_1 c_2 a_3} + \overset{3(+)}{c_1 a_2 b_3} - \overset{4(-)}{a_3 b_2 c_1} - \overset{5(-)}{b_3 c_2 a_1} - \overset{6(-)}{c_3 a_2 b_1}$$

$$\therefore \Delta = a_1 b_2 c_3 + b_1 c_2 a_3 + c_1 a_2 b_3 - a_3 b_2 c_1 - b_3 c_2 a_1 - c_3 a_2 b_1$$

Example: Find x and y:

$$\begin{aligned} -x + 2y &= 3 \\ 3x - 2y &= -2 \end{aligned} \Rightarrow x = \frac{\begin{vmatrix} 3 & 2 \\ -2 & -2 \end{vmatrix}}{\begin{vmatrix} -1 & 2 \\ 3 & -2 \end{vmatrix}} = \frac{(3)(-2) - (-2)(2)}{(-1)(-2) - (3)(2)} = \frac{-2}{-4} = \frac{1}{2}$$

$$\text{and } y = \frac{\begin{vmatrix} -1 & 3 \\ 3 & -2 \end{vmatrix}}{\begin{vmatrix} -1 & 2 \\ 3 & -2 \end{vmatrix}} = \frac{(-1)(-2) - (3)(3)}{-4} = \frac{-7}{-4} = \frac{7}{4}$$

Example

EE3

Find x, y and z , for the following simultaneous equations.

$$x - 2z = -1$$

$$3y + z = 2$$

$$x + 2y + 3z = 0$$

Solution

Arrange the equations to be as:

$$1x + 0y - 2z = -1$$

$$0x + 3y + 1z = 2$$

$$1x + 2y + 3z = 0$$

then

$$x = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} -1 & 0 & -2 & -1 & 0 \\ 2 & 3 & 1 & 2 & 3 \\ 0 & 2 & 3 & 0 & 2 \end{vmatrix}}{\begin{vmatrix} 1 & 0 & -2 & 1 & 0 \\ 0 & 3 & 1 & 0 & 3 \\ 1 & 2 & 3 & 1 & 2 \end{vmatrix}}$$

$$\therefore x = \frac{(-1)(3)(3) + (0)(1)(0) + (-2)(2)(2) - [(0)(3)(-2) + (2)(1)(-1) + (3)(2)(0)]}{(1)(3)(3) + (0)(1)(1) + (-2)(0)(2) - [(1)(3)(-2) + (2)(1)(1) + (3)(0)(0)]}$$

$$= \frac{-15}{13} = -\frac{15}{13}$$

and

$$y = \frac{\begin{vmatrix} 1 & -1 & -2 & 1 & -1 \\ 0 & 2 & 1 & 0 & 2 \\ 1 & 0 & 3 & 1 & 0 \end{vmatrix}}{\Delta} = \frac{\begin{vmatrix} 1 & -1 & -2 & 1 & -1 \\ 0 & 2 & 1 & 0 & 2 \\ 1 & 0 & 3 & 1 & 0 \end{vmatrix}}{13}$$

$$= \frac{(1)(2)(3) + (-1)(1)(1) + (-2)(0)(0) - [(1)(2)(-2) + (0)(1)(1) + (3)(0)(-1)]}{13}$$

$$\therefore y = \frac{5+4}{13} = \frac{9}{13}$$

$$z = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 1 & 0 & -1 & 1 & 0 \\ 0 & 3 & 2 & 0 & 3 \\ 1 & 2 & 0 & 1 & 2 \end{vmatrix}}{13}$$

$$\therefore z = \frac{(1)(3)(0) + (0)(2)(1) + (-1)(0)(2) - [(1)(3)(-1) + (2)(2)(1) + (0)(0)(0)]}{13}$$

$$\Rightarrow z = \frac{0-1}{13} = -\frac{1}{13}$$

2.4 Source Transformation

EE2

It is often necessary or convenient to have a voltage source rather than a current source or a current source rather than a voltage source.

In the ckt. shown, we have a voltage source connected to a load resistance R_L

We have:


$$I_L = \frac{E}{R_T} = \frac{E}{R_S + R_L}$$

Multiplying the numerator by $(R_S/R_S = 1)$, we have:

$$I_L = \frac{(R_S/R_S)E}{R_S + R_L} = \frac{R_S(E/R_S)}{R_S + R_L}$$


$$I = \frac{E}{R_S}$$
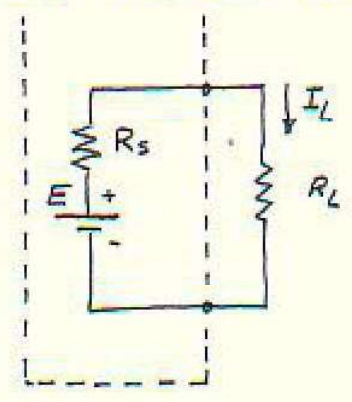
$$\therefore I_L = \frac{R_S \cdot I}{R_S + R_L}$$



Voltage Source



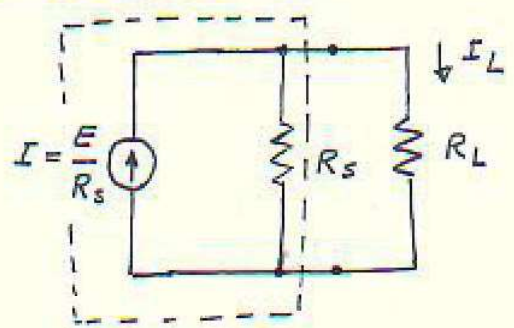
This is a current divider equation, which can be represented by the circuit below; which is the equivalent ckt. of the voltage source.



Current source

In general

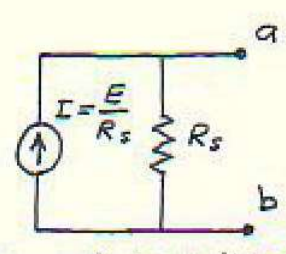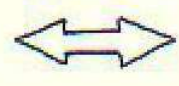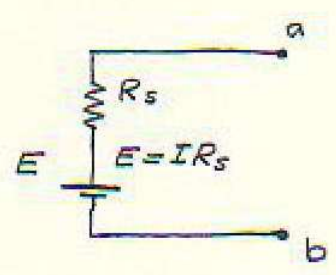A voltage source with voltage E and series resistor R_S can be replaced by a current source with a current I and parallel resistor R_S as shown:




← current to voltage source

voltage source to current source →

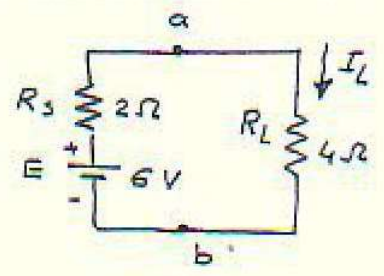Example

EE2

Convert the voltage source, in the cct below, to a current source, then calculate the current through the load for each source.



Solution

* For the voltage source cct;


$$I_L = \frac{E}{R_s + R_L} = \frac{6}{2 + 4}$$

$$= \underline{\underline{1 A}}$$

* For the current source cct;

$$I_L = \frac{I R_s}{R_s + R_L} = \frac{(3)(2)}{2 + 4}$$


$$= \underline{\underline{1 A}}$$

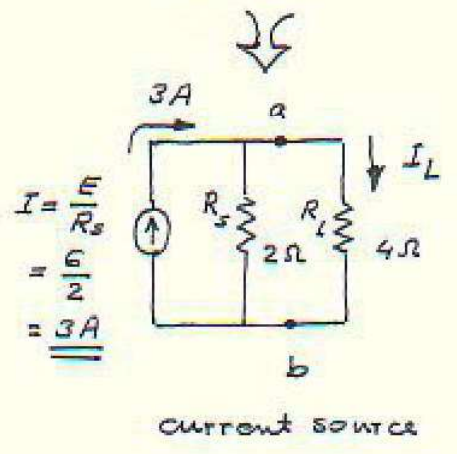

نفساً ان I_L متساوية في الحالتين وهذا صحيح.

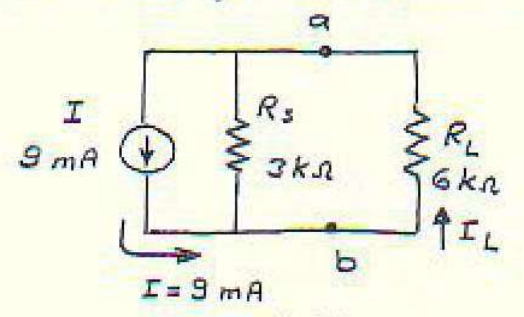Example

Convert the current source, in the cct. shown, to a voltage source and determine I_L for each source.



Solution

* For the current source cct;


$$I_L = \frac{I \cdot R_s}{R_s + R_L} = \frac{(9 \times 10^{-3})(3 \times 10^3)}{(3 + 6) \times 10^3}$$

$$= 3 \times 10^{-3} = \underline{\underline{3 mA}}$$

* For the voltage source cct;

$$I_L = \frac{E}{R_T} = \frac{E}{R_s + R_L} = \frac{27}{(3 + 6) \times 10^3}$$
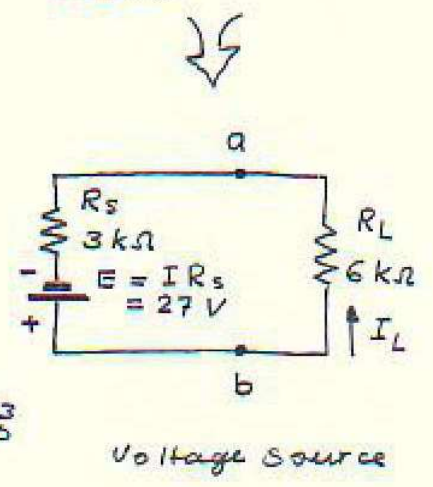
$$= 3 \times 10^{-3} = \underline{\underline{3 mA}}$$




current divider rule ⇒

3.2 Loop (Mesh) Current Method

EE3


Consider the circuit shown below:

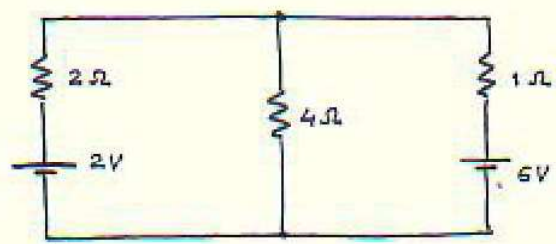

To analyze this circuit using the loop (mesh) method, the following steps must be followed.

STEP 1

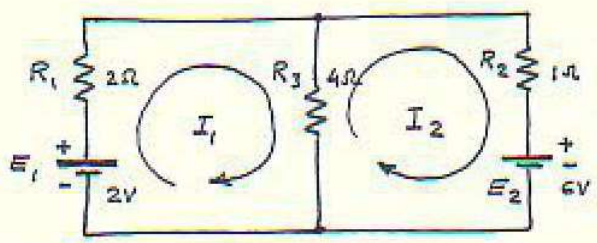
Assign a distinct current in the clockwise direction to each independent loop of the network



Note: there are only two independent loops.

STEP 2

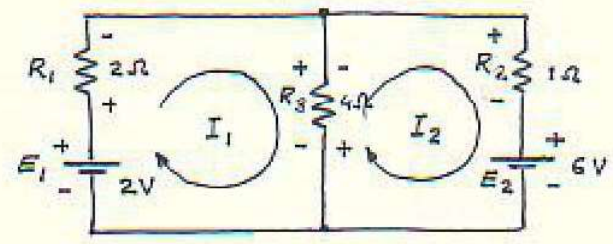Indicate the polarities within each loop for each resistor as determined by the assumed direction of loop current for that loop.



STEP 3

Apply (KVL) around each closed loop in the clockwise direction.

لتكتب هذه الصورة
 تحويلها الى عبارات
 رياضية.

for loop 1 $\Rightarrow E_1 - V_1 - V_3 = 0 \Rightarrow E_1 - I_1 R_1 - (I_1 - I_2) R_3 = 0$
 $2 - 2 I_1 - 4 (I_1 - I_2) = 0$

for loop 2 $\Rightarrow -E_2 - V_3 - V_2 = 0 \Rightarrow -E_2 - R_3 (I_2 - I_1) - I_2 R_2 = 0$
 $-6 - 4 (I_2 - I_1) - 1 I_2 = 0$

Notes: * If a resistor has two or assumed currents through it, the total current must be taken into account.

* The polarity of the voltage source is unaffected by the loop currents passing through it.

STEP 4

Solve the resulting simultaneous equations for the assumed loop currents.

⇒ The equations for loop 1 and loop 2 are rewritten to be as:

Loop 1
2 = 6 I₁ - 4 I₂

Loop 2
-6 = -4 I₁ + 5 I₂

Solving by determinants, then:


I₁ = $\frac{\begin{vmatrix} 2 & -4 \\ 6 & 5 \end{vmatrix}}{\begin{vmatrix} 6 & -4 \\ -4 & 5 \end{vmatrix}} = \frac{(2)(5) - (6)(4)}{(6)(5) - (4)(4)} = \frac{-14}{+14} = \underline{\underline{-1 A}}$

and I₂ = $\frac{\begin{vmatrix} 6 & 2 \\ -4 & -6 \end{vmatrix}}{\begin{vmatrix} 6 & -4 \\ -4 & 5 \end{vmatrix}} = \frac{(-6)(6) - (4)(2)}{+14} = \frac{-28}{+14} = \underline{\underline{-2 A}}$

∴ I_{4Ω} = I₁ - I₂
= -1 - (-2)
= 1 A in the direction of I₁

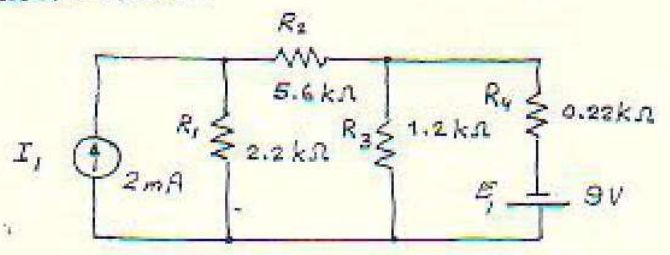Example


Using the mesh analysis, determine the current through the 9V battery for the network shown.




Solution

EEJ

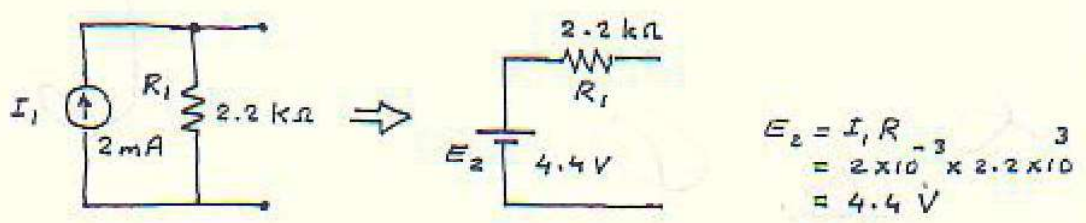* First, the current source has to be converted to a voltage source as shown:



* The original circuit will be as shown;

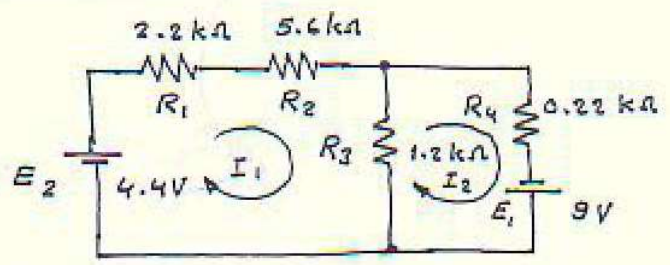

∴ For loop 1, we have:

$$E_2 - I_1 (R_1 + R_2 + R_3) + I_2 R_3 = 0$$

$$4.4 - I_1 (2.2 \times 10^3 + 5.6 \times 10^3 + 1.2 \times 10^3) - 1.2 \times 10^3 I_2 = 0$$

$$\Rightarrow 9 \times 10^3 I_1 - 1.2 \times 10^3 I_2 = 4.4$$

for loop 2, we have:

$$E_1 - I_2 (R_3 + R_4) + I_1 R_3 = 0$$

$$\Rightarrow -1.2 \times 10^3 I_1 + 1.42 \times 10^3 I_2 = 9$$

Solving for I_2

$$\therefore I_2 = \frac{\begin{vmatrix} 9 \times 10^3 & 4.4 \\ -1.2 \times 10^3 & 9 \end{vmatrix}}{\begin{vmatrix} 9 \times 10^3 & -1.2 \times 10^3 \\ -1.2 \times 10^3 & 1.42 \times 10^3 \end{vmatrix}}$$


$$= \frac{86.28}{11.34 \times 10^3} = 7.608 \times 10^{-3}$$

$$\therefore I_2 = \underline{7.608 \text{ mA}}$$

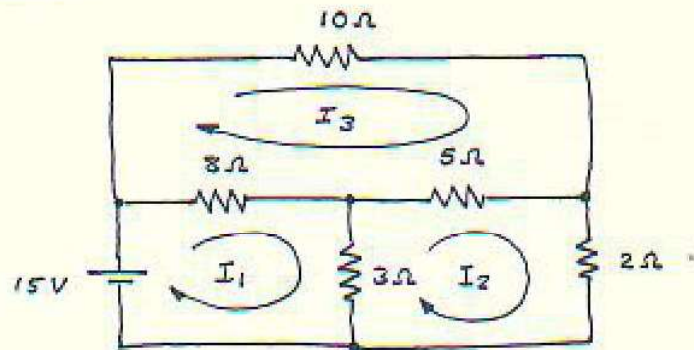Example

EE3

Find the current through the $10\ \Omega$ resistor of the network shown.



Solution

The loop equations are:

Loop 1

:

$$(8+3)I_1 - 3I_2 - 8I_3 = 15$$

Loop 2

:

$$(3+5+2)I_2 - 3I_1 - 5I_3 = 0$$

Loop 3

:

$$(5+8+10)I_3 - 8I_1 - 5I_2 = 0$$

Rearrange, then:

$$11I_1 - 3I_2 - 8I_3 = 15$$

$$-3I_1 + 10I_2 - 5I_3 = 0$$

$$-8I_1 - 5I_2 + 23I_3 = 0$$


$$\therefore I_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 11 & -3 & 15 \\ -3 & 10 & 0 \\ -8 & -5 & 0 \end{vmatrix}}{\begin{vmatrix} 11 & -3 & -8 \\ -3 & 10 & -5 \\ -8 & -5 & 23 \end{vmatrix}} = \underline{1.22\ A}$$

$$\therefore I_3 = I_{10\ \Omega} = 1.22\ A$$

ملفظة : جميع ائلة الكتاب المنهجي وادئلة المحلوله فيه مطلوبه

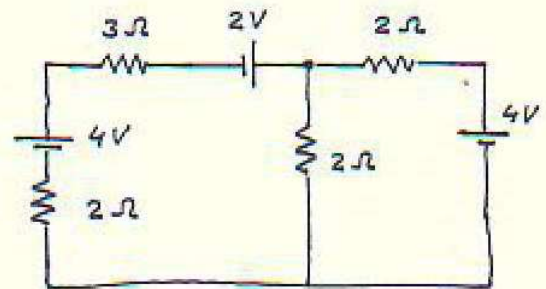Example (1)

For the circuit shown, find the current in the $3\ \Omega$ resistor using: (a) loop current method, (b) nodal voltage method.



Solution

(a) Using loop current method;

Loop 1

$$4 + 2 = I_1(2 + 3 + 2) - I_2(2)$$

$$\Rightarrow 7I_1 - 2I_2 = 6$$


Loop 2

$$-4 = I_2(2 + 2) - I_1(2)$$

$$\Rightarrow -2I_1 + 4I_2 = -4$$


$$\therefore I_1 = \frac{\begin{vmatrix} 6 & -2 \\ -4 & 4 \end{vmatrix}}{\begin{vmatrix} 7 & -2 \\ -2 & 4 \end{vmatrix}} = \frac{(6)(4) - (-2)(-4)}{(7)(4) - (-2)(-2)} = \frac{24 - 8}{28 - 4} = \frac{16}{24}$$
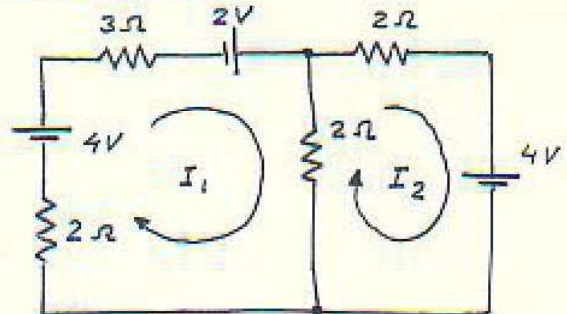
$$\therefore I_1 = \frac{2}{3} \text{ A}$$



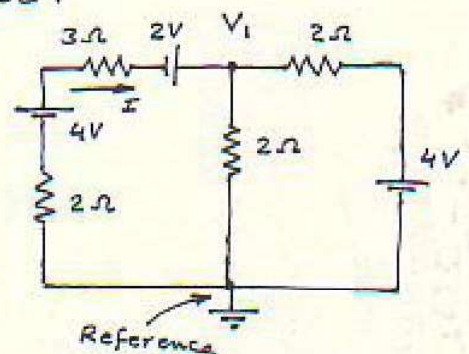(b) using nodal voltage method:

* There is one independent node and a reference node as shown;



* Converting the voltage sources to current sources as shown;


T53

* We have only ONE independent node (V_1),
So we have one equation to find V_1 ,

$$\therefore V_1 \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2} \right) = \frac{6}{5} + 2$$

Simplifying, we get;
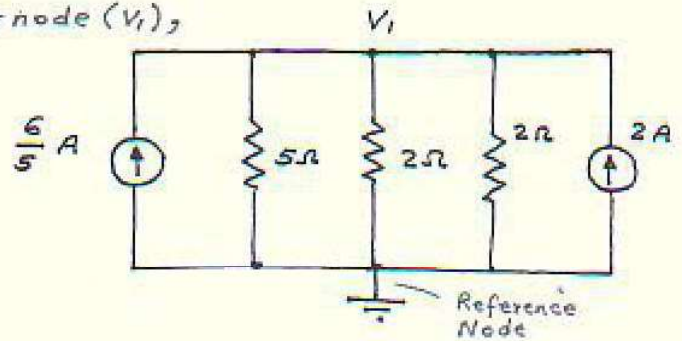
$$\Rightarrow V_1 = \frac{8}{3} \text{ V}$$



Returning to the original circuit, the current through the 3 ohm resistor is:

$$I_1 = \frac{4 + 2 - V_1}{3 + 2} = \frac{6 - (8/3)}{5}$$

$$\therefore I = \frac{2}{3} \text{ A}$$

Example

Determine the current in the 4 ohm resistor for the circuit shown, using loop current method. All resistor values are in Ohms.

Solution

Loop 1


$$I_1(4 + 1 + 3) - I_2(1) - I_3(3) = 24$$

Loop 2

$$I_2(1 + 2 + 12) - I_1(1) - I_3(12) = 12$$

Loop 3
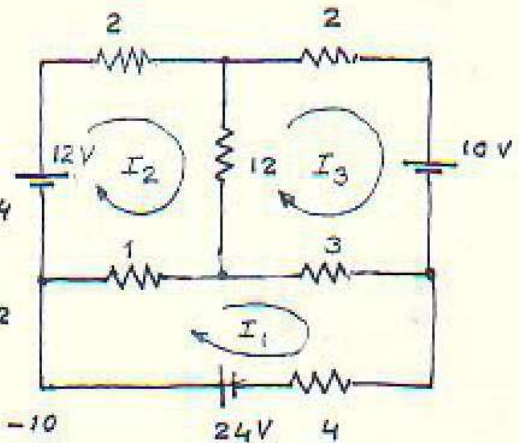
$$I_3(3 + 12 + 2) - I_2(12) - I_1(3) = -10$$



Rearrange, we get

$$8I_1 - I_2 - 3I_3 = 24$$

$$-I_1 + 15I_2 - 12I_3 = 12$$

$$-3I_1 - 12I_2 + 17I_3 = -10$$


$$\Rightarrow I_1 = \frac{2730}{664} = \underline{4.1 \text{ A}}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 24 & -1 & -3 \\ 12 & 15 & -12 \\ -10 & -12 & 17 \end{vmatrix}}{\begin{vmatrix} 8 & -1 & -3 \\ -1 & 15 & -12 \\ -3 & -12 & 17 \end{vmatrix}}$$

Practice Problem

T53

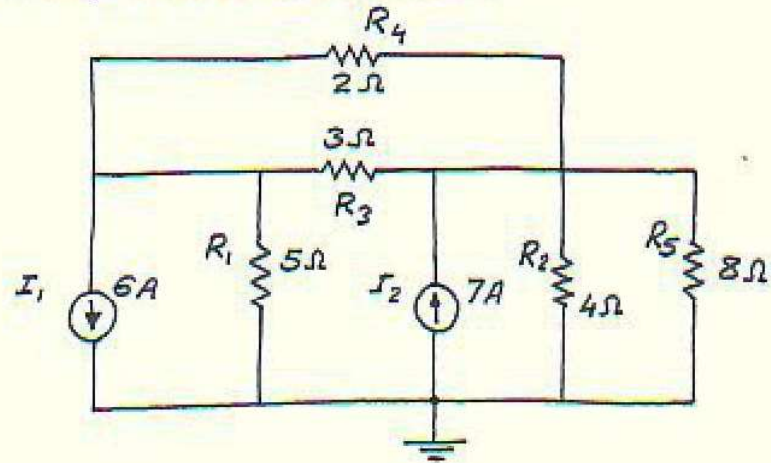- a. Write the nodal equations for the circuit shown; and solve for the nodal voltages.
 b. Determine the magnitude and polarity of the voltage across each resistor.



Answer

$$V_1 = -2.556 \text{ V}, \quad V_2 = 4.03 \text{ V}$$

$$V_{R_1} = V_1 = -2.556 \text{ V}$$


$$V_{R_2} = V_{R_5} = V_2 = 4.03 \text{ V}$$

$$V_{R_4} = V_{R_3} = V_2 - V_1 = 6.586 \text{ V}$$

T53

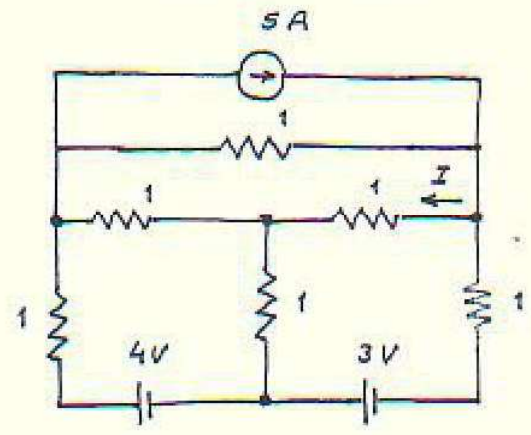Example

Using the nodal voltage method, find, the current I in the circuit shown. All resistors are in Ohms.



Solution * First Convert voltage sources to current sources.

There are three independent nodes and a reference node as shown.

For node 1

$$V_1(1+1+1) - V_2(1) - V_3(1) = 4 - 5$$

$$\rightarrow 3V_1 - V_2 - V_3 = -1$$

For node 2

$$V_2(1+1+1) - V_1(1) - V_3(1) = 5 - 3$$

$$\rightarrow -V_1 + 3V_2 - V_3 = 2$$

For node 3


$$V_3(1+1+1) - V_2(1) - V_1(1) = 0$$

$$\rightarrow -V_1 - V_2 + 3V_3 = 0$$

$$I = \frac{V_2 - V_3}{1\Omega} = \frac{\frac{3}{4} - \frac{1}{4}}{1} = \frac{1}{2} A$$

$$\therefore I = 0.5 A$$

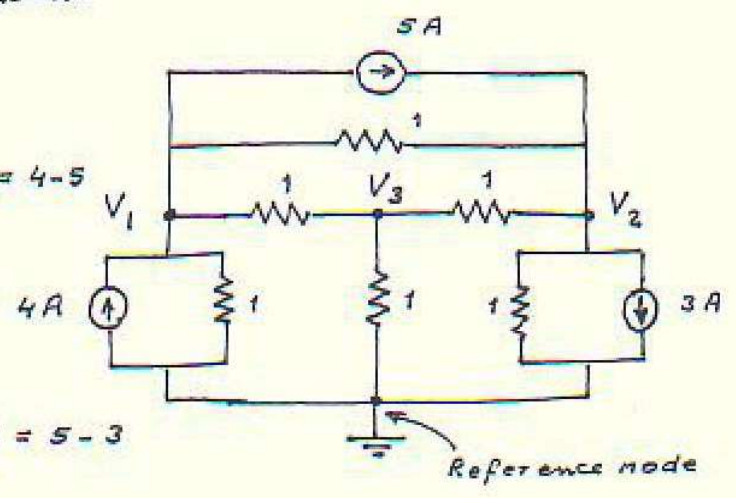ملاحظة: أعدد الحل باستخدام طريقة Loop current method
 تدبر مع الحمول على النتيجة نفسها




$$V_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 3 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & 0 & 3 \end{vmatrix}}{\begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix}} = \frac{12}{16} = \frac{3}{4} V$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & 2 \\ -1 & -1 & 0 \end{vmatrix}}{16} = \frac{4}{16} = \frac{1}{4} V$$

Practice Problem

TS3

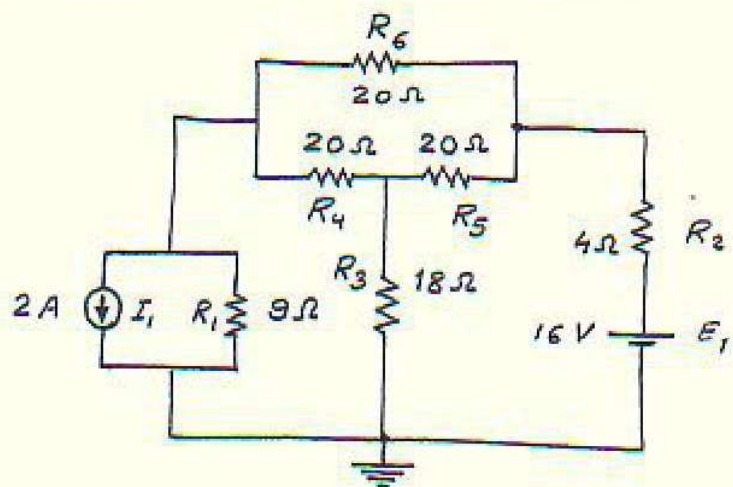For the network shown in the Fig. below, write the nodal equations and solve for the nodal voltages.




Answer

: $V_1 = -6.64 \text{ V}$, $V_2 = 1.288 \text{ V}$ and $V_3 = 10.676 \text{ V}$

Practice Problem

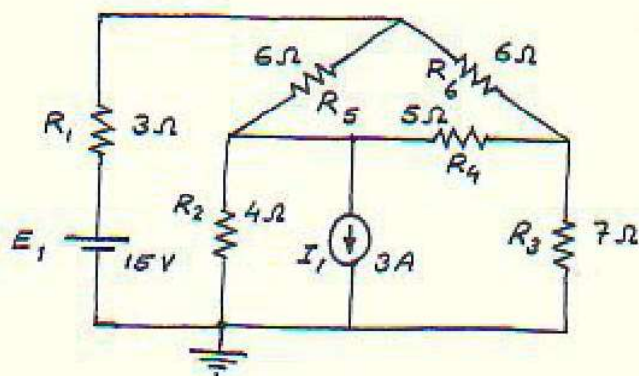For the circuit shown, write the nodal equations and solve for the nodal voltages.




Answer

: $V_1 = 7.238 \text{ V}$
 $V_2 = -2.453 \text{ V}$
 $V_3 = 1.405 \text{ V}$

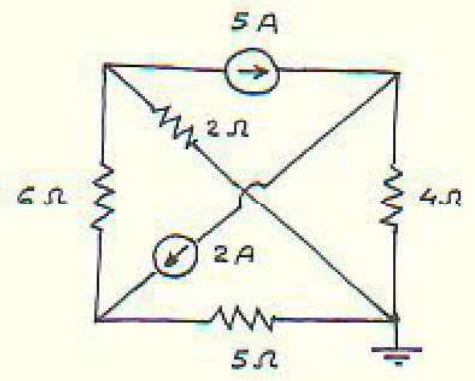Example

753

For the network shown, write the nodal equations and solve for the nodal voltages.



Solution

There are 3 independent nodes and a reference node as shown;

* The independent nodes are $V_1, V_2,$ and V_3

for node 1:


$$V_1 \left(\frac{1}{2} + \frac{1}{6} \right) - V_3 \left(\frac{1}{6} \right) = -5$$

for node 2:

$$V_2 \left(\frac{1}{4} \right) = 5 - 2 = 3$$

for node 3:
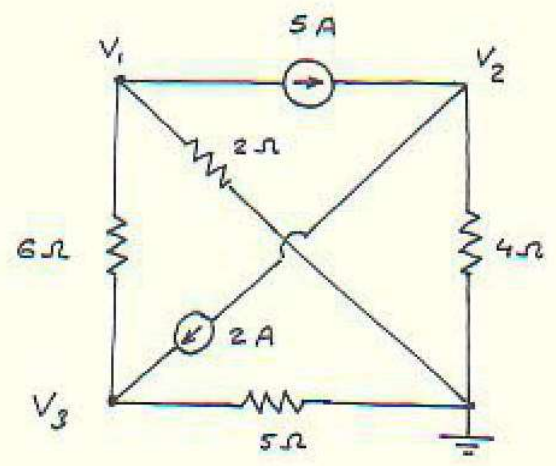
$$V_3 \left(\frac{1}{5} + \frac{1}{6} \right) - V_1 \left(\frac{1}{6} \right) = 2$$



Solving the three equations results in:

$$V_1 = -6.917 \text{ V}$$


$$V_2 = 12 \text{ V}$$

$$V_3 = 2.3 \text{ V}$$

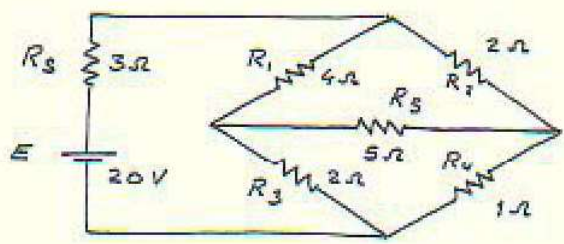
Example

T33

For the bridge network shown, using the loop current method find the current in R_5 .



Solution

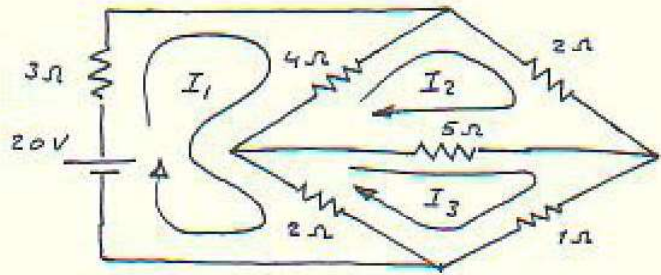

Loop 1

$$I_1(3 + 4 + 2) - (4)I_2 - (2)I_3 = 20$$

Loop 2

$$I_2(4 + 2 + 5) - (4)I_1 - (5)I_3 = 0$$

Loop 3

$$I_3(2 + 5 + 1) - (2)I_1 - (5)I_2 = 0$$

Rearrange, we have:

$$\begin{aligned} 9I_1 - 4I_2 - 2I_3 &= 20 \\ -4I_1 + 11I_2 - 5I_3 &= 0 \\ -2I_1 - 5I_2 + 8I_3 &= 0 \end{aligned}$$

Solving using determinants, we have

$$I_1 = 4 \text{ A}$$

$$I_2 = 2.67 \text{ A}$$

$$I_3 = 2.67 \text{ A}$$

$$\begin{aligned} \Rightarrow \therefore I_{R_5} &= I_2 - I_3 \\ &= 2.67 - 2.67 \\ &= \underline{\underline{0}} \end{aligned}$$

4. Circuit Theorems

EE4

3.1 Superposition Theorem


The theorem states that: "the current through (or the voltage across) an element in a linear bilateral network is equal to the algebraic sum of the currents (or voltages) produced independently by each source.

* To apply this theorem to find the current (or voltage) in a certain part of a network, remove the sources of the network and find the current (or voltage) in the existence of only one source each time. The resultant current (or voltage) will be the algebraic sum of currents (or voltages) due to all sources when acting independently once a time.

* Removing the sources means: SHORT CIRCUITING the voltage source and OPEN CIRCUITING the current source.

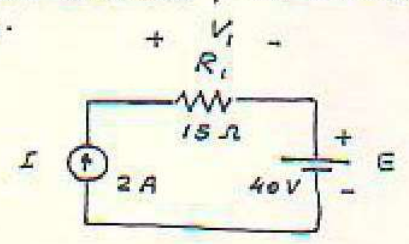Example


Using the superposition theorem, determine V_i for the network shown.



Solution


* Due to the current source:
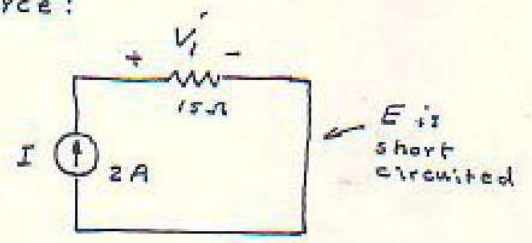
$$\begin{aligned} V_i' &= I R_i \\ &= (2)(15) \\ &= 30 \text{ V} \end{aligned}$$



* Due to the voltage source:
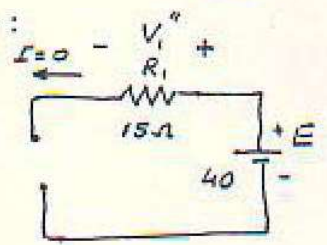
$$\begin{aligned} V_i'' &= I_1 R_i \\ &= (0)(15) \\ &= 0 \text{ V} \end{aligned}$$




$$\begin{aligned} \therefore V_i &= V_i' + V_i'' \\ &= 30 - 0 = 30 \text{ V} \end{aligned}$$

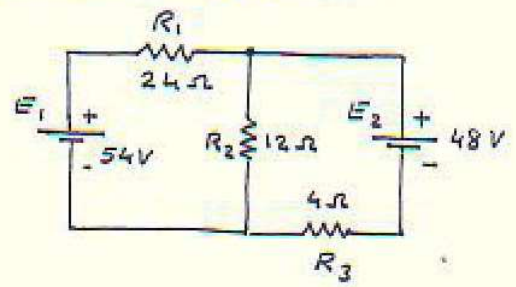Example

EE4

: Using the superposition theorem, determine the current through the 4-Ω resistor for the network shown.




Solution

: Consider the effect of E_1

$$I = \frac{E_1}{R_T} = \frac{54}{27} = 2 \text{ A}$$

Using the current division rule ∴
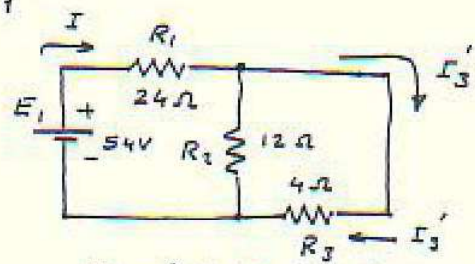
$$\begin{aligned} \therefore I_3' &= I \frac{R_2}{R_2 + R_3} \\ &= 2 \frac{12}{12 + 4} = \underline{1.5 \text{ A}} \end{aligned}$$




$$\begin{aligned} R_T &= (R_2 \parallel R_3) + R_1 \\ &= (12 \parallel 4) + 24 = 3 + 24 \\ &= 27 \Omega \end{aligned}$$

* Consider the effect of E_2 :

$$\begin{aligned} I &= I_3'' = \frac{E_2}{R_T} \\ R_T &= (24 \parallel 12) + 4 \\ &= 8 + 4 \\ &= 12 \Omega \end{aligned}$$

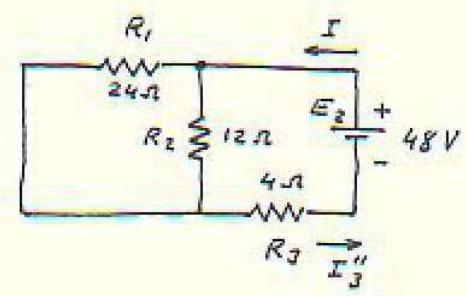
$$\therefore I_3'' = \frac{48}{12} = \underline{4 \text{ A}}$$



$$\begin{aligned} \therefore I_3 &= I_3'' - I_3' \\ &= 4 - 1.5 = \underline{2.5 \text{ A}} \quad (\text{in the direction of } I_3'') \end{aligned}$$

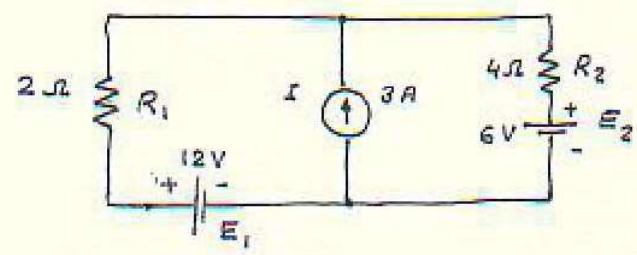Example

: Using the superposition theorem, find the current through the 2-Ω resistor of the network shown.




Solution :

* The effect of E_1

Remove the voltage source E_2 (short circuited) and the current source I (open circuited); the network will be as shown:

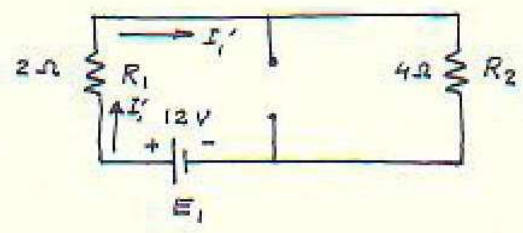
$$\therefore I_1' = \frac{E_1}{R_T} = \frac{12}{2+4} = 2A$$



* The effect of E_2

removing E_1 & I , the network will be as shown:
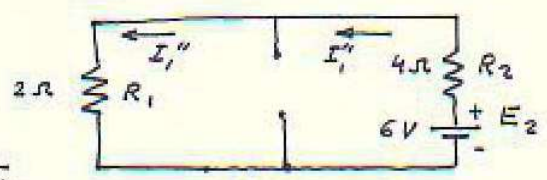
$$\therefore I_1'' = \frac{E_2}{R_T} = \frac{6}{2+4} = 1A$$




* The effect of I

removing E_1 and E_2 , the network will be as shown:

$$\therefore I_1''' = I \frac{R_2}{R_1 + R_2} = (3) \frac{4}{4+2} = 2A$$


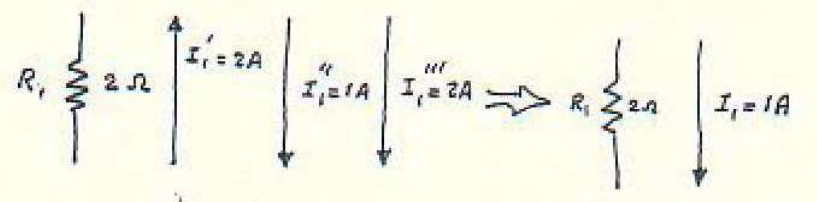
$$\therefore I_1 = \underbrace{I_1'' + I_1'''}_{\text{same direction}} - \underbrace{I_1'}_{\text{opposite direction}} \Rightarrow I_1 = 1 + 2 - 1 = \underline{1A}$$




Resulting current in R_2

3.2 Thevenin's Theorem

EE4

Thevenin's theorem states that "Any two-terminal linear bilateral DC network can be replaced by an equivalent circuit consisting of a voltage source and a series resistor."

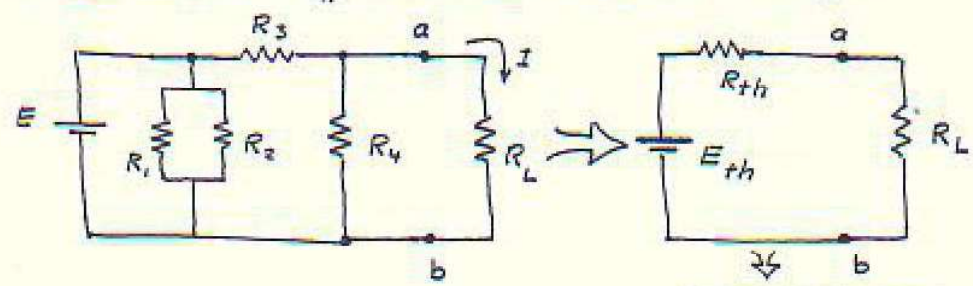Consider the network shown, it can be replaced by the voltage source E_{th} and the series resistor R_{th} :




* To find I through the resistance R_L \Rightarrow
$$I = \frac{E_{th}}{R_{th} + R_L}$$


* Steps to find E_{th} and R_{th} :

- STEP 1: Remove that portion of the network across which the Thevenin equivalent circuit is to be found.
- STEP 2: Mark the terminals of the remaining two-terminal network.
- STEP 3 (R_{th}): Calculate R_{th} by first setting all sources to zero (voltage sources are replaced by short circuits and current sources are replaced by open circuits), and finding the resultant resistance between the two marked terminals.
- STEP 4 (E_{th}): Calculate E_{th} by first returning all sources to their original positions and finding the open circuit voltage between the marked terminals.
- STEP 5: Draw the Thevenin equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.

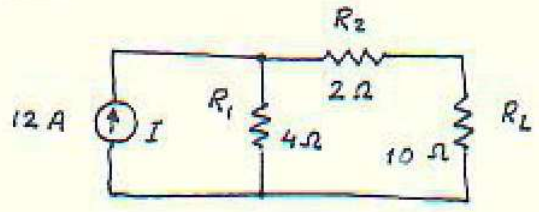Example: Using Thevenin's theorem, find the current in the $R_L = 10 \Omega$ of the network shown. EE4




Solution: steps 1 and 2:

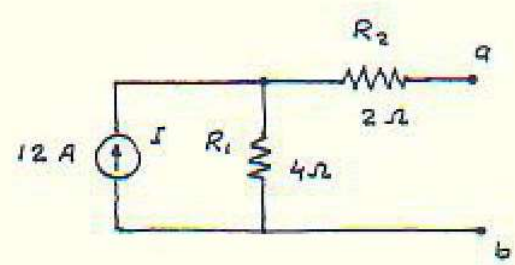

step 3: $R_{th} = ?$

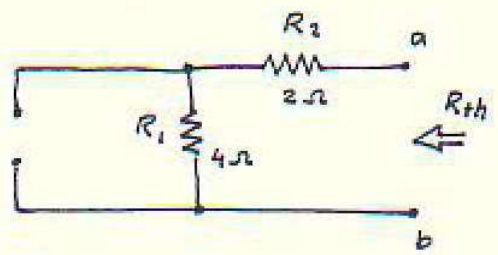Remove the current source I , then calculate R_{th} between the terminals a and b ;




$$\therefore R_{th} = R_1 + R_2 = 4 + 2 = 6 \Omega$$

step 4: $E_{th} = ?$

Return the current source to its original position then determine E_{th} across the open circuit terminals a and b .

Then

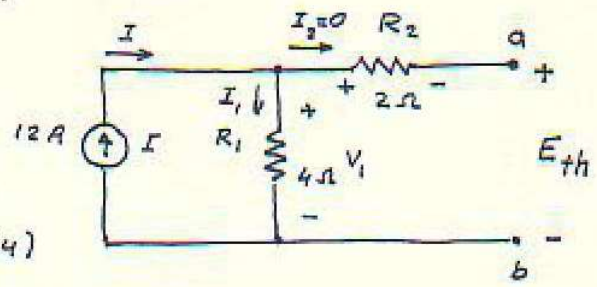
$$I_2 = 0$$
$$\Rightarrow I_2 R_2 = 0$$
$$E_{th} = I_1 R_1 - I_2 R_2$$
$$= I_1 R_1 = 12(4)$$
$$= 48 \text{ V}$$




step 5: Draw the Thevenin equivalent circuit representing the network between points a and b with R_L added.

EE4

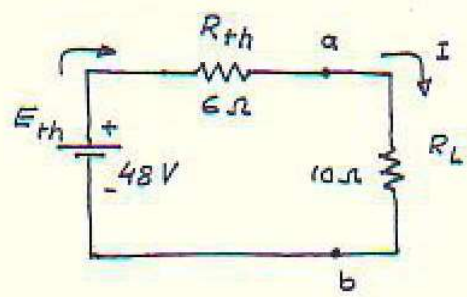
$$\begin{aligned} \therefore I &= \frac{E_{th}}{R_{th} + R_L} \\ &= \frac{48}{6 + 10} = 3 \text{ A} \end{aligned}$$



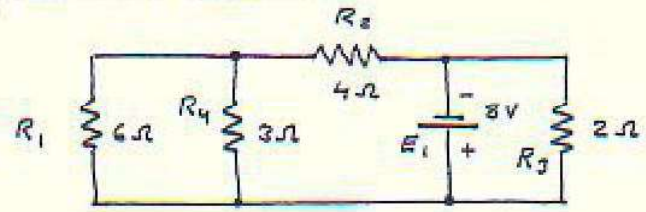
Example: For the circuit shown, find the current in the 3-Ω resistor using Thevenin's theorem.



Solution: steps 1 and 2

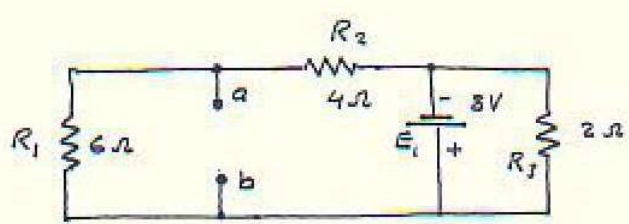


step 3: $R_{th} = ?$

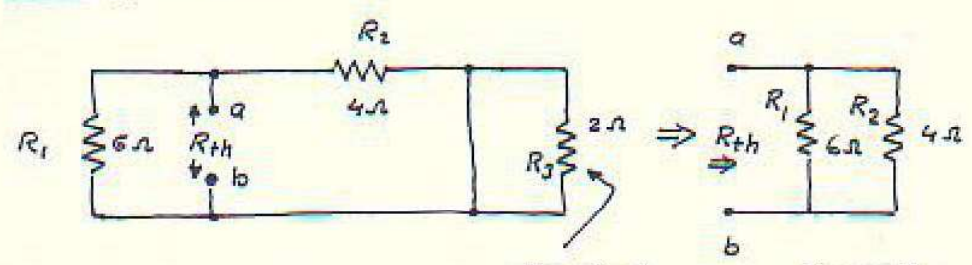

$$\therefore R_{th} = \frac{6(4)}{6+4} = 2.4 \Omega$$

R_3 short circuited
 $R_{th} = 6 \parallel 4 = 2.4 \Omega$


step 4: $E_{th} = ?$

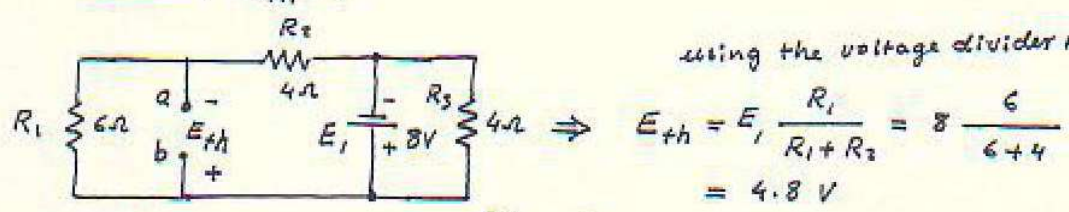

using the voltage divider rule,

$$\begin{aligned} E_{th} &= E_1 \frac{R_1}{R_1 + R_2} = 8 \frac{6}{6+4} \\ &= 4.8 \text{ V} \end{aligned}$$

step 5

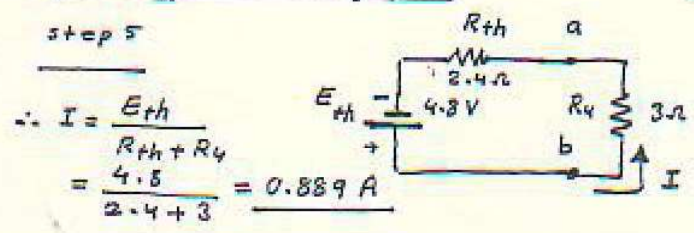


$$\begin{aligned} \therefore I &= \frac{E_{th}}{R_{th} + R_4} \\ &= \frac{4.8}{2.4 + 3} = 0.889 \text{ A} \end{aligned}$$

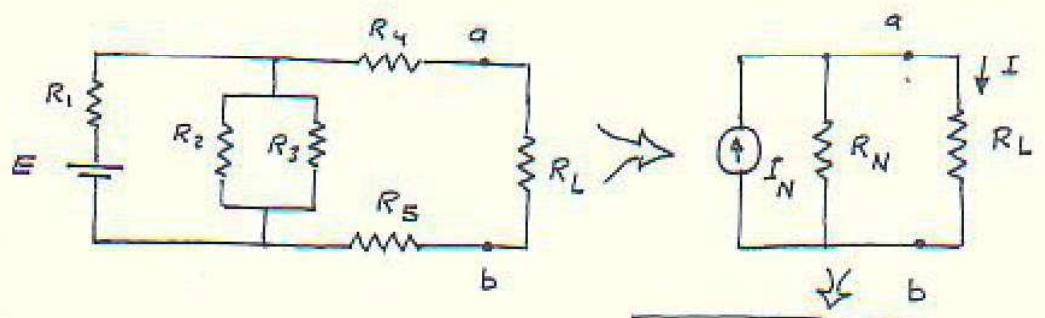3.3. Norton's Theorem

Norton's Theorem: Norton's theorem states that "Any two terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor."

Consider the network shown, it can be replaced by the current source I_N and the parallel resistor R_N ;



To find the current through $R_L \Rightarrow$
$$I = \frac{I_N R_N}{R_N + R_L}$$

How to find I_N and R_N

STEP 1

Remove that portion of the network across which the Norton equivalent circuit is found.

STEP 2

Mark the terminals of the remaining two-terminal network.

STEP 3 (R_N)

Calculate R_N by first removing all the sources (voltage sources replaced by short circuits and current sources replaced by open circuits) and then finding the resultant resistance between the two marked terminals.

STEP 4 (I_N)


Calculate I_N by first returning all sources to their original position and then finding the short circuit current between the marked terminals.

STEP 5

Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.


Relation between Norton equivalent circuit and Thevenin's equivalent circuit

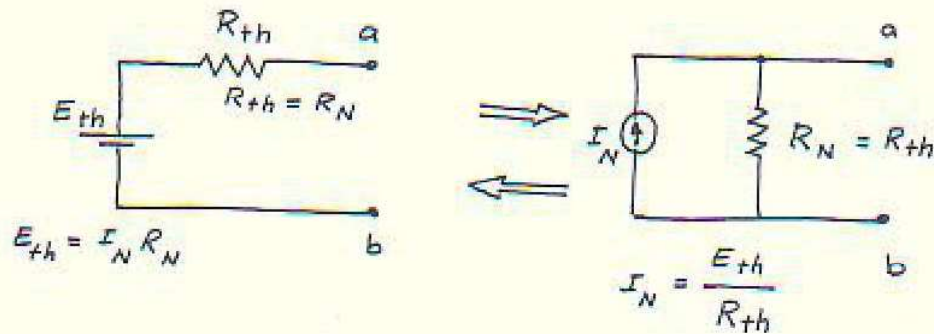The Norton and Thevenin equivalent circuits can also be found from each other by using the source transformation previously discussed, as shown;



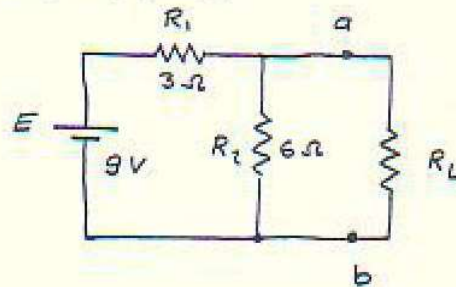
Example

For the circuit shown, find the Norton equivalent circuit for the network to the left of (a-b).




Solution

steps 1 and 2

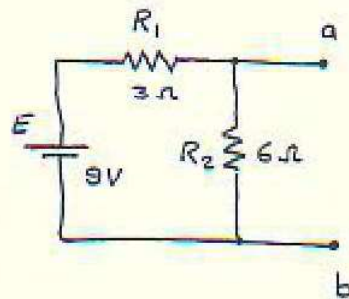

step 3 $R_N = ?$

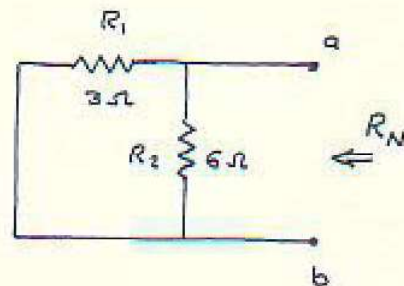
$$\begin{aligned} R_N &= R_1 \parallel R_2 \\ &= \frac{3(6)}{3+6} \\ &= 2 \Omega \end{aligned}$$




STEP 4 $I_N = ?$

$$I_N = I = \frac{E}{R_1} = \frac{9}{3}$$

$$= 3 \text{ A}$$

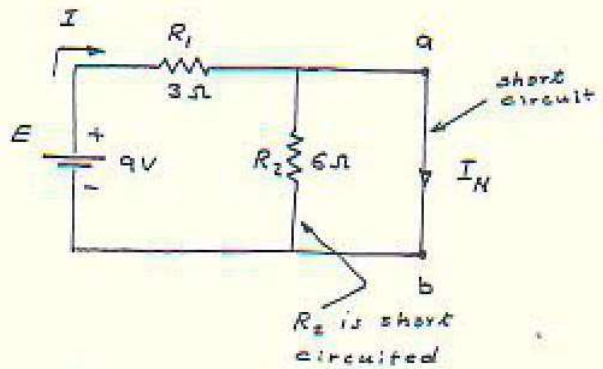


∴ step 5

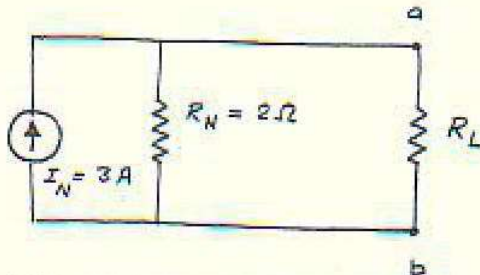

which is the Norton equivalent circuit of the network.


Note

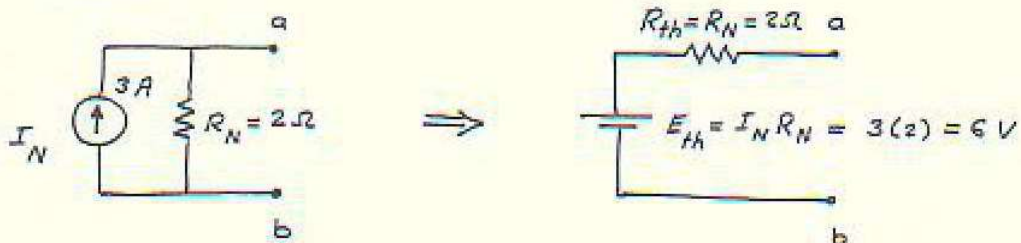—: Thevenin's theorem can be determined by Norton's theorem as shown:



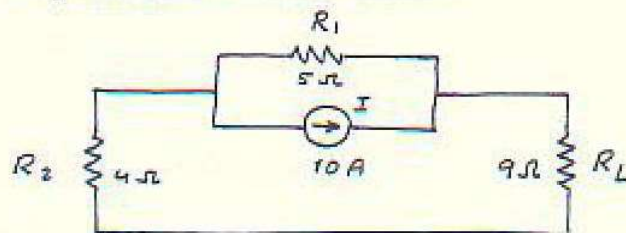
Example

—: Using Norton theorem find the current through the load resistor R_L in the network shown.




Solution

step 1 and 2


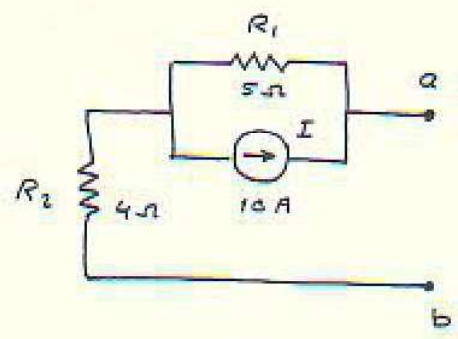


step 3 : $R_N = ?$
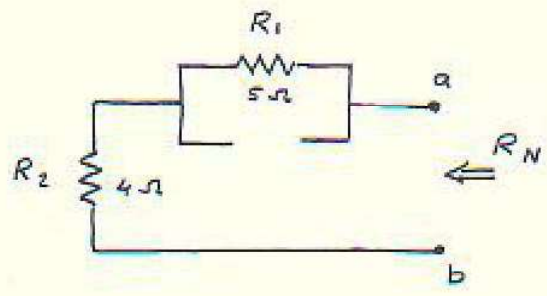
$$\begin{aligned}
 R_N &= R_1 + R_2 \\
 &= 5 + 4 \\
 &= 9 \Omega
 \end{aligned}$$



step 4 $I_N = ?$

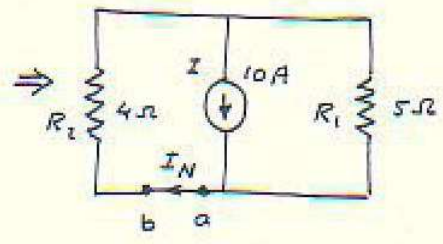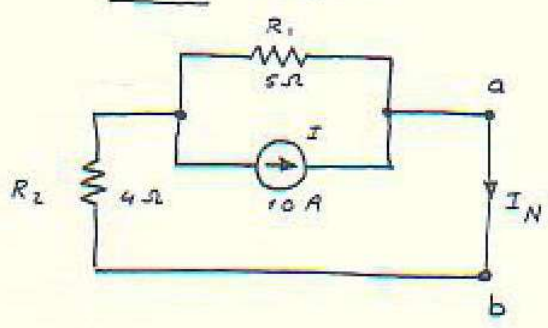

$$\begin{aligned}
 \therefore I_N &= I \cdot \frac{R_1}{R_1 + R_2} \\
 &= 10 \cdot \frac{5}{5 + 4} \\
 &= 5.556 \text{ A}
 \end{aligned}$$

step 5




$$\therefore I = \frac{I_N}{2} = 2.778 \text{ A}$$

ملزمة : جميع أسئلة الكتاب للبرامج والسنة المطلوبة .

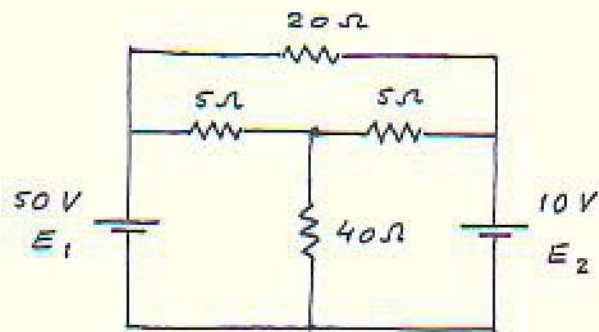
Example

Use the superposition theorem, find the current in the $40\ \Omega$ resistor of the circuit shown.




Solution

* The effect of E_1

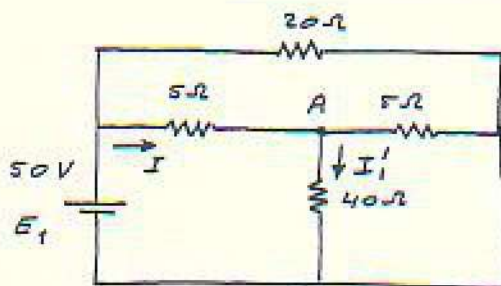

$5 // 40$

\Rightarrow

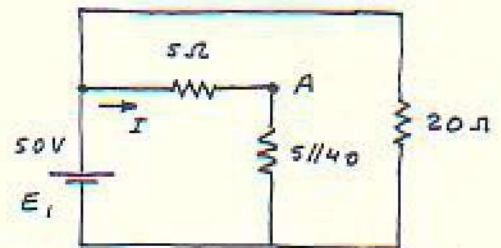

$5 // 40 = 4.44\ \Omega$


$$\therefore I = \frac{50}{5 + 4.44} = 5.296\ \text{A}$$

$$\therefore I'_1 = I \frac{5}{5 + 40} = 5.296 \frac{5}{45} = 0.589\ \text{A}$$

* The effect of E_2

$$I = \frac{10}{(5 // 40) + 5} = 1.059\ \text{A}$$
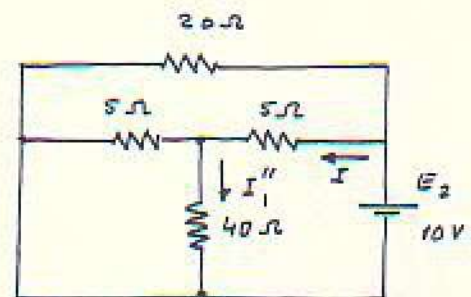
$$I''_1 = I \frac{5}{40 + 5} = 1.059 \frac{5}{45} = 0.118\ \text{A}$$




$$\therefore I_1 = I'_1 + I''_1 = 0.589 + 0.118 = 0.707\ \text{A}$$

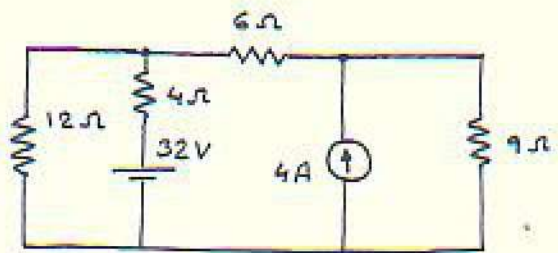Example


TS4

For the circuits shown, calculate the current through the $9\ \Omega$ resistor using the superposition theorem.



Solution

* The effect of the voltage source

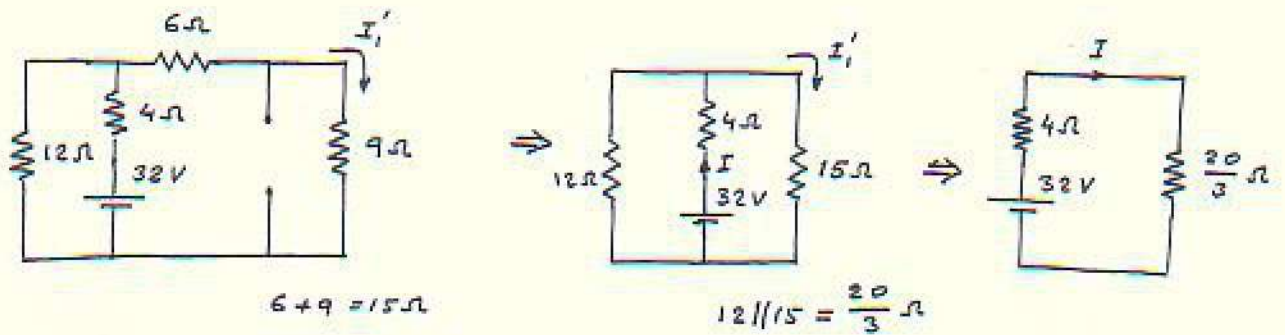


$$R_T = 4 + \frac{20}{3} = \frac{32}{3}\ \Omega$$

$$\therefore I = \frac{E}{R_T} = \frac{32}{(32/3)} = 3\ \text{A}$$

$$\therefore I_1' = I \frac{12}{12 + 15} = \frac{4}{3}\ \text{A}$$

* The effect of the current source

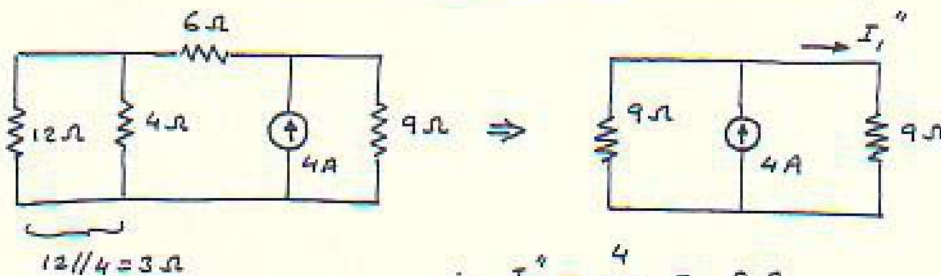


$$\therefore I_1'' = \frac{4}{2} = 2\ \text{A}$$

$$\therefore I_1 = I_1' + I_1'' = \frac{4}{3} + 2 = \frac{10}{3}\ \text{A}$$

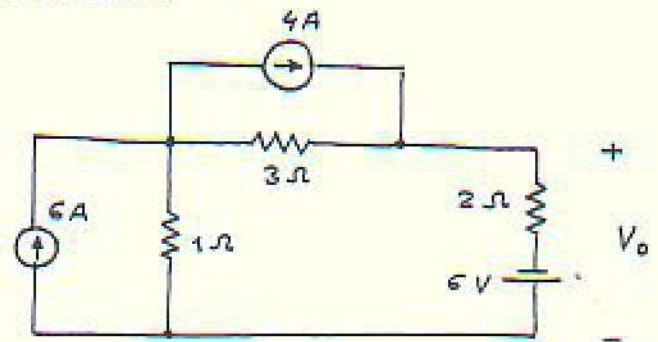Example

T34

Using the superposition theorem, find the value of the output voltage V_o in the circuit shown.



Solution


Effect of 6A source

Using the current divider rule:

$$I_1' = 6 \frac{1}{(1+2+3)}$$

$$= 1 \text{ A}$$
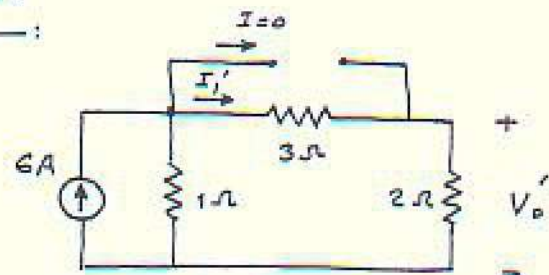
$$\therefore V_o' = I_1'(2) = 2 \text{ V}$$



Effect of 4A source


current divider rule

$$I_1'' = 4 \frac{3}{(1+2)+3}$$

$$= 2 \text{ A}$$

$$\therefore V_o'' = I_1''(2)$$

$$= 4 \text{ V}$$

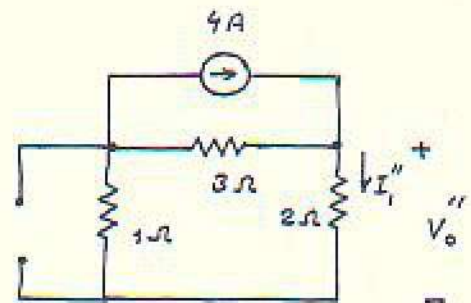


Effect of 6V source

$$I_1''' = \frac{6}{1+3+2} = 1 \text{ A}$$

$$\therefore V_2 = I_1'''(2) = 2 \text{ V}$$
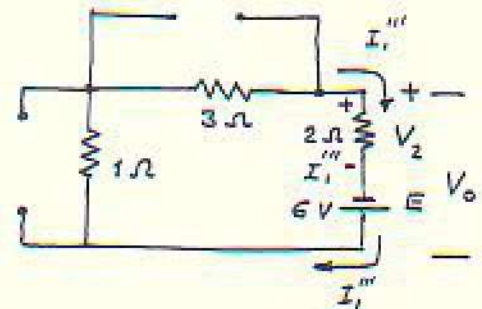
$$\therefore V_o''' = E - V_2 = -6 + 2 = -4 \text{ V}$$




$$\therefore V_o = V_o' + V_o'' - V_o''' = 2 + 4 - 4$$

$$= 2 \text{ V}$$

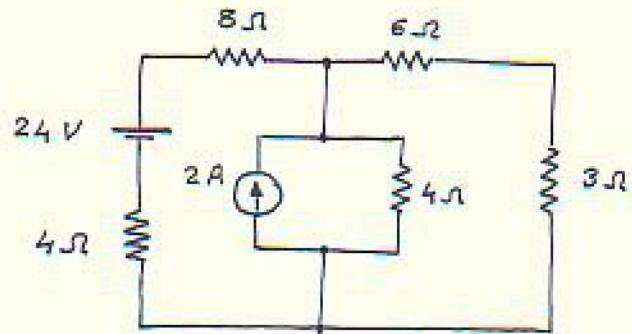Example


T54

Use the Thevenin's theorem to find the current in the $3\ \Omega$ resistor in the network shown.




Solution

$E_{th} = ?$

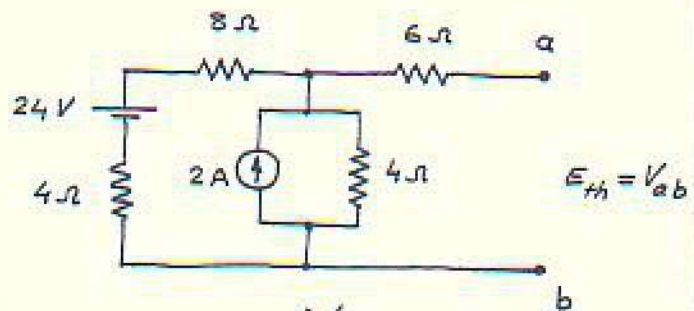

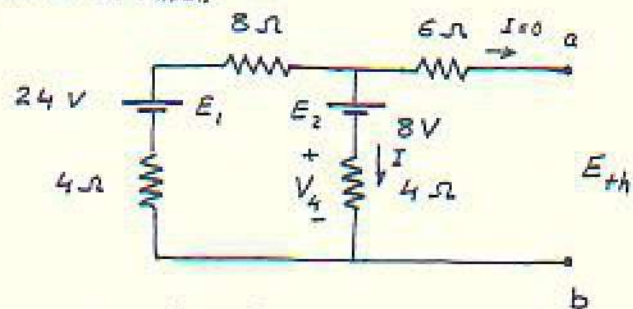convert the current source to voltage source as shown



$$\therefore E_{th} = E_2 + V_4$$

$$V_4 = I(4\ \Omega)$$


$$I = \frac{E_1 - E_2}{4 + 8 + 4} = \frac{24 - 8}{16} = 1\ \text{A}$$

$$\therefore V_4 = (1)(4) = 4\ \text{V}$$


$$\therefore E_{th} = 8 + 4 = 12\ \text{V}$$

$$R_{th} = ?$$
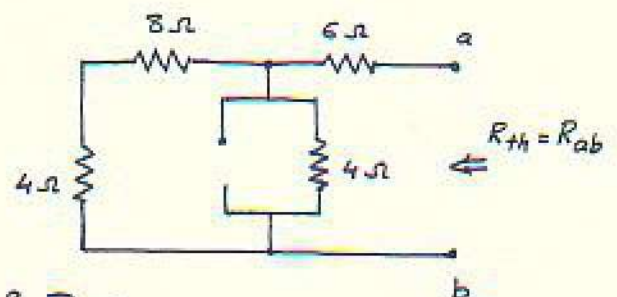
$$R_{th} = [(8 + 4) \parallel 4] + 6 = 9\ \Omega$$


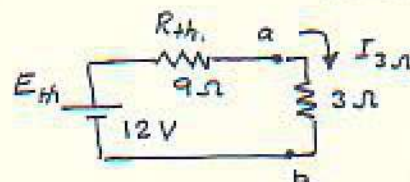
$$\therefore I_{3\ \Omega} = \frac{12}{9 + 3} = 1\ \text{A}$$




Note: Repeat this example to find the value of R_L for max. power transfer and compute $P_{L\ \text{max}}$

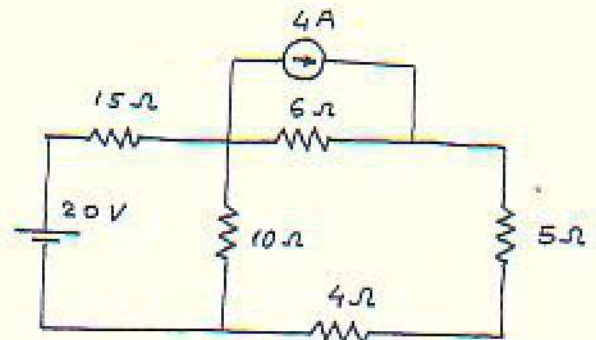Example

TS 4


For the circuit shown, find the value of the current passing through the $5\ \Omega$ resistor using Norton's theorem. Calculate the power absorbed by this resistor.



Solution

$R_N = ?$
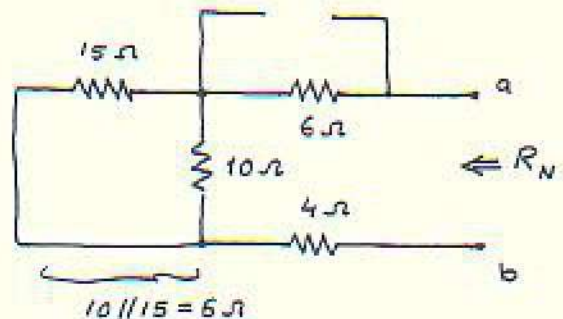
$$R_N = (15 \parallel 10) + 6 + 4 = 16\ \Omega$$





$I_{sc} = ?$

We have two sources; we can use superposition theorem to find the resulting I_{sc} .

Effect of 4A source

current divider rule
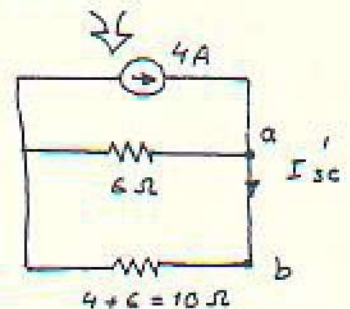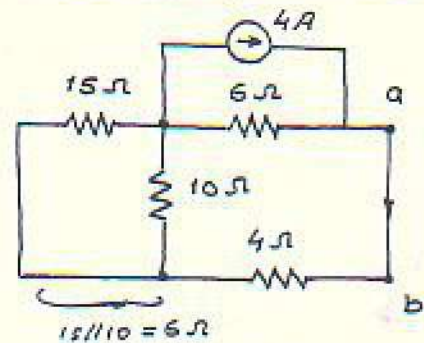
$$I'_{sc} = 4 \frac{6}{6+10} = \frac{4(6)}{16} = \frac{3}{2} = 1.5\ A$$



Effect of 20V source

$$I_T = \frac{E}{R_T}$$

$$R_T = \left[\frac{6+4}{10} \right] + 15$$

$$= 20 \Omega$$

$$\therefore I_T = \frac{20}{20} = 1 \text{ A}$$



$$\therefore I_{sc}'' = \frac{I_T}{2} = \frac{1}{2} = 0.5 \text{ A}$$

$$\therefore I_N = I_{sc}' + I_{sc}'' = 1.5 + 0.5 = \underline{2 \text{ A}}$$

$$\begin{aligned} \therefore I_{R_{5\Omega}} &= I_N \frac{R_N}{R_N + R_{5\Omega}} \\ &= 2 \frac{16}{16+5} = 1.52 \text{ A} \end{aligned}$$

and the power $P = I_{R_{5\Omega}}^2 \cdot R_{5\Omega}$
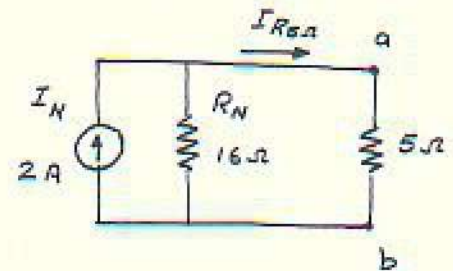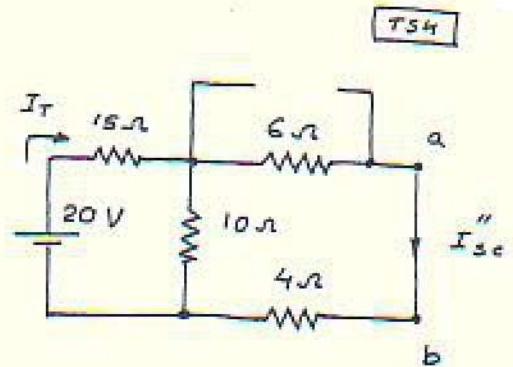
$$= (1.52)^2 \cdot (5) = 11.6 \text{ W}$$




ملاحظة : مع المبدأ استخراج E_{th} ومع ثم تحويلها إلى دائرة نورتن المكافئة ومع ثم الحصول على التيار

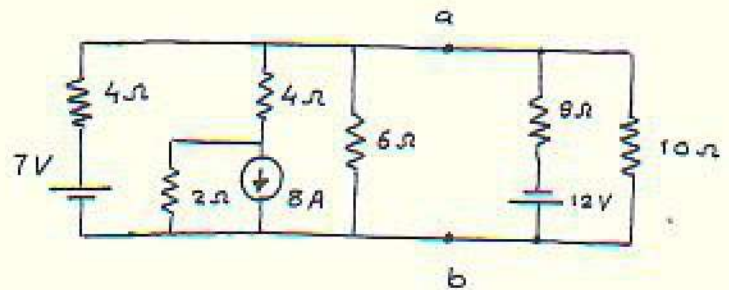
Example

T54

Find the Norton equivalent circuit for the portion of the network to the left of (a-b) in the circuit shown.




Solution

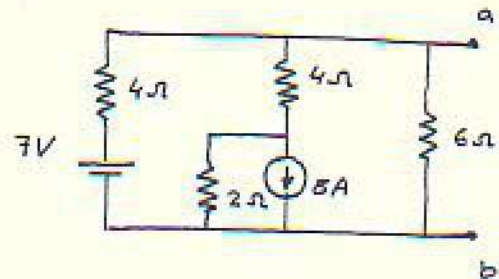

$R_N = ?$

$R_N = 6 \parallel 9$
 $= 1.714 \Omega$

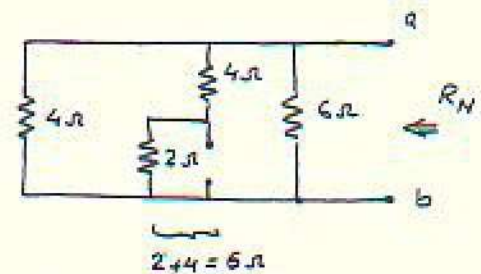


$I_N = ?$

We have 2 sources, it is recommended to use the superposition theorem to find I_N

بما أننا نريد إيجاد I_N فإننا نستخدم نظرية التراكب

- Effect of 7V source


$\therefore I'_N = \frac{7}{4} = 1.75 A$

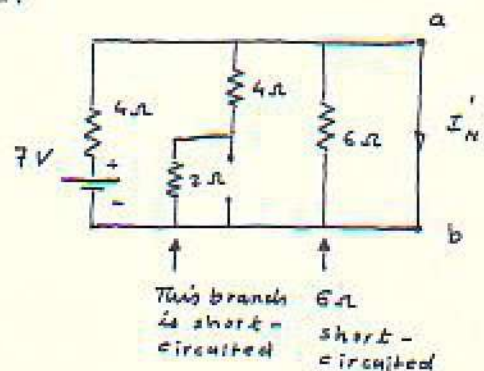

- Effect of 8 A source


Current divider rule
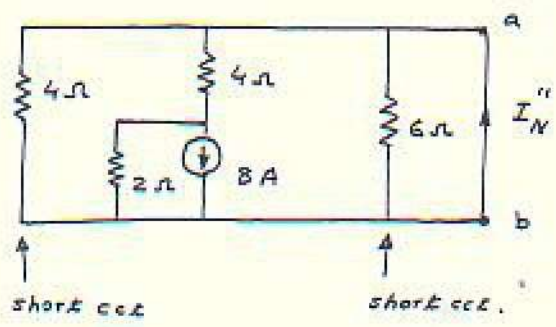
$$\therefore I_N'' = 8 \frac{2}{2+4} = 2.667 \text{ A}$$



$$\therefore I_N = I_N' - I_N'' = 2.667 - 1.75 = 0.917 \text{ A (in the direction of } I_N')$$

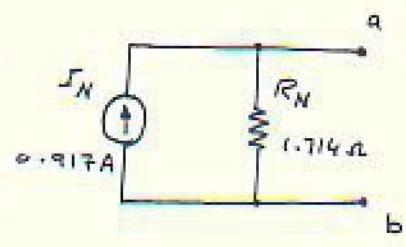
∴ The Norton equivalent ckt of the portion of the network to the left of (a-b) is:



(Thevenin) *نقطة*

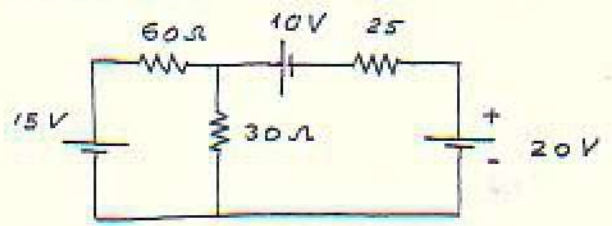Example

∴ For the circuit shown, find the current through the 20V voltage source using Thevenin's theorem.




AC Circuit

Definitions Related to AC Waveforms

EE6

* The Cycle

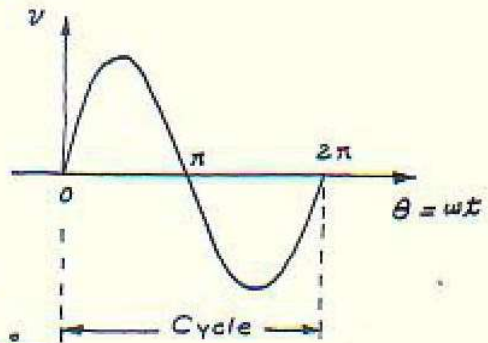 : One complete set of positive and negative values of an alternating quantity is called a (cycle). Complete cycle is said to spread over 360° or 2π radians



$$\therefore 360^\circ = 2\pi \text{ radians}$$

$$\Rightarrow 1 \text{ rad.} = \frac{360^\circ}{2\pi} = \frac{180^\circ}{\pi}$$

$$\therefore 1 \text{ rad.} = 57.3^\circ$$

- To convert from degrees to radians

$$\text{Radians} = \left(\frac{\pi}{180} \right) \times \text{degrees}$$

- To convert from radians to degrees

$$\text{Degrees} = \left(\frac{180}{\pi} \right) \times \text{radians}$$

For examples

$$90^\circ \rightarrow \text{rad.} = \frac{\pi}{180} \times 90^\circ = \frac{\pi}{2}$$



$$30^\circ \rightarrow \text{rad.} = \frac{\pi}{180} \times 30 = \frac{\pi}{6}$$

$$\frac{\pi}{3} \rightarrow \text{deg.} = \frac{180}{\pi} \times \frac{\pi}{3} = 60^\circ$$

$$\frac{3\pi}{2} \rightarrow \text{deg.} = \frac{180}{\pi} \times \frac{3\pi}{2} = 270^\circ$$

* Time Period (T)

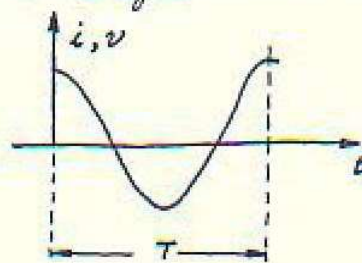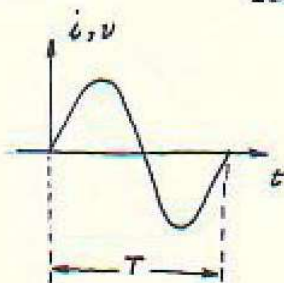 : It is the time taken by an alternating quantity to complete one cycle.



$$T = \frac{1}{f}$$

$\Rightarrow f$ is the frequency.

* Instantaneous Value


: The magnitude of a waveform (alternating voltage or current) at any instant of time. It is denoted by small letters such as $v, e, e_1, e_2, i_1, i_2, p \dots$ etc.

* Amplitude (or Peak Value or Maximum Value)

: The maximum value (positive or negative) of an alternating quantity is called amplitude. It is denoted by capital letters, such as E_m, V_m, I_m, \dots etc.

* Frequency

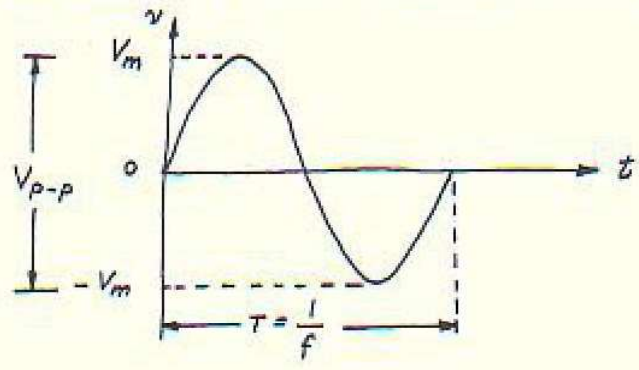: It is the number of cycles that occur in one second



* Peak to Peak Value

: It is denoted by E_{p-p} or V_{p-p} and represents the full voltage between positive and negative peaks of the waveform (see the figure above).

In general form for the sinusoidal voltage or current

$e = E_m \sin \theta$	θ in deg.
-----------------------	------------------

$e = E_m \sin \omega t$	$\theta = \omega t$
-------------------------	---------------------

$e = E_m \sin 2\pi f t$	$\omega = 2\pi f$
-------------------------	-------------------


$e = E_m \sin \frac{2\pi}{T} t$	$f = \frac{1}{T}$
---------------------------------	-------------------

6.4 Phase Relations


A sinusoidal waveform may start from zero as had been shown earlier, or it may be shifted to the left or to the right as shown.

$$e = E_m \sin \omega t$$

* it has zero phase shift.

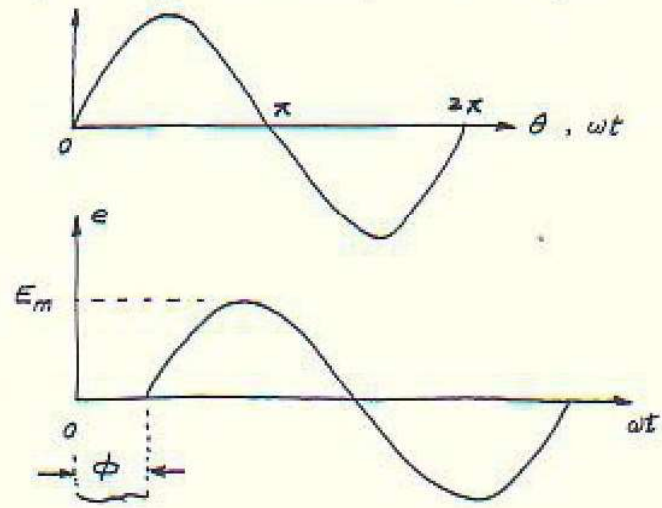


$$e = E_m \sin(\omega t - \phi)$$

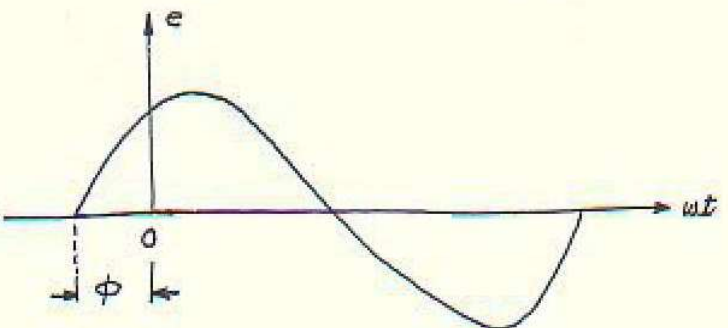

$$e = E_m \sin(\omega t + \phi)$$

In the figure shown, three sinusoidal waveform are plotted with different phases:
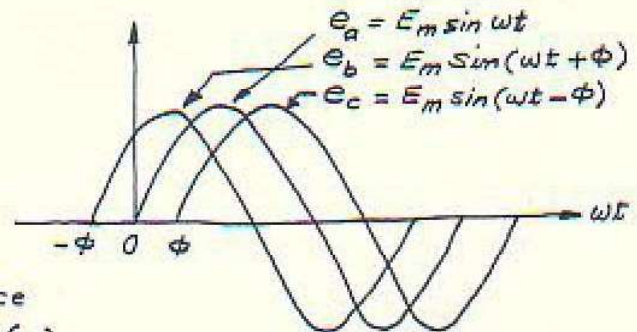
$$\begin{aligned} e_a &= E_m \sin \omega t \\ e_b &= E_m \sin(\omega t + \phi) \\ e_c &= E_m \sin(\omega t - \phi) \end{aligned}$$



⊕ A plus (+) sign when used in connection with phase difference denotes (lead) whereas minus (-) sign denotes (lag).

Some Useful Relations

$$\begin{aligned} \sin(\omega t + 90^\circ) &= \sin(\omega t + \frac{\pi}{2}) = \cos(\omega t) \\ \cos(\omega t - 90^\circ) &= \cos(\omega t - \frac{\pi}{2}) = \sin \omega t \\ \sin(-\theta) &= -\sin \theta \\ \cos(-\theta) &= \cos \theta \\ -\sin(\theta) &= \sin(\theta \pm 180^\circ) \\ -\cos(\theta) &= \cos(\theta \pm 180^\circ) \end{aligned}$$

Examples

What is the phase difference between the following sets of voltages and currents?

(a). $v = 10 \sin(\omega t + 30^\circ)$
 $i = 5 \sin(\omega t + 70^\circ)$

(b). $v = 10 \sin(\omega t - 20^\circ)$
 $i = 15 \sin(\omega t + 60^\circ)$


(c). $i = 2 \cos(\omega t + 10^\circ)$
 $v = 3 \sin(\omega t - 10^\circ)$

(d). $i = -2 \cos(\omega t - 60^\circ)$
 $v = 3 \sin(\omega t - 150^\circ)$

(e). $i = -\sin(\omega t + 30^\circ)$
 $v = 2 \sin(\omega t + 10^\circ)$

Solutions


(a).

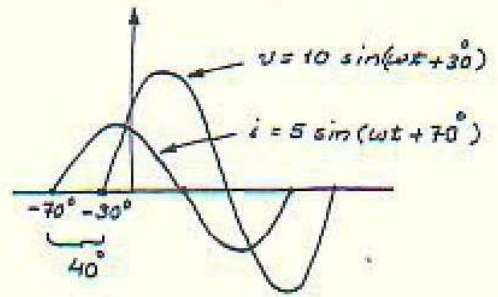

The phase difference = 40°
 i leads v by 40°

or v lags i by 40°

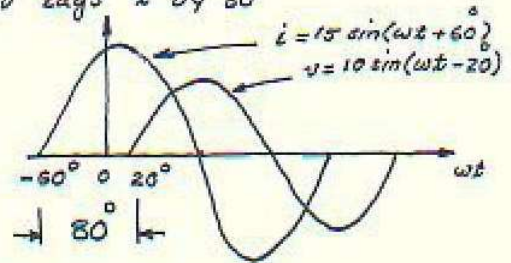(b). The phase difference $60^\circ + 20^\circ = 80^\circ$
 $\therefore i$ leads v by 80°
 or v lags i by 80°



Similarly you can find the results of c, d and e, and the results are:

(c).

$i = 2 \cos(\omega t + 10^\circ) = 2 \sin(\omega t + 10^\circ + 90^\circ) = 2 \sin(\omega t + 100^\circ)$
 $\therefore i = 2 \sin(\omega t + 100^\circ)$
 $v = 3 \sin(\omega t - 10^\circ)$ } \Rightarrow The phase difference = $(100 + 10) = 110^\circ$

$\therefore i$ lead v by 110°

(e). $i = -\sin(\omega t + 30^\circ) = \sin(\omega t + 30^\circ + 180^\circ) = \sin(\omega t - 150^\circ)$
 $\therefore i = \sin(\omega t - 150^\circ)$
 $v = 2 \sin(\omega t + 10^\circ)$ } \Rightarrow The phase difference = $(150 + 10) = 160^\circ$

$\therefore v$ leads i by 160°

or $i = -\sin(\omega t + 30^\circ) = \sin(\omega t + 30^\circ + 180^\circ) = \sin(\omega t + 210^\circ)$
 $\therefore i = \sin(\omega t + 210^\circ)$
 $v = 2 \sin(\omega t + 10^\circ)$ } \Rightarrow The phase difference is 200°

$\therefore i$ lead v by 200°

(d). $i = -2 \cos(\omega t - 60^\circ) = 2 \cos(\omega t - 60^\circ - 180^\circ) = 2 \cos(\omega t - 240^\circ)$

$= 2 \sin(\omega t - 240^\circ + 90^\circ) = 2 \sin(\omega t - 150^\circ)$
 $v = 3 \sin(\omega t - 150^\circ)$ } \Rightarrow The phase diff. = 0°

v and i are in phase

Circuit Elements in the Phasor Domain

⊕ AC Through Pure Ohmic Resistor Alone


In the cct. shown, let the applied voltage be given by:

$$e = E_m \sin \omega t = E_m \sin \theta$$


$$\therefore i = \frac{e}{R} = \frac{E_m}{R} \sin \omega t$$

$$\therefore i = I_m \sin \omega t$$

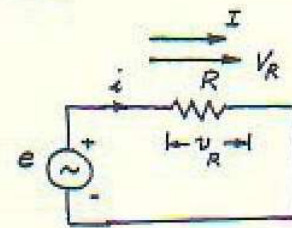
and
$$v_R = iR = I_m R \sin \omega t = V_m \sin \omega t$$



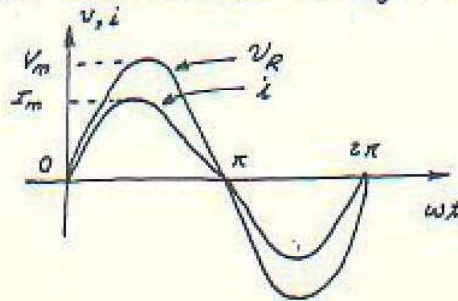⊕ In resistors, the current and voltage are **in phase**




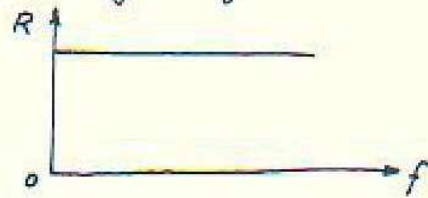- * The frequency response of the resistive load is uniform, i.e., the value of the resistance doesn't change as the frequency changes.



* The Average Power (Real Power)

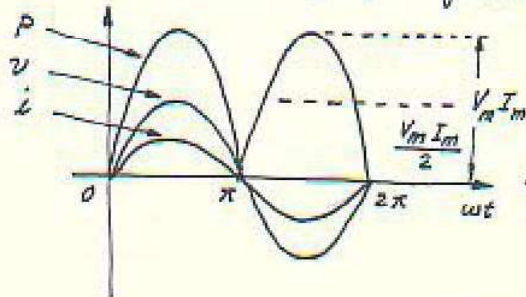: The instantaneous power to the resistive load is given by :



$$p = v i$$

$$= V_m I_m \sin^2 \omega t = V_m I_m \frac{(1 - \cos 2\omega t)}{2}$$

$$\therefore p = \underbrace{\frac{V_m I_m}{2}}_{\text{constant term}} - \underbrace{\frac{V_m I_m}{2} \cos 2\omega t}_{\text{Time varying term with average value = 0}}$$



$$\therefore P_{av} = P = \frac{V_m I_m}{2}$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$= V_{rms} I_{rms} = V_{eff} I_{eff}$$

$$\text{or } P_{av} = P = V_{rms} I_{rms}$$

- * The Power factor is defined as the cosine of the phase angle between the voltage and current, i.e.,

$$\text{Power factor} = P.f = F_p = \cos \phi$$

where ϕ is the phase difference angle between i and v . Since the voltage and current are in phase (i.e., the phase difference = 0), then; $\phi = 0$

$$\therefore \cos \phi = \cos 0^\circ = 1$$

$$\Rightarrow \text{power factor} = 1$$

\Rightarrow For resistive load only.

⊛ AC Through Pure Inductance Alone

EEG


$$v_L = L \frac{di}{dt}$$

If the current i is given by:

$$i = I_m \sin \omega t$$

$$\Rightarrow v_L = L \cdot \frac{d}{dt} (I_m \sin \omega t) = \omega L I_m \cos \omega t$$
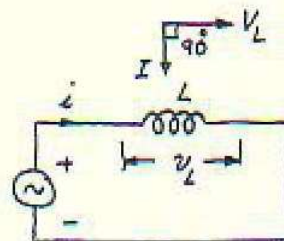
$$\text{or } v_L = V_m \cos \omega t = V_m \sin(\omega t + 90^\circ) \quad \Leftarrow V_m = \omega L I_m$$



From the equations of i and v_L , it is clear that v_L lead i by an angle of (90°) , or the current i lags v_L by (90°) .

- Let us define the reactance of an inductor, in a way similar to Ohm's law:

$$\text{Reactance} = \frac{\text{Cause}}{\text{Effect}} = \frac{\text{Voltage}}{\text{Current}}$$


$$\therefore \text{Reactance of an inductor} = X_L = \frac{V_m}{I_m} = \frac{\omega L I_m}{I_m} = \omega L$$

$$\therefore X_L = \omega L$$

* The frequency response of the pure inductor is derived from the relation:

$$X_L = \omega L = 2\pi f L$$

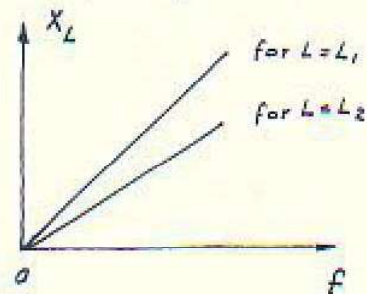and is shown in the figure. X_L increases as the frequency is increased in a linear relationship.



Power factor

: The power factor $p.f = \cos \phi$
since $\phi = 90^\circ$

$$\Rightarrow \therefore p.f = \cos 90^\circ = 0$$

The average power

: The instantaneous power for the pure inductive circuit is:


$$p = v_L i$$

$$\Rightarrow p = v_L \cdot i = V_m I_m \sin \omega t \cdot \sin(\omega t + 90^\circ)$$

EEG

$$\therefore p = \frac{V_m I_m}{2} \sin 2\omega t$$

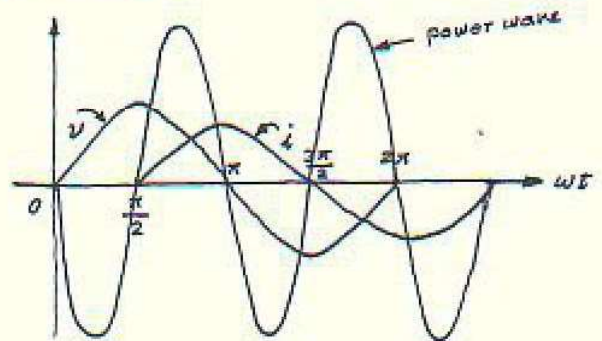The average value of p is zero $\Rightarrow P_{av} = 0$



* AC Through a Pure Capacitor


For the capacitor of the figure shown:

$$i_c = C \frac{dv_c}{dt}$$

$$\text{Let } v_c = V_m \sin \omega t$$

$$\therefore i_c = C \frac{d}{dt} (V_m \sin \omega t)$$
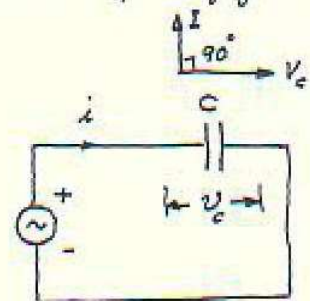
$$\Rightarrow i_c = \omega C V_m \cos \omega t = \omega C V_m \sin(\omega t + 90^\circ) = I_m \sin(\omega t + 90^\circ)$$



It is clear, from the equations of i_c and v_c , that i_c leads v_c by an angle of 90° or v_c lags i_c by 90°


* The capacitive reactance (X_c) is:

$$X_c = \frac{V_m}{I_m} = \frac{V_m}{\omega C V_m} = \frac{1}{\omega C}$$

$$\therefore X_c = \frac{1}{\omega C}$$

* The frequency response of a pure capacitor is derived from the relation above and is shown in the figure.

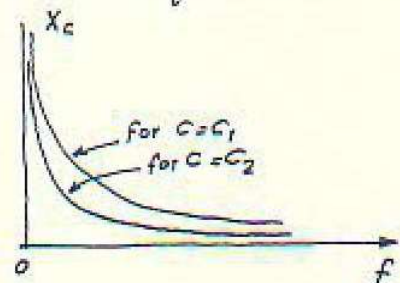X_c is decreasing as the frequency is increased in a non-linear behaviour.



* Power factor

EE6

Since the phase difference between i_c and v_c is 90° , this means that $\phi = 90^\circ$, then:

$$p.f = \cos \phi = \cos 90^\circ = 0$$

* The average power


The instantaneous power p is given as:

$$p = v_c i_c = V_m I_m \sin \omega t \sin(\omega t + 90^\circ)$$

$$\Rightarrow p = \frac{V_m I_m}{2} \sin 2\omega t$$

This quantity has an average value of zero

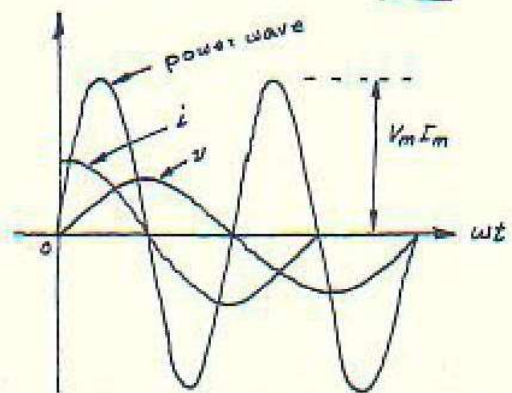\therefore The average power of a pure capacitive load is zero.




Summary of AC parameters for R, L & C

Element Parameter	R	L	C
Power factor $\cos \phi$	1	0	0
Average Power $P_{av} = P$	$\frac{V_m I_m}{2} = V_{rms} I_{rms}$	0	0
Impedance Z	R	$X_L = \omega L$	$X_C = \frac{1}{\omega C}$
Phase difference ϕ between v & i	0	90° v_L leads i_L or i_L lags v_L	90° v_C lags i_C or i_C leads v_C
Frequency Response	Uniform (constant)	Linear (Increasing)	Non-linear (Decreasing)

Complex Numbers

EE6

Complex Numbers: A complex number is a number that represents a point in a two dimensional plane located with reference to two distinct axes. It defines a vector drawn from the origin to that point. The plane used to represent complex numbers is called the complex plane; the two axes are called the real and imaginary. It is important that the scale on the axis of imaginaries must be the same as that on the axis of reals.

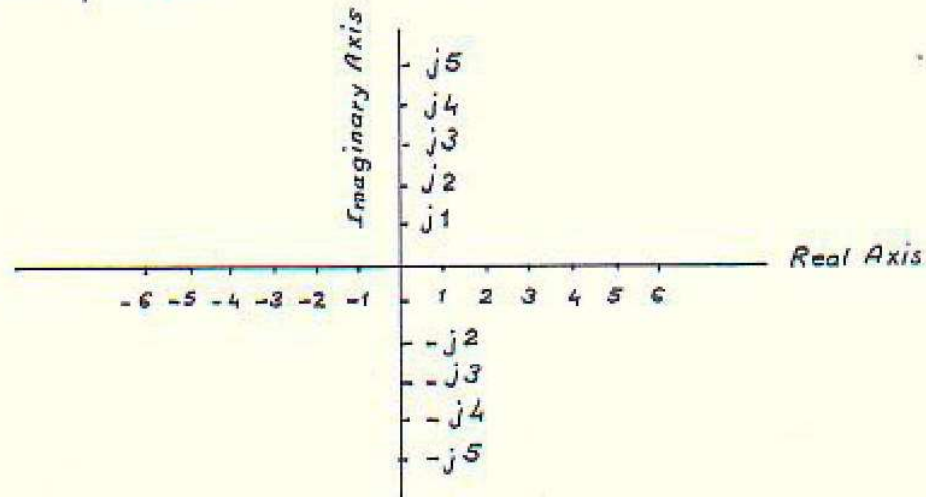

The complex plane

Complex numbers can be represented in the following forms:

- | | |
|-----------------------|---|
| 1. Rectangular form | $\Rightarrow \bar{E} = a + jb$ |
| 2. Polar form | $\Rightarrow \bar{E} = E_m \angle \phi$ |
| 3. Trigonometric form | $\Rightarrow \bar{E} = E_m (\cos \phi + j \sin \phi)$ |
| 4. Exponential form | $\Rightarrow \bar{E} = E_m e^{j\phi}$ |

* Rectangular form

: It is customary in this form to denote the complex numbers as:

$$\bar{Z} = R + jX$$


where; \bar{Z} is the complex number.

R is the real part.

X is the imaginary part.

j is an operator $= \sqrt{-1}$ and is equivalent to 90° phase angle.

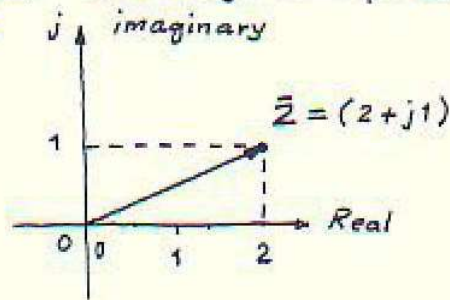For example, the complex number $\bar{Z} = 2 + j1$ is represented EE6 in the complex plane as shown:



Mathematical Operations in the Rectangular Form:

* Equality

If we have two complex numbers $Z = x + jy$ and $\bar{W} = u + jv$, then if $\bar{Z} = \bar{W}$, then it follows that $x = u$ and $y = v$

Example

Given that $\bar{Z}_1 = 5 + j10$, and $Z_2 = 5 + jX$. If $\bar{Z}_1 = \bar{Z}_2$, find the value of X

Solution

$X = 10$

* Addition and Subtraction


The sum of two complex numbers has a real number equal to the sum of the real components and an imaginary number equal to the sum of the imaginary components.

Example

Given $\bar{Z}_1 = (2 + j3)$, and $\bar{Z}_2 = (4 + j1)$. Find \bar{Z}_T , if $\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2$.

Solution
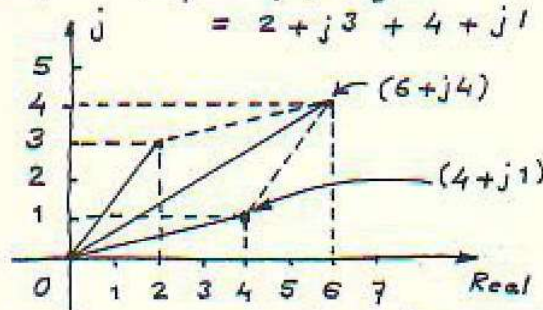
$$\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 = 2 + j3 + 4 + j1 = 6 + j4$$



The parallelogram method is used for adding and subtraction of quantities in the complex plane.

* Multiplication

EE6

- The product of a real and imaginary number is imaginary; Thus:

$$2(j3) = j6$$

- The product of two positive imaginary numbers is real and negative, thus:

$$(j2)(j3) = -6$$

and

$$(j3)(-j4) = +12$$

$$\text{since } (j)(j) = -1$$

Complex numbers are multiplied by the ordinary rules of algebra.
As an example;

$$\begin{aligned}(2 + j3)(4 + j1) &= (2)(4) + (2)(j1) + (j3)(4) + (j3)(j1) \\ &= 8 + j2 + j12 - 3 = 5 + j14\end{aligned}$$

In general;

$$(a + jb)(c + jd) = (ac - bd) + j(ad + bc)$$

* Division

By way of illustration, let us consider the division of $\bar{V} = (5 + j10)$ by $\bar{I} = (2 + j1)$.

$$\Rightarrow \frac{5 + j10}{2 + j1}$$

* The first step

is to multiply both numerator and denominator by $(2 - j1)$ which is called complex conjugate of the denominator and usually denoted by asterisk,

$$\bar{I} = 2 + j1$$

$$\bar{I}^* = 2 - j1 \leftarrow \text{complex conjugate of } \bar{I}.$$

$$(\bar{I})(\bar{I}^*) = \text{Real value}$$

$$\text{then; for } \frac{5 + j10}{2 + j1} = \frac{(5 + j10)(2 - j1)}{(2 + j1)(2 - j1)} = \frac{20 + j15}{5}$$

$$\therefore \frac{5 + j10}{2 + j1} = 4 + j3$$

$$\text{In general: } \frac{a + jb}{c + jd} = \frac{ac + bd}{c^2 + d^2} + j \frac{bc - ad}{c^2 + d^2}$$

* The j operator

EEG

$$j = \sqrt{-1} \Rightarrow 90^\circ \text{ ccw rotation}$$

$$j^2 = -1 \Rightarrow 180^\circ \text{ ccw rotation}$$

$$j^3 = j^2 \cdot j = -j \Rightarrow 270^\circ \text{ ccw rotation}$$

$$j^4 = j^2 \cdot j^2 = +1 \Rightarrow 360^\circ \text{ ccw rotation}$$

and we have also:


$$\frac{1}{j} = -j$$

Polar Form

In this form, the complex number is represented as


$$\bar{C} = C \angle \phi$$

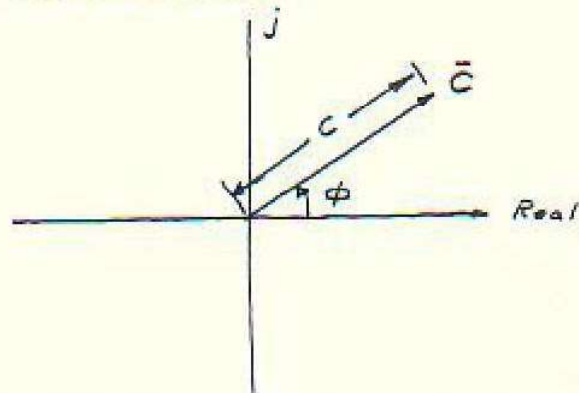where C is the magnitude only, and ϕ is always measured counter-clockwise



* A negative sign has the effect shown in the figure
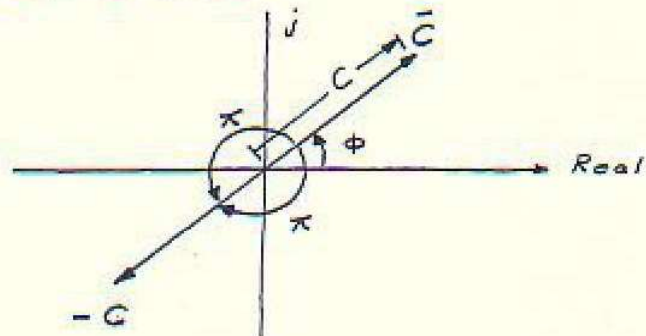
$$-\bar{C} = -C \angle \phi = C \angle \phi \mp \pi$$




Example

Sketch the following complex numbers in the complex plane.

- a. $\bar{A} = 5 \angle 30^\circ$
- $\bar{B} = 3.7 \angle 120^\circ$
- $\bar{C} = -4.2 \angle 60^\circ$

Solution

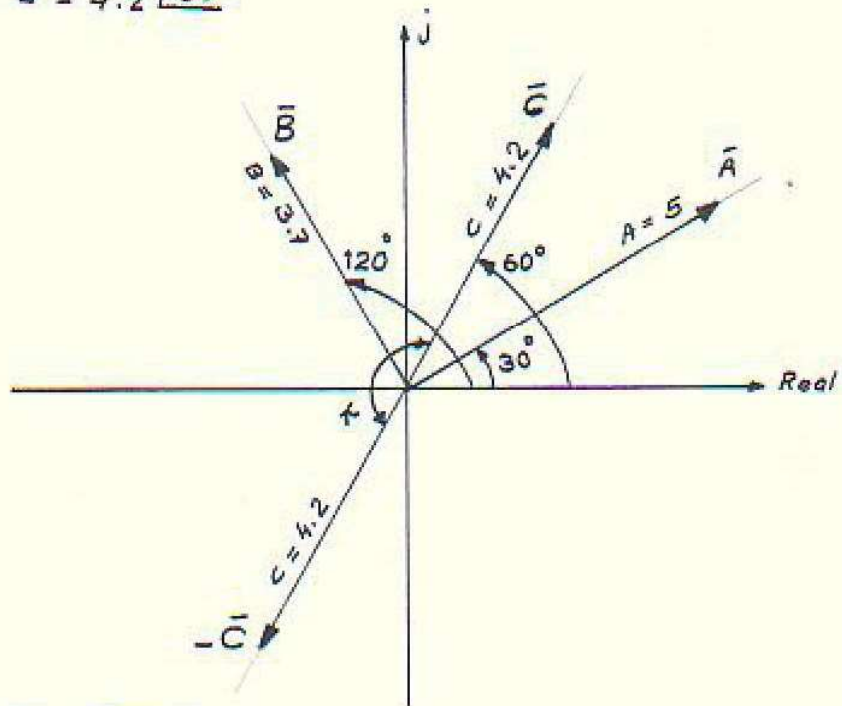

Conversion Between Forms

* Rectangular to Polar


Example

Convert the following from rectangular to polar form.

$\bar{C} = 3 + j4$

The magnitude $C = \sqrt{3^2 + 4^2} = 5$

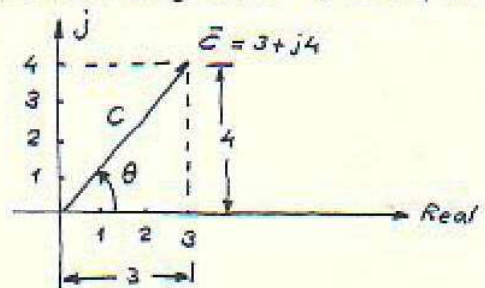The angle $\phi = \tan^{-1}\left(\frac{4}{3}\right) = 53.13^\circ$



$\therefore \bar{C}$ in the polar form is $\bar{C} = 5 \angle 53.13^\circ$

* Polar to Rectangular


Example

convert the following from polar to rectangular form:

$\bar{C} = 10 \angle 45^\circ$

$\bar{C} = \text{Real} + j \text{Imaginary}$

$\therefore \bar{C} = 7.07 + j 7.07$

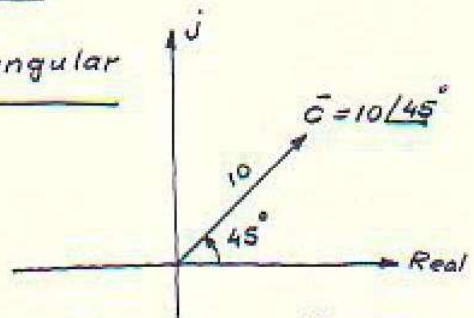

$\text{Real} = 10 \cos 45^\circ = 7.07$

$\text{Imaginary} = 10 \sin 45^\circ = 7.07$

Example

EEG

_____ : Convert the following from rectangular to polar form.

$$\bar{C} = -6 + j3$$

Solution

_____ : $C = \sqrt{(-6)^2 + (3)^2} = \sqrt{45} = 6.71$


$$\theta = \tan^{-1}\left(\frac{3}{6}\right)$$

$$= 26.57^\circ$$

$$\Rightarrow \phi = 180^\circ - 26.57^\circ$$
$$= 153.43^\circ$$

\(\therefore \bar{C}\) in polar form is:
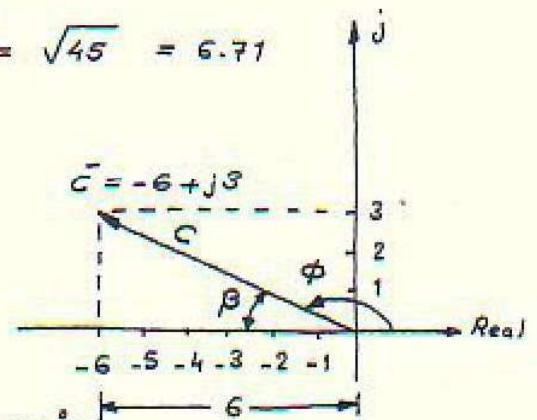
$$\bar{C} = C \angle \phi = 6.71 \angle 153.43^\circ$$



Example

_____ : Convert from polar to rectangular form.

$$\bar{C} = 10 \angle 230^\circ$$

Solution


_____ :

$$A = 10 \cos \beta$$
$$= 10 \cos (230^\circ - 180^\circ)$$
$$= 10 \cos 50^\circ$$
$$= 6.428$$

$$B = 10 \sin \beta$$
$$= 10 \sin (230^\circ - 150^\circ)$$
$$= 10 \sin 50^\circ$$
$$= 7.66$$

\(\therefore \bar{C}\) in rectangular form is

$$\bar{C} = -6.428 - j 7.66$$

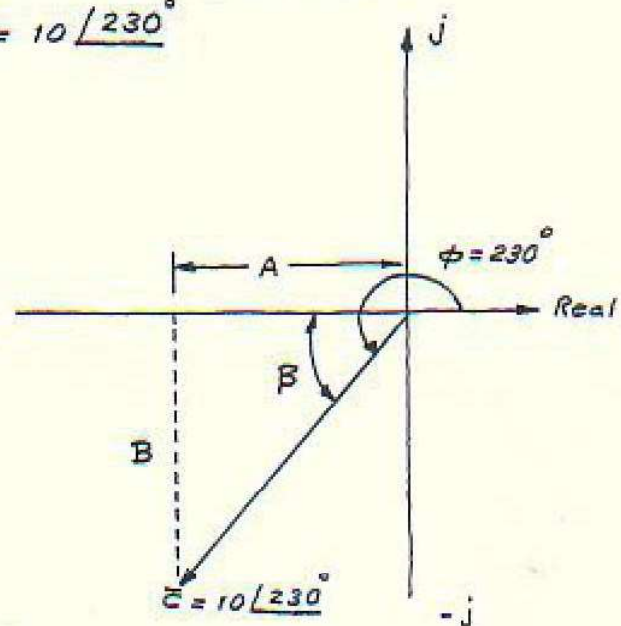


Mathematical Operations in the Polar Form

EE6


* Addition and Subtraction

_____ : Addition or subtraction cannot be performed in polar form unless the complex numbers have the same angle ϕ or differ only by multiples of 180°
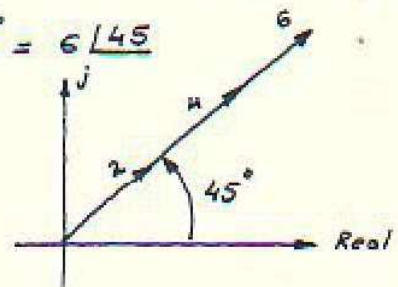
$$\text{Ex: } 2 \angle 45^\circ + 4 \angle 45^\circ = 6 \angle 45^\circ$$


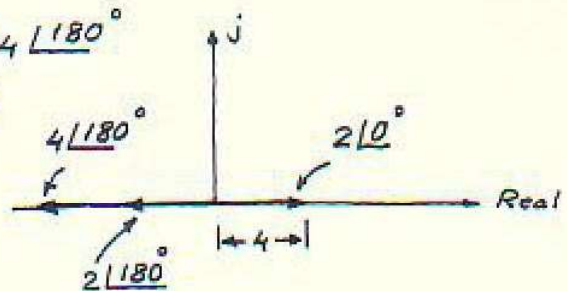
$$\text{Ex: } 2 \angle 0^\circ + 4 \angle 180^\circ = 2 \angle 180^\circ$$



* Multiplication

_____ If we have two complex numbers

$$\bar{C}_1 = C_1 \angle \phi_1$$

$$\bar{C}_2 = C_2 \angle \phi_2$$

$$\text{Then } \bar{C}_1 \cdot \bar{C}_2 = C_1 C_2 \angle \phi_1 + \phi_2$$

$$\text{Ex: Find } \bar{C}_1 \bar{C}_2, \text{ if } \bar{C}_1 = 5 \angle 20^\circ, \text{ and } \bar{C}_2 = -10 \angle 30^\circ$$

$$\bar{C}_1 \bar{C}_2 = (5)(-10) \angle 20^\circ + 30^\circ = \underline{\underline{-50 \angle 50^\circ}}$$

* Division

_____ : If we have two complex numbers

$$\bar{C}_1 = C_1 \angle \phi_1 \text{ and } \bar{C}_2 = C_2 \angle \phi_2,$$

$$\text{Then } \frac{\bar{C}_1}{\bar{C}_2} = \frac{C_1}{C_2} \angle \phi_1 - \phi_2$$

$$\text{Ex: Given } \bar{C}_1 = 15 \angle 10^\circ \text{ and } \bar{C}_2 = 2 \angle 7^\circ, \text{ find } \frac{\bar{C}_1}{\bar{C}_2}$$

$$\frac{C_1}{C_2} = \frac{15}{2} \angle 10^\circ - 7^\circ = \underline{\underline{7.5 \angle 3^\circ}}$$


1 Series AC Circuits

1.1 AC Through R and L

Consider the circuit shown below;

V = the rms value of the applied voltage.

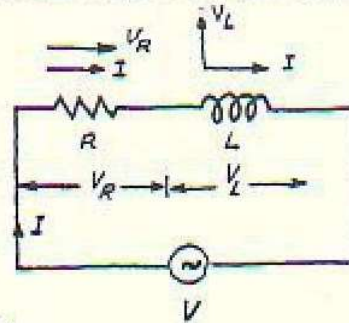I = the rms value of the resultant current.



$$\vec{V} = \vec{V}_R + \vec{V}_L$$

$$\Rightarrow V_R = IR \quad (\text{in phase with } I)$$


$$V_L = IX_L \quad (\text{leading } I \text{ by } 90^\circ)$$

The vector diagram for these voltage drops can be obtained as:

$$\Rightarrow V = \sqrt{V_R^2 + V_L^2}$$

$$= \sqrt{(IR)^2 + (IX_L)^2}$$

$$= I\sqrt{R^2 + X_L^2}$$

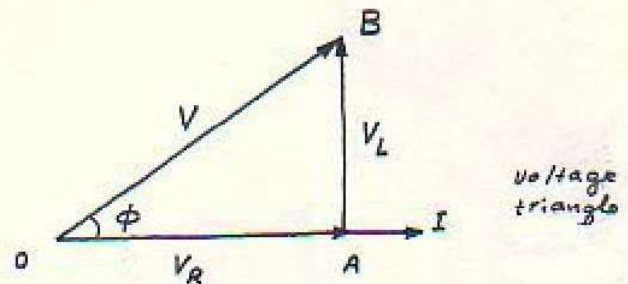

$$\Rightarrow I = \frac{V}{\sqrt{R^2 + X_L^2}} = \frac{V}{Z_T}$$

* The phase difference angle ϕ can be determined as:


$$\tan \phi = \frac{V_L}{V_R} = \frac{IX_L}{IR} = \frac{\omega L}{R}$$

$$\therefore \phi = \tan^{-1} \frac{X_L}{R}$$

Z is known as the impedance of the circuit

$$Z_T = \sqrt{R^2 + X_L^2}$$

$$Z_T^2 = R^2 + X_L^2$$

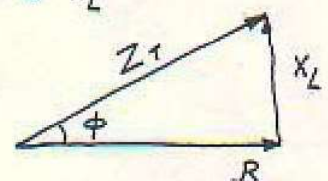

Impedance triangle


It is clear that the current I lags behind the applied voltage V by an angle (ϕ).

$$\cos \phi = \frac{R}{Z_T}$$

* In phasor notation

$$\begin{aligned}\bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 \\ &= R \angle 0^\circ + X_L \angle 90^\circ\end{aligned}$$

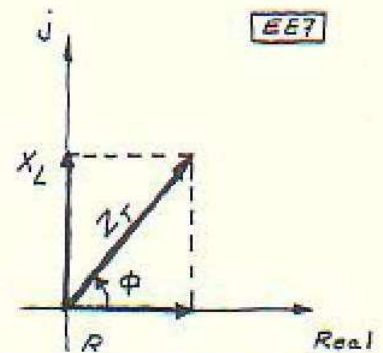
$$\Rightarrow \therefore \bar{Z}_T = R + jX_L$$



Impedance diagram

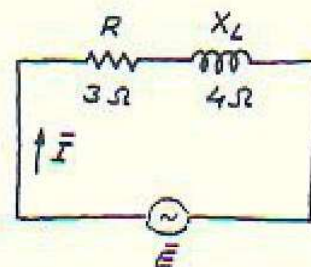Example

For the circuit shown, determine the total impedance and draw the impedance diagram




Solution

$$\begin{aligned}\bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 = R \angle 0^\circ + X_L \angle 90^\circ = R + jX_L \\ &= 3 + j4\end{aligned}$$

$$\Rightarrow \therefore \bar{Z}_T = 5 \angle 53.13^\circ$$

Note that, the angle ϕ ($= 53.13^\circ$ in this example) is always positive in the impedance diagram.
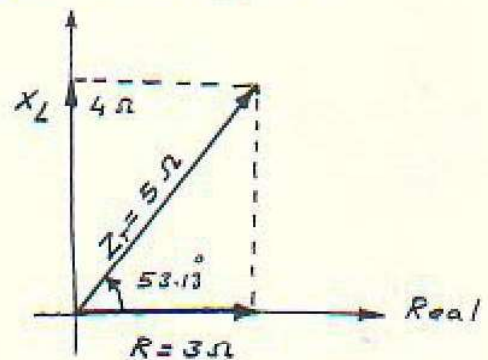
$$\begin{aligned}\phi &= \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{4}{3} \\ &= 53.13^\circ\end{aligned}$$



* Active, Reactive and Apparent Power
(The Power Triangle)

EE7

* The Apparent Power

: It is the product of the rms values of the applied voltage and the circuit current

$$\Rightarrow \text{Apparent power} = S = VI = (IZ) \cdot I = I^2 Z$$

وحدات
volt-amperes (VA)

* The Active Power

: It is the power which is actually dissipated in the circuit resistance.

$$\Rightarrow \text{Active power} = P = I^2 R = VI \cos \phi \quad \text{watts (W)}$$

* The Reactive Power

: It is the power developed in the inductive reactance of the circuit.

$$\Rightarrow \text{Reactive Power} = Q = I^2 X_L = I^2 (Z \sin \phi)$$

$$\therefore Q = VI \sin \phi$$


وحدات
Volt-amper reactive (VAR)

These three powers are shown in the power triangle:
From the power triangle:

$$S^2 = P^2 + Q^2$$

or


$$S = \sqrt{P^2 + Q^2}$$

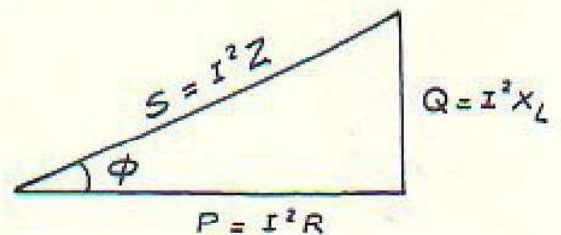

The power triangle

* The quality factor of the Coil

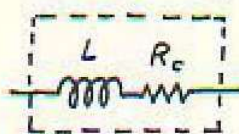: It is defined as the reciprocal of the power factor of the coil. Hence:



coil


$$\Rightarrow Q \text{ factor} = \frac{1}{\text{power factor}} = \frac{1}{\cos \phi} = \frac{Z}{R_c} = \frac{\sqrt{R_c^2 + X_L^2}}{R_c}$$

if R_c is too small compared with X_L , then:

$$Q \text{ factor} = \frac{X_L}{R_c}$$

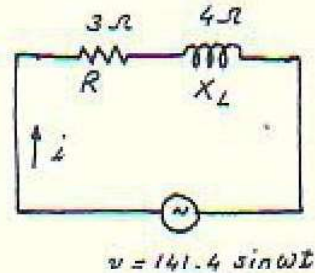Example

For the circuit shown, draw the phasor diagram of the voltages across each element and the applied voltage, and determine :-
 - The power factor.
 - The active and reactive power.
 - The apparent power.



Solution

* $\therefore v = 141.4 \sin \omega t \Rightarrow \vec{V} = 100 \angle 0^\circ$

* $\vec{Z}_T = \vec{Z}_1 + \vec{Z}_2 = R + jX_L$
 $= 3 + j4$
 $= 5 \angle 53.13^\circ$

* The current $\vec{I} \Rightarrow \vec{I} = \frac{\vec{V}}{\vec{Z}_T}$
 $\therefore \vec{I} = \frac{100 \angle 0^\circ}{5 \angle 53.13^\circ} = 20 \angle -53.13^\circ$

* The voltage drops \vec{V}_R and \vec{V}_L :

$\vec{V} = \vec{V}_R + \vec{V}_L$

$\therefore \vec{V} = 36 - j48 + 64 - j48$
 $= 100$
 $= 100 \angle 0^\circ$

$\Rightarrow \vec{V}_R = \vec{I}R = (20 \angle -53.13^\circ)(3)$
 $= 60 \angle -53.13^\circ$
 $= 36 - j48$


$\Leftarrow \vec{V}_L = \vec{I}X_L = (20 \angle -53.13^\circ)(4 \angle 90^\circ)$
 $= 80 \angle 36.87^\circ$
 $= 64 + j48$

كما في الصورة يلاحظ

* The phasor diagram



* Powers

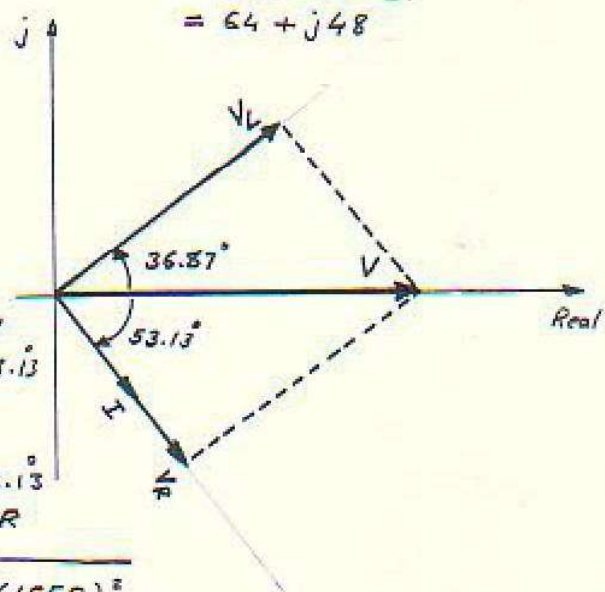

active power (real) (average)

$P = I^2 R = (20)^2 (3) = 1200 \text{ W}$
 or $P = VI \cos \phi = (100)(20) \cos 53.13^\circ$
 $= 1200 \text{ W} = 1.2 \text{ kW}$

reactive power

$Q = VI \sin \phi = (100)(20) \sin 53.13^\circ$
 $= 1600 \text{ VAR} = 1.6 \text{ kVAR}$

$S = \sqrt{P^2 + Q^2} = \sqrt{(1200)^2 + (1600)^2}$
 $= 1968 \text{ VA} = 1.968 \text{ kVA}$

* The power factor :

$P.f = \cos \phi = \cos 53.13^\circ = 0.6 \text{ lagging}$

اعتقاداً على التيار بالنسبة في التوليد

1.2 AC Through R and C

Consider the circuit shown, where

V = rms value of the applied voltage.
 I = rms value of the resultant current.

$$V_R = IR \quad (\text{in phase with } I)$$

$$V_C = IX_C \quad (\text{lagging } I \text{ by } 90^\circ)$$

* In Vector Notations:

$$\begin{aligned} \bar{V} &= \sqrt{\bar{V}_R^2 + \bar{V}_C^2} \\ &= \sqrt{I^2 R^2 + I^2 X_C^2} \\ &= I \sqrt{R^2 + X_C^2} \end{aligned}$$

$$\text{or } I = \frac{V}{\sqrt{R^2 + X_C^2}} = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \frac{X_C}{R}$$

$$\therefore \text{p.f.} = \cos \phi = \frac{R}{Z}$$

It is clear that I lead V by an angle ϕ . Hence if:

$$v = V_m \sin \omega t$$

then:

$$i = I_m \sin(\omega t + \phi)$$

so that the current i lead the applied voltage v by an angle ϕ , and

$$v_R = I_m R \sin(\omega t + \phi)$$

$$v_C = I_m X_C \sin(\omega t + \phi - 90^\circ)$$





⊙ The phasor diagram of the voltages of the series RC circuit can be as shown:

$$\bar{V} = V \angle 0$$

$$\bar{I} = I \angle \phi$$

$$\bar{V}_R = V_R \angle \phi$$
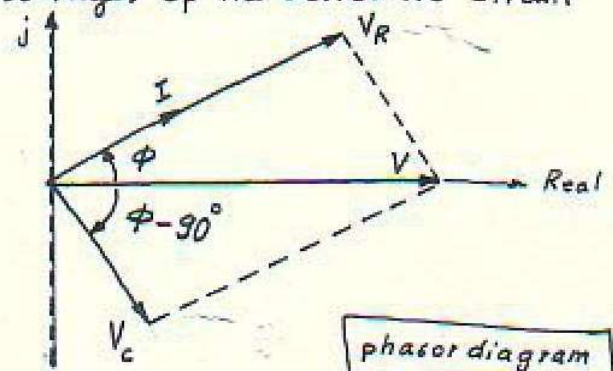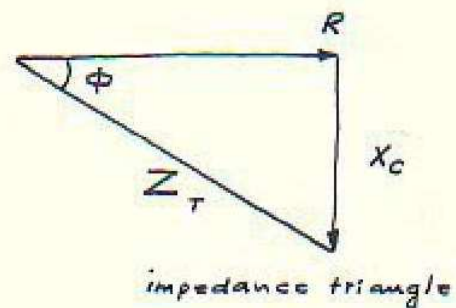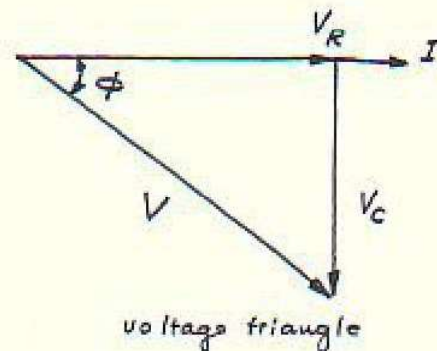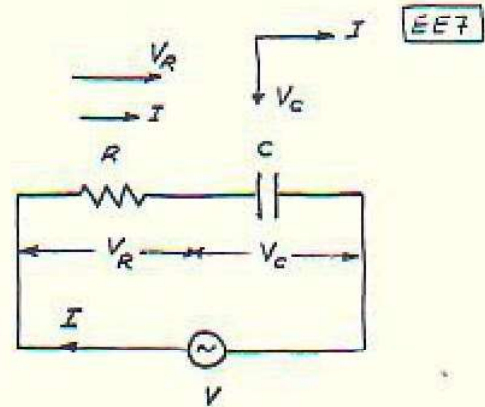
$$\bar{V}_C = V_C \angle \phi - 90^\circ$$



* The impedance diagram


EE?

in phasor notation

$$\begin{aligned}\bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 = R \angle 0^\circ + X_C \angle -90^\circ \\ &= R - jX_C\end{aligned}$$

$$\begin{aligned}\therefore \bar{Z}_T &= \sqrt{R^2 + X_C^2} \\ &= Z_T \angle \phi\end{aligned}$$

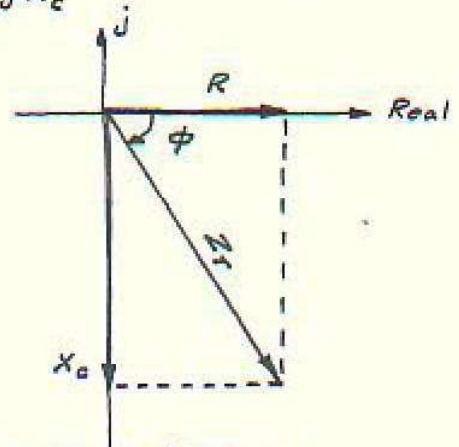
⇒ Note that ϕ is always negative for RC circuits.



Example

For the circuit shown, draw the phasor diagram.

$$R = 6\Omega \quad X_C = 8\Omega$$

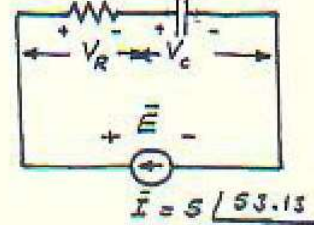

Solution

$$\begin{aligned}\bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 \\ &= 6 \angle 0^\circ + 8 \angle -90^\circ \\ &= 6 - j8 = 10 \angle -53.13^\circ\end{aligned}$$

* \bar{E} ?

$$\begin{aligned}\bar{E} &= \bar{I} \bar{Z}_T = (5 \angle 53.13^\circ)(10 \angle -53.13^\circ) \\ &= 50 \angle 0^\circ\end{aligned}$$

* \bar{V}_R ?

$$\begin{aligned}\bar{V}_R &= \bar{I} R = (5 \angle 53.13^\circ)(6) \\ &= 30 \angle 53.13^\circ\end{aligned}$$


* \bar{V}_C ?

$$\begin{aligned}\bar{V}_C &= \bar{I} X_C = (5 \angle 53.13^\circ)(8 \angle -90^\circ) \\ &= 40 \angle -36.87^\circ\end{aligned}$$

* you can find that:

$$\bar{E} = \bar{V}_R + \bar{V}_C$$

using the above values.

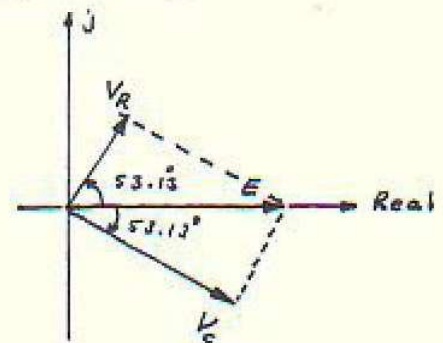

* Similarly, as in the case of series RL circuit, the active (average or true) power, reactive power can be determined.

* The active power P is

$$P = VI \cos \phi$$

$$P = I^2 R$$

* The reactive power Q is:

$$Q = VI \sin \phi$$


$$Q = I^2 X_c$$

* and the apparent power $S = \sqrt{P^2 + Q^2}$

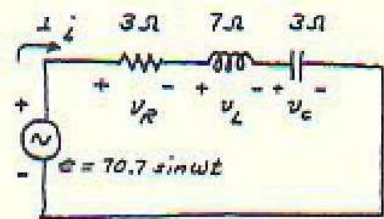Example

_____ : For the circuit shown, determine :

- \bar{Z}_T , and draw the impedance diagram.
- \bar{I} , \bar{V}_R , \bar{V}_L , \bar{V}_C in the phasor domain, and draw the phasor diagram.
- i , v_R , v_L , v_C in the time domain.
- The power factor of the circuit.
- The active, reactive and the apparent powers.



Solution

_____ : In phasor notation the circuit is redrawn as :

$$\begin{aligned} * \quad \bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3 \\ &= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\ &= 3 + j7 - j3 \\ &= 3 + j4 \end{aligned}$$

$$\therefore \bar{Z}_T = 5 \angle 53.13^\circ$$



* The impedance diagram is \Rightarrow

$$\bar{I} = \frac{\bar{E}}{\bar{Z}} = \frac{50 \angle 0^\circ}{5 \angle 53.13^\circ} = 10 \angle -53.13^\circ$$


$$\begin{aligned} \bar{V}_R &= \bar{I}R = (10 \angle -53.13^\circ)(3 \angle 0^\circ) \\ &= 30 \angle -53.13^\circ \end{aligned}$$

$$\begin{aligned} \bar{V}_L &= \bar{I}X_L = (10 \angle -53.13^\circ)(7 \angle 90^\circ) \\ &= 70 \angle 36.87^\circ \end{aligned}$$
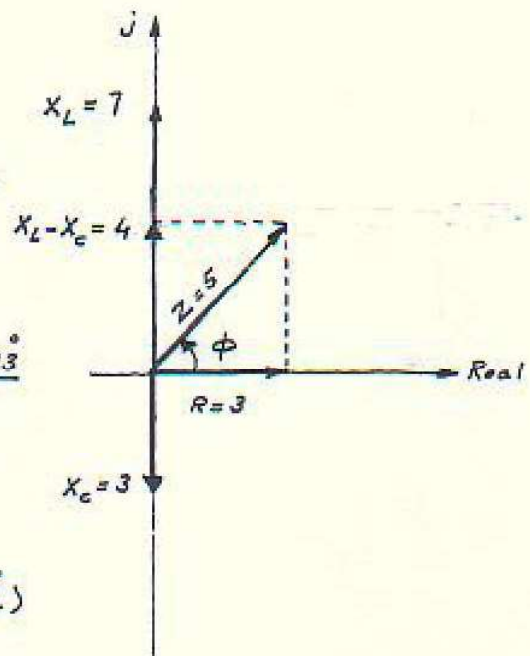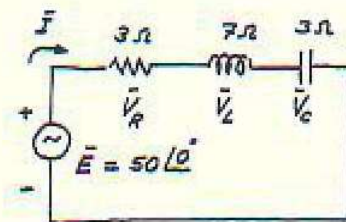
$$\begin{aligned} \bar{V}_C &= \bar{I}X_C = (10 \angle -53.13^\circ)(3 \angle -90^\circ) \\ &= 30 \angle -143.13^\circ \end{aligned}$$



* The phasor diagram

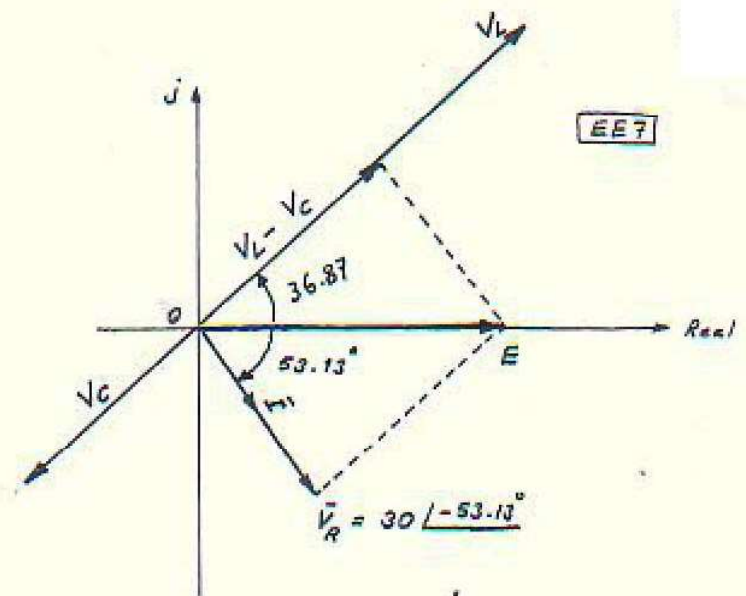

* The time domain

$$\begin{aligned}
 i &= \sqrt{2} (10) \sin(\omega t - 53.13^\circ) = 14.14 \sin(\omega t - 53.13^\circ) \\
 v_R &= \sqrt{2} (30) \sin(\omega t - 53.13^\circ) = 42.42 \sin(\omega t - 53.13^\circ) \\
 v_L &= \sqrt{2} (70) \sin(\omega t + 36.87^\circ) = 98.98 \sin(\omega t + 36.87^\circ) \\
 v_C &= \sqrt{2} (30) \sin(\omega t - 143.13^\circ) = 42.42 \sin(\omega t - 143.13^\circ)
 \end{aligned}$$

* The total power

$$P_T = VI \cos \phi = (50)(10) \cos 53.13^\circ = \underline{300 \text{ W}}$$

$$\text{or } P_T = I^2 R = (10)^2 (3) = \underline{300 \text{ W}}$$

from the voltage phasor diagram \Rightarrow * The power factor

$$\begin{aligned}
 \text{p.f.} &= \cos \phi = \cos 53.13^\circ \\
 &= \underline{0.6 \text{ lagging}}
 \end{aligned}$$

$$\text{or } \text{p.f.} = \cos \phi = \frac{R}{Z_T} = \frac{3}{5} = 0.6 \text{ lagging}$$

P \Rightarrow * Active power = true power = $VI \cos \phi = (50)(10) \cos 53.13^\circ = 300 \text{ W}$


Q \Rightarrow Reactive power = $Q = VI \sin \phi = (50)(10) \sin 53.13^\circ = 400 \text{ VAR}$

S \Rightarrow Apparent power = $S = \sqrt{P^2 + Q^2} = \sqrt{(300)^2 + (400)^2} = 500 \text{ VA}$

\therefore The power triangle


$$\bar{S} = P + jQ$$

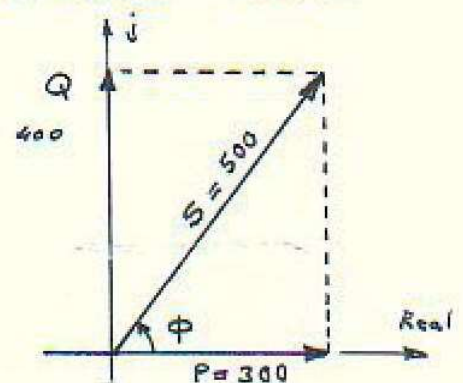$\bar{S} \Rightarrow$ Complex apparent power.



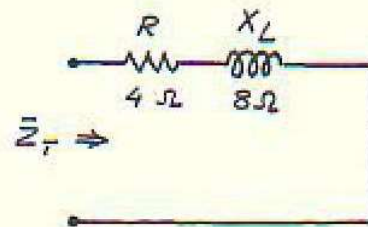Example

: Draw the impedance diagram for the circuit shown and find the total impedance.




Solution

$$\vec{Z}_T = \vec{Z}_1 + \vec{Z}_2$$

$$= R \angle 0^\circ + X_L \angle 90^\circ = R + jX_L = 4 + j8$$
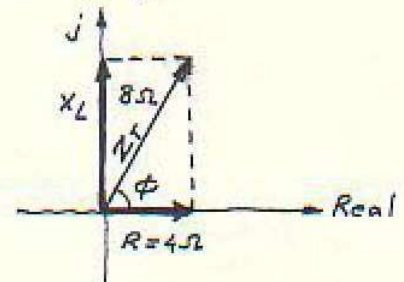
$$\therefore \vec{Z}_T = 8.944 \angle 63.43^\circ \Omega$$



Example

: Determine the input impedance to the series network shown

Solution

$$\vec{Z}_T = \vec{Z}_1 + \vec{Z}_2 + \vec{Z}_3$$

$$= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ$$


$$= R + jX_L - jX_C$$

$$= R + j(X_L - X_C)$$

$$= 6 + j(10 - 12)$$

$$= 6 - j2$$
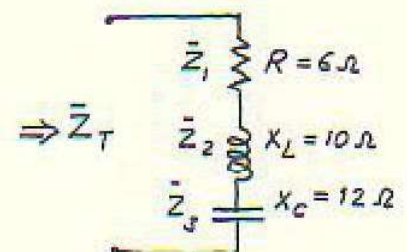
$$\Rightarrow \vec{Z}_T = 6.325 \angle -18.43^\circ \Omega$$




Example

_____ : A 60 Hz sinusoidal voltage ($v = 141 \sin \omega t$) is applied to a series R-L circuit. The values of the resistance and the inductance are 3Ω and 0.0106 H respectively.

- (a). Compute the rms value of the current in the circuit and its phase angle with respect to the voltage.
- (b). Write the expression for the instantaneous current in the circuit.
- (c). Find the average power dissipated by the circuit.
- (d). Calculate the p.f of the circuit.

Solution

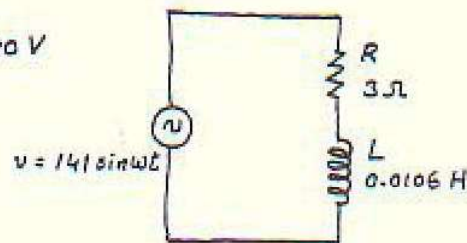_____ : We have ; $v = V_m \sin \omega t$
 $\Rightarrow V = \frac{V_m}{\sqrt{2}} = \frac{141}{\sqrt{2}} = 100 \text{ V}$
 $\therefore \bar{V} = 100 \angle 0$



(a). $\bar{I} = \frac{\bar{V}}{\bar{Z}}$

$$\begin{aligned} \bar{Z} &= R + jX_L \\ &= R + j(2\pi fL) \\ &= 3 + j(2\pi \times 60 \times 0.0106) \\ &= 3 + j4 \\ \therefore \bar{Z} &= 5 \angle 53.1^\circ \end{aligned}$$

$$\begin{aligned} \Rightarrow \bar{I} &= \frac{100 \angle 0}{20 \angle 53.1^\circ} \\ \therefore \bar{I} &= 20 \angle -53.1^\circ \end{aligned}$$

\Rightarrow the current lags the voltage by 53.1°

(b). $i = I_m \sin(\omega t - 53.1^\circ)$
 $= \sqrt{2}(20) \sin(\omega t - 53.1^\circ) = \underline{28.28 \sin(\omega t - 53.1^\circ)}$

(c). $P = VI \cos \phi$
 $= (100)(20) \cos 53.1^\circ = 1200 \text{ W}$
 or $P = I^2 R = (20)^2(3) = 1200 \text{ W}$

(d). p.f = $\cos \phi$
 $= \cos 53.1^\circ$
 $= 0.6$ lagging

Example

_____ : A two elements series circuit is connected across an ac circuit having a source ($e = \sqrt{2}(200) \sin(\omega t + 20^\circ) \text{ V}$). The current in the circuit is then found to be $i = \sqrt{2}(10) \cos(341t - 25^\circ)$. Determine the parameters of the circuit.

Solution

_____:

The applied voltage is:

$$v = \sqrt{2}(200)\sin(\omega t + 20^\circ)$$

$$\Rightarrow \bar{V} = 200 \angle 20^\circ$$

The current is:

$$i = \sqrt{2}(10)\cos(\omega t - 25^\circ)$$

$$= \sqrt{2}(10)\sin(\omega t - 25^\circ - 90^\circ)$$

$$\therefore i = \sqrt{2}(10)\sin(\omega t + 65^\circ)$$

$$\Rightarrow \bar{I} = 10 \angle 65^\circ$$

$$\Rightarrow \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{200 \angle 20^\circ}{10 \angle 65^\circ} = 20 \angle -45^\circ$$

$$= 14.14 - j 14.14$$

Note $\phi = -45^\circ$
(leading)

This impedance represents a series circuit with $R = 14.14 \Omega$ and a capacitive reactance (because of the $-j$) of $X_c = 14.14 \Omega$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

* من معادلة التيار
 $\omega = 314 \text{ rad/sec.}$

$$\therefore 14.14 = \frac{1}{314 C} \Rightarrow C = \frac{1}{(14.14)(314)} = 2.25 \times 10^{-4} \text{ F}$$

\therefore The circuit has $R = 14.14 \Omega$
and $C = 225 \mu\text{F}$

Example


_____:

Two coils A and B are connected in series across 240 V, 50 Hz supply. The resistance of A is 5Ω and the inductance of B is 0.015 H . If the input supply is 3 kW and 2 kVAR , find the resistance of B and the inductance of A. Calculate the voltage across each coil.

Solution

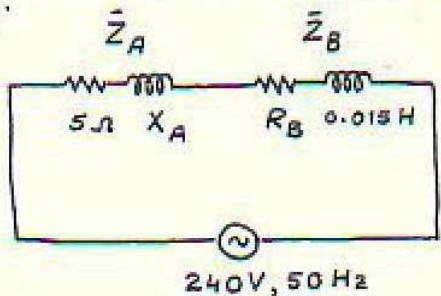_____:

* From the power triangle, and the circuit shown,



$$S = \sqrt{P^2 + Q^2} = \sqrt{3^2 + 2^2}$$

$$= 3.606 \text{ KVA}$$

$$S = VI \Rightarrow I = \frac{S}{V} = \frac{3606}{240} = 15.025 \text{ A}$$

$$\text{But, } P = 3 \text{ kW} = 3000 \text{ W}$$

$$= I^2 R_T = I^2 (R_A + R_B)$$

$$\therefore 3000 = (15.025)^2 (R_A + R_B)$$

$$\Rightarrow R_A + R_B = 13.3 \Omega$$

$$\therefore \text{Since } R_A = 5 \Omega \Rightarrow R_B = 13.3 - 5 = \underline{8.3 \Omega}$$

Similarly, we have:

مرفقة : مع إشكالية حل هذا المثال
بالكثير من طريقة والموصولة إلى
النتيجة نفسها .

$$Q = 2 \text{ kVAR} = 2000 \text{ VAR}$$
$$= I^2 X_{LT} = (15.03)^2 X_{LT}$$

$$\therefore X_{LT} = \frac{2000}{(15.03)^2} = 8.85 \Omega$$

$$X_{LT} = X_A + X_B \Rightarrow X_A = 8.85 - X_B$$
$$= 8.85 - (2\pi f L_B)$$
$$= 8.85 - (2\pi \times 50 \times 0.015)$$
$$= 8.85 - 4.713 = 4.13 \Omega$$

$$\therefore \bar{Z}_A = R_A + jX_A = 5 + j4.13 = 6.48 \angle 39.57^\circ$$

$$\text{and } \bar{Z}_B = R_B + jX_B = 8.3 + j4.713 = 9.54 \angle 29.59^\circ$$

$X_B = 2\pi f L_B$
 $= 2\pi \times 50 \times 0.015$

$$\therefore \bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 = 5 + j4.13 + 8.3 + j4.713$$
$$=$$

$$\therefore \bar{V}_A = \bar{I} \bar{Z}_A = \checkmark$$

$$\bar{V}_B = \bar{I} \bar{Z}_B = \checkmark$$

$$\text{or } \bar{V}_A = \frac{\bar{V} \bar{Z}_A}{\bar{Z}_A + \bar{Z}_B} = \checkmark$$

and


$$\bar{V}_B = \frac{\bar{V} \bar{Z}_B}{\bar{Z}_A + \bar{Z}_B} = \checkmark$$

The results must be the same.

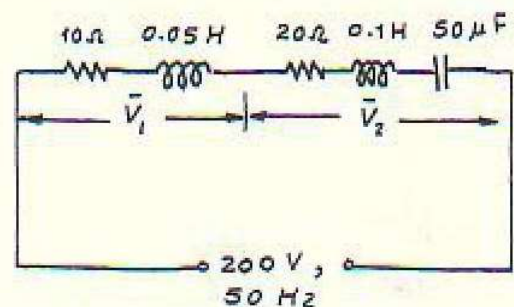Example

Draw the phasor diagram for the circuit shown, indicating the resistance and the reactance drop, the terminal voltages \bar{V}_1 and \bar{V}_2 and the current. Find the values of:

- The current \bar{I} .
- \bar{V}_1
- \bar{V}_2
- The power factor



Solution

$$R_T = 10 + 20 = 30 \Omega$$

$$L_T = 0.05 + 0.1 = 0.15 \text{ H}$$

$$\Rightarrow X_L = \omega L = 2\pi f L_T = 2\pi(50)(0.15) = 47.1 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi(50)(50 \times 10^{-6})} = 63.7 \Omega$$

$$\begin{aligned} \therefore \bar{Z}_T &= \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(30)^2 + (47.1 - 63.7)^2} \\ &= 34.3 \angle -28.96^\circ \end{aligned}$$

$$(a). \therefore \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{200 \angle 0^\circ}{34.3 \angle -28.96^\circ} = 5.83 \angle 28.96^\circ \quad \text{leading}$$

(b). $\bar{V}_1 = ?$

T57

$$\begin{aligned}\bar{V}_1 &= \bar{I} \bar{Z}_1 & \Rightarrow \bar{Z}_1 &= 10 + jX_{L1} \\ & & &= 10 + j(2\pi fL_1) \\ & & &= 10 + j(2\pi(50)0.05) \\ & & &= 10 + j15.7 \\ \therefore \bar{V}_1 &= (5.83 \angle 28.96^\circ)(18.6 \angle 57.5^\circ) & \therefore \bar{Z}_1 &= 18.6 \angle 57.5^\circ \\ &= 108.4 \angle 86.46^\circ\end{aligned}$$

(c). $\bar{V}_2 = ?$


$$\begin{aligned}\bar{V}_2 &= \bar{I} \bar{Z}_2 & \Rightarrow \bar{Z}_2 &= 20 + jX_{L2} - jX_{C2} \\ & & &= 20 + j(2\pi fL_2) - \frac{1}{2\pi fC_2} \\ & & &= 20 + j31.4 - j63.7 \\ & & &= 20 - j32.3 \\ \therefore \bar{Z}_2 &= 37.74 \angle -58.2^\circ \\ \therefore \bar{V}_2 &= \bar{I} \bar{Z}_2 = (5.83 \angle 28.96^\circ)(37.74 \angle -58.2^\circ) \\ &= 220.1 \angle -52.37^\circ\end{aligned}$$

(d). The combined (overall) power factor of the circuit :

- from part (a) \Rightarrow p.f = $\cos \phi = \cos 28.96^\circ$
 $= 0.87$ leading

- or p.f = $\frac{R}{Z_T} = \frac{30}{34.3} = 0.87$ (leading)

The phasor diagram

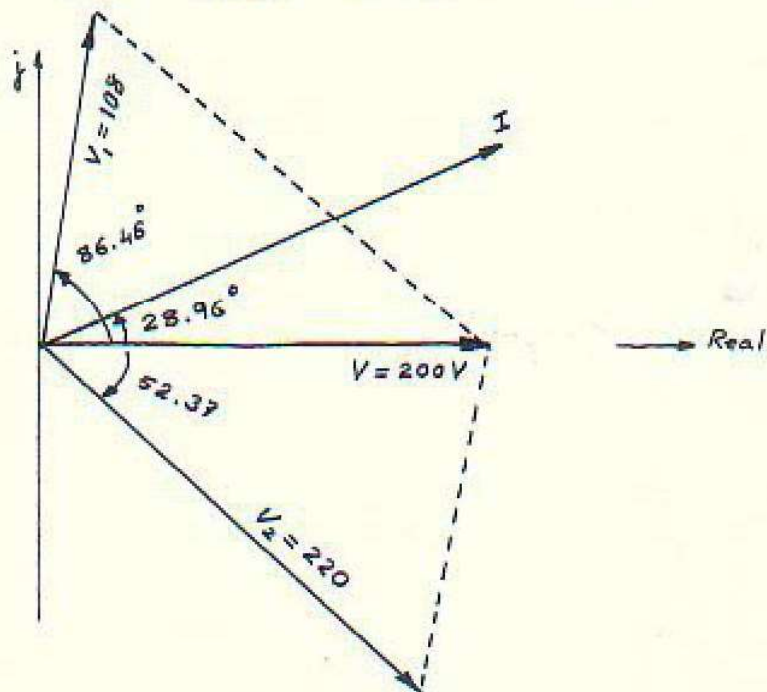

7.2 Parallel AC Circuits

EE7


* Admittance and Susceptance

- In the dc circuit analysis, we had used the term conductance to represent the reciprocal of the resistance R ; i.e:

$$G = \frac{1}{R} \quad \text{where } G \text{ is the conductance}$$

The total conductance of the parallel circuit is then found by adding the conductance of each branch.

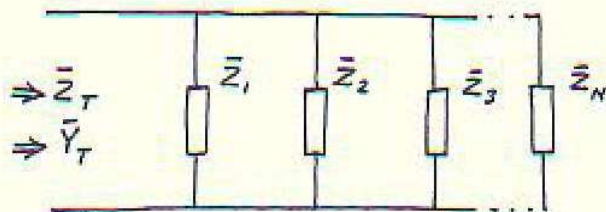- In AC circuit analysis, we define the admittance (\bar{Y}) as equal to $1/\bar{Z}$. For the parallel circuit shown:



* The total admittance \bar{Y}_T :

$$\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 + \dots + \bar{Y}_N$$

then since $\bar{Y} = \frac{1}{\bar{Z}}$; so the total impedance \bar{Z}_T :

$$\frac{1}{\bar{Z}_T} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3} + \dots + \frac{1}{\bar{Z}_N}$$

- As mentioned earlier, for 2 branches parallel ac circuit, then:

$$\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$$

- Also for 3 parallel branches;

$$\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2 \bar{Z}_3}{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}$$

⊛ IN GENERAL, we have: $\bar{Z}_T = R \mp jX$, the

$$\bar{Y}_T = \frac{1}{R} \mp \frac{1}{jX} = \boxed{G \pm jB}$$

where: $G \Rightarrow$ Conductance = $\frac{1}{R}$

$B \Rightarrow$ Susceptance = $\frac{1}{X}$

(Siemens, S) سيمنس

(Siemens, S)

$$\therefore \bar{Z}_T = \bar{Z}_1 + \bar{Z}_{23}$$

T57

$$\bar{Z}_{23} = \frac{\bar{Z}_2 \bar{Z}_3}{\bar{Z}_2 + \bar{Z}_3}$$

$$= \frac{(10 - j12)(6 + j10)}{(16 - j2)} = 10.9 + j3.1$$

$$\Rightarrow \bar{Z}_T = (4 + j6) + (10.9 + j3.1) = 14.9 + j9.1 = 17.5 \angle 31.4^\circ \quad \Omega$$

* Now, finding $\bar{I} = ?!$

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{200 \angle 0^\circ}{17.5 \angle 31.4^\circ} = 11.4 \angle -31.4^\circ \quad A$$


* To draw the phasor diagram, we have (till now) \bar{V} and \bar{I} , then we have to find the following quantities:

$$\begin{aligned} * \bar{V}_{AB} &= \bar{I} \bar{Z}_1 = (11.4 \angle -31.4^\circ)(7.2 \angle 56.3^\circ) \\ &= 82.2 \angle 24.9^\circ \quad \text{volts} \end{aligned}$$

$$\begin{aligned} * \bar{V}_{BC} &= \bar{I} \bar{Z}_{23} = (11.4 \angle -31.4^\circ)(11.3 \angle 15.9^\circ) \\ &= 128.8 \angle -15.5^\circ \quad \text{volts} \end{aligned}$$

$$\begin{aligned} * \bar{I}_2 &= \frac{\bar{V}_{BC}}{\bar{Z}_2} = \frac{128.8 \angle -15.5^\circ}{15.6 \angle -50.2^\circ} \\ &= 8.25 \angle 34.7^\circ \quad A \end{aligned}$$
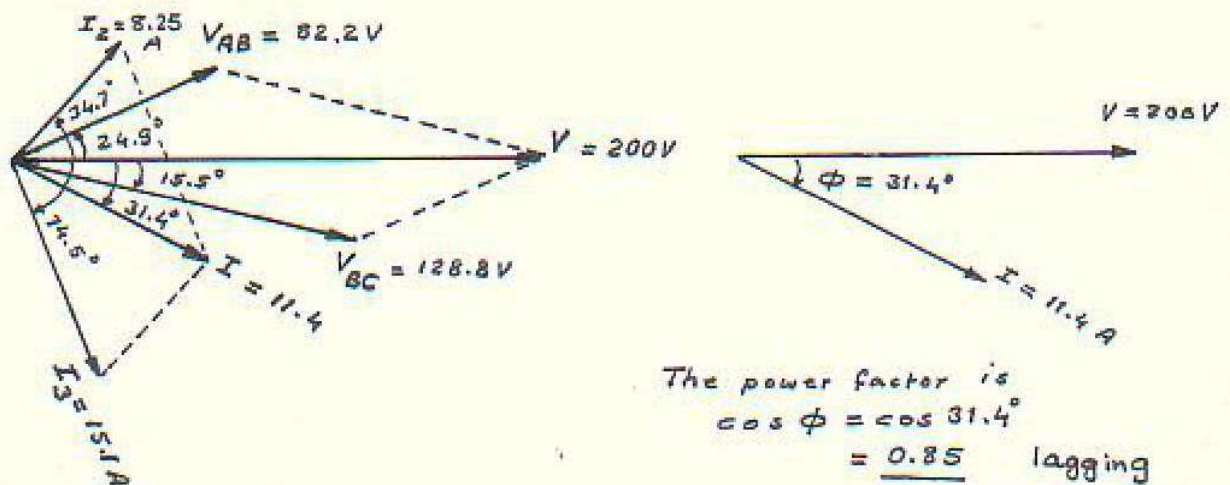
$$\begin{aligned} * \bar{I}_3 &= \frac{128.8 \angle -15.5^\circ}{11.7 \angle 58^\circ} \\ &= 15.1 \angle -74.5^\circ \quad A \end{aligned}$$




Example

EE7

For the circuit shown;

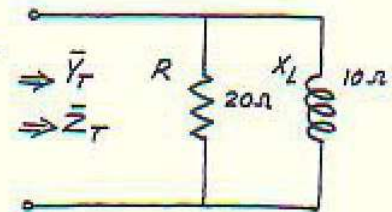- a. Determine the admittance of each branch.
- b. Find the input admittance.
- c. Calculate the input impedance.
- d. Draw the admittance diagram.



Solution

Ⓐ:

$$\begin{aligned}
 - \bar{Y}_1 &= \bar{G} = G \angle 0 = \frac{1}{R} \angle 0 = \frac{1}{20} \angle 0 = 0.05 \angle 0 \\
 &= 0.05 + j0 \\
 &= 0.05 \\
 - \bar{Y}_2 &= \bar{B}_L = \frac{1}{X_L} \angle -90^\circ = \frac{1}{10} \angle -90^\circ = 0.1 \angle -90^\circ \\
 &= 0 - j0.1 \\
 &= -j0.1
 \end{aligned}$$

Ⓑ: $\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 = 0.05 - j0.1 = G - jB_L$


Ⓒ: $\bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.05 - j0.1} = \frac{1}{0.112 \angle -63.43^\circ} = 8.93 \angle 63.43^\circ$

OR

$$\begin{aligned}
 \bar{Z}_T &= \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} = \frac{(20 \angle 0)(10 \angle 90^\circ)}{20 + j10} \\
 &= \frac{200 \angle 90^\circ}{22 \angle 26.57^\circ} \\
 &= 8.93 \angle 63.43^\circ
 \end{aligned}$$

← which is the same as calculated above.

Ⓓ: The admittance diagram:

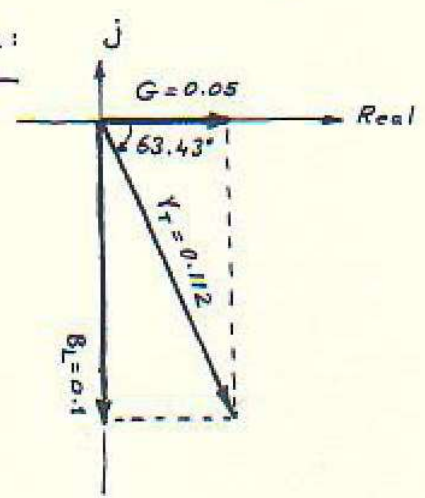


Example

EE7

For the circuit show;

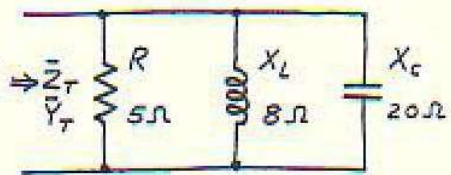- Determine the admittance of each branch.
- Find the input admittance.
- Calculate the input impedance.
- Draw the admittance diagram.



Solution

①:

$$\bar{Y}_1 = \bar{G} = \frac{1}{RL} = \frac{1}{5} \angle 0^\circ = 0.2 \angle 0^\circ = 0.2 + j0 = 0.2$$

$$\bar{Y}_2 = \bar{B}_L = \frac{1}{X_L \angle 90^\circ} = \frac{1}{8 \angle 90^\circ} = \frac{1}{8} \angle -90^\circ = 0.125 \angle -90^\circ = -j0.125$$

$$\bar{Y}_3 = \bar{B}_C = \frac{1}{X_C \angle -90^\circ} = \frac{1}{20 \angle -90^\circ} = \frac{1}{20} \angle 90^\circ = 0.05 \angle 90^\circ = +j0.05$$

②:

$$\begin{aligned} \bar{Y}_T &= \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 \\ &= 0.2 - j0.125 + j0.05 \\ &= 0.2 - j0.075 \\ &= 0.2136 \angle -20.56^\circ \end{aligned}$$


③:

$$\begin{aligned} \bar{Z}_T &= \frac{1}{\bar{Y}_T} = \frac{1}{0.2136 \angle -20.56^\circ} \\ &= 4.68 \angle 20.56^\circ \end{aligned}$$

or

$$\begin{aligned} \bar{Z}_T &= \frac{\bar{Z}_1 \bar{Z}_2 \bar{Z}_3}{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3} \\ &= \frac{(5 \angle 0^\circ)(8 \angle 90^\circ)(20 \angle -90^\circ)}{(5 \angle 0^\circ)(8 \angle 90^\circ) + (8 \angle 90^\circ)(20 \angle -90^\circ) + (5 \angle 0^\circ)(20 \angle -90^\circ)} \\ &= \frac{800 \angle 0^\circ}{40 \angle 90^\circ + 160 \angle 0^\circ + 100 \angle -90^\circ} \\ &= \frac{800 \angle 0^\circ}{j40 + 160 - j100} = \frac{800 \angle 0^\circ}{160 - j60} \\ &= \frac{800 \angle 0^\circ}{170.88 \angle -20.56^\circ} = 4.68 \angle 20.56^\circ \end{aligned}$$


④. The Admittance Diagram

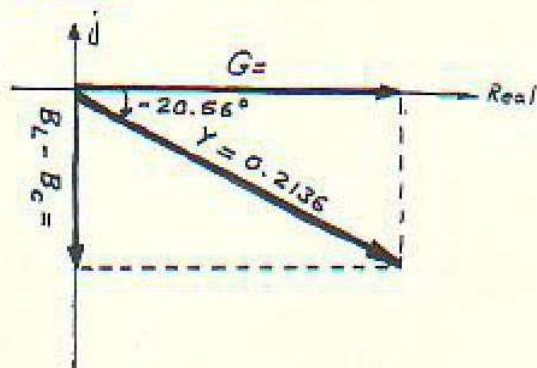

Example

EE7

Find the admittance of the circuit shown

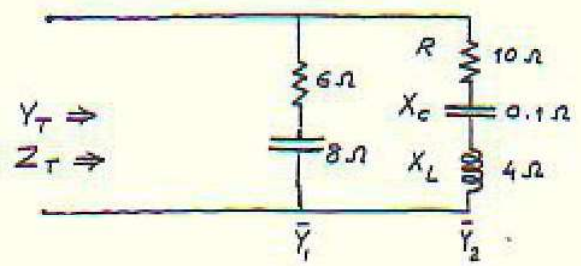

Solution

$\bar{Z}_1 = 6 - j8$

$$\Rightarrow \bar{Y}_1 = \frac{1}{\bar{Z}_1} = \frac{1}{6 - j8} = \frac{6 + j8}{6^2 + 8^2} = \frac{6}{100} + j \frac{8}{100} = 0.06 + j0.08$$

$$\bar{Z}_2 = 10 + j4 - j0.1 = 10 + j3.9$$

$$\Rightarrow \bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{10 + j3.9} = \frac{10 - j3.9}{10^2 + 3.9^2} = \frac{10}{115.21} - j \frac{3.9}{115.21} = 0.087 - j0.034$$

$$\begin{aligned} \therefore \bar{Y}_T &= \bar{Y}_1 + \bar{Y}_2 \\ &= 0.06 + j0.08 + 0.087 - j0.034 \\ &= 0.147 + j0.046 \\ &= 0.154 \angle 17.3762^\circ \end{aligned}$$

* \Rightarrow OR you can try again to get \bar{Y}_T as follows:

$$\begin{aligned} \bar{Z}_T &= \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} \\ &= \frac{(6 - j8)(10 + j3.9)}{(6 - j8) + (10 + j3.9)} \end{aligned}$$

and proceed to get $\bar{Z}_T \Rightarrow Y_T$ must be the same value

$$\bar{Y}_T = \frac{1}{\bar{Z}_T} = 0.154 \angle 17.3762^\circ$$

Illustrative Examples on R-L, R-C, and R-L-C Parallel AC Circuits


EE7

* R-L parallel ac circuits

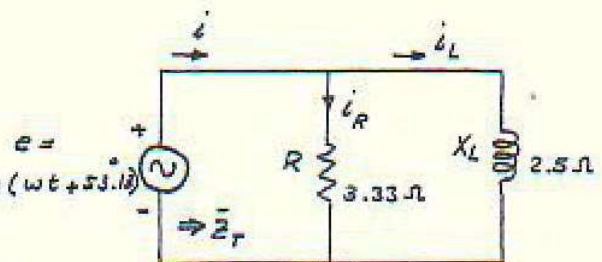Example


For the circuit shown;

- \bar{Z}_T
- Draw the admittance diagram
- The currents \bar{I} , \bar{I}_R , and \bar{I}_L
- Draw the current phasor diagram.
- Calculate the active, reactive, and complex apparent powers.
- Determine the power factor.



Solution

Draw the circuit with phasor notation

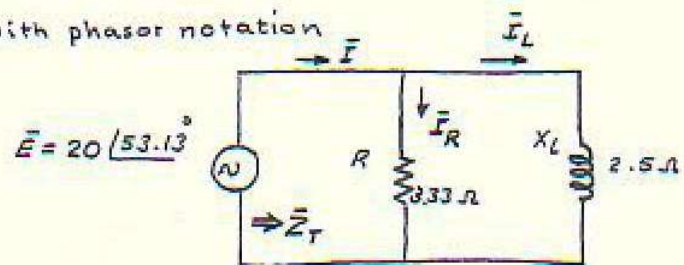


(a) \bar{Z}_T :

$$\begin{aligned} \bar{Y}_T &= \bar{Y}_1 + \bar{Y}_2 = G + B_L = \frac{1}{3.33} \angle 0^\circ + \frac{1}{2.5} \angle -90^\circ \\ &= 0.3 - j0.4 \\ &= 0.5 \angle -53.13^\circ \end{aligned}$$

$$\therefore \bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.5 \angle -53.13^\circ} = 2 \angle 53.13^\circ$$

(b) The admittance diagram

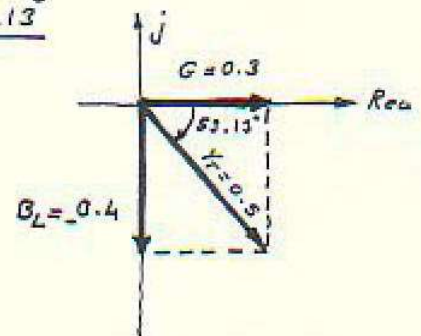

$$\textcircled{c}. \bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{20 \angle 53.13^\circ}{2 \angle 53.13^\circ} = 10 \angle 0^\circ$$

EE7

$$\bar{I}_R = \frac{\bar{E}}{R} = \frac{20 \angle 53.13^\circ}{3.33 \angle 0^\circ} = 6 \angle 53.13^\circ$$

$$\bar{I}_L = \frac{\bar{E}}{\bar{X}_L} = \frac{20 \angle 53.13^\circ}{2.5 \angle 90^\circ} = 8 \angle -36.87^\circ$$


* For check

$$\text{using KCL} \Rightarrow \bar{I} = \bar{I}_R + \bar{I}_L$$

$$\begin{aligned} \Rightarrow \bar{I} &= 6 \angle 53.13^\circ + 8 \angle -36.87^\circ \\ &= (3.6 + j4.8) + (6.4 - j4.8) \\ &= 10 + j0 \\ &= 10 \angle 0^\circ \end{aligned}$$

which is the same as calculated above

ⓓ. The current phasor diagram

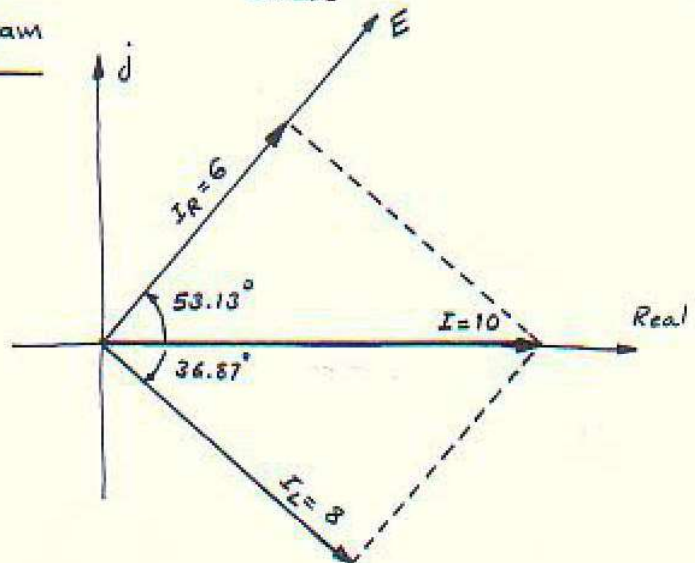

$$\textcircled{e}. \text{Active power} = P = EI \cos \phi = (20)(10) \cos 53.13^\circ = 120 \text{ W}$$

$$\text{Reactive power} = Q = EI \sin \phi = (20)(10) \sin 53.13^\circ = 160 \text{ VAR}$$

$$\therefore \text{Complex apparent power} = \bar{S} = P + jQ = 120 + j160$$

$$\therefore \bar{S} = \sqrt{P^2 + Q^2} = 200 \text{ VA}$$

from the phasor dig.

ⓕ. The power factor $p.f = \cos \phi = \cos 53.13^\circ = 0.6$ lagging


$$\text{or } \cos \phi = \frac{P}{EI} = \frac{E^2/R}{EI} = \frac{EG}{I} = \frac{G}{Y_T}$$

ملاحظة: يمكن حساب \bar{Z}_T عبر العلاقة $\frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$ والمبرور على النتيجة نفس

* R-C parallel AC circuit

Example

$\bar{I} = 10 \angle 0^\circ$

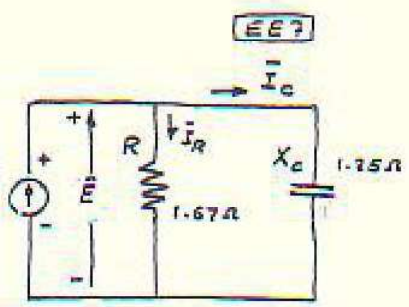

- a. Determine \bar{Z}_T .
- b. Draw the admittance diagram.
- c. Calculate \bar{E} , \bar{I}_R , and \bar{I}_C , and draw the current phasor diagram.
- d. Active, reactive, and apparent powers.
- e. Determine the power factor for the circuit.

Solution

a. $\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 = \frac{1}{R \angle 0^\circ} + \frac{1}{X_c \angle -90^\circ} = \frac{1}{1.67} \angle 0^\circ + \frac{1}{1.25} \angle 90^\circ$
 $= 0.6 + j0.8 = 1 \angle 53.13^\circ$
 $\Rightarrow \bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{1 \angle 53.13^\circ} = 1 \angle -53.13^\circ$

Also:
 $\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$


b. $\bar{E} = \frac{\bar{I}}{\bar{Y}_T} = \frac{10 \angle 0^\circ}{1 \angle 53.13^\circ} = 10 \angle -53.13^\circ$ or $\bar{E} = \bar{I} \bar{Z}_T$

$\bar{I}_R = \bar{E} \bar{G} = (10 \angle -53.13^\circ)(0.6) = 6 \angle -53.13^\circ$ or $\bar{I}_R = \frac{\bar{E}}{R}$

$\bar{I}_C = \bar{E} \bar{B}_C = (10 \angle -53.13^\circ)(0.8 \angle 90^\circ) = 8 \angle 36.87^\circ$ or $\bar{I}_C = \frac{\bar{E}}{X_c}$

As a check?
 $\bar{I} = \bar{I}_R + \bar{I}_C$
 $= 6 \angle -53.13^\circ + 8 \angle 36.87^\circ$
 $= 10 \angle 0^\circ$

c. The phasor diagram

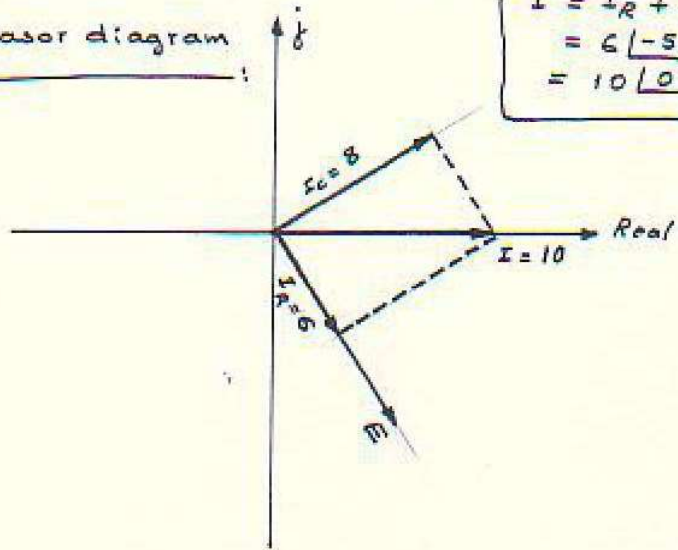

d. Active power = $P = EI \cos \phi$
 $= (10)(10) \cos 53.13^\circ$
 $= 60 \text{ W}$

EE7

* or $P = E^2 G$
 $= (10)^2 (0.6)$
 $= 60 \text{ W}$

Reactive power = $Q = EI \sin \phi$
 $= (10)(10) \sin 53.13^\circ$
 $= 80 \text{ VAR}$

\therefore Apparent power $S = \sqrt{P^2 + Q^2} = \sqrt{(60)^2 + (80)^2}$
 $= 100 \text{ VA}$

e. The power factor

p.f = $\cos 53.13$
 $= 0.6$ leading


← from the phasor diagram
 \bar{I} leads \bar{E}

* R-L-C parallel AC circuit

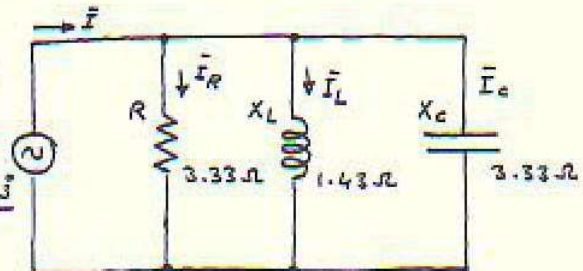Example

For the circuit shown;

- Determine \bar{Z}_T .
- Calculate \bar{I} , \bar{I}_R , \bar{I}_L & \bar{I}_C
- Draw the phasor diag. $\bar{E} = 100 \angle 53.13^\circ$
- Calculate the active (real) power
- Determine the power factor



Solution

a. $\bar{Z}_T = ?$

$$\begin{aligned} \bar{Y}_T &= \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 \\ &= \frac{1}{R} \angle 0^\circ + \frac{1}{X_L} \angle -90^\circ + \frac{1}{X_C} \angle 90^\circ \\ &= \frac{1}{3.33} \angle 0^\circ + \frac{1}{1.43} \angle -90^\circ + \frac{1}{3.33} \angle 90^\circ \\ &= 0.3 - j0.7 + j0.3 \\ &= 0.3 - j0.4 \\ &= 0.5 \angle -53.13^\circ \end{aligned}$$

$\therefore \bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.5 \angle -53.13^\circ} = 2 \angle 53.13^\circ$

b. $\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{100 \angle 53.13^\circ}{2 \angle 53.13^\circ} = 50 \angle 0^\circ$

$\bar{I}_R = \frac{\bar{E}}{R} = \sqrt{\dots}$ ←

$I_R = \bar{E} \bar{G} = (100 \angle 53.13^\circ)(0.3 \angle 0^\circ)$
 $= 30 \angle 53.13^\circ$


$$\Rightarrow \vec{I}_L = \frac{\vec{E}}{X_L}$$

$$\vec{I}_L = \vec{E} \vec{B}_L = (100 \angle 53.13^\circ)(0.7 \angle -90^\circ) = 70 \angle -36.87^\circ \quad \boxed{EE?}$$

$$\vec{I}_C = \vec{E} \vec{B}_C = (100 \angle 53.13^\circ)(0.3 \angle 90^\circ) = 30 \angle 143.13^\circ$$

$$\text{Prove that : } \vec{I} = \vec{I}_R + \vec{I}_L + \vec{I}_C$$

Ⓒ. The current phasor diagram:

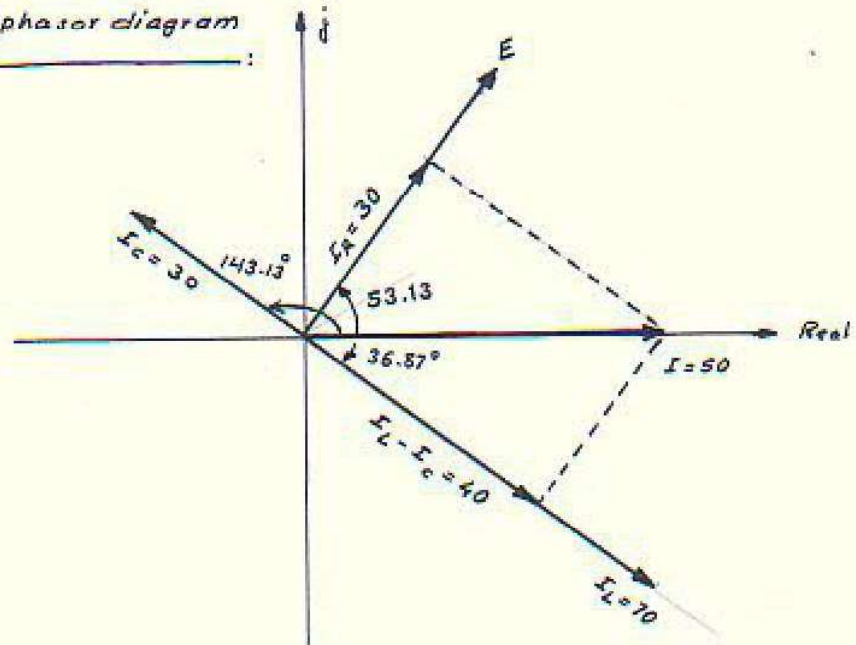

$$\begin{aligned} \text{Ⓓ. Active power} &= P = EI \cos \phi \\ (\text{Real power}) &= (100)(50) \cos 53.13^\circ \\ &= 3000 \text{ W} \\ &= 3.0 \text{ kW} \end{aligned}$$

$$\begin{aligned} \Rightarrow \text{or } P &= E^2 G \\ &= (100^2)(0.3) \\ &= 3.0 \text{ kW} \end{aligned}$$


$$\begin{aligned} \text{Ⓔ. The power factor} &\Rightarrow \text{p.f} = \cos \phi \\ &= \cos 53.13 \\ &= 0.6 \text{ lagging} \quad \leftarrow \text{from the phasor diagram.} \end{aligned}$$

$$\vec{Z}_T = \frac{\vec{Z}_1 \vec{Z}_2 \vec{Z}_3}{\vec{Z}_1 \vec{Z}_2 + \vec{Z}_2 \vec{Z}_3 + \vec{Z}_1 \vec{Z}_3}$$

⚡ ملاحظة: من المهم كذلك حساب دوائر على النتيجة نفسها.

Example


_____ : Draw the impedance diagram for the circuit shown and find the total impedance.

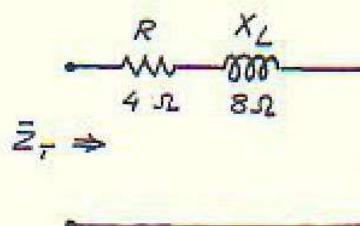Solution

$$\underline{\hspace{2cm}} : \bar{Z}_T = \bar{Z}_1 + \bar{Z}_2$$

$$= R \angle 0^\circ + X_L \angle 90^\circ = R + jX_L = 4 + j8$$

$$\therefore \bar{Z}_T = 8.944 \angle 63.43^\circ \Omega$$

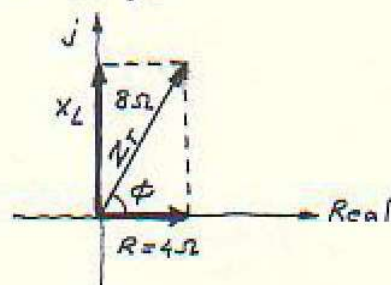Example

_____ : Determine the input impedance to the series network shown

Solution

$$\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3$$

$$= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ$$


$$= R + jX_L - jX_C$$

$$= R + j(X_L - X_C)$$

$$= 6 + j(10 - 12)$$

$$= 6 - j2$$
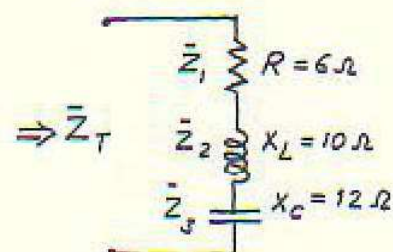
$$\Rightarrow \bar{Z}_T = 6.325 \angle -18.43^\circ \Omega$$




Example

_____ : A 60 Hz sinusoidal voltage ($v = 141 \sin \omega t$) is applied to a series R-L circuit. The values of the resistance and the inductance are 3Ω and 0.0106 H respectively.

- (a). Compute the rms value of the current in the circuit and its phase angle with respect to the voltage.
- (b). Write the expression for the instantaneous current in the circuit.
- (c). Find the average power dissipated by the circuit.
- (d). Calculate the p.f of the circuit.

Solution

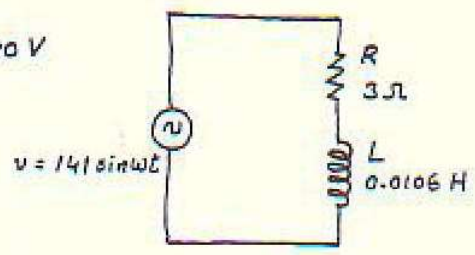_____ : We have ; $v = V_m \sin \omega t$
 $\Rightarrow V = \frac{V_m}{\sqrt{2}} = \frac{141}{\sqrt{2}} = 100 \text{ V}$
 $\therefore \bar{V} = 100 \angle 0$



(a). $\bar{I} = \frac{\bar{V}}{\bar{Z}}$

$$\begin{aligned} \bar{Z} &= R + jX_L \\ &= R + j(2\pi fL) \\ &= 3 + j(2\pi \times 60 \times 0.0106) \\ &= 3 + j4 \\ \therefore \bar{Z} &= 5 \angle 53.1^\circ \end{aligned}$$

$$\Rightarrow \bar{I} = \frac{100 \angle 0}{20 \angle 53.1^\circ}$$

$$\therefore \bar{I} = 20 \angle -53.1^\circ \quad \Rightarrow \text{the current lags the voltage by } 53.1^\circ$$

(b). $i = I_m \sin(\omega t - 53.1^\circ)$
 $= \sqrt{2}(20) \sin(\omega t - 53.1^\circ) = \underline{28.28 \sin(\omega t - 53.1^\circ)}$

(c). $P = VI \cos \phi$
 $= (100)(20) \cos 53.1^\circ = 1200 \text{ W}$

or $P = I^2 R = (20)^2(3) = 1200 \text{ W}$

(d). p.f = $\cos \phi$
 $= \cos 53.1^\circ$
 $= 0.6$ lagging

Example

_____ : A two elements series circuit is connected across an ac circuit having a source ($e = \sqrt{2}(200) \sin(\omega t + 20^\circ) \text{ V}$). The current in the circuit is then found to be $i = \sqrt{2}(10) \cos(341t - 25^\circ)$. Determine the parameters of the circuit.

Solution :

The applied voltage is :

$$v = \sqrt{2}(200)\sin(\omega t + 20^\circ)$$

$$\Rightarrow \bar{V} = 200 \angle 20^\circ$$

The current is :

$$i = \sqrt{2}(10)\cos(\omega t - 25^\circ)$$

$$= \sqrt{2}(10)\sin(\omega t - 25^\circ - 90^\circ)$$

$$\therefore i = \sqrt{2}(10)\sin(\omega t + 65^\circ)$$

$$\Rightarrow \bar{I} = 10 \angle 65^\circ$$

$$\Rightarrow \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{200 \angle 20^\circ}{10 \angle 65^\circ} = 20 \angle -45^\circ$$

Note $\phi = -45^\circ$ (leading)

$$= 14.14 - j 14.14$$

This impedance represents a series circuit with $R = 14.14 \Omega$ and a capacitive reactance (because of the $-j$) of $X_c = 14.14 \Omega$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$\omega = 314 \text{ rad/sec.}$

$$\therefore 14.14 = \frac{1}{314 C} \Rightarrow C = \frac{1}{(14.14)(314)} = 2.25 \times 10^{-4} \text{ F}$$


\therefore The circuit has $R = 14.14 \Omega$ and $C = 225 \mu\text{F}$

Example

Two coils A and B are connected in series across 240 V, 50 Hz supply. The resistance of A is 5Ω and the inductance of B is 0.015 H . If the input supply is 3 kW and 2 kVAR , find the resistance of B and the inductance of A. Calculate the voltage across each coil.

Solution :

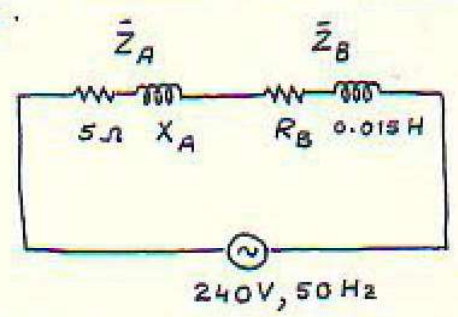* From the power triangle, and the circuit shown,



$$S = \sqrt{P^2 + Q^2} = \sqrt{3^2 + 2^2}$$

$$= 3.606 \text{ KVA}$$

$$S = VI \Rightarrow I = \frac{S}{V} = \frac{3606}{240} = 15.025 \text{ A}$$

But, $P = 3 \text{ kW} = 3000 \text{ W}$

$$= I^2 R_T = I^2 (R_A + R_B)$$

$$\therefore 3000 = (15.025)^2 (R_A + R_B)$$

$$\Rightarrow R_A + R_B = 13.3 \Omega$$

$$\therefore \text{Since } R_A = 5 \Omega \Rightarrow R_B = 13.3 - 5 = \underline{8.3 \Omega}$$

T57

Similarly, we have:

معرفة: من شكله عن هذا المثال
بالكيفية والوصول إلى
النتيجة.

$$Q = 2 \text{ kVAR} = 2000 \text{ VAR}$$

$$= I^2 X_{LT} = (15.03)^2 X_{LT}$$

$$\therefore X_{LT} = \frac{2000}{(15.03)^2} = 8.85 \Omega$$

$$X_{LT} = X_A + X_B \Rightarrow X_A = 8.85 - X_B$$

$$= 8.85 - (2\pi f L_B)$$

$$= 8.85 - (2\pi \times 50 \times 0.015)$$

$$= 8.85 - 4.713 = 4.13 \Omega$$

$$\therefore \bar{Z}_A = R_A + jX_A = 5 + j4.13 = 6.48 \angle 39.57^\circ$$

$$\text{and } \bar{Z}_B = R_B + jX_B = 8.3 + j4.713 = 9.54 \angle 29.59^\circ$$

$X_B = 2\pi f L_B$
 $= 2\pi \times 50 \times 0.015$

$$\therefore \bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 = 5 + j4.13 + 8.3 + j4.713$$

$$=$$

$$\therefore \bar{V}_A = \bar{I} \bar{Z}_A = \checkmark$$

$$\bar{V}_B = \bar{I} \bar{Z}_B = \checkmark$$

$$\text{or } \bar{V}_A = \frac{\bar{V} \bar{Z}_A}{\bar{Z}_A + \bar{Z}_B} = \checkmark$$

The results must be the same.

and

$$\bar{V}_B = \frac{\bar{V} \bar{Z}_B}{\bar{Z}_A + \bar{Z}_B} = \checkmark$$

Example

A 240 V, 50 Hz series R-C circuit takes an rms current of 20 A. The maximum value for the current occurs 1/900 seconds before the maximum value of the voltage. Calculate:

- (a). The power factor.
- (b). Average power.
- (c). The parameters of the circuit.

Solution

The time duration of the voltage (T) = 0.02 = 0.02 sec.

$$\therefore 0.05 \text{ sec.} \Rightarrow 360^\circ, \text{ then}$$

$$(1/900) \text{ sec} \Rightarrow \left[\frac{360^\circ (1/900)}{0.02} \right]^\circ = \text{The phase shift angle } (\phi)$$

$$\therefore \phi = 20^\circ$$

$$(a). \therefore \text{p.f.} = \cos \phi = \cos 20^\circ \\ = 0.9397 \quad (\text{leading})$$

T57

$$(b). \text{Average power} = P = VI \cos \phi \\ = 240(20) \cos 20^\circ \\ = 4510 \text{ W} \\ = 4.510 \text{ kW}$$

$$(c). \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{240 \angle 0^\circ}{20 \angle 20^\circ} = 12 \angle -20^\circ \\ = 20 \cos(-20) + j 12 \sin(-20) \\ = 11.28 - j 4.1$$

$\therefore \bar{Z}$ is composed of $R = 11.28 \Omega$, and $X_c = 4.1 \Omega$




$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} \\ \therefore C = \frac{1}{2\pi f X_c} = 7.76 \times 10^{-4} \text{ F} \\ = 776 \mu\text{F}$$

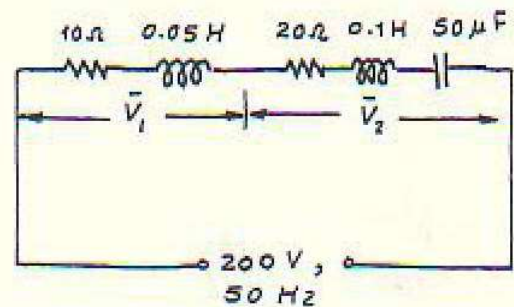Example

Draw the phasor diagram for the circuit shown, indicating the resistance and the reactance drop, the terminal voltages \bar{V}_1 and \bar{V}_2 and the current. Find the values of:

- The current \bar{I} .
- \bar{V}_1
- \bar{V}_2
- The power factor



Solution

$$R_T = 10 + 20 = 30 \Omega \\ L_T = 0.05 + 0.1 = 0.15 \text{ H} \\ \Rightarrow X_L = \omega L = 2\pi f L_T = 2\pi(50)(0.15) \\ = 47.1 \Omega$$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi(50)(50 \times 10^{-6})} = 63.7 \Omega$$

$$\therefore \bar{Z}_T = \sqrt{R^2 + (X_L - X_c)^2} = \sqrt{(30)^2 + (47.1 - 63.7)^2} \\ = 34.3 \angle -28.96^\circ$$

$$(a). \therefore \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{200 \angle 0^\circ}{34.3 \angle -28.96^\circ} = 5.83 \angle 28.96^\circ \quad \text{leading}$$

(b). $\bar{V}_1 = ?$

TST

$$\begin{aligned} \bar{V}_1 &= \bar{I} \bar{Z}_1 & \Rightarrow \bar{Z}_1 &= 10 + jX_{L1} \\ & & &= 10 + j(2\pi fL_1) \\ & & &= 10 + j(2\pi(50)0.05) \\ & & &= 10 + j15.7 \\ \therefore \bar{V}_1 &= (5.83 \angle 28.96^\circ)(18.6 \angle 57.5^\circ) & \therefore \bar{Z}_1 &= 18.6 \angle 57.5^\circ \\ &= 108.4 \angle 86.46^\circ \end{aligned}$$

(c). $\bar{V}_2 = ?$


$$\begin{aligned} \bar{V}_2 &= \bar{I} \bar{Z}_2 & \Rightarrow \bar{Z}_2 &= 20 + jX_{L2} - jX_{C2} \\ & & &= 20 + j(2\pi fL_2) - \frac{1}{2\pi fC_2} \\ & & &= 20 + j31.4 - j63.7 \\ & & &= 20 - j32.3 \\ \therefore \bar{Z}_2 &= 37.74 \angle -58.2^\circ \\ \therefore \bar{V}_2 &= \bar{I} \bar{Z}_2 = (5.83 \angle 28.96^\circ)(37.74 \angle -58.2^\circ) \\ &= 220.1 \angle -52.37^\circ \end{aligned}$$

(d). The combined (overall) power factor of the circuit :

$$\begin{aligned} \text{— from part (a)} \Rightarrow \text{p.f.} &= \cos \phi = \cos 28.96^\circ \\ &= 0.87 \quad \text{leading} \end{aligned}$$

$$\text{— or } \text{p.f.} = \frac{R}{Z_T} = \frac{30}{34.3} = 0.87 \quad (\text{leading})$$

The phasor diagram

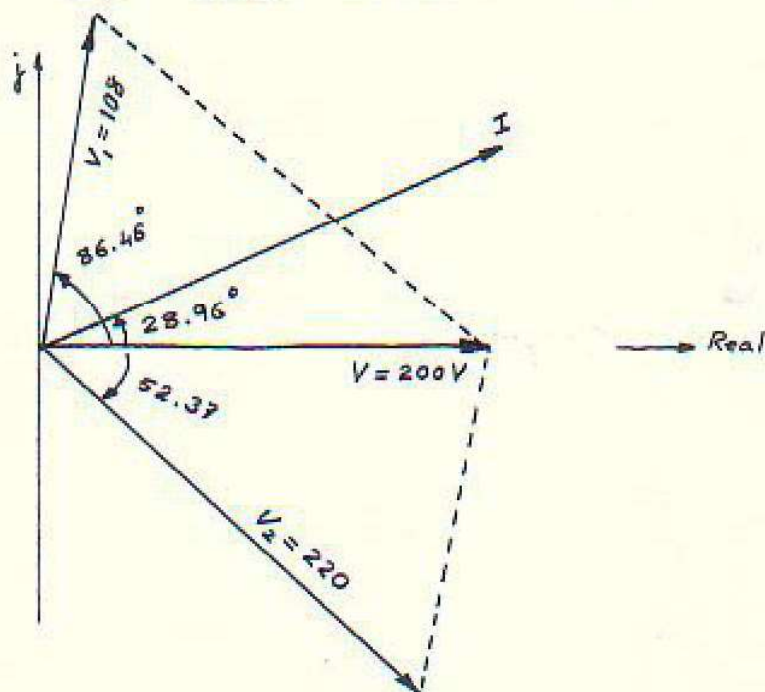

Example

T57

_____ : In a circuit it is found that the applied voltage is to lag the current by 30° .

- Is the power factor lagging or leading?
- What is the value of the power factor?
- Is the circuit inductive or capacitive?


Solution

- The power factor is leading, since the current leads the voltage.
- The power factor is
$$\begin{aligned} \text{p.f} &= \cos \phi \\ &= \cos 30 \\ &= 0.866 \text{ (lead)} \end{aligned}$$
- The circuit is capacitive.

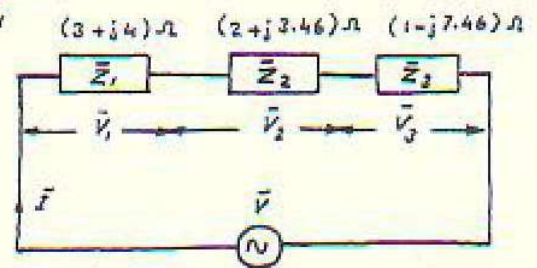Example

_____ : In the circuit diagram of the Fig. shown, the voltage drop across \bar{Z}_1 is $(10 + j0)$ volts. Find out:

- The current in the circuit.
- The voltage drop across \bar{Z}_2 and \bar{Z}_3
- The voltage of the source.



Solution

$$\text{_____ : (a). } \bar{I} = \frac{\bar{V}}{\bar{Z}_T} \Rightarrow \begin{aligned} \bar{Z}_T &= \checkmark \\ \bar{V} &= ? \end{aligned}$$

$$\begin{aligned} \text{or } I &= \frac{\bar{V}_1}{\bar{Z}_1} = \frac{10 + j0}{3 + j4} = \frac{10 \angle 0^\circ}{5 \angle 53.1^\circ} = 2 \angle -53.1^\circ \\ &= 2 (\cos 53.1^\circ - j \sin 53.1^\circ) = \underline{1.2 - j1.6} \end{aligned}$$

$$\text{(b). } \bar{V}_2 = \bar{I} \bar{Z}_2 = (1.2 - j1.6)(2 + j3.46) = \underline{7.936 + j0.952} \text{ volts}$$

$$\bar{V}_3 = \bar{I} \bar{Z}_3 = (1.2 - j1.6)(1 - j7.46) = -10.74 - j10.55 \text{ volts}$$


$$\begin{aligned} \text{(c). } \bar{V} &= \bar{V}_1 + \bar{V}_2 + \bar{V}_3 \\ &= (10 + j0) + (7.936 + j0.952) + (-10.74 - j10.55) \\ &= 7.2 - j9.6 = 12 \angle -53.1^\circ \text{ volts} \end{aligned}$$

نلاحظ ان العنصرية الخلية والتيار المار في الدائرة كلاهما بنفس الطور والسبب في ذلك ان \bar{Z}_T في هذه الدائرة لا تمثل عددا مركبا بل قيمة حقيقية فقط (real part) اي انها تمثل مقاومة فقط والتي بدورها لا تتأثر في إلتواء بين العنصرية والتيار.

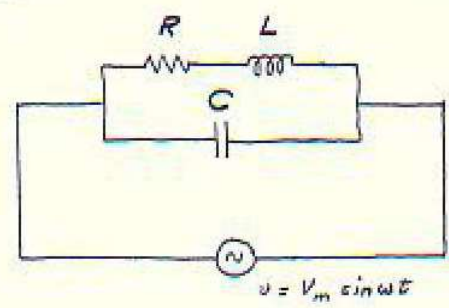Example (HW)

TST

_____ : Derive expressions for the equivalent impedance and (or) the admittance for the circuit shown.



Answer

$$\bar{Z}_T = \frac{R + j\omega [L(1 - \omega^2 LC^2) - CR^2]}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2}$$

and


$$\bar{Y}_T = \frac{R - j\omega [L(1 - \omega^2 LC) - CR^2]}{R^2 + \omega^2 L^2}$$

* Please check the answers.

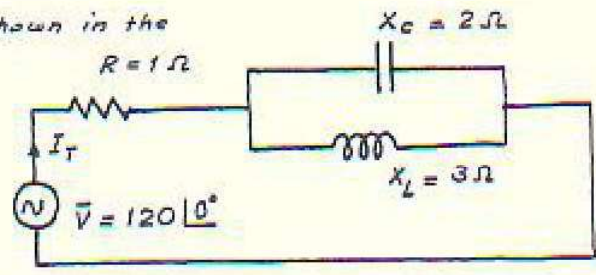Example

_____ : For the circuit shown in the Fig., determine :

- (a). \bar{Z}_T
- (b). \bar{I}_T
- (c). I_C
- (d). \bar{V}_R
- (e). \bar{V}_C
- (f). Average power
- (g). The power factor of the circuit.



Solution


_____ : Redraw the circuit (option) :

Let $\bar{Z}_1 = R = 1 \angle 0^\circ \Omega$
 $\bar{Z}_2 = X_C \parallel X_L$

$$= \frac{X_C X_L}{X_C + X_L} = \frac{(-j2)(j3)}{-j2 + j3}$$

$$= \frac{6 \angle 0^\circ}{j1} = \frac{6 \angle 0^\circ}{1 \angle 90^\circ}$$

$$= 6 \angle -90^\circ = -j6 \Omega$$

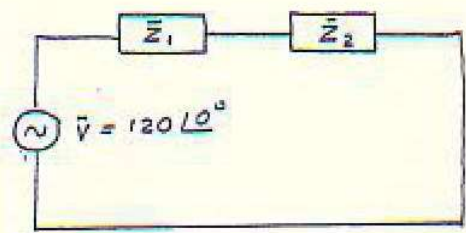

$$(a). \therefore \bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 = 1 - j6 = 6.08 \angle -80.54^\circ \quad \Omega \quad \boxed{T37}$$

$$(b). \bar{I}_T = \frac{\bar{V}}{\bar{Z}} = \frac{120 \angle 0^\circ}{6.08 \angle -80.54^\circ} = 19.74 \angle 80.54^\circ \quad A$$

$$(c). I_c = ?$$

Using the current divider rule, I_c can be calculated as:

$$\begin{aligned} \bar{I}_c &= I_T \frac{X_L}{X_L + X_C} = 19.74 \angle 80.54^\circ \cdot \frac{3 \angle 90^\circ}{1 \angle 90^\circ} \\ &= 59.22 \angle 80.54^\circ \quad A. \end{aligned}$$

$$(d). \bar{V}_R = ?$$

$$\begin{aligned} \bar{V}_R &= \bar{I}_T \bar{Z}_1 = (19.74 \angle 80.54^\circ)(1 \angle 0^\circ) \\ &= 19.74 \angle 80.54^\circ \quad V \end{aligned}$$

$$(e). \bar{V}_c = ?$$

$$\begin{aligned} \bar{V}_c &= \bar{I}_T \bar{Z}_2 = (19.74 \angle 80.54^\circ)(6 \angle -90^\circ) \\ &= 118.44 \angle -9.46^\circ \quad V \end{aligned}$$

$$\begin{aligned} \boxed{\text{OR}} \quad \bar{V}_c &= \bar{I}_c \bar{X}_c = (59.22 \angle 80.54^\circ)(2 \angle -90^\circ) \\ &= 118.44 \angle -9.46^\circ \end{aligned}$$

(f). Average power = Active power

$$P = I_r^2 R = (19.74)^2 \times 1 = 389.67 \text{ W}$$

$$\text{or } P = VI \cos \phi = 389.67 \text{ W}$$


$$(g). \text{Power factor} = \cos \phi \quad \phi = 80.54^\circ$$

$$\begin{aligned} \therefore \text{p.f} &= \cos 80.54^\circ \\ &= 0.164 \quad \underline{\text{leading}} \end{aligned}$$

Example (HW)

(a). Calculate the voltage V_c using the voltage divider rule.

(b). Calculate the current I

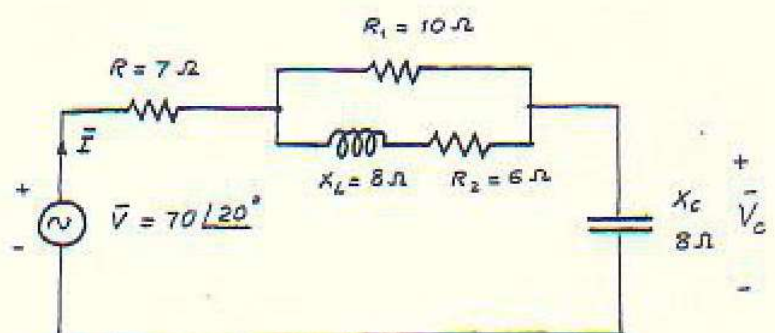


Answer

$$(a). \bar{V}_c = 42.42 \angle -45.38^\circ \quad \text{volts}$$

$$(b). \bar{I} = 5.3 \angle 44.62^\circ \quad A$$

Example

Find the current I in the circuit shown.

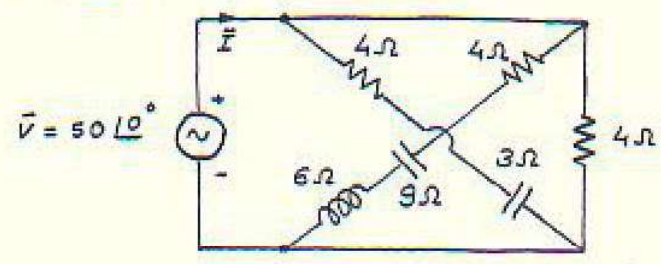

Solution

Let $\bar{Z}_1 = 4 - j3$

$$\bar{Z}_2 = 4 + j6 - j9 = 4 - j3$$

and

$$\bar{Z}_3 = 4 + j0 = 4 \Omega$$

تدفعان \bar{Z}_1 و \bar{Z}_2 مربوطة على التوازي

$\bar{Z}_1 = \bar{Z}_2$ تدفعان

$$\bar{Z}_T = \bar{Z}_1 // \bar{Z}_2 // \bar{Z}_3$$

since $\bar{Z}_1 = \bar{Z}_2 \Rightarrow \bar{Z}_{12} = \frac{\bar{Z}_1}{2} = \frac{4-j3}{2}$

$$\therefore \bar{Z}_T = \frac{\bar{Z}_{12} // \bar{Z}_3}{\bar{Z}_{12} + \bar{Z}_3} = \frac{4(2-j1.5)}{4+2-j1.5}$$

$$\therefore \bar{Z}_T = \frac{8-j6}{6-j1.5} = \frac{10 \angle -36.87^\circ}{6.18 \angle -14.04^\circ} = 1.62 \angle -22.83^\circ$$

$$\therefore \bar{I}_T = \frac{\bar{V}}{\bar{Z}_T} = \frac{50 \angle 0^\circ}{1.62 \angle -22.83^\circ} = 30.86 \angle 22.83^\circ$$

Note

\bar{Z}_T can be calculated from :

$$\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2 \bar{Z}_3}{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}$$

or $\bar{Z}_T = \frac{1}{\bar{Y}_T}$

where $\bar{Y}_T = Y_1 + Y_2 + Y_3$


$$\bar{Y}_1 = \frac{1}{\bar{Z}_1}, \bar{Y}_2 = \frac{1}{\bar{Z}_2}, \bar{Y}_3 = \frac{1}{\bar{Z}_3}$$

والصرك على النتيجة نفسها

Example

- For the circuit shown,
- Compute \bar{I} .
 - Find \bar{I}_1 , \bar{I}_2 and \bar{I}_3 .
 - Verify Kirchhoff's Current law by showing that:

$$\bar{I} = \bar{I}_1 + \bar{I}_2 + \bar{I}_3$$
 - Find the total impedance of the circuit.

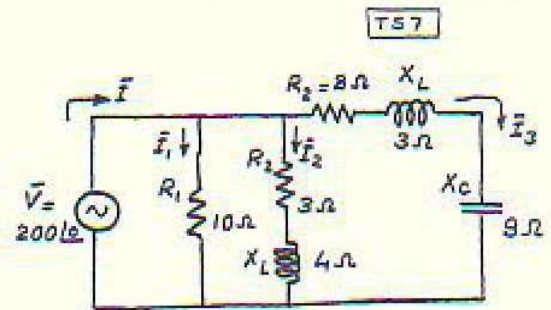**Solution**


Redraw the circuit as shown in the Fig. below;

where;

$$\bar{Z}_1 = 10 \angle 0^\circ = 10 \Omega$$

$$\bar{Z}_2 = 3 + j4$$

$$\bar{Z}_3 = 8 + j3 - j9 \\ = 8 - j6$$

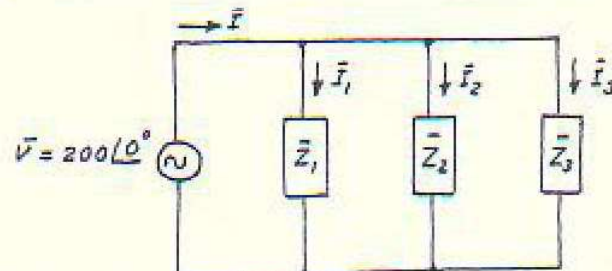

$$\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3}$$

$$= \frac{1}{10} + \frac{1}{3+j4} + \frac{1}{8-j6}$$

$$= \left(\frac{1}{10}\right) + \frac{3}{9+16} - j \frac{4}{9+16} + \frac{8}{64+36} + j \frac{6}{64+36}$$

$$= \frac{1}{10} + \frac{3}{25} + \frac{8}{100} - j \frac{4}{25} + j \frac{6}{100}$$

$$\therefore \bar{Y}_T = 0.3 - j0.1 \quad (\text{S})$$

(a). $\bar{I} = ?$

$$\bar{I} = \bar{V} \cdot \bar{Y}_T = 200 \angle 0^\circ (0.3 - j0.1) \\ = \underline{\underline{60 - j20}}$$

(b).

$$\bar{I}_1 = \frac{\bar{V}}{\bar{Z}_1} = \frac{200 \angle 0^\circ}{10 \angle 0^\circ} = 20 \angle 0^\circ \quad \text{A}$$

$$\bar{I}_2 = \frac{\bar{V}}{\bar{Z}_2} = \frac{200 \angle 0^\circ}{5 \angle 53.13^\circ} = 40 \angle -53.13^\circ \quad \text{A}$$

and

$$\bar{I}_3 = \frac{\bar{V}}{\bar{Z}_3} = \frac{200 \angle 0^\circ}{10 \angle -36.87^\circ} = 20 \angle 36.87^\circ$$

(c)

$$\bar{I} = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 \\ 60 - j20 = 20 \angle 0^\circ + 40 \angle -53.13^\circ + 20 \angle 36.87^\circ \\ = (20 + j0) + (24 - j32) + (16 + j12)$$

$$\therefore \underline{\underline{60 - j20 = 60 - j20}}$$

(d). $\bar{Z}_T = ?$

$$\bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.3 - j0.1} = \frac{0.3}{(0.3)^2 + (0.1)^2} + j \frac{0.1}{(0.3)^2 + (0.1)^2}$$


$$\therefore \bar{Z}_T = 3 + j1$$

For check

$$\begin{aligned} \bar{V} &= \bar{I} \bar{Z}_T \\ &= (60 - j20)(3 + j1) \\ &= 180 - j60 + j60 + 20 \\ &= 200 + j0 = 200 \angle 0^\circ \end{aligned}$$

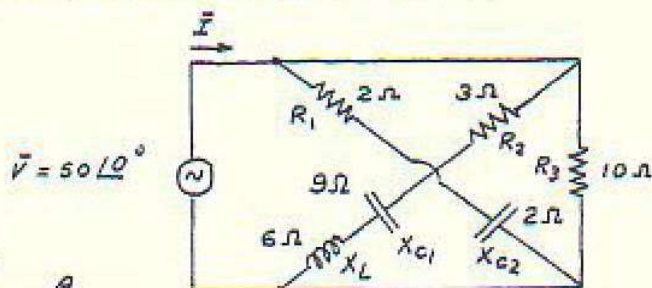Example (HW)

Find the current I in the circuit shown in the Fig.



Answer

$$\bar{I} = 33.201 \angle 38.89^\circ \text{ A}$$

Example

The load taken from a supply consists of: (a). lamp load of 10 kW at unity power factor, (b). motor load of 80 kVA at 0.8 power factor (lag), and (c). motor load of 40 kVA at 0.7 power factor leading.

Calculate the total load taken from the supply in kW and in kVA and the power factor of the combined load.

Solution

ملاحظة: سر إنسابه لأن هذا المثال ان يكون بشكل جدول يفهم انواع القدرة المختلفة للمحولات الكهربائية كما يأتي:

Load	kVA	cos φ	sin φ	kW	kVAR
(a)	10	1	0	10	0 (p.f = 1)
(b)	80	0.8	0.6	64	-48 (p.f lag)
(c)	40	0.7	0.714	28	+28.6 (p.f lead)
TOTAL →				102	-19.4



TS7

∴ Total kW = 102 ⇒ P_T
 Total kVAR = -19.4 (lagging) ⇒ Q_T

∴ Total kVA taken from the supply S_T

$$S_T = \sqrt{P_T^2 + Q_T^2}$$

$$= \sqrt{(102)^2 + (-19.4)^2} = 103.9 \text{ kVA}$$



and the power factor = $\cos \phi = \frac{P_T}{S_T} = \frac{102}{103.9} = 0.982$

وبما أن ذلك هو الجهد الكلي، فنضرب كما يأتي

$$S_T = S_1 + S_2 + S_3$$

$$= P_1 + jQ_1 + P_2 + jQ_2 + P_3 + jQ_3$$

$$= [10 \cos 0 + j0 + 80 \cos \phi_2 + j80 \sin \phi_2 + 40 \cos \phi_3 + j40 \sin \phi_3] \times 10^3$$

$$= [(10 + 64 + 28) + j(0 - 48 + 28.6)] \times 10^3$$


∴ $\bar{S}_T = 102 - j19.4 \text{ kVA}$

$$= 103.9 \angle -10.77 \text{ kVA}$$

∴ S = 103.9 kVA
 p.f = $\cos(-10.77)$
 = 0.982 (lagging)

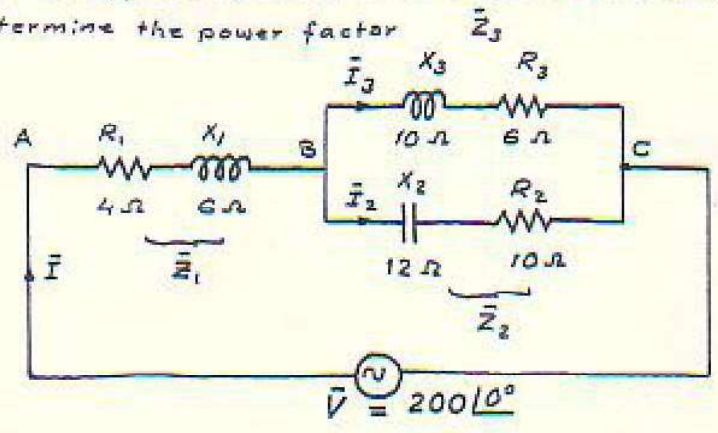Example

_____ : Determine the current drawn by the following circuit, where a voltage of 200 V is applied across its terminals. Draw the phasor diagram, and determine the power factor of the circuit.



Solution

_____ : $\bar{Z}_1 = 4 + j6 = 7.2 \angle 56.3^\circ \ \Omega$

$$\bar{Z}_2 = 10 - j12 = 15.6 \angle -50.2^\circ \ \Omega$$

$$\bar{Z}_3 = 6 + j10 = 11.7 \angle 58^\circ \ \Omega$$

AC Network Analysis


EE8
T59

Demonstrative Examples:

* Mesh (Loop) Analysis:

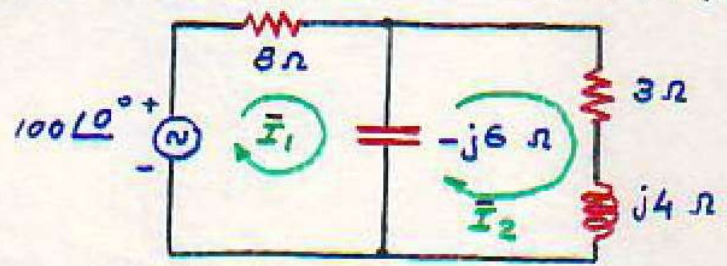Example

: Find the power output of the voltage source in the circuit shown; prove that this power equals the power in the circuit resistors. Use mesh analysis in your solution.



Solution

* Loop 1:

$$100\angle 0^\circ = \bar{I}_1(8 - j6) - \bar{I}_2(-j6)$$

$$\Rightarrow 100\angle 0^\circ = \bar{I}_1(8 - j6) + \bar{I}_2(j6) \quad \text{--- (1)}$$

* Loop 2:

$$0 = \bar{I}_2(3 + j4 - j6) - \bar{I}_1(-j6)$$

$$= \bar{I}_1(j6) + \bar{I}_2(3 - j2) \quad \text{--- (2)}$$

$$\bar{I}_1 = \frac{\Delta_1}{\Delta} \quad \text{and} \quad \bar{I}_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta = \begin{vmatrix} (8 - j6) & j6 \\ j6 & (3 - j2) \end{vmatrix} = (8 - j6)(3 - j2) - (j6)^2$$

$$\Rightarrow \Delta = 58.703 \angle -35.33^\circ$$

Similarly $\Delta_1 = \begin{vmatrix} 100 \angle 0^\circ & j6 \\ 0 & (3-j2) \end{vmatrix} = (300 - j2) = 360 \angle -33.69^\circ$

and $\Delta_2 = \begin{vmatrix} (8-j6) & 100 \angle 0^\circ \\ j6 & 0 \end{vmatrix} = j600 = 600 \angle 90^\circ$

$\therefore \bar{I}_1 = \frac{\Delta_1}{\Delta} = \frac{360 \angle -33.69^\circ}{58.703 \angle -35.33^\circ} = 6.133 \angle 1.64^\circ$

$\bar{I}_2 = \frac{\Delta_2}{\Delta} = \frac{600 \angle 90^\circ}{58.703 \angle -35.33^\circ} = 10.22 \angle 125.33^\circ$

\therefore Total Power output = total power absorbed by resistors


$\therefore V I_1 = I_1^2 (8) + I_2^2 (3)$

$(100)(6.133) = 300.4 + 313.3$

$\therefore \underline{\underline{613.3 \text{ W} \approx 613.7 \text{ W}}}$

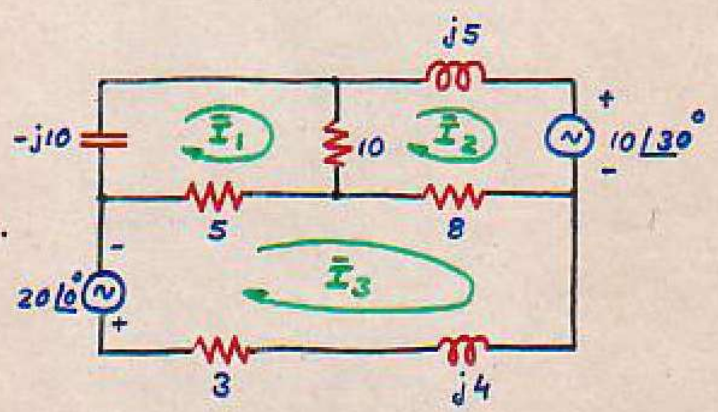Example :

Write the mesh current equations for the circuit shown.



Solution

_____ : The three mesh current equations are

* Loop 1

$$0 = (15 - j10)\bar{I}_1 - 10\bar{I}_2 - 5\bar{I}_3$$

* Loop 2

$$-10\angle 30^\circ = -10\bar{I}_1 + (18 + j5)\bar{I}_2 - 8\bar{I}_3$$

* Loop 3

$$-20\angle 0^\circ = -5\bar{I}_1 - 8\bar{I}_2 + (16 + j4)\bar{I}_3$$


$$\therefore \Delta = \begin{vmatrix} (15 - j10) & -10 & -5 \\ -10 & (18 + j5) & -8 \\ -5 & -8 & (16 + j4) \end{vmatrix} = ?$$

Then you can find $\bar{I}_1 = \frac{\Delta_1}{\Delta}$, $\bar{I}_2 = \frac{\Delta_2}{\Delta}$

and $\bar{I}_3 = \frac{\Delta_3}{\Delta}$

Homework

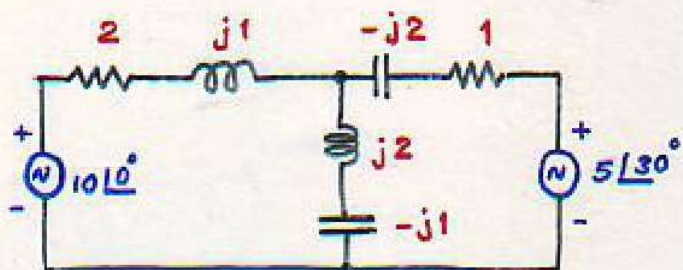For the ckt. shown, determine the branch voltages and currents and the power delivered by the source using mesh analysis.




* All resistance and reactance values are in Ohms.

HW

* Nodal Analysis

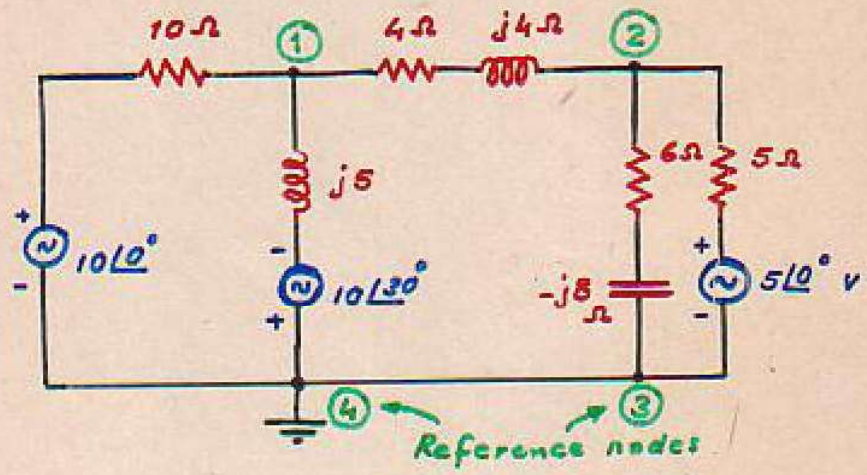Example: Write the nodal equations for the circuit shown;



Solution: We have two independent node 1 and 2, so two equations have to be written:

Node 1:

$$\bar{V}_1 \left(\frac{1}{10} + \frac{1}{4+j4} + \frac{1}{j5} \right) - \bar{V}_2 \left(\frac{1}{4+j4} \right) = \frac{10\angle 0^\circ}{10} - \frac{10\angle 30^\circ}{j5}$$

Node 2:

$$\bar{V}_2 \left(\frac{1}{4+j4} + \frac{1}{5} + \frac{1}{6-j8} \right) - \bar{V}_1 \left(\frac{1}{4+j4} \right) = \frac{5\angle 0^\circ}{5}$$


From these two equations, the unknown voltages \bar{V}_1 and \bar{V}_2 must be determined.

HW

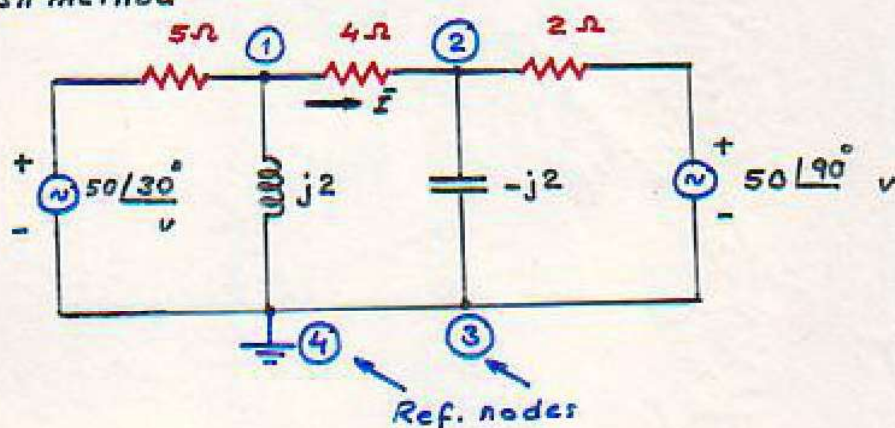Example

For the circuit shown in the Fig. below, determine the current flowing through the branch of 4-Ω resistance using:

- (a). Nodal Analysis
- (b). Thevenin's theorem.
- (c). Mesh method



Solution

(a). By Nodal Analysis Method

Node 1

$$\bar{V}_1 \left(\frac{1}{5} + \frac{1}{4} + \frac{1}{j2} \right) - \bar{V}_2 \left(\frac{1}{4} \right) = \frac{50 \angle 30^\circ}{5}$$

$$\therefore \Rightarrow \bar{V}_1 (9 - j10) - 5 \bar{V}_2 = 200 \angle 30^\circ \quad \text{--- (1)}$$

Node 2

$$\bar{V}_2 \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{-j2} \right) - \bar{V}_1 \left(\frac{1}{4} \right) = \frac{50 \angle 90^\circ}{2}$$

$$\therefore \Rightarrow \bar{V}_2 (3 + j2) - \bar{V}_1 = j100 \quad \text{--- (2)}$$

Solving Equ. 1 and 2; we find:

$$\bar{V}_1 = j27.26 \text{ volts}$$

and

$$\bar{V}_2 = 19.58 + j29.36$$


The current $\bar{I} = \frac{V_1 - V_2}{4} = \frac{j27.26 - 19.58 - j29.36}{4}$

$$= \frac{19.69 \angle 186.12^\circ}{4} = 4.92 \angle 186.12^\circ \text{ A}$$

⊛ Try to solve again using the methods of (b), and (c) and getting the same results.

Homework (B)

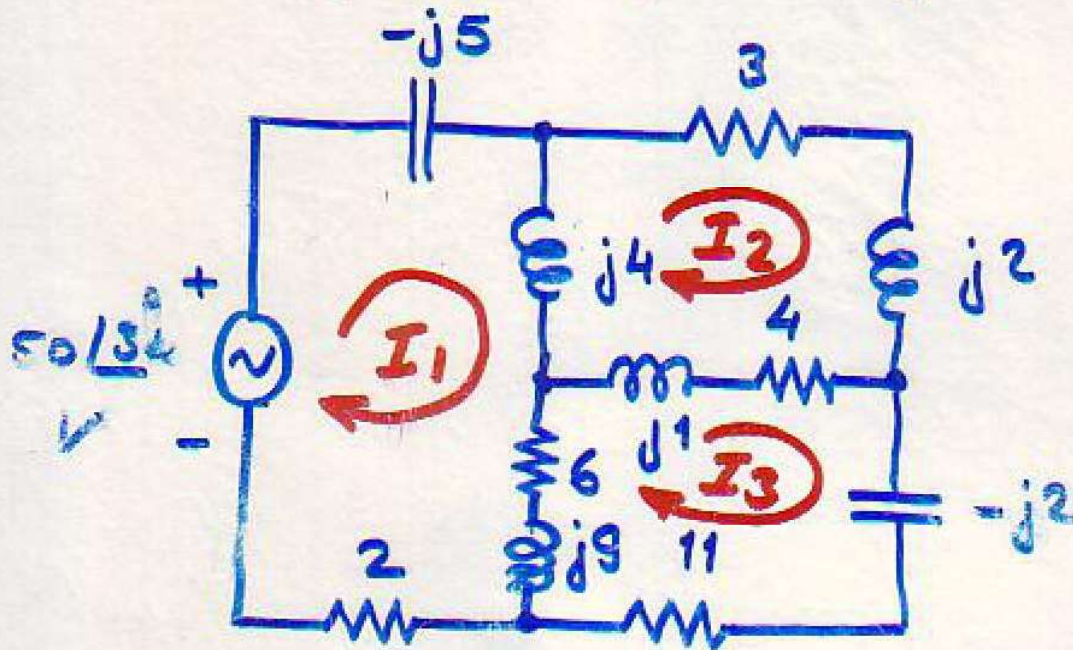
For the circ. shown, find the current I_1 using the loop Method



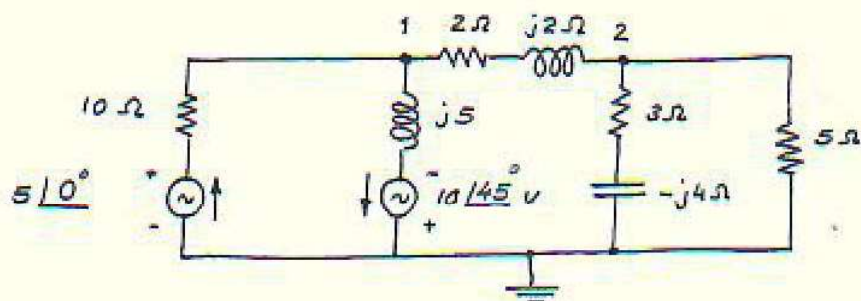Example

TSS

Write the nodal voltage equations for the circuit shown.



Solution

The nodal voltage equations are ;

For Node 1

_____ :

$$\left(\frac{1}{10} - \frac{1}{j5} + \frac{1}{2+j2} \right) \bar{V}_1 - \left(\frac{1}{2+j2} \right) \bar{V}_2 = \frac{5 \angle 0^\circ}{10} - \frac{10 \angle 45^\circ}{j5}$$

and

For Node 2


_____ :

$$- \left(\frac{1}{2+j2} \right) \bar{V}_1 + \left(\frac{1}{2+j2} + \frac{1}{3-j4} + \frac{1}{5} \right) \bar{V}_2 = 0$$

Solving the above equations to determine \bar{V}_1 & \bar{V}_2 .

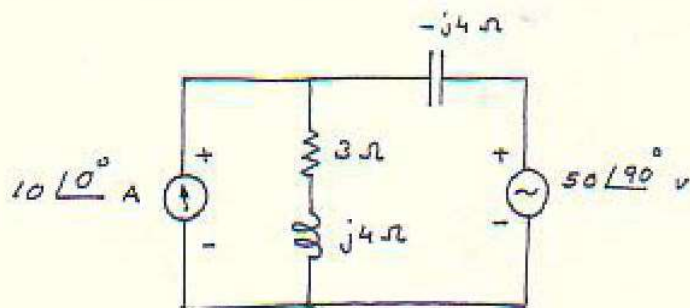Example

Apply the superposition theorem to determine the voltage drop across the $(3+j4) \Omega$ impedance, in the circuit shown.



Solution


_____ :

* The effect of $(10 \angle 0^\circ \text{ A})$ source alone ; Removing the $50 \angle 90^\circ \text{ V}$ source and substitute it by a short circuit, then :



* using the current divider rule, then:
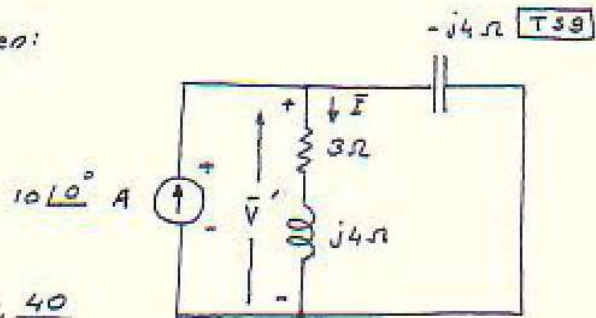
$$\begin{aligned}\bar{I} &= \bar{I}_T \frac{\bar{Z}_1}{\bar{Z}_1 + \bar{Z}_2} \\ &= (10 \angle 0^\circ) \frac{(-j4)}{(-j4) + (3+j4)} \\ &= (10 \angle 0^\circ) \frac{(-j4)}{3} = -j \frac{40}{3}\end{aligned}$$




$$\therefore \bar{V}' = \bar{I}(3+j4) = -j \frac{40}{3} (3+j4) = \underline{53.3 - j40}$$

* The effect of ($50 \angle 90^\circ$ V) voltage source; the circuit will be in this case as:

using the voltage divider rule, then:
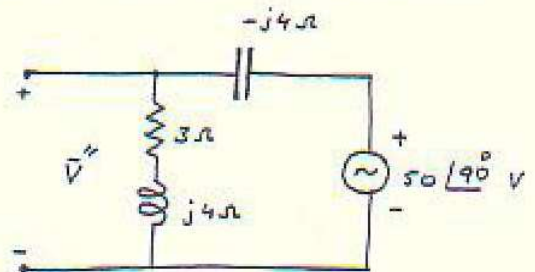
$$\begin{aligned}\bar{V}'' &= V_T \frac{\bar{Z}_2}{\bar{Z}_2 + \bar{Z}_1} \\ &= (50 \angle 90^\circ) \left(\frac{3+j4}{(3+j4) + (-j4)} \right) \\ &= -66.7 + j50\end{aligned}$$




$$\begin{aligned}\therefore \bar{V} &= \bar{V}' + \bar{V}'' = (53.3 - j40) + (-66.7 + j50) \\ &= -13.4 + j10 = 16.72 \angle 143.27^\circ\end{aligned}$$

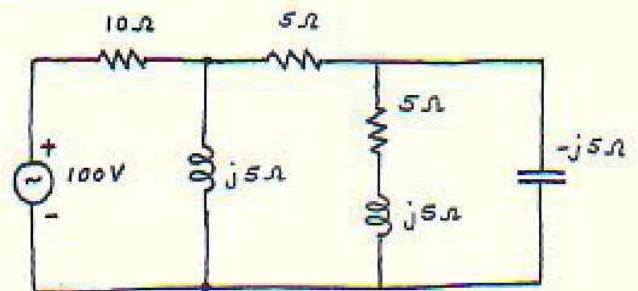Example

_____ : For the network shown, determine the voltage across the capacitor, using:

- Thevenius's theorem.
- Mesh current method.




Solution

: (a). Using Thevenin's theorem

$$\textcircled{*} V_{th} = ?$$

Voltage divider rule \Rightarrow
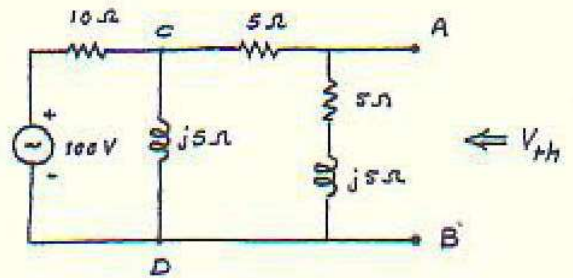
$$\begin{aligned} \bar{V}_{th} &= \bar{V}_{AB} \\ &= \bar{V}_{CD} \frac{(5+j5)}{(5+j5)+5} \\ &= \bar{V}_{CD} \frac{(5+j5)}{(10+j5)} \end{aligned}$$




$$\begin{aligned} \bar{V}_{CD} &= V_T \frac{(j5)}{10+j5} = 100 \frac{(j5)}{10+j5} \\ &= 20 + j40 \end{aligned}$$

Check

$$\begin{aligned} \therefore \bar{V}_{th} &= 21.1 \angle 71.57^\circ \text{ V} \\ &= 6.67 + j20 \end{aligned}$$

$$\textcircled{*} \bar{Z}_{th} = ?$$

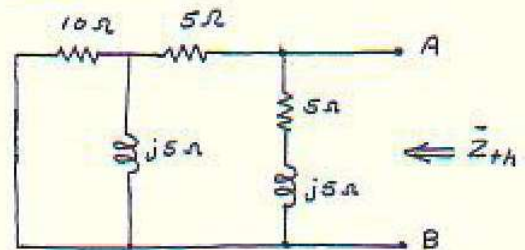When looking through terminals A and B, the voltage source removed; the equivalent impedance \bar{Z}_{th} is determined from the circuit:




$$\bar{Z}_{th} = [(10 \parallel j5) + 5] \parallel (5 + j5)$$

$$\therefore \bar{Z}_{th} = 3 + j2.33 \Omega$$

Check

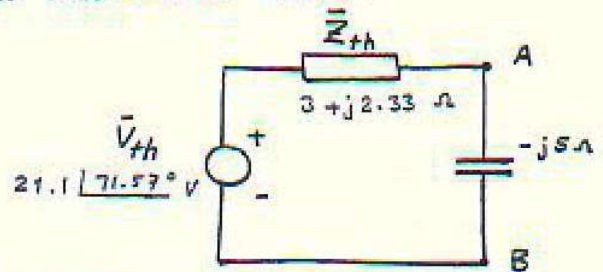$\textcircled{*}$ Thevenin's equivalent circuit will be as shown:




\therefore Total impedance

$$\begin{aligned} \bar{Z}_T &= (3 + j2.33) + (-j5) \\ &= 3 - j2.67 = 4.02 \angle -41.67^\circ \Omega \end{aligned}$$

$$\therefore I = \frac{V_{th}}{\bar{Z}_T} = \frac{21.1 \angle 71.57^\circ}{4.02 \angle -41.67^\circ} = \underline{\underline{5.25 \angle 113.24^\circ \text{ A}}}$$

(b). Using the mesh method

$\bar{I}_3 = ?$

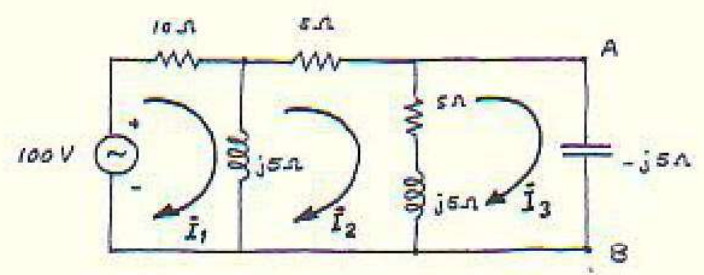

$\bar{I}_3 = \frac{\Delta_3}{\Delta}$


$$\therefore \bar{I}_3 = \frac{\begin{vmatrix} 10+j5 & -j5 & 100 \\ -j5 & 10+j10 & 0 \\ 0 & -(5+j5) & 0 \end{vmatrix}}{\begin{vmatrix} 10+j5 & -j5 & 0 \\ -j5 & 10+j10 & -(5+j5) \\ 0 & -(5+j5) & 5 \end{vmatrix}} = \frac{3535 \angle 135^\circ}{673 \angle 21.8^\circ}$$

$\Rightarrow \bar{I}_3 = \underline{\underline{5.25 \angle 113.2^\circ \text{ A}}}$

which is the same result.

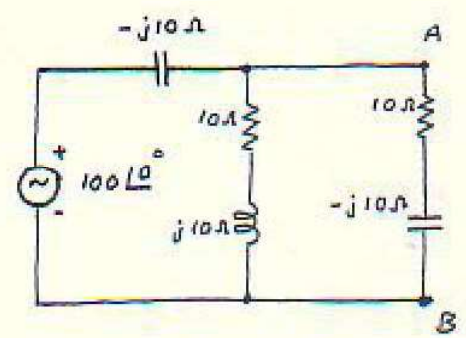Example


Use Norton's theorem to find the current in the load connected across terminals A and B of the circuit shown.



Solution

$\bar{I}_N = ? \Rightarrow$ the current in the short circuit terminals A & B
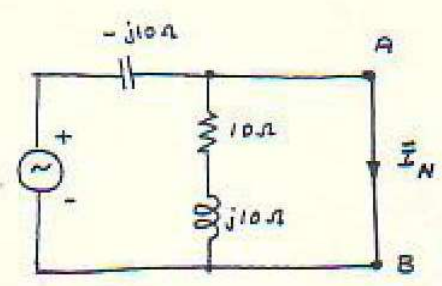
$$\begin{aligned} \therefore \bar{I}_N &= \frac{\bar{V}_T}{\bar{Z}_T} = \frac{100 \angle 0^\circ}{-j10} \\ &= \frac{100 \angle 0^\circ}{-10 \angle 90^\circ} = \frac{100 \angle 0^\circ}{10 \angle -90^\circ} \\ &= \underline{\underline{10 \angle 90^\circ \text{ A}}} \end{aligned}$$




* $\bar{Z}_N = \bar{Z}_{Th} = ?$

$$\bar{Z}_N = (-j10) \parallel (10 + j10)$$

$$= \frac{(-j10)(10 + j10)}{(-j10) + (10 + j10)}$$

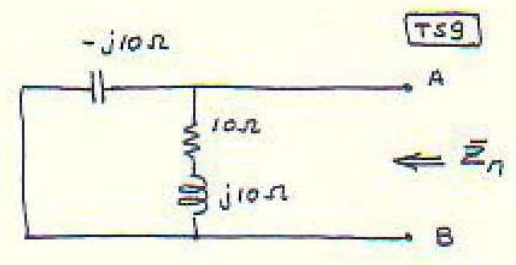
$\therefore \bar{Z}_N = \underline{\underline{10 - j10}}$



* The Norton's equivalent circuit is :

$$\bar{I}_L = \frac{\bar{I}_N}{2} = \frac{10 \angle 90^\circ}{2}$$
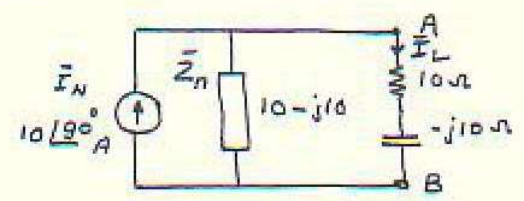
$$= \underline{\underline{5 \angle 90^\circ \text{ A}}}$$




Since \bar{I}_N is equally divided between the two equal impedances.

Example

T39

For the circuit shown, determine the currents \bar{I}_A , \bar{I}_B and \bar{I}_C , using the mesh current analysis method.

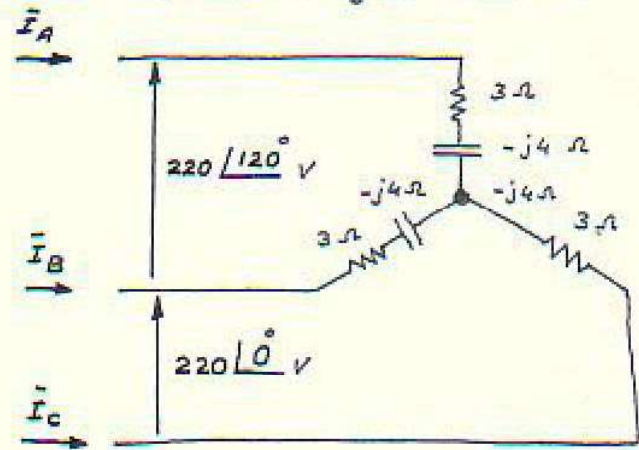**Solution**

Using the mesh method, we have to determine the currents

\bar{I}_1 and \bar{I}_2 , then:

Mesh Equations


$$(6 - j8)\bar{I}_1 - (3 - j4)\bar{I}_2 = 220 \angle 120^\circ$$

and

$$-(3 - j4)\bar{I}_1 + (6 - j8)\bar{I}_2 = 220 \angle 0^\circ$$

$$\therefore \bar{I}_1 = \frac{\begin{vmatrix} 220 \angle 120^\circ & -(3 - j4) \\ 220 \angle 0^\circ & (6 - j8) \end{vmatrix}}{\begin{vmatrix} (6 - j8) & -(3 - j4) \\ -(3 - j4) & (6 - j8) \end{vmatrix}}$$
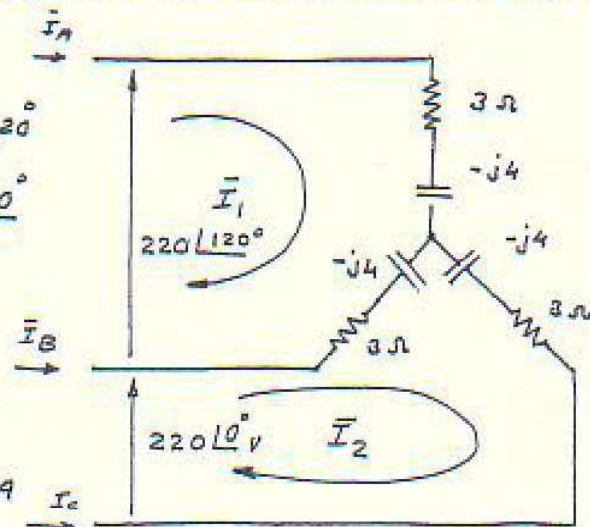
$$= \frac{1905 \angle 36.9^\circ}{75 \angle -106.2^\circ} = 25.4 \angle 143.1^\circ \text{ A}$$



and

$$\bar{I}_2 = \frac{\begin{vmatrix} (6 - j8) & 220 \angle 120^\circ \\ -(3 - j4) & 220 \angle 0^\circ \end{vmatrix}}{\Delta} = \frac{1905 \angle -23.2^\circ}{75 \angle -106.2^\circ} = 25.4 \angle 83^\circ \text{ A}$$

$$\therefore \bar{I}_A = \bar{I}_1 = 25.4 \angle 143^\circ \text{ A}$$

$$\bar{I}_B = \bar{I}_2 - \bar{I}_1 = 25.4 \angle 83^\circ - 25.4 \angle 143.1^\circ = 25.4 \angle 23.1^\circ \text{ A}$$

$$\bar{I}_C = -I_2 = -(25.4 \angle 83^\circ) = 25.4 \angle -97^\circ \text{ A}$$